 


# Memory Structures

- SRAM
- DRAM
- DDR Memory


# SRAM Applications

- Embedded RAM for ASICs
- Configuration Bits for FPGAs
- CPU cache memory



 
# DRAM - Applications

- Main memory desktops, laptops, workstations




# SRAM Cell

 


Consists of cross coupled inverters – more compact than a D-Type flip-flop.

 A memory controller on the memory chip handles the complexity of writing and reading data leaving a simpler interface to the user.




6T SRAM CELL

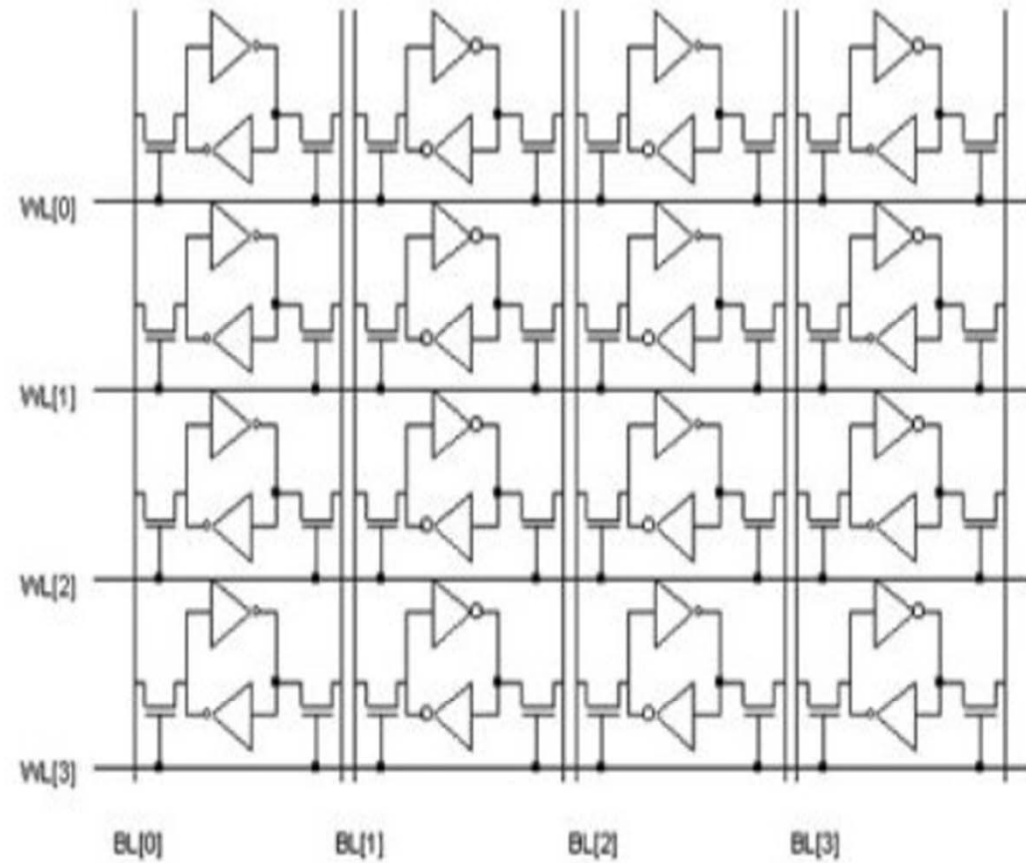


4 x 4 SRAM Memory Array

# SRAM Cell WRITE

 


To write to the cell, *bitline* is set to the required data value and  $\overline{\text{bitline}}$  is set to the complement. The controller then sets wordline = 1 which turns on transistors  $T_1$  and  $T_2$ . The data values then appear in the inverter loop overwriting any previous value.

# SRAM Cell READ

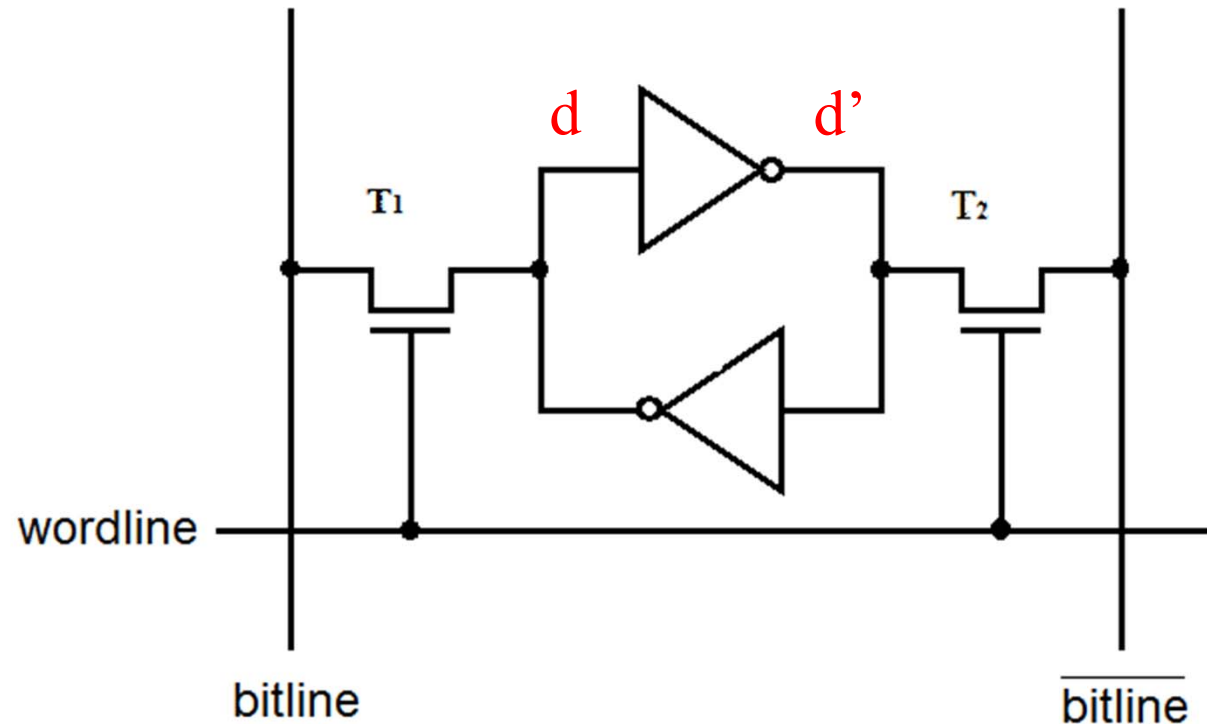


 To read from the cell, *bitline* and  $\overline{\text{bitline}}$  are both precharged to 1. Wordline is then set to 1. One of the enabled transistors will have a 0 at one end which will cause the corresponding precharged 1 to drop to a slightly lower voltage than a normal 1. Both of the bitlines are connected to a *sense amplifier* which can detect this variation.






# SRAM Cell READ

 

If the voltage on  $\text{bitline}$  is slightly higher than  $\overline{\text{bitline}}$  then a logic 1 is stored.

If the voltage on  $\overline{\text{bitline}}$  is slightly higher than  $\text{bitline}$  then a logic 0 is stored.

# Dynamic RAM structure

 

1-bit DRAM cell  
Information stored  
on small capacitor  
accessed through a  
MOS transistor


## WRITE

Access by setting the word line HIGH

To store a '1' access cell, set the bit line HIGH, capacitor will charge

To store a '0' access cell, set the bit line LOW, capacitor will discharge

# Dynamic RAM structure

 

1-bit DRAM cell  
Information stored  
on small capacitor  
accessed through a  
MOS transistor

## READ

Precharge bit line to a voltage halfway between HIGH and LOW  
Set wordline HIGH, precharged bit line will be pulled slightly higher or lower dependent on capacitor charge. Sense amplifier detects this and recovers '1' or '0'

**DRAM** – The original DRAM used in PCs was asynchronous. Once a memory access is started, it finishes a certain period of time later. It is only suitable for slower memory bus systems.

**SDRAM** – Synchronous DRAM is synchronized to the system clock. This allows tighter control of the timing and improved performance.

**SDR SDRAM** – Single data rate SDRAM can transfer one data word per clock cycle.

**DDR SDRAM** – Double data rate SDRAM can transfer two data word per clock cycle. It achieves this by transferring data on both the rising and falling edge of a clock cycle.

**DDR4** – There have been several generations of DDR memory each having performance improvements over the previous generation. DDR4 is expected to have mass adoption by 2015.