

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Autumn Semester 2009 (30 minutes)

EEE 101 CIRCUITS AND SIGNALS MID TERM TEST

Answer **ALL** questions. The numbers given after each question indicate the relative weighting of that question. A total of 26 marks can be obtained from the seven questions.

REGISTRATION NUMBER:

WRITE YOUR ANSWERS ON THIS QUESTION PAPER

- 1 Figure 1 shows three resistors labelled with voltages and currents in specified directions. R , V and I are positive. Indicate by ticking the appropriate box which of the three resistors is marked with the correct convention. **{1 mark}**

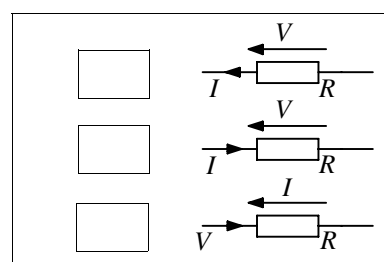


figure 1

- 2 Figure 2 shows two sources, (a) and (b). By circling either (a) or (b) on the diagram, identify the current source. Label figure 2 with voltage differences and currents that have directions appropriate for the voltage source delivering energy to a load and the current source absorbing energy from a load. (Note, the loads are not shown on the diagram.) **{5 marks}**

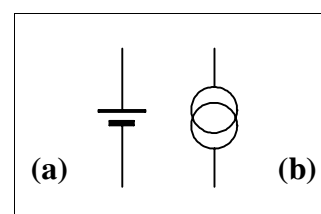


figure 2

- 3 Figure 3 shows four resistive circuits. If each circuit is attached to a 10V source, work out the magnitude of the current through R_2 in each case and put your answer in the box provided. **{4 marks}**

Q3 work space

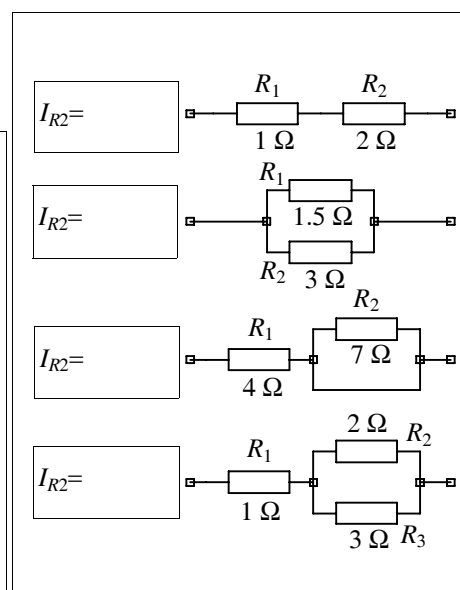


figure 3

- 4 Figure 4 contains a voltage source and a current source, both of which are ideal, and two resistors. Work out the power dissipation in R_2 . {4 marks}

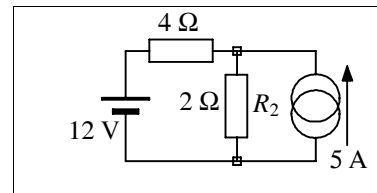


Figure 4

Q4 *work space*

- 5 Figure 5 shows a Thevenin equivalent circuit and a Norton equivalent circuit. Find values of I and R_N that will make the two circuits indistinguishable from the load's point of view. Label the current source to show the direction in which its current I will flow. {3 marks}

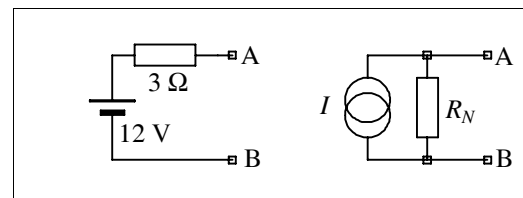


Figure 5

Q5 *work space*

- 6 Write down the loop equation for the I_2 loop in the circuit of figure 6. {6 marks for correct answer minus one mark per error}

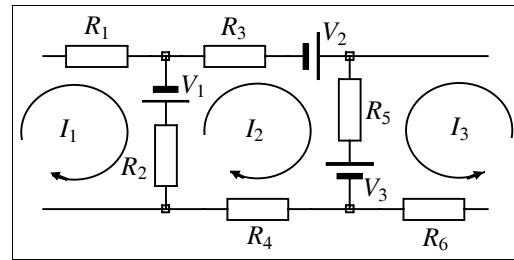


Figure 6

Q6 work space

- 7 Calculate the current I_S in the circuit of figure 7. {3 marks}

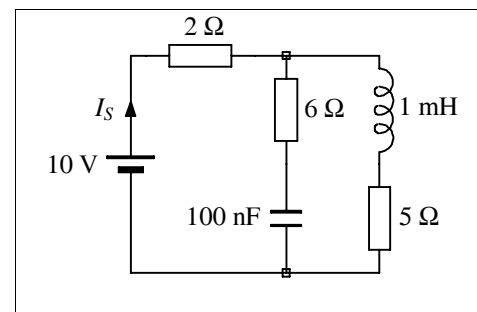


Figure 7

Q7 work space