

# Analog-to-Digital Conversion (ADC)


- Flash (Parallel) Converter
- Successive Approximation ADC

# Flash (Parallel) ADC


Comparators are used to compare a reference voltage with the analog input voltage  $V_{in}$ . If the input to a certain comparator is greater than the reference voltage, then a 'HIGH' is output from that comparator.

The reference voltage for each comparator is obtained from the resistor voltage-divider circuit.

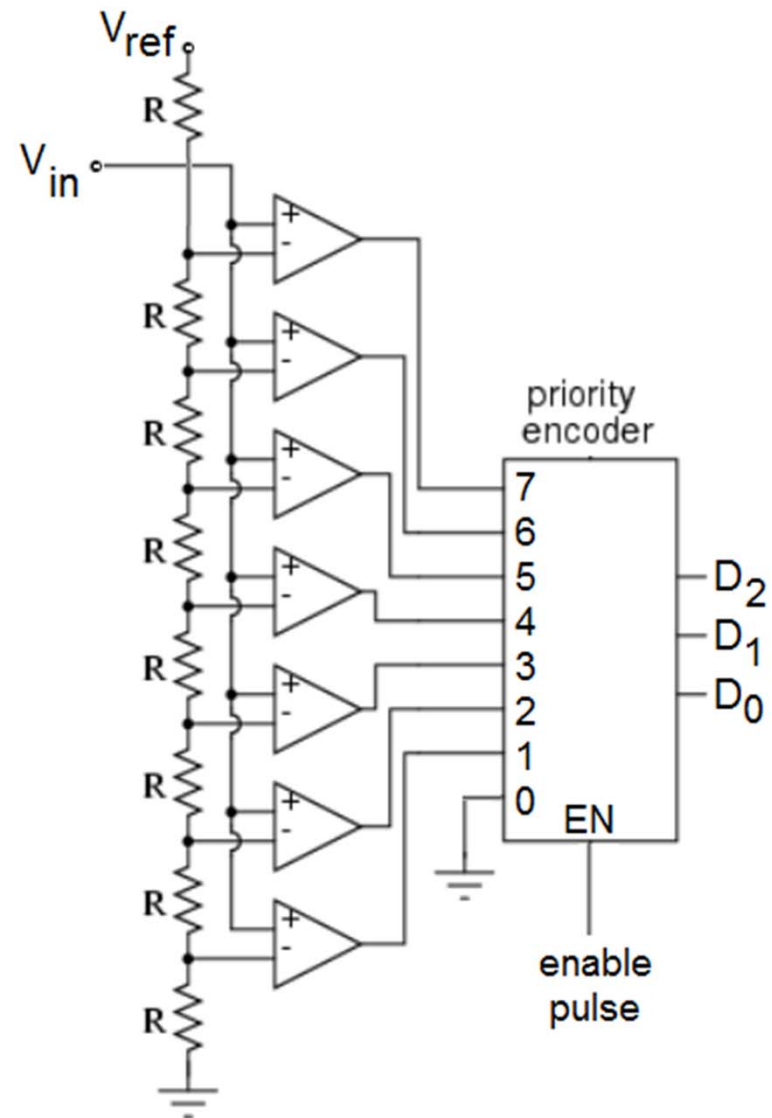When the priority encoder is enabled by a 'HIGH' enable pulse, a 3-bit code representing the input voltage is produced. It is obtained from the highest order input having a 'HIGH'.




 Example: A 3-bit flash ADC takes the analog input shown from a sample-and-hold circuit. What is the output from the ADC using the enable pulses shown and reference voltage of +8V .




The digital output sequence is:

 100, 110, 111, 110, 100, 010, 000, 001, 011, 101, 110, 111



Flash converters have the advantage of being fast but a disadvantage is the large number of comparators required.

# Successive-Approximation ADC

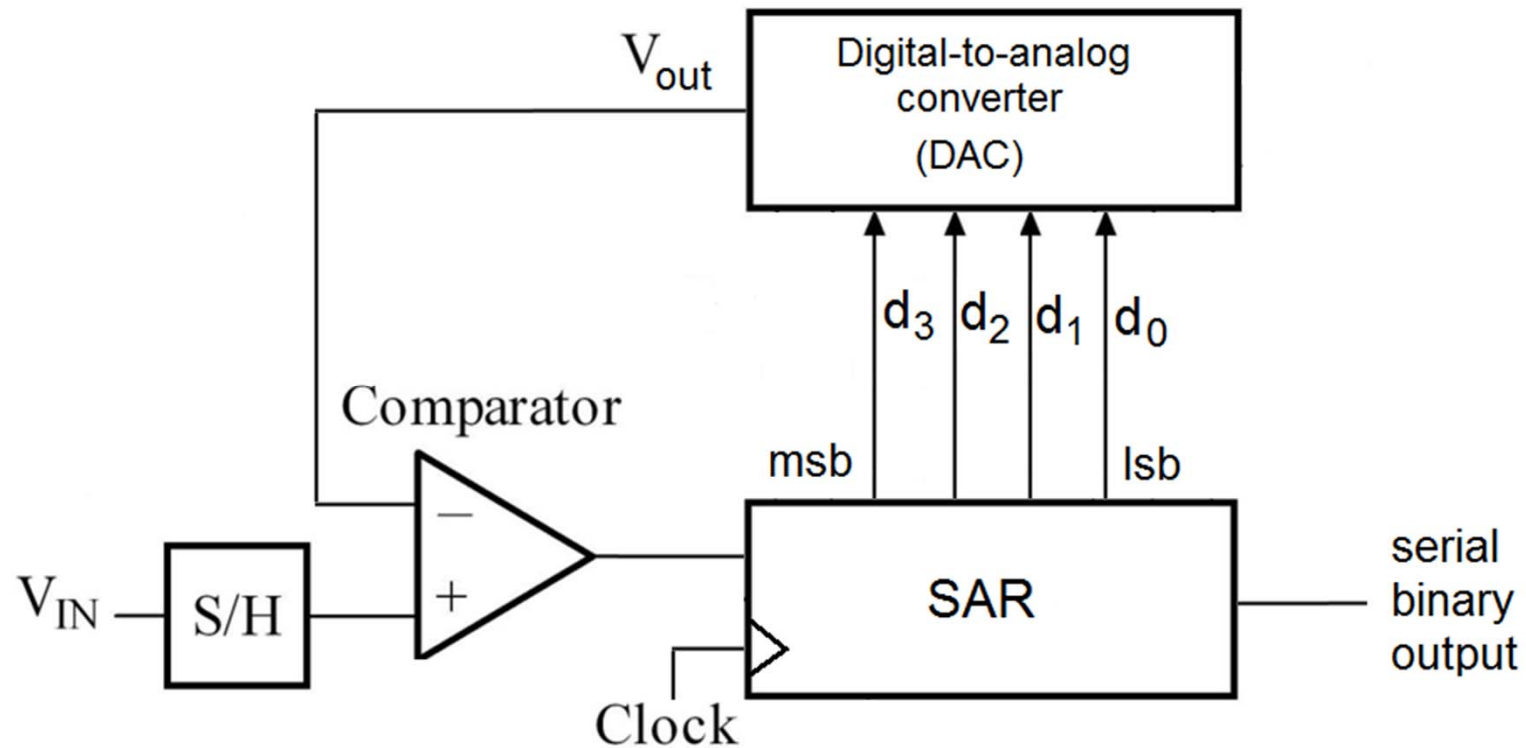

SAR – Successive Approximation Register

- Starting with the msb, set each input to the DAC to a '1' one at a time
- For each setting, the DAC produces an output  $V_{\text{out}}$
- Compare  $V_{\text{out}}$  with the input voltage  $V_{\text{in}}$
- If the DAC output is greater than the input ( $V_{\text{out}} > V_{\text{in}}$ ) the comparator will give a low output
- A low on the comparator output resets the set bit in the register
- If the DAC output is less than the input ( $V_{\text{out}} < V_{\text{in}}$ ) the comparator will give a high output and the set bit in the register is retained.
- The msb is examined first, then the next most significant bit, then the next until all bits have been tried.
- When all bits have been tried, the conversion is complete


Consider the four bit conversion of a constant input voltage of 5.2V.

Assume the DAC outputs : 8V for the  $2^3$  bit (msb)

4V for the  $2^2$  bit

2V for the  $2^1$  bit

1V for the  $2^0$  bit (lsb)

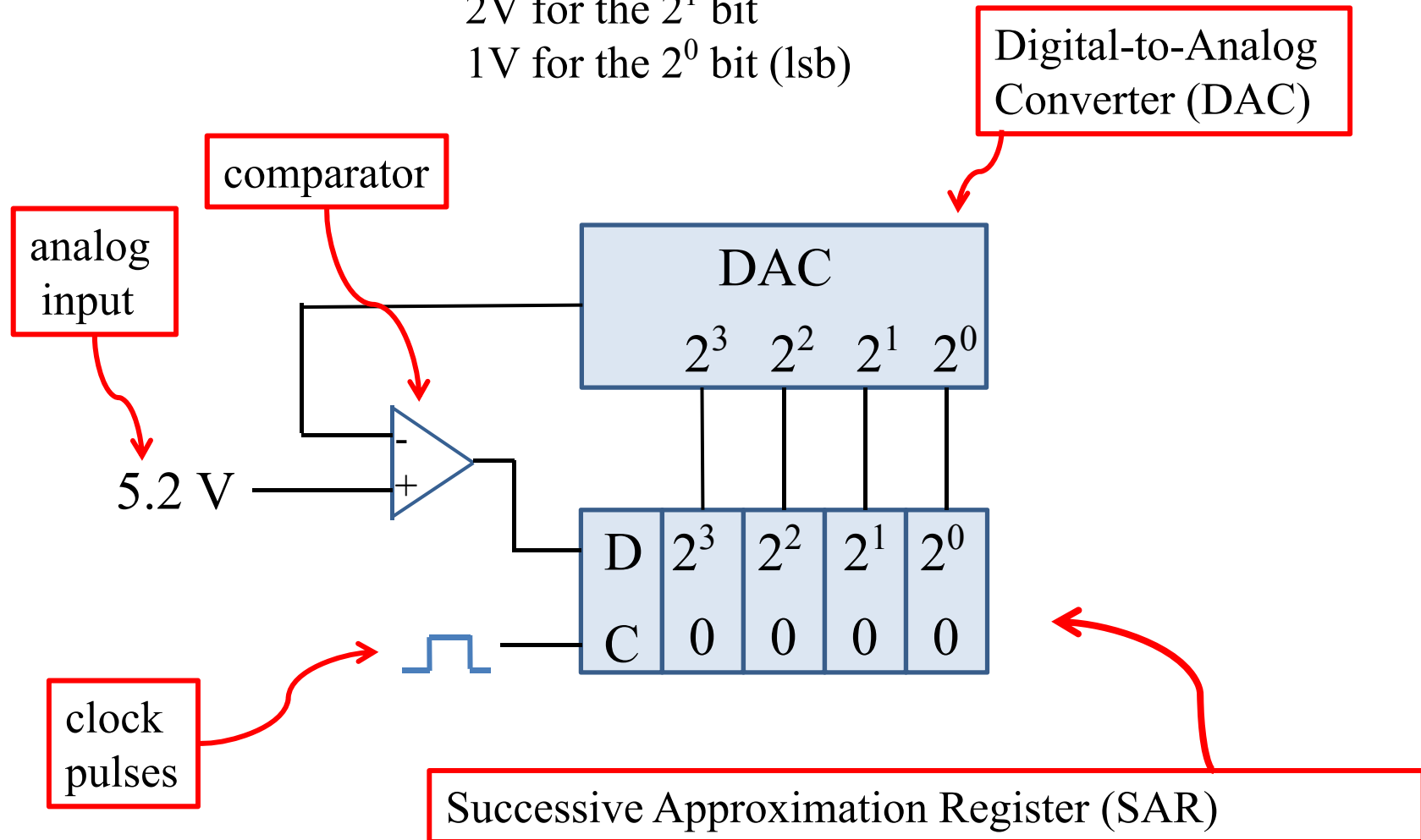

$2^3$  trial – DAC output 8V which is greater than

