


EEE101 Circuits + Signals

AUTUMN 06/07 Exam Solutions

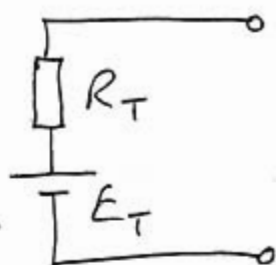Q1(a) Thevenin

R_T - Thevenin resistance, obtained by s/c voltage sources and o/c current sources


and then calculating equivalent resistance between the terminals.



E_T - Thevenin voltage, equal to the voltage appearing across the terminals with no load connected


Norton

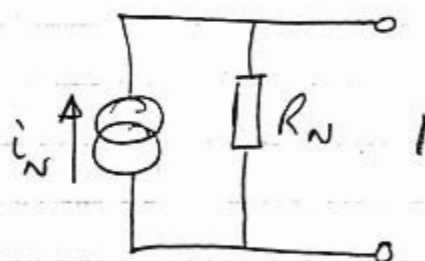R_N - Norton resistance, obtained as above



i_N - Norton current source, equal to the current flowing in a short circuit placed across the terminals.


(b) Find R_T

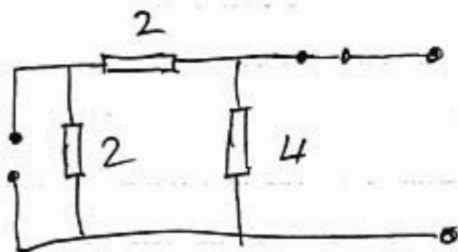

$$R_T = (2+2) // 4 = \frac{4 \times 4}{4+4} = 2 \Omega$$

②

EEE 101 06/07

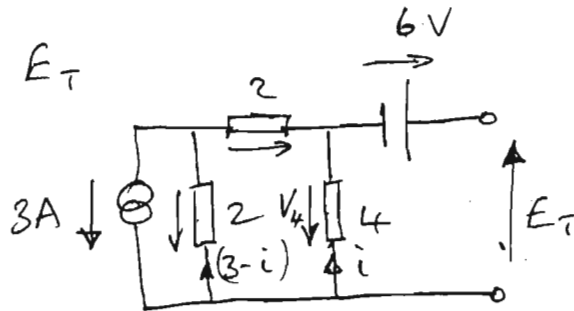
Find E_T 

$$(4+2)i - 2(3-i) = 0$$


$$\Rightarrow i = 0.75 \text{ A}$$

$$V_4 = 4 \times 0.75 = 3 \text{ V}$$

$$\therefore E_T = 6 \text{ V} - 3 \text{ V} = \underline{3 \text{ V}} \quad 3$$

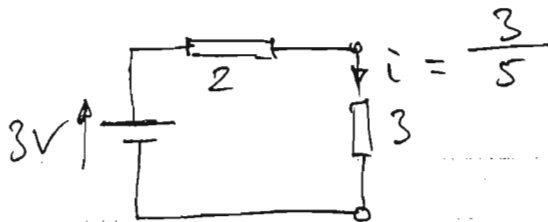Power in 3Ω resistor = $i^2 R$ 

$$= \underline{1.08 \text{ W}} \quad 2$$

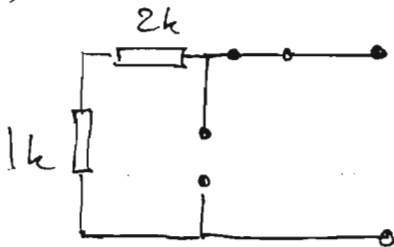
(c) Find R_T 

$$R_T = 2k + 1k = \underline{3k\Omega} \quad 2$$

Find V_T 2 mA flows through $1k + 2k$ resistors

$$\therefore V_{AB} = 2 \times 10^{-3} \times 3 \times 10^3 = 6 \text{ V}$$
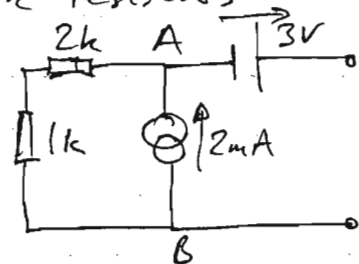
$$\therefore V_T = V_{AB} + 3 \text{ V} = 9 \text{ V}$$



3

For $5k\Omega$ load $I = \frac{9}{8 \times 10^3} = 1.13 \times 10^{-3} \text{ A} \therefore \text{Power} = I^2 R = \underline{6.33 \text{ mW}}$

For $25k\Omega$ load $I = \frac{9}{28 \times 10^3} = 0.32 \text{ mA} \therefore \text{Power} = 2.58 \text{ W}$
 \therefore Power range $\underline{2.58 \rightarrow 6.33 \text{ mW}} \quad 2$

EEE 101 06/07

Q2

- (a) Inductor - energy stored as a magnetic field - extracted by interruption of current to produce spark or arrange to disconnect power supply and allow current to dissipate through resistor. 2

Capacitor - energy stored as an electric field - connect to resistor and discharging current produces heat. 2

Energy Stored in Inductor

Absorbed power $p = vi = L i \frac{di}{dt}$

Energy absorbed in a time interval t

$$\begin{aligned} E_L &= \int_0^t p dt' = L \int_0^I i \frac{di}{dt'} dt' \\ &= L \int_0^I i di = \frac{1}{2} L I^2 \end{aligned} \quad 4$$


(where I is current at t and $I=0$ at $t=0$)

(b)

$$\omega L = 300$$

$$\frac{V}{I} = \frac{V}{\omega L}$$

$$= 0.033 \text{ A}$$

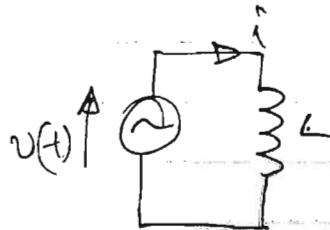


$$i = 0.033 \sin(100t + 90^\circ) \quad (\text{lags voltage by } 90^\circ) \quad 1$$

$$\text{Stored energy} = \frac{1}{2} L i^2$$


$$= 1.5 \times (0.033)^2 \sin^2(100t + 90^\circ)$$

$$= 1.6 \times 10^{-3} \sin^2(100t + 90^\circ)$$
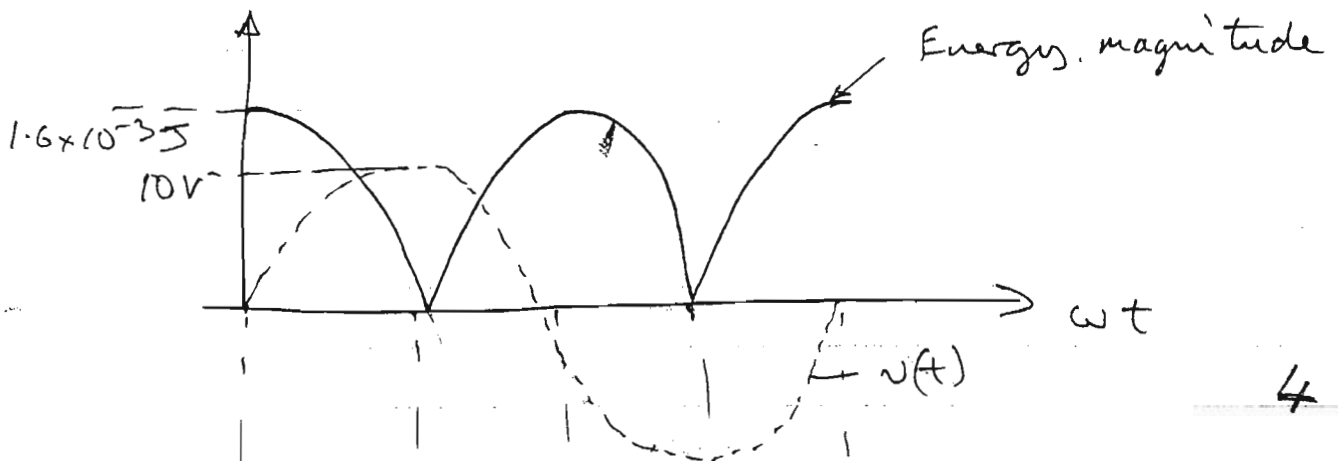
$$\text{Peak stored energy} = \underline{1.6 \times 10^{-3} \text{ J.}}$$



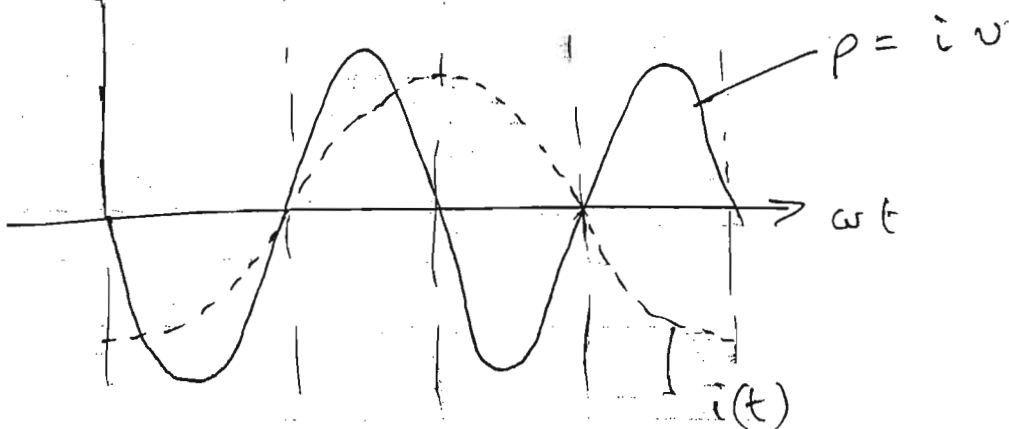ie. energy follows current since $E \propto i^2$




$$\text{power} = i \times v$$

EEE101 06/07

Q.3

(a)

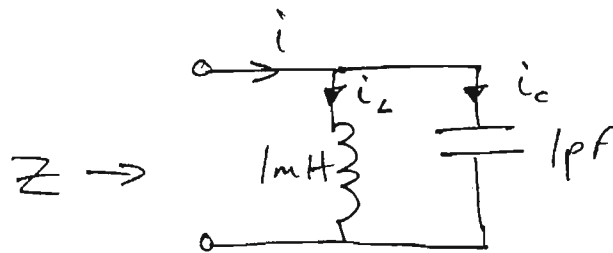

$$Z = \frac{j\omega L \times \frac{1}{j\omega C}}{j\omega L + \frac{1}{j\omega C}} = \frac{j\omega L}{\frac{1}{\omega C} - \omega L}$$


Z is infinite when $\frac{1}{\omega C} = \omega L$

$$\text{ie. } \omega = \frac{1}{\sqrt{CL}} = \frac{1}{\sqrt{10^{-8} \times 1}} = 1 \text{ kHz}$$

$$\bar{I}_L = \frac{\bar{V}}{j\omega L} = -\frac{j\bar{V}}{\omega L}$$

$$\bar{I}_C = \frac{\bar{V}}{\frac{1}{j\omega C}} = j\omega C \bar{V}$$
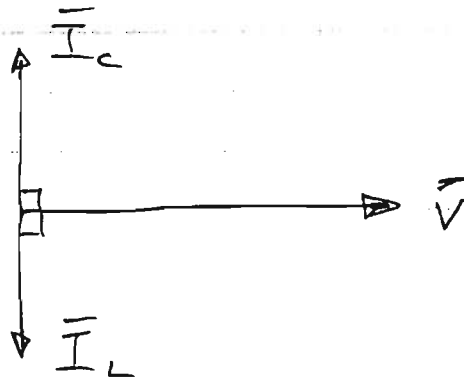
$$\therefore \bar{I} = \bar{I}_L + \bar{I}_C = j\bar{V}\left(\omega C - \frac{1}{\omega L}\right)$$




ie. Zero current
drawn (infinite
impedance) when
 $|\bar{I}_C| = |\bar{I}_L|$

$$\text{ie. } \omega C = \frac{1}{\omega L}$$

2

(6)

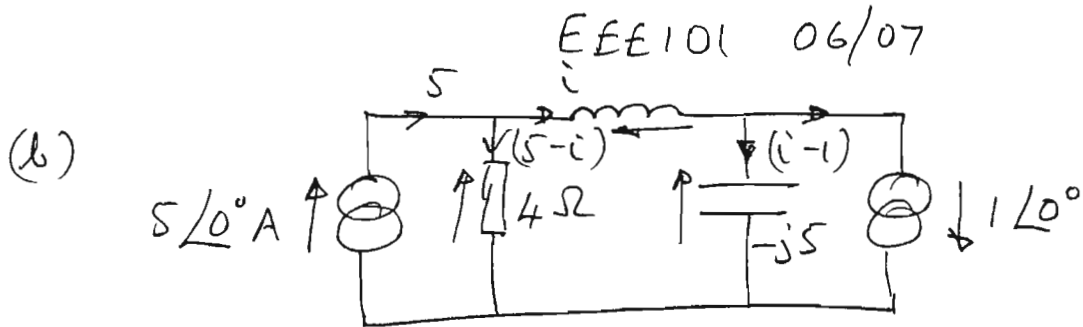

1K2 round inner loop $-4(5-i) + j2i + (-j5(i-1)) = 0$ 2

$$\therefore i = \frac{20-j5}{4-j3} = \frac{(20-j5)(4+j3)}{16+9}$$

$$= \underline{3.8 + j1.6 \text{ A}} \quad 2$$

Magnitude of $i = \sqrt{3.8^2 + 1.6^2} = 4.12 \text{ A}$ $\phi_L = \tan^{-1}\left(\frac{1.6}{3.8}\right)$
 $= 22.83^\circ$

$\therefore \underline{i = 4.12 \angle 22.83^\circ}$ (relative to current source) 2

Current in capacitor $= i - 1 = 2.8 + j1.6 \text{ A}$

magnitude $= \sqrt{2.8^2 + 1.6^2} = 3.22 \text{ A}$

$\phi_C = \tan^{-1}\left(\frac{1.6}{2.8}\right) = 29.74^\circ$

$\therefore \underline{\text{current in capacitor} = 3.22 \angle 29.74^\circ}$ 2

$\bar{V}_C = (i-1)(-j5) = 8 - j14$; $|\bar{V}_C| = \sqrt{8^2 + 14^2} = 16.12 \text{ V}$

$\phi_{V_C} = \tan^{-1}\left(\frac{-14}{8}\right) = -60.25^\circ \therefore \underline{\bar{V}_C = 16.12 \angle -60.25^\circ}$ 2

Phase angle between current and voltage
in capacitor from above


2

$= 29.74 + 60.25 \approx \underline{90^\circ}$ as expected-

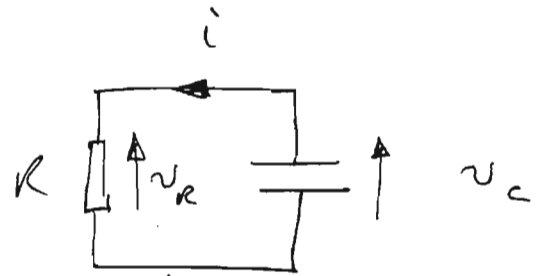Q4 (a)

$$v_c = V_0 \text{ at } t=0$$

$$\therefore i = V_0/R \text{ at } t \geq 0$$



$$\therefore v_c - v_R = 0 = V_0 - \frac{1}{C} \int_0^t i dt' - iR$$

differentiate $i/C + R \frac{di}{dt} = 0$

separate variables + integrate

$$RC \int \frac{di}{i} = \int -dt'$$


$$\Rightarrow RC \ln i = -t + A \quad \text{--- ①}$$

when $t=0$, $i = \frac{V_0}{R} \Rightarrow A = RC \ln \frac{V_0}{R}$

subst. into ① $RC \ln(i/V_0/R) = -t$


$$\therefore i = \frac{V_0}{R} \exp -t/CR$$

3

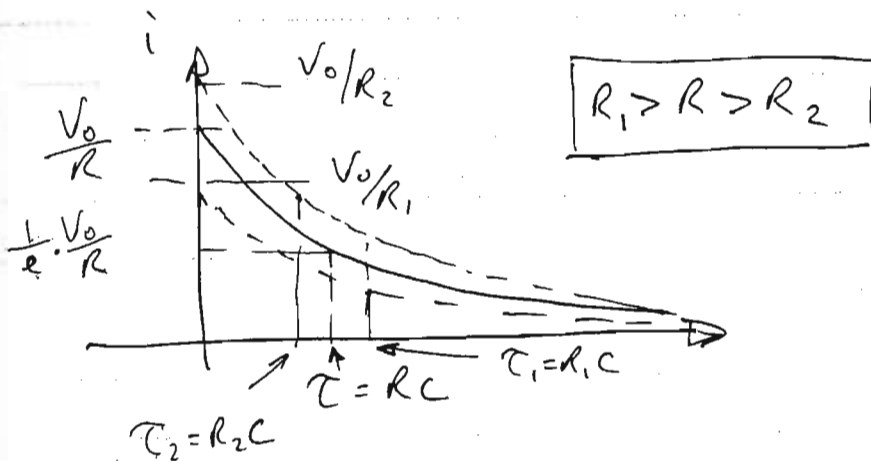

4

Q4 (b)

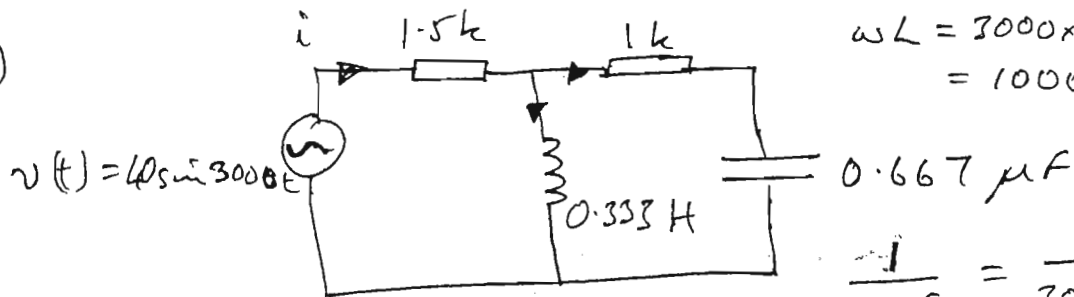

$$\omega L = 3000 \times 0.333 = 1000 \Omega$$

$$\frac{1}{\omega C} = \frac{1}{3000 \times 0.667 \times 10^{-6}} = 2000 \Omega$$

$$\text{Total impedance } Z = 1.5 + \frac{j(1-j2)}{j + (1+j2)} \text{ k}\Omega$$

$$= 1.5 + \frac{j+2}{1-j}$$

$$= 1.5 + \frac{(2+j)(1+j)}{1^2 + 1^2}$$

$$= 1.5 + \frac{2 - 1 + j1 + j^2}{2}$$

$$= \underline{2 + j1.5 \text{ k}\Omega}$$

$$|Z| = \sqrt{2^2 + 1.5^2} = 2.5$$

$$\phi = \tan^{-1}\left(\frac{1.5}{2}\right) = 36.87^\circ$$

current i

$$\bar{I} = \frac{\bar{V}}{Z} = \frac{40 \angle 0^\circ}{2.5 \angle 36.87^\circ}$$

$$= 1.6 \angle -36.87^\circ \text{ mA}$$

$$\text{or } \underline{i(t) = 1.6 \sin(3000t - 36.87^\circ) \text{ mA}}$$

Current is lagging voltage hence inductive in character.

As ω is increased the capacitor impedance would decrease and tend to take more current resulting in the overall impedance becoming more capacitive.