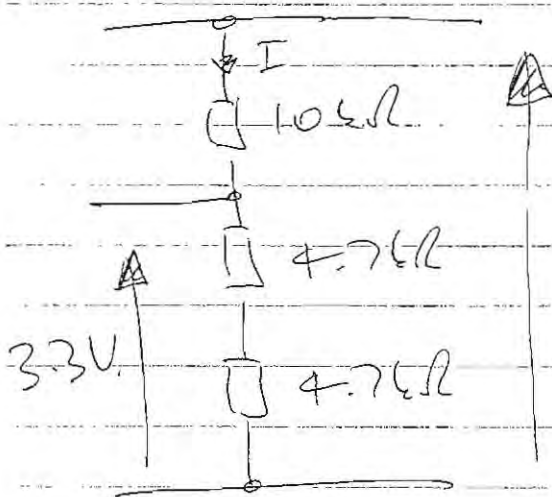


Q1

a) Output voltage range


 R_w wiper set to max.

$$I = \frac{3.3}{2 \times 4.7k} = 3.51 \times 10^{-4} A$$

$$V_o = R_{tot} \times I$$

$$= (10k + 2 \times 4.7k) \times 3.51 \times 10^{-4}$$

$$= 6.81V$$

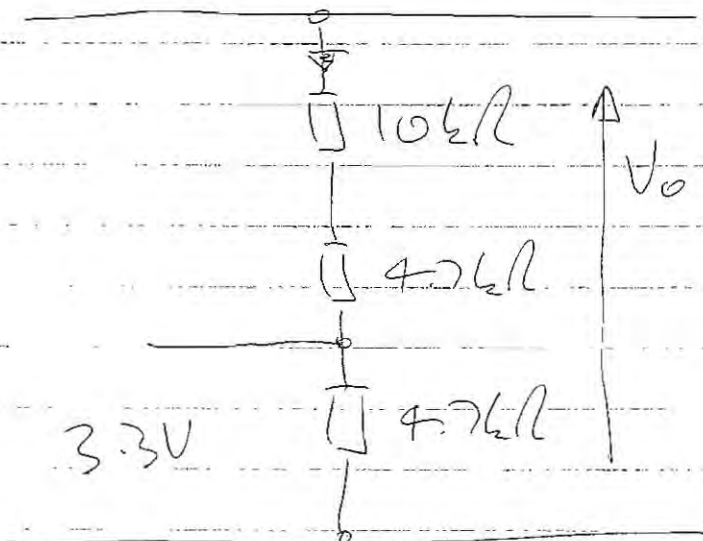 R_w wiper set to min

$$I = \frac{3.3}{4.7k} = 7.02 \times 10^{-4} A$$

$$V_o = R_{tot} \times I$$

$$= (10k + 2 \times 4.7k) \times 7.02 \times 10^{-4}$$

$$= 13.62V$$

$$\text{Max } V_o = 13.62V$$

$$\text{Min } V_o = 6.81V$$

b) Determine max value for R

Worst case is when V_i is minimum and V_o is maximum.

$$R = \frac{V_{i \min} - V_{o \max}}{I_{out} + I_s} = \frac{18 - 13.61}{0.04 + 0.01}$$

$$R = \underline{\underline{87.6 \Omega}}$$

c) Determine power dissipated in R

For short ckt all of V_i applied across R .

$$P_R = \frac{V_i^2}{R} = \frac{25^2}{87.6}$$

$$= \underline{\underline{7.13 W}}$$

For normal conditions P will be max when voltage across R is max.

$$P_R = \frac{(V_{i \max} - V_{o \min})^2}{R} = \frac{(25 - 6.81)^2}{87.6}$$

$$= \underline{\underline{3.77 W}}$$

d) Max power for T_1

$$P_{T_1} = I_{T_1} \times V_{T_1} = \frac{(V_i - V_o)}{R} V_o = \frac{V_i V_o}{R} - \frac{V_o^2}{R}$$


Need to find value of V_o that maximise P_{T_1}

$$\frac{dP_{Ti}}{dV_o} = \frac{V_i}{R} - \frac{2V_o}{R}$$

$$\therefore V_o = \frac{V_i}{2}, \text{ since } P_{Ti} \text{ is max when } V_i \text{ is max}$$

$$P_{Ti} = \left(\frac{V_{i\max} - V_{i\max}/2}{R} \right) \frac{V_{i\max}}{2}$$
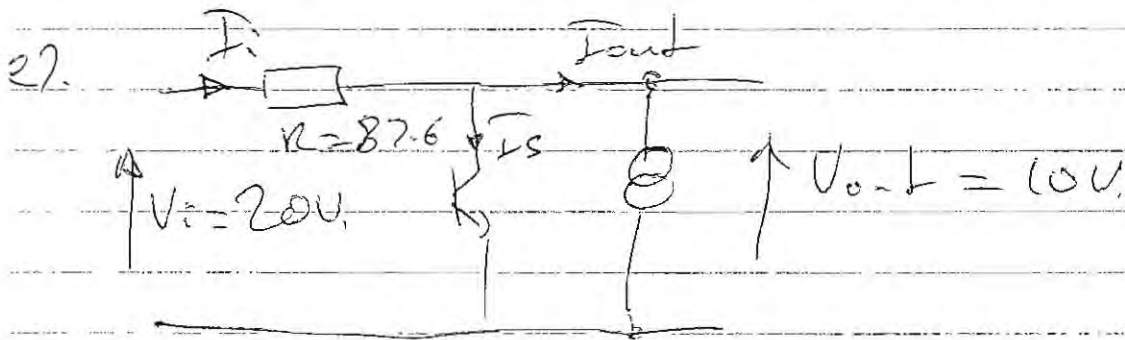
$$= \frac{25 - 12.5}{87.6} \times 12.5 = \underline{\underline{1.78W}}$$



$$I_i = \frac{20 - 10}{87.6} = 114.15 \text{ mA}$$

$$I_{out} = \frac{10}{500} = 20 \text{ mA}$$

$$I_s = I_i - I_{out} = 114.15 - 20 = 94.15 \text{ mA}$$

$$P_{Ti} = I_s \times V_o = 10 \times 94.15 \times 10^{-3} = 0.94 \text{ W}$$


$$P_R = \frac{10^2}{87.6} = 1.14 \text{ W}, \quad P_{out} = \frac{10^2}{500} = 0.2 \text{ W}$$

$$\text{Efficiency } \eta = \frac{P_{out}}{P_{out} + P_R + P_{Ti}} = \frac{0.2}{0.2 + 1.14 + 0.94} = 8.77\%$$

Q2.


a) Hysteresis is used to reduce a comparator's susceptibility to noise.
Applications include waveform zero crossing detection

b).

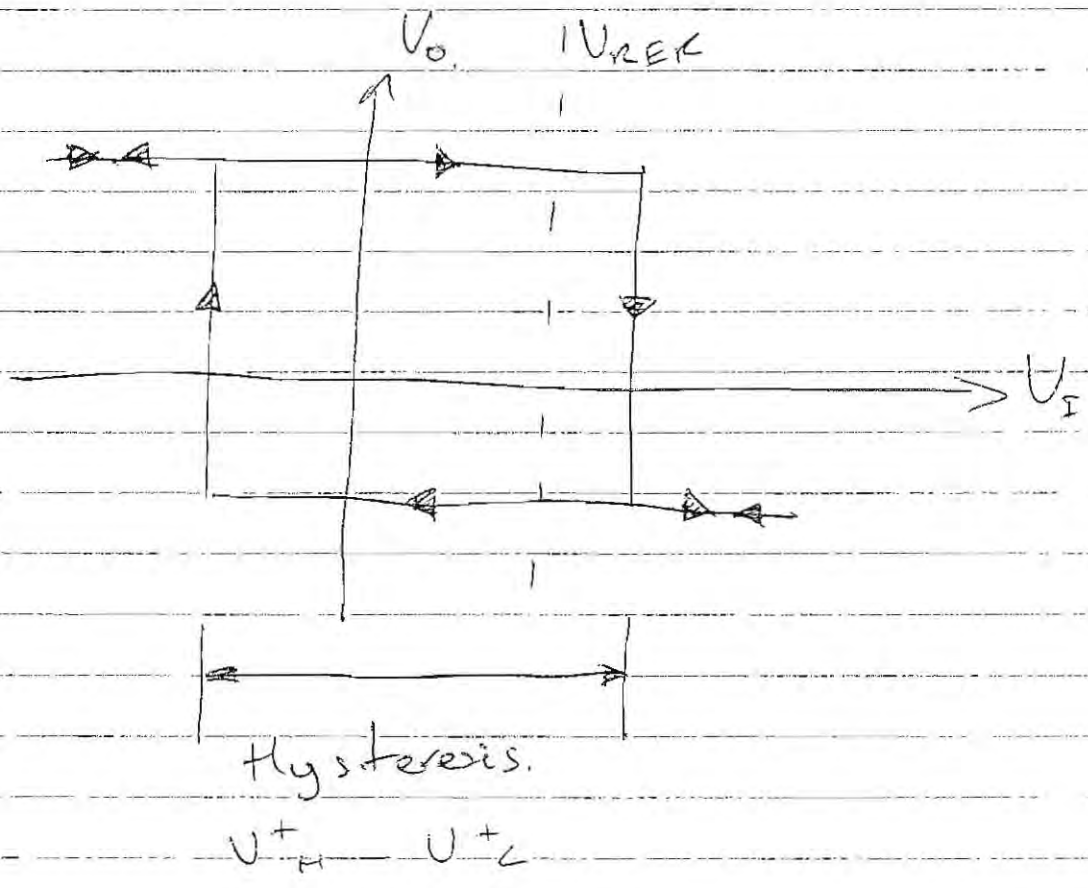

$$V^+_H = (V_{OH} - V_{REF}) \frac{R_1}{R_1 + R_2} + V_{REF}$$
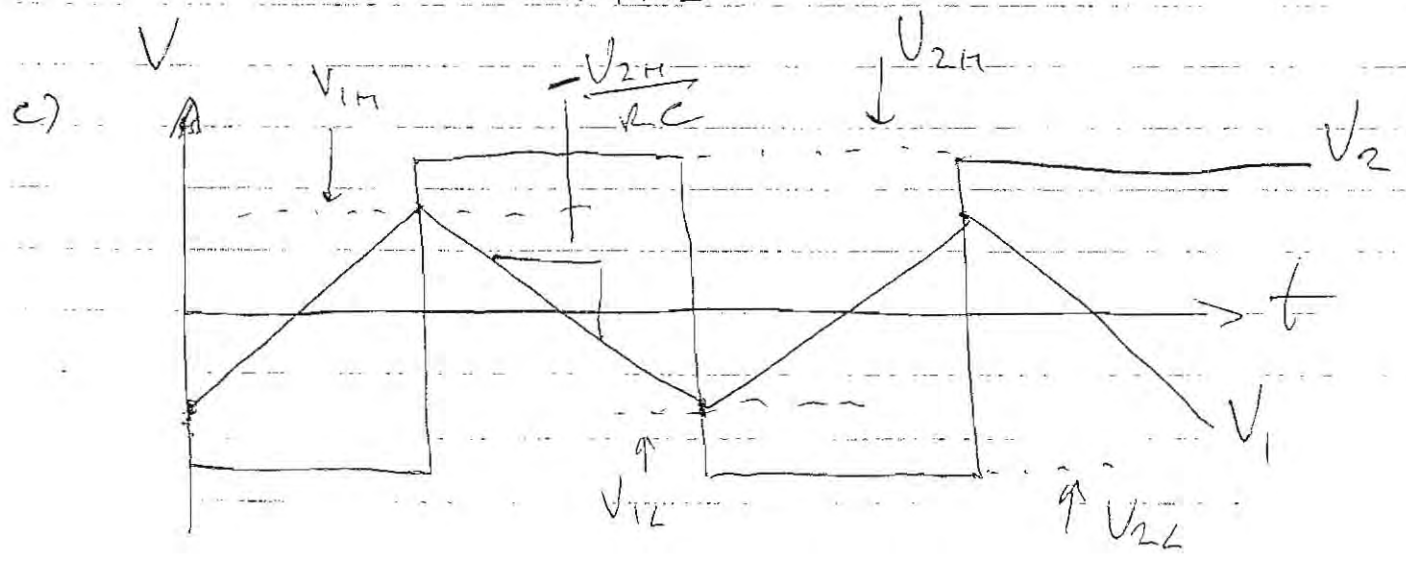
$$V^+_L = (V_{OL} - V_{REF}) \frac{R_1}{R_1 + R_2} + V_{REF}$$



(5)

d) A_1 is an inverting integrator and so V_1 travels from V_{1L} to V_{1H} at a rate of $-\frac{V_{2L}}{RC} \frac{V}{s}$.

A_2 will change state when $V^+ = 0$

$$V^+ = \frac{V_2 - V_1 \times R_1 + V_1}{R_1 + R_2} = 0$$

$$\text{Thus } V_{1L} = -\frac{R_1}{R_2} V_{2H} \text{ or } V_{1H} = -\frac{R_1}{R_2} V_{2L}$$

$$V_1(t) = -\frac{V_{2L}}{RC} t, \text{ so from } 0 \text{ to } V_{1H}.$$

$$V_{1H} = -\frac{V_{2L}}{RC} t_1 \quad \therefore \quad t_1 = -\frac{V_{1H} RC}{V_{2L}} = \frac{R_1}{R_2} RC$$

$$\text{The time taken for a half period } \frac{T}{2} = 2 \frac{R_1}{R_2} RC$$

$$\text{whole period is given by } T = 4 \frac{R_1}{R_2} RC$$

Thus the oscillation frequency is given by


$$f = \frac{R_1}{4 R_2 RC}$$

$$\text{With } f = 4 \text{ kHz, } RC = \frac{1}{4 \times 4000} = 6.25 \times 10^{-5} \text{ Sec.}$$

⑥

3.



a)

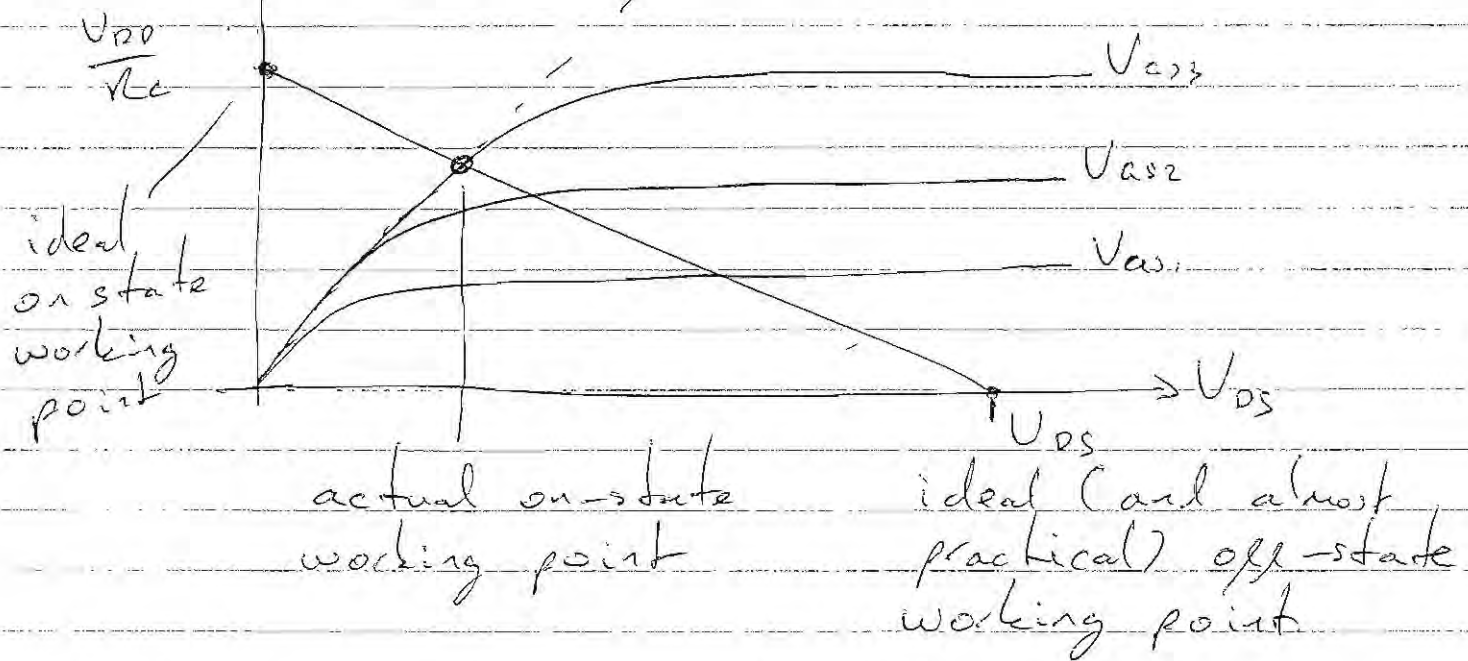

1 mark for V_{AS} characteristic
3 marks for operating points
1 mark for regions

b)

V_i

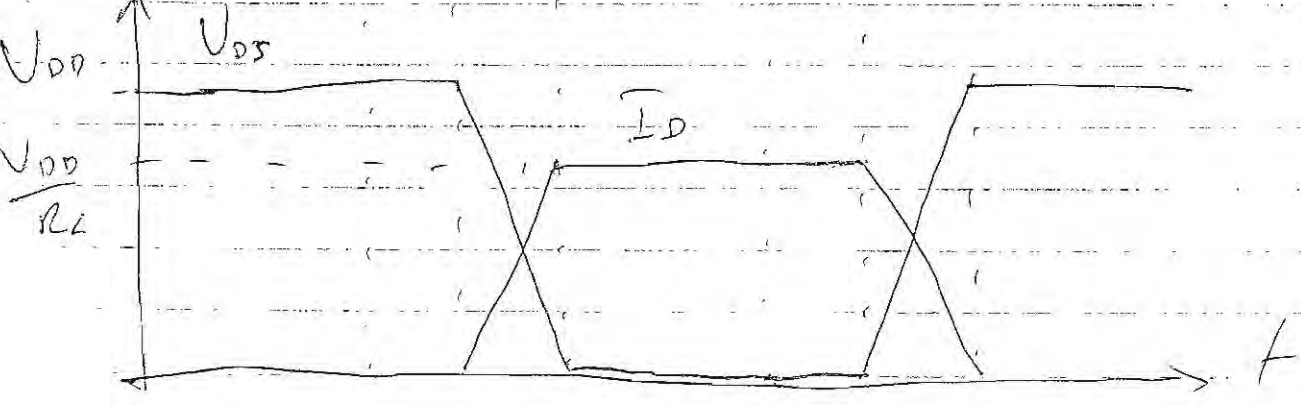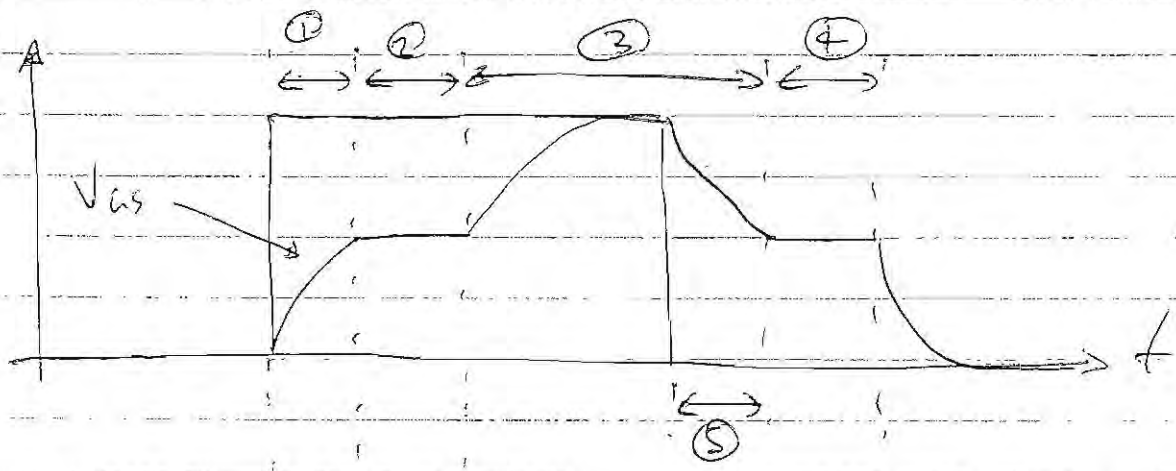


- ① turn-on delay t_{don}
- ② turn-on switching time t_{son}
- ③ on time t_{on}
- ④ turn-off switching time t_{soff}
- ⑤ turn-off delay t_{doff}

0.5 mark for each event time.

1 mark for each wave form.

0.5 mark for voltage and current label.

c). Turn on delay

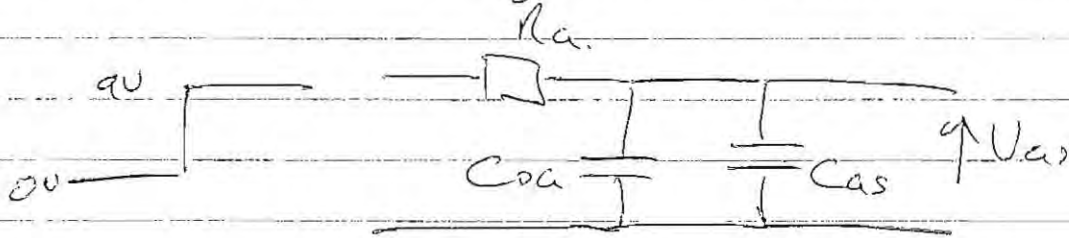

$$V_{gs}(t) = V_i (1 - e^{-\frac{t}{\tau}}) \quad \tau = R_a [C_{oa} + C_{as}]$$

$$= 23.94 \text{ ns}$$

$$V_{gs}(t_{don}) = V_{TH} = V_i (1 - e^{-\frac{t_{don}}{\tau}})$$

$$t_{don} = -\tau \ln \left[1 - \frac{V_{TH}}{V_i} \right] = \underline{\underline{140.07 \mu s}}$$

turn on switching time.

$$i_g = \frac{V_i - V_{TH}}{R_a} = C_{oa} \frac{dV_o}{dt} = C_{oa} \left(-\frac{V_{DD}}{t_{son}} \right)$$

$$\underline{\underline{t_{son} = 71.3 \mu s}}$$

d). The inclusion of the parallel diode resistor combination modifies the gate resistor value during turn-off.

$$R_{goff} = R_g || R = 45 \Omega$$

$$\tau_{off} = R_{goff} [C_{ou} + C_{as}] = 5.99 \text{ ns}$$

$$V_{gs}(t) = V_i e^{-\frac{t}{\tau}}$$

$$V_{TH} = V_i \times e^{-\frac{t_{doff}}{\tau_{off}}}$$

$$t_{doff} = -\tau_{off} \ln \left(\frac{V_{TH}}{V_i} \right) = 4.85 \text{ ns}$$


$$i_{goff} = \frac{V_{TH}}{R_{uoff}} = C_{ou} \frac{V_{DD}}{t_{soff}}$$

$$t_{soff} = 22.26 \text{ ns}$$


Q4

(9)

a) T_1 on

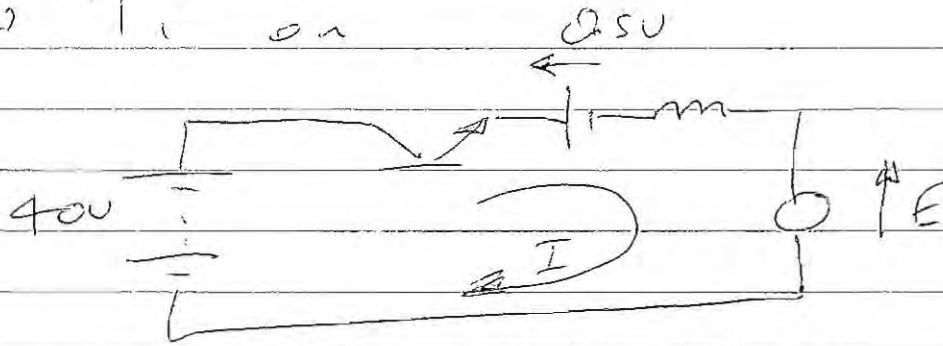

T_1 off

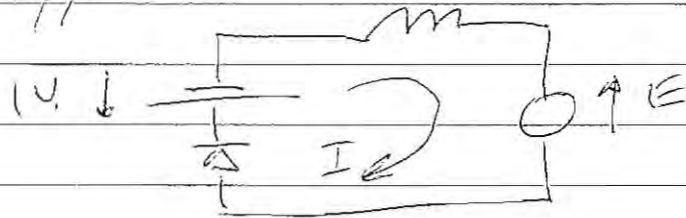

2.5 marks for each circuit.


b) $E = \Psi \omega = \text{average diode voltage} = V_{AV}$

$$\omega = \frac{2\pi}{60} \times 2000 = 209.44 \text{ rad/sec}$$

$$E = 0.071 \times 209.44 = 14.87 \text{ V}$$

$$V_{AV} = E = \frac{1}{T} \int V_{\text{diode}} dt = \frac{1}{T} \left[(V_{dc} - 0.5)t_{on} - (T - t_{on}) \right]$$
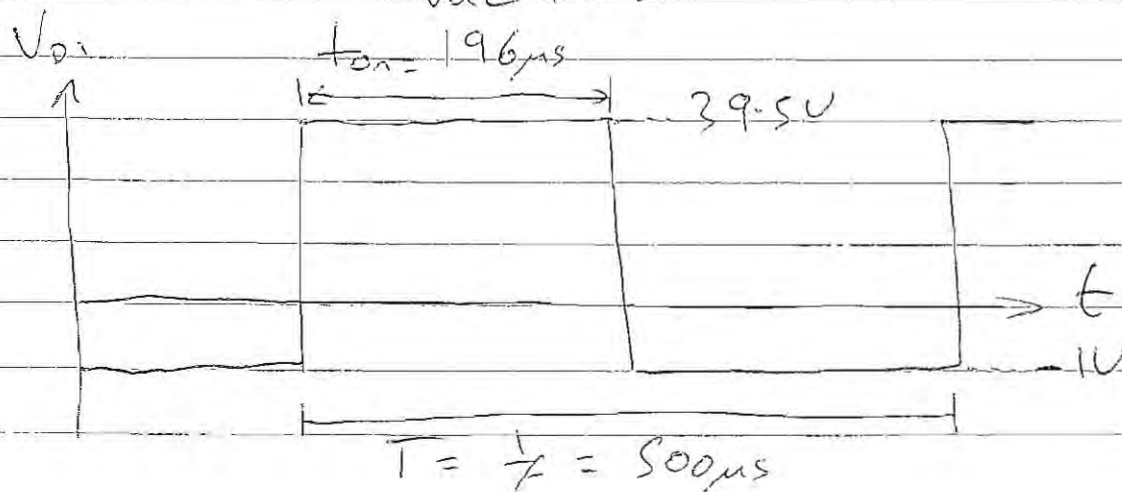
$$\therefore t_{on} = T \frac{E + 1}{V_{dc} + 0.5} = 195.93 \mu\text{s}$$



(10)


$$c) T_m = 4I = 0.15 = 0.071 I$$

$$I = \frac{0.15}{0.071} = \underline{\underline{2.11 A}} \text{ - average current}$$

The ripple superimposed on this is given by

$$V = L \frac{di}{dt}, \quad V_i - E = L \frac{\Delta I}{t_{on}}$$
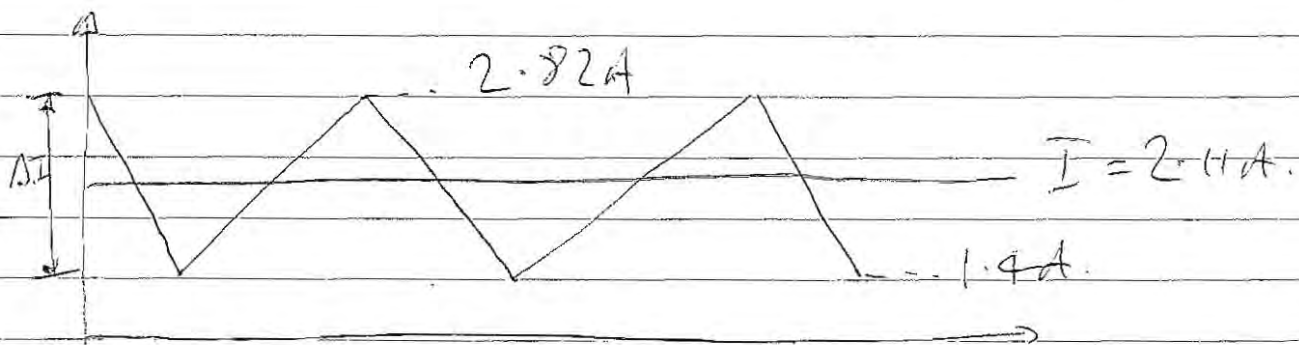
$$\text{Ripple} = \Delta I = \frac{t_{on}(V_i - E)}{L} = \frac{196 \times 10^{-6} (39.5 - 14.8)}{3.4 \times 10^{-3}} \\ = 1.419 A$$



$$I_{\text{average}} = 2.11 A, \quad I_{\text{max}} = 2.82 A, \quad I_{\text{min}} = 1.40 A.$$

$$d) E = 4\omega = 0.071 \times \frac{2\pi}{60} \times 1000 = 7.44 V$$

$$\text{Duty } \delta = \frac{t_{on}}{T} = \frac{E}{V_i} = \frac{7.44}{40} = 0.186$$

$$V_i - E = L \frac{\Delta I}{\delta T} \quad \therefore T = L \Delta I = 2.8 \times 10^{-4}$$

$$f = \frac{1}{T} = 3570 \text{ Hz}$$