

$$\frac{V_s}{I} = \frac{R + j\omega L}{1 - \omega^2 LC + j\omega CR}$$

$$\frac{V_s}{I} = \frac{(R + j\omega L)(1 - \omega^2 LC) - j\omega CR}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2}$$

looking at j terms in numerator product

$$j\omega L(1 - \omega^2 LC) - j\omega CR^2 = 0$$

This must be equated to zero

$$L - \omega^2 L^2 C - CR^2 = 0$$

lets find the  $\omega$  that will make j terms vanish

$$L - CR^2 = \omega^2 L^2 C$$

$$\frac{L}{L^2 C} - \frac{CR^2}{L^2 C} = \omega^2$$


$$\frac{1}{LC} - \frac{R^2}{L^2} = \omega^2$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Wein Bridge



look at parallel bit

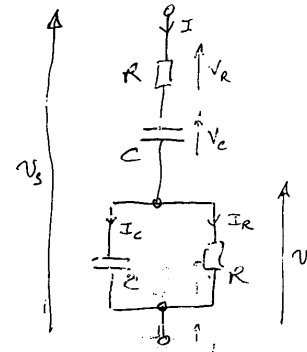


look at parallel bit

$$I = I_C + I_R$$

$$\frac{V_0}{\frac{1}{\omega C}} + \frac{V_0}{R}$$


$$V_0 \omega C + \frac{V_0}{R}$$

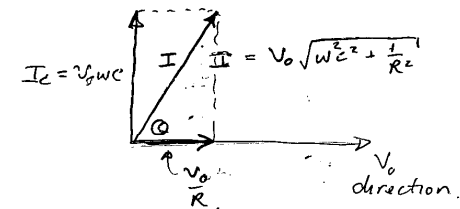

$$\phi = \tan^{-1} \frac{V_0 \omega C}{\frac{V_0}{R}} = \tan^{-1} \omega CR$$

for the whole ckt

$$V_0 + V_C + V_R = V_s$$

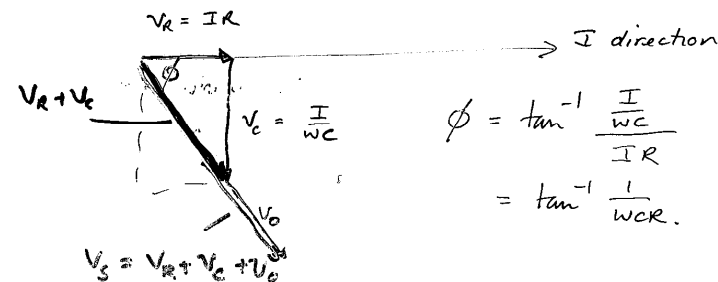

$$\phi = \tan^{-1} \frac{I \omega L}{I R}$$

$$= \tan^{-1} \frac{\omega L}{R}$$



$$\frac{V_o}{V_s} = \frac{\frac{R/j\omega C}{R + 1/j\omega C}}{R + \frac{1}{j\omega C} + \frac{R/j\omega C}{R + 1/j\omega C}}$$

$$= \frac{R}{1 + j\omega CR}$$

$$R + \frac{1}{j\omega C} + \frac{R}{1 + j\omega CR}$$

$$= \frac{\left[ \frac{R}{1 + j\omega CR} \right]}{\left[ \frac{(R + \frac{1}{j\omega C})(1 + j\omega CR) + R}{1 + j\omega CR} \right]}$$

$$= \frac{R}{R + \frac{1}{j\omega C} + j\omega CR^2 + R + R}$$

$$= \frac{R}{3R + j(\omega CR^2 - \frac{1}{\omega C})}$$

equating j terms to zero



$$j(\omega CR^2 - \frac{1}{\omega C}) = 0$$

$$\omega CR^2 = \frac{1}{\omega C} \quad \text{or} \quad \omega^2 CR^2 = 1$$

$$\text{or} \quad \omega^2 = \frac{1}{CR^2}$$


$$\text{or} \quad \omega = \frac{1}{CR}$$

$V_i$

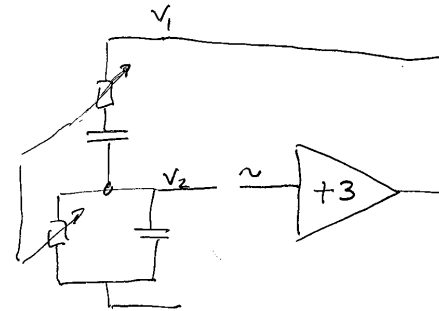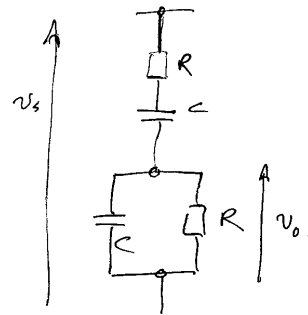

when phase shift = 0  $\frac{V_2}{V_1} = \frac{1}{3}$

Polar + Cartesian Representations:

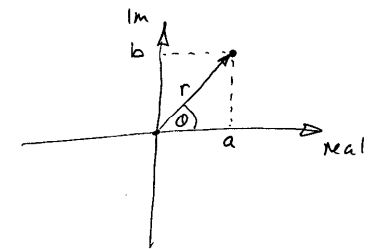

Cartesian approach  $\Rightarrow a + jb$

Polar approach  $\Rightarrow (r \angle \phi)$   
 $(re^{j\phi})$

If I want to add two quantities together  
 cartesian is more convenient.

$$(a+jb) + (c+jd) = (a+c) + j(b+d)$$

If I want to divide two quantities

$$\frac{r_1 \angle \theta_1}{r_2 \angle \theta_2} = \frac{r_1 e^{j\theta_1}}{r_2 e^{j\theta_2}}$$

$$\text{but } \frac{1}{e^{j\theta_2}} = e^{-j\theta_2}$$

$$\begin{aligned} \frac{r_1 e^{j\theta_1}}{r_2 e^{j\theta_2}} &= \frac{r_1}{r_2} e^{j\theta_1} e^{-j\theta_2} \\ &= \frac{r_1}{r_2} e^{j(\theta_1 - \theta_2)} \\ &\equiv \frac{r_1}{r_2} \angle (\theta_1 - \theta_2) \end{aligned}$$


complicated.

$$\frac{a+jb}{c+jd} = \frac{(a+jb)(c-jd)}{(c+jd)(c-jd)} = \frac{ac+bd+j(bc-ad)}{c^2+d^2}$$

to switch between polar + cartesian

$$a = r \cos \alpha \quad b = r \sin \alpha$$
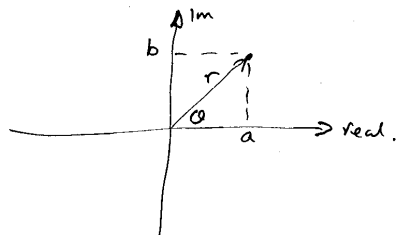
$$r^2 = a^2 + b^2 \quad \alpha = \tan^{-1} \frac{b}{a}$$



### Power with a.c

$$\text{Power integral } P = \frac{1}{T} \int_0^T V(t) I(t) dt$$

$$\text{— here } V(t) = V_p \sin \omega t$$

$$P = \frac{1}{T} \int_0^T V_p \sin \omega t \frac{V_p}{R} \sin \omega t dt$$

$$= \frac{1}{R} \cdot \frac{V_p^2}{T} \int_0^T \sin^2 \omega t dt$$

$$= \frac{1}{R} \times \text{mean squared voltage}$$

$$= \frac{1}{R} \frac{V_p^2}{T} \int_0^T \frac{1 - \cos 2\omega t}{2} dt$$

$$= \frac{1}{R} \frac{V_p^2}{T} \left[ \frac{t}{2} - \frac{1}{4\omega} \sin 2\omega t \right]_0^T$$


$$\omega = 2\pi f \quad f = \frac{1}{T}$$

$$\omega = \frac{2\pi}{T} \quad \text{or } T = \frac{2\pi}{\omega}$$

$$= \frac{1}{R} \frac{V_p^2}{T} \left[ \frac{2\pi}{2\omega} - \frac{1}{4\omega} \sin \cancel{\omega 2\pi} - 0 - 0 \right]$$


$$= \frac{1}{R} V_p^2 \frac{\omega}{2\pi} \left[ \frac{2\pi}{2\omega} \right]$$

1.2 1

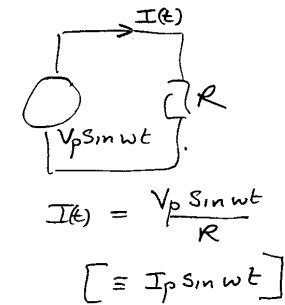

$$= \frac{V_p^2}{2} \cdot \frac{1}{R}$$
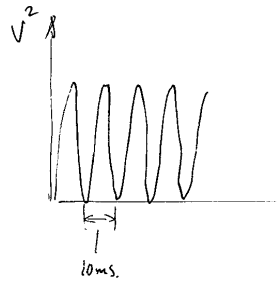
$$= \frac{V_{rms}^2}{R} \quad V_{rms} = \sqrt{\frac{V_p^2}{2}} = \frac{V_p}{\sqrt{2}} \text{ for a sinusoid.}$$



What if

$$V = V_p \sin \omega t$$

$$I = I_p \sin(\omega t + \phi)$$

$$\frac{V_p}{I_p} = |Z|$$

Power integral becomes

$$P = \frac{1}{T} \int_0^T V_p \sin \omega t \cdot I_p \sin(\omega t + \phi) dt$$

$$= \frac{V_p I_p}{T} \int_0^T \sin \omega t \cdot \sin(\omega t + \phi) dt$$

$$2 \sin A \sin B = \cos(A-B) - \cos(A+B)$$

$$= \frac{V_p I_p}{2T} \int_0^T [\cos \omega t - (\omega t + \phi) - \cos(\omega t + \omega t + \phi)] dt$$

answer is

$$P = V_{rms} I_{rms} \cos \phi$$

$$= \frac{V_p I_p}{2} \cos \phi$$

$$= \frac{V_{rms}^2}{|Z|} \cos \phi$$

↑  
power factor

Power dissipation with more than one source.  
with 2 dc sources.

$$V = V_{dc1} + V_{dc2}$$

$$P \propto \overline{V^2} \text{ ie } \propto \overline{(V_{dc1} + V_{dc2})^2}$$

$$\propto \overline{V_{dc1}^2} + 2\overline{V_{dc1} V_{dc2}} + \overline{V_{dc2}^2}$$

with 1 dc source + 1 ac source

$$V = V_{dc1} + V_p \sin \omega t$$

$$P \propto \overline{(V_{dc1} + V_p \sin \omega t)^2}$$



$$P \propto \underbrace{\overline{V_{dc1}^2}}_A + \underbrace{2\overline{V_{dc1} V_p \sin \omega t}}_{=0} + \underbrace{\overline{V_p^2 \sin^2 \omega t}}_A$$

Resonance


— occurs when a reactive network has a purely resistive behaviour — ie at a



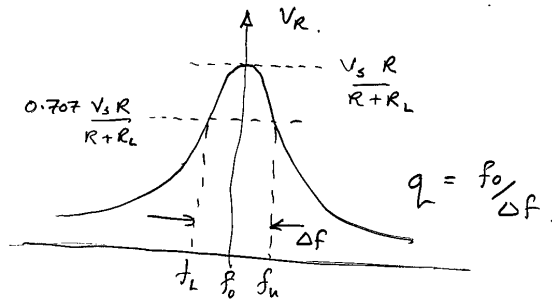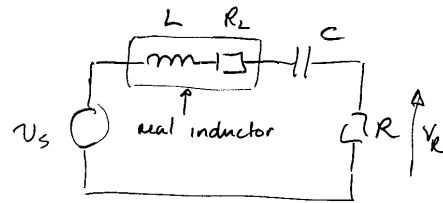Inductors usually have some series resistance.



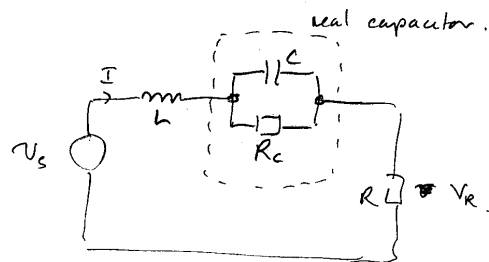Capacitors main problem is parallel resistance — mostly caused by dielectric losses



$$Z = \frac{V_s}{I} = j\omega L + \frac{R_C / j\omega C}{1} + R$$

$$\begin{aligned} Z &= \frac{V_s}{I} = j\omega L + \frac{R_C / j\omega C}{1 + j\omega C R_C} + R \\ &= j\omega L + \frac{R_C}{1 + j\omega C R_C} + R \\ &= \frac{j\omega L - \omega^2 L C R_C + R_C + R + j\omega C R R_C}{1 + j\omega C R_C} \\ &= \frac{j\omega(L + C R R_C) + (R + R_C - \omega^2 L C R_C)}{1 + j\omega C R_C} \\ &= \frac{[(R + R_C - \omega^2 L C R_C) + j\omega(L + C R R_C)](1 - j\omega C R_C)}{1 + \omega^2 C^2 R_C^2} \end{aligned}$$

$$j\omega(L + C R R_C - C R_C(R + R_C - \omega^2 L C R_C)) = 0$$

to make j terms disappear

$$L + C R R_C = C R_C(R + R_C - \omega^2 L C R_C)$$

$$L + C R R_C = C R R_C + C R_C^2 - \omega^2 L C^2 R_C^2$$



$$\therefore \omega^2 L C^2 R_C^2 = C R_C^2 - L$$

$$\therefore \omega^2 = \frac{\cancel{L C}^{\cancel{L C}}}{\cancel{L C}^{\cancel{L C}} \cancel{R_C}^{\cancel{R_C}}} = \frac{1}{LC} - \frac{1}{C^2 R_C^2}$$

— it's the process that matter

... ..


## Parallel Resonance.

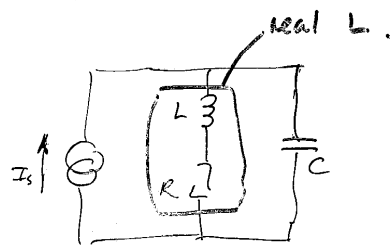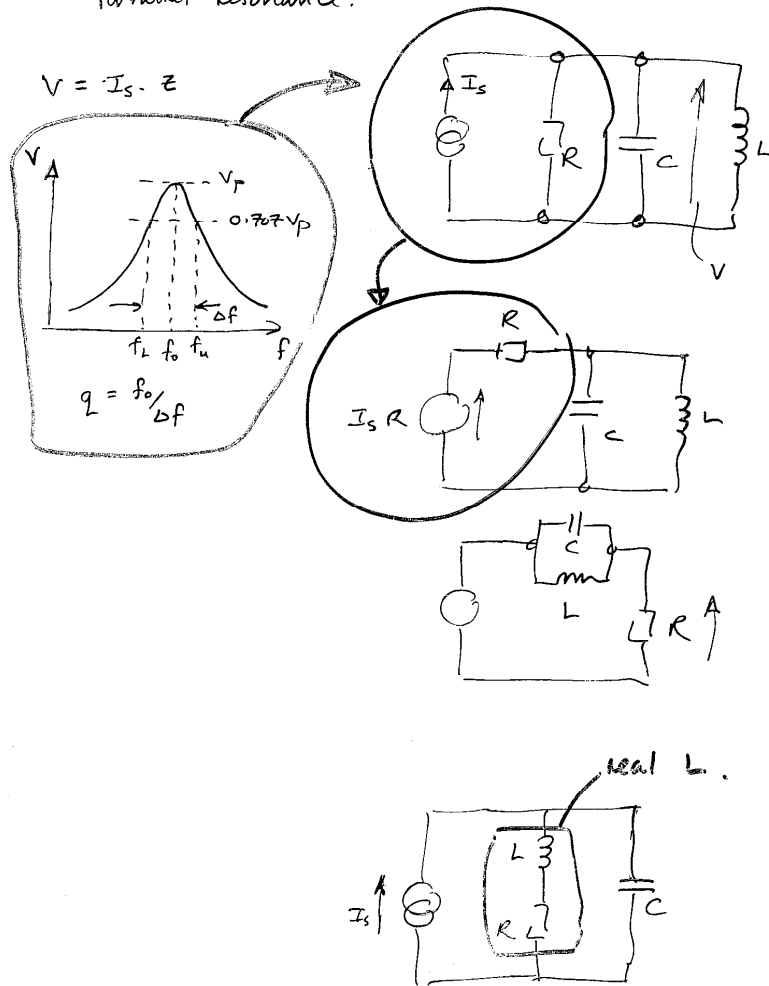

$$\omega_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

Transient behaviour of circuits

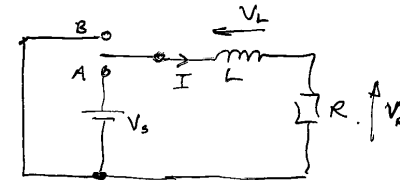Lets assume that switch has been in position A for a long time



~at  $t=0$  we switch it to B. How does  $I$  change with time for  $t>0$ .

$$V_L = L \frac{dI}{dt} \quad V_R = IR$$

$$V_B = V_L + V_R$$

$$\text{or } 0 = L \frac{dI}{dt} + IR$$

$$-IR = L \frac{dI}{dt}$$

$$-\frac{R}{L} dt = \frac{dI}{I}$$

$$-\frac{R}{L} t + C = \ln I$$

$$e^{(-\frac{R}{L} t + C)} = I$$


$$e^{-\frac{R}{L} t} \cdot e^C =$$

$$A e^{-\frac{R}{L} t} = I$$

$$\text{when } t=0 \quad I = V_s / R$$

$$\therefore I = \frac{V_s}{R} e^{-\frac{Rt}{L}} = \frac{V_s}{R} e^{-\frac{t}{\tau}}$$


Transient behaviour of circuits

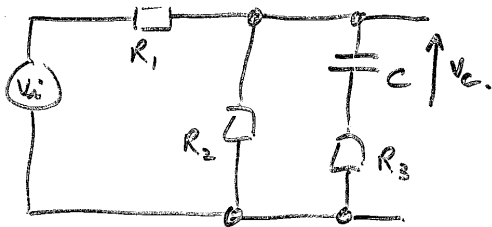

at  $t=0^-$   $V_c = V_1 \frac{R_2}{R_2+R_1}$  since  $I_c = 0$

at  $t=0^+$   $V_c = V_1 \frac{R_2}{R_2+R_1}$  since C will not allow its terminal voltage to change in zero time.


equivalent circuit at  $t=0^+$  is.

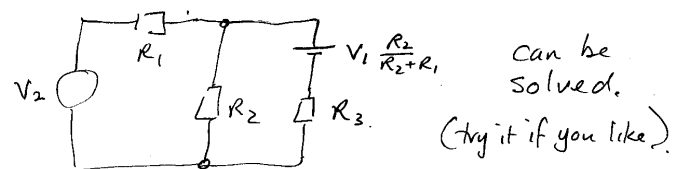

What happens at  $t \Rightarrow \infty$ ?



— same situation as at  $t=0^-$  except that the ckt is driven by  $V_2$ .

$$V_c = V_2 \frac{R_2}{R_1+R_2}$$

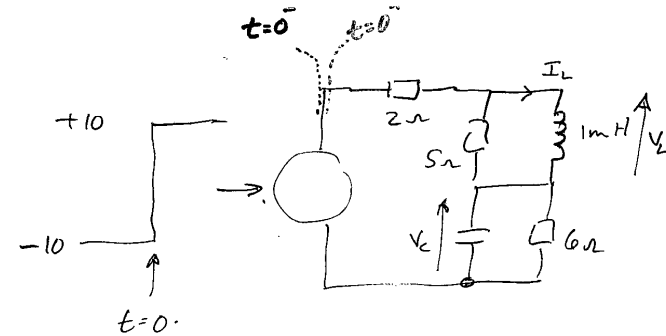

at  $t=0^-$   $V_L = 0$ ,  $I_L = -\frac{10}{8} = -1.25 A$ .

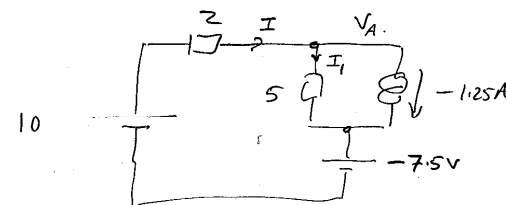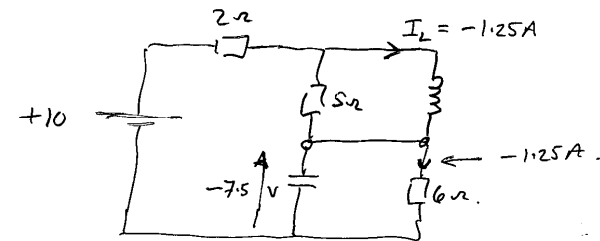$V_c = -7.5 V$ . (= voltage developed across the  $6\Omega$ .)




$$I = I_1 + (-1.25 A)$$

$$\frac{10 - V_A}{2} = \frac{V_A - (-7.5)}{5} + (-1.25)$$



$$+1.25 + \frac{10}{2} - \frac{7.5}{5} = \frac{V_A}{5} + \frac{V_A}{2} = \frac{7V_A}{10}$$
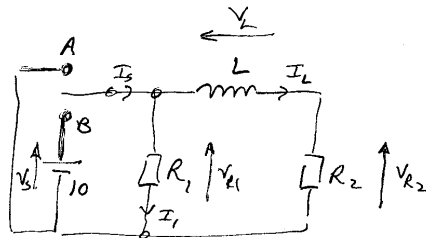
$$1.25 + 5 - 1.5 = \frac{7V_A}{10} \quad V_A = \frac{47.5}{7} \approx 6.8 \text{ V.}$$



Assume switch has been in position A for a long time  $\rightarrow$  then suddenly switched to B

$$V_s = V_L + V_{R2}$$

$$V_s = L \frac{dI_L}{dt} + I_L R_2$$

$$\frac{V_s}{L} = \frac{dI_L}{dt} + I_L \frac{R_2}{L}$$

$$\frac{V_s}{L} - I_L \frac{R_2}{L} = \frac{dI_L}{dt}$$

$$dt = \frac{dI_L}{\frac{1}{L}(V_s - I_L R_2)}$$

$$dt = \frac{dI_L}{\frac{R_2}{L}(\frac{V_s}{R_2} - I_L)}$$

$$-\frac{R_2}{L} dt = \frac{dI_L}{I_L - \frac{V_s}{R_2}}$$

$$+ C e^{-\frac{R_2}{L}t} = \ln(I_L - \frac{V_s}{R_2})$$

$$e^{(C - \frac{R_2}{L}t)} = I_L - \frac{V_s}{R_2}$$


$$A e^{-\frac{R_2}{L}t} = I_L - \frac{V_s}{R_2}$$

$$\text{When } t=0^+ \quad I_L = 0$$

$$\therefore A = 0 - \frac{V_s}{R_2}$$

$$\therefore -\frac{V_s}{R_2} e^{-\frac{R_2}{L}t} = I_L - \frac{V_s}{R_2}$$

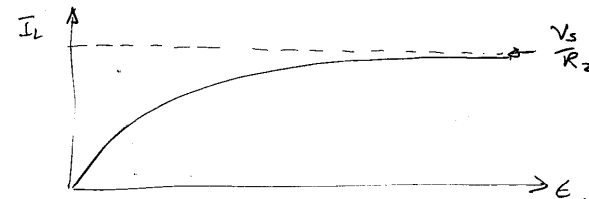
$$\frac{V_s}{R_2} (1 - e^{-\frac{R_2}{L}t}) = I_L$$





key integral...

$$\int \frac{dx}{a+bx} = \frac{1}{b} \ln(a+bx)$$

Admittance Conductance + Susceptance.

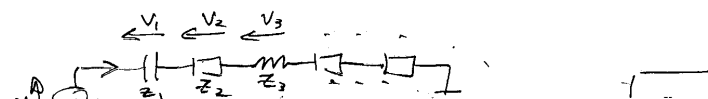

Admittance Conductance + Susceptance.

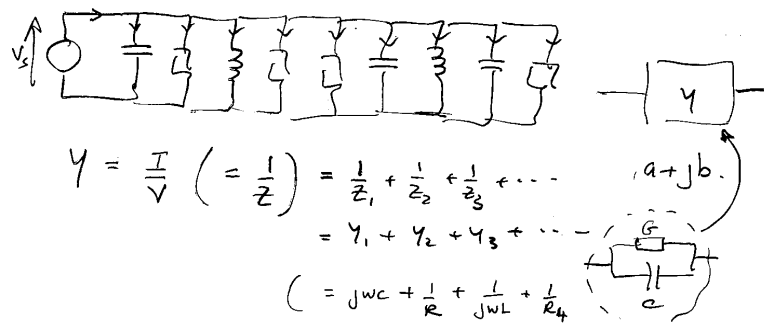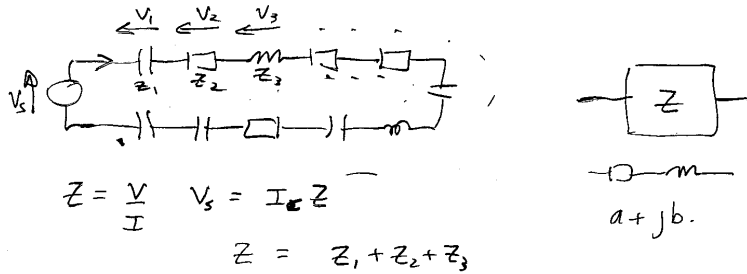

Filter circuits


$$i = \frac{V_s}{Z}$$

$$V_o = R i = \frac{V_s R}{Z}$$

$$Z = j\omega L + R$$

$$V_o = V_s \cdot \frac{R}{R + j\omega L}$$



$$\text{so } \frac{V_o}{V_s} = \frac{R}{R + j\omega L} = \frac{R/R}{R/R + j\omega L/R} = \frac{1}{1 + j\omega L/R}$$

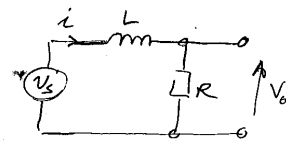 $\tau = \text{time constant}$  $\tau = \text{time constant}$ 

$$\text{Let } \omega_0 = \frac{1}{\tau R}$$

frequency domain constant related to time constant.

$$\text{so } \frac{V_o}{V_s} = \frac{1}{1 + j\omega/\omega_0} = \frac{1}{1 + j f/f_0}$$

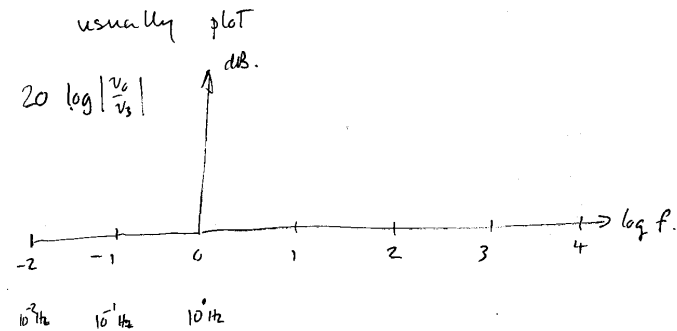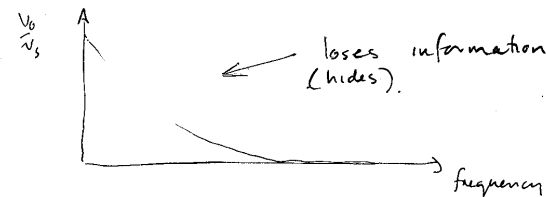
 $\log |V_o/V_s|$  usually expressed as dB or decibels

$$\boxed{\text{gain in dB} = 20 \log |V_o/V_s|} \left[ = 10 \log \frac{P_o}{P_i} \right]$$

or  $20 \log |V_o/V_s|$  or  $10 \log \frac{P_o}{P_i}$

$$\left[ \text{or } 20 \log \left[ \frac{V_o}{V_{ref}} \right] \right] \text{ or } 10 \log \frac{P_o}{P_{ref}}$$

$$\text{dBV} = 20 \log \left| \frac{V}{V_{rms}} \right|$$

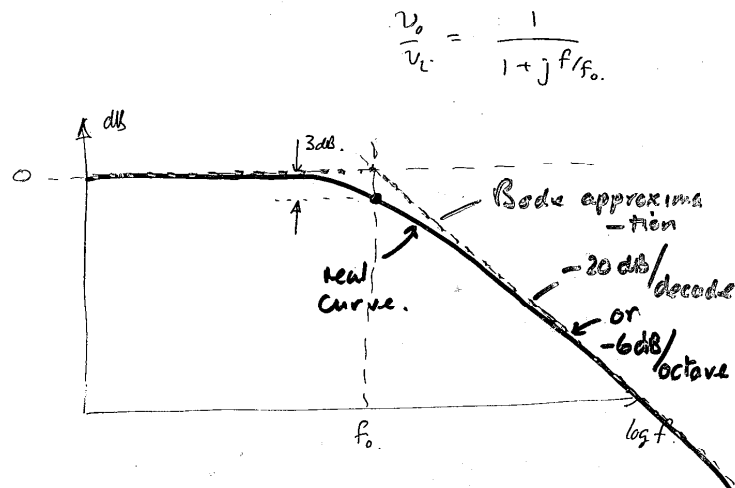

$$\left| \frac{V_o}{V_i} \right| = \left| \frac{1}{1 + j f/f_o} \right| = \left[ \frac{1}{1 + (f/f_o)^2} \right]^{1/2}$$

if  $f \ll f_o$   $\left| \frac{V_o}{V_i} \right| \Rightarrow 1$  as  $f \rightarrow 0$ .


if  $f = f_o$   $\left| \frac{V_o}{V_i} \right| = \left[ \frac{1}{2} \right]^{1/2} = \frac{1}{\sqrt{2}}$   
 $20 \log \frac{1}{\sqrt{2}} \approx -3 \text{ dB}$

if  $f \gg f_o$   $\left| \frac{V_o}{V_i} \right| \Rightarrow \frac{f_o}{f}$  as  $f \Rightarrow \infty$

$\phi$   
(linear scale)

$f_o$

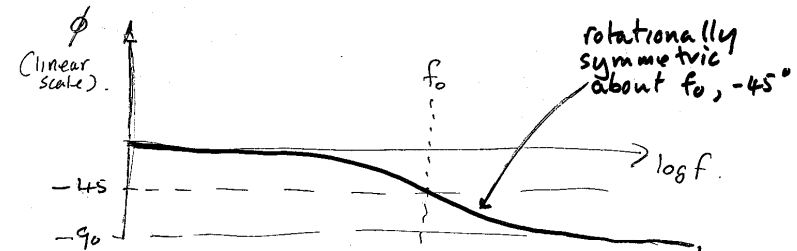rotationally  
symmetric  
about  $f_o, -45^\circ$




$$\phi \left[ \frac{1}{1 + j f/f_o} \right] \text{ is } -\tan^{-1} f/f_o$$

if  $f \ll f_o$   $\phi = -\tan^{-1}(\text{a small number}) \Rightarrow 0$   
-ie  $\ll 1$  from below

if  $f = f_o$   $\phi = -\tan^{-1} 1 = -45^\circ$

if  $f \gg f_o$   $\phi = -\tan^{-1}(\text{a large no.}) \Rightarrow -90$   
ie  $\gg 1$  from above

Another first order low pass

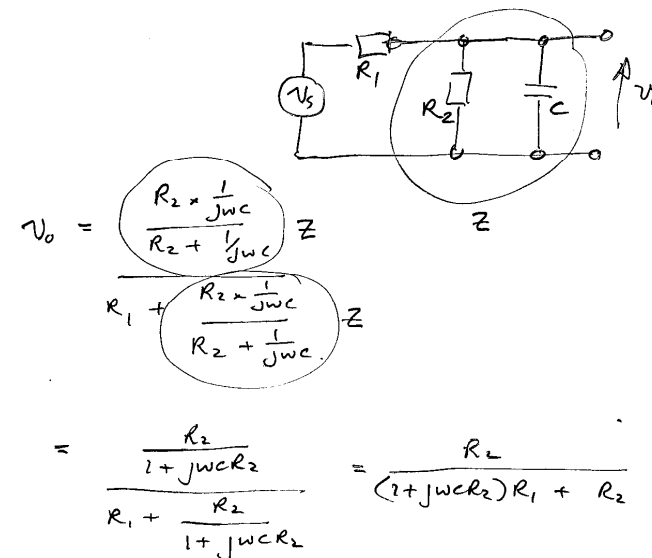

$$= \frac{R_2}{R_1 + j\omega C R_2 R_1 + R_2} = \frac{R_2}{(R_1 + R_2) + j\omega C R_1 R_2}$$

$\nearrow$   
 need to  
 force this  
 to unity.

$$= \frac{R_2}{(R_1 + R_2) \left( 1 + j\omega \frac{C R_1 R_2}{R_1 + R_2} \right)}$$

$$= \underbrace{\left( \frac{R_2}{R_1 + R_2} \right)}_k \frac{1}{1 + j\omega/\omega_0}$$

$$\omega_0 = \frac{1}{\left( \frac{C R_1 R_2}{R_1 + R_2} \right)}$$

$$20 \log \left| k \cdot \frac{1}{1 + j\omega/\omega_0} \right|$$

$$= 20 \log k + 20 \log \left| \frac{1}{1 + j\omega/\omega_0} \right|$$