

## MEC 316 Tutorial Sheet 2 Solutions

1) Each cell generates current  $I_1, I_2$

$$\text{Total } I = I_1 + I_2 = I_{d1} - I_{L1} + I_{d2} - I_{L2}$$

Voltages across both cells have to be identical for parallel cell configuration, so:

$$\begin{aligned} I &= I_{01} [\exp(eV/kT) - 1] - I_{L1} + I_{02} [\exp(eV/kT) - 1] - I_{L2} \\ &= (I_{01} + I_{02}) [\exp(eV/kT) - 1] - (I_{L1} + I_{L2}) \end{aligned}$$

Under open circuit condition,  $I = 0$  and exponent term  $\gg 1$ ,

$$\therefore \exp(eV_{oc}/kT) \approx \frac{I_L}{I_0}$$

$$V_{oc} \approx \frac{kT}{e} \ln\left(\frac{I_L}{I_0}\right)$$

Under short circuit,  $V = 0$ ,  $I_L = -(I_{L1} + I_{L2}) = -2.8 \text{ A}$

Need  $I_{01}$  and  $I_{02}$

$$\text{Cell 1 : } 0.6 \approx \frac{kT}{e} \ln\left(\frac{1.5}{I_{01}}\right) \Rightarrow I_{01} = 5.66 \times 10^{-11} \text{ A}$$

$$\text{Cell 2 : } 1.2 \approx \frac{kT}{e} \ln\left(\frac{1.3}{I_{02}}\right) \Rightarrow I_{02} = 1.85 \times 10^{-21} \text{ A}$$

$$\therefore V_{oc} \approx \frac{kT}{e} \ln\left(\frac{2.8}{5.66 \times 10^{-11}}\right) = 0.615 \text{ V}$$

$$\text{Equation for array is : } I = 5.66 \times 10^{-11} [\exp(eV/kT) - 1] - 2.8$$

V(V)	:	0.1	0.2	0.3	0.4	0.45	0.5	0.53	0.55
I(A)	:	2.8	2.8	2.8	2.8	2.79	2.77	2.71	2.60
Power(W)	:	0.28	0.56	0.84	1.12	1.26	1.39	1.44	1.43

$$\text{Maximum power} = 1.44 \text{ W}$$

$$2) \quad I = I_0 [\exp(eV/kT) - 1] - I_L$$

$$I = \text{current through resistor} = -\frac{V}{R} = -\frac{0.5}{2} = -0.25 \text{ A}$$

substituting and rearranging equation gives:

$$I_L = 2 \times 10^{-10} [\exp(e \cdot 0.5/kT) - 1] + 0.25 = 0.347 \text{ A}$$

$$V_{oc} = \frac{kT}{e} \ln \left( \frac{I_L}{I_0} + 1 \right) \approx \frac{kT}{e} \ln \left( \frac{I_L}{I_0} \right) = 0.025 \times 21.27 \\ = 0.532 \text{ V}$$

$$\text{Power} = V \cdot I = 0.5 \times 0.25 = 0.125 \text{ W}$$

$$V_{oc} \times I_{sc} = 0.532 \times 0.347 = 0.184 \text{ W}$$

$$\text{Fill factor} = \frac{\text{Power}}{V_{oc} \times I_{sc}} = \frac{0.125}{0.184} = 0.68$$

This is a reasonable fill factor, so  $2 \Omega$  load is close to optimum

When the temperature decreases,  $I_0$  decreases, hence  $V_{oc}$  would increase. The minority carrier diffusion length would also increase slightly, so  $I_L$  would increase. The higher  $V$  and larger  $I$  will result in more power being developed by the cell.

3) Power =  $V \times I = V I_0 [\exp(eV/kT) - 1] - V I_L$

Maximum in power occurs when  $\frac{dP}{dV} = 0$  and  $V = V_m$

so we get,

$$\left(1 + \frac{eV_m}{kT}\right) \times \exp(eV_m/kT) = \frac{I_L}{I_0} + 1$$

since  $V_m \gg kT/e$  and  $\frac{I_L}{I_0} \gg 1$  and  $I_L = I_{sc}$

$$\ln\left(\frac{eV_m}{kT}\right) \approx \ln\left(\frac{I_{sc}}{I_0}\right) - \frac{eV_m}{kT}$$

$I_0 = 10^{-10} \text{ A}$  and  $I_{sc} = 50 \text{ mA}$ , assume  $\frac{kT}{e} = 25 \text{ mV}$

$$\ln\left(\frac{V_m}{0.025}\right) - \left(\frac{V_m}{0.025}\right) \approx \ln\left(\frac{50 \times 10^{-3}}{10^{-10}}\right) = 20.03$$

Substituting different values for  $V_m$  in L.H.S. of above gives 20.89 for  $V_m = 0.45$ , so good enough

$$I_{max} = I_0 [\exp(e \cdot 0.45/kT) - 1] - I_L = 43.44 \text{ mA}$$

$$\text{Max. Power} = V_m \times I_{max} = 19.5 \text{ mW}$$

Cell develops maximum power when optimum  $R$  (load) is chosen, so  $R = \frac{V_m}{I_{max}} = 0.45 / 43.44 \times 10^{-3} = 10.36 \Omega$

$$V_{oc} \approx \frac{kT}{e} \ln\left(\frac{I_L}{I_0}\right) = 0.025 \times \ln(5 \times 10^8) = 0.5 \text{ V}$$

$$I_{sc} \times V_{oc} = 0.025 \text{ W}$$

$$\therefore \text{Fill factor} = \frac{19.5}{25} = 0.78 \text{ i.e., a good high value.}$$

$$4) \quad V_{oc} = \frac{kT}{e} \ln\left(\frac{I_L}{I_0} + 1\right), \quad \frac{kT}{e} = 0.025V \text{ at } RT, \quad V_{oc} = 0.5V$$

$$I_0 = 2 \times 10^{-10} A$$

substituting into above gives,  $I_L = 97 \text{ mA}$

$$\text{Load current, } I = I_d - I_L = I_0 [\exp(eV/kT) - 1] - I_L$$

$I$  at  $V = 0.45V$  given by

$$I = 2 \times 10^{-10} [\exp(0.45/0.025) - 1] - 0.097 = 84 \text{ mA}$$

$$\text{Power} = VI = 0.45 \times 0.084 = 37.8 \text{ mW}$$

$$\text{Efficiency} = \frac{P_{out}}{P_{in}} \times 100\%$$

$$P_{in} = \text{area of cell} \times 1 \text{ kW}$$

$$\text{Eff.} = \frac{37.8 \times 10^{-3}}{(25 \times 10^{-3})^2 \times 1000} = 6\%$$

5) For cells in parallel equations, see Question 1.

First need  $I_0$  for each cell.

$$\text{Si cell: } V_{oc} = 0.7 = \frac{kT}{e} \ln\left(\frac{1.4}{I_0}\right) \Rightarrow I_0 = 9.68 \times 10^{-13} A$$

$$\text{HGaAs cell: } V_{oc} = 1.0 = \frac{kT}{e} \ln\left(\frac{1.3}{I_0}\right) \Rightarrow I_0 = 5.52 \times 10^{-18} A$$

For array under short circuit conditions,

$$V = 0, \quad I_{sc} = -1.4 - 1.3 = -2.7 A$$

Under open circuit conditions,  $I = 0$

$$2.7 = 5.52 \times 10^{-18} [\exp(eV_{oc}/kT) - 1] + 9.68 \times 10^{-13} [\exp(eV_{oc}/kT) - 1]$$

$$2.7 \approx 9.68 \times 10^{-13} [\exp(eV_{oc}/kT) - 1]$$

$$V_{oc} \approx 0.716 V$$

I-V of array is therefore

$$I = [9.68 \times 10^{-13} + 5.52 \times 10^{-18}] [\exp(eV/kT) - 1] - 2.7 \text{ A}$$

$$\text{Power} = V \times I$$

V(V)	:	0	0.2	0.4	0.55	0.6	0.65	0.7
I(A)	:	2.7	2.7	2.7	2.7	2.68	2.51	1.3
Power(W)	:	0	0.54	1.08	1.485	1.608	1.631	0.91

Maximum power is  $\sim 1.631 \text{ W}$

$$\text{Fill factor} = \frac{\text{Max. Power}}{V_{oc} \times I_{sc}} = \frac{1.631}{0.716 \times 2.7} = 0.84$$

6) See question 3 for first part.

$$I_{sc} = 100 \text{ mA}, \quad I_0 = 10^{-9} \text{ A}$$

$$\left(1 + \frac{eV_m}{kT}\right) \exp\left(\frac{eV_m}{kT}\right) = 1 + \frac{I_{sc}}{I_0}$$

substitute values for  $V_m$  until above is approx. true

$V_m = 0.4$  gives L.H.S.  $\approx$  R.H.S.

For max. power, we need max. current,

$$I_{max} = 10^{-9} [\exp(0.4/0.025) - 1] - 0.1 \text{ A} = 91 \text{ mA}$$

$$P = I_{max} \times V_{max} = 91 \text{ mA} \times 0.4 = 36.4 \text{ mW}$$

$$\begin{aligned} \text{Need } V_{oc} \text{ for fill factor; } V_{oc} &= \frac{kT}{e} \ln\left(\frac{I_{sc}}{I_0}\right) = 0.025 \times 18.42 \\ &= 0.46 \text{ V} \end{aligned}$$

$$\text{Fill factor} = \frac{I_{max} \times V_{max}}{I_{sc} \times V_{oc}}$$

$$= \frac{36.4 \text{ mW}}{0.1 \times 0.46 \text{ W}} = 0.79$$

7) For cells in parallel, see Question 1.

$$I = [I_{01} + I_{02}] [\exp(eV/kT) - 1] - (I_{L1} + I_{L2})$$

$$I = [4 \times 10^{-10} + 5 \times 10^{-10}] [\exp(V/0.025) - 1] - (0.25 + 0.1)$$

$$= [5.4 \times 10^{-10}] [\exp(V/0.025) - 1] - 0.35 \text{ A}$$

$V(V)$ :	0	0.2	0.4	0.42	0.44	0.46	0.48
$I(A)$ :	0.35	0.35	0.345	0.339	0.326	0.297	0.232
$P(W)$ :	0	0.07	0.138	0.142	0.143	0.137	0.115

Maximum power  $\sim 143 \text{ mW}$

This occurs at  $0.44 \text{ V}$  when a current of  $0.326 \text{ A}$  flows, so optimum load resistor is:

$$R = \frac{V}{I} = \frac{0.44}{0.326} = 1.35 \Omega$$

$$V_{oc} \text{ for array} = \frac{kT}{e} \ln \left( \frac{I_{L1} + I_{L2}}{I_{01} + I_{02}} \right) = 0.025 \ln \left( \frac{0.35}{5.4 \times 10^{-10}} \right)$$

$$= 0.507 \text{ V}$$

$$\text{Fill factor} = \frac{V_{max} \times I_{max}}{V_{oc} \times I_{sc}} = \frac{143 \text{ mW}}{0.507 \times 0.35} = 0.805$$