

The  
University  
Of  
Sheffield.

**Data Provided: Smith Chart (3 copies),  
Useful equations are given at the end  
of the paper**

## DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

**Autumn Semester 2012-2013 (2 hours)**

### High Speed Electronic Circuit Design

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1.
  - a. Explain and define briefly what is meant by return losses. (2)
  - b. A lossless transmission line with a length of 10 cm and a characteristic impedance of  $50\Omega$  is terminated with a complex load impedance of  $(90+j20)\Omega$  at a frequency of 3GHz. Use the required transmission line equations to calculate the input impedance, input reflection coefficient, voltage standing wave ratio, and insertion losses. (5)
  - c. Using the appropriate transmission lines equations, show how the input impedance of a lossless transmission line can be made equivalent to a lumped capacitor or inductor when the line is terminated by a short or an open circuit load. (6)
  - d. Show that the voltage standing wave ratio along a transmission line is given by  $VSWR = (1+\rho)/(1-\rho)$ , where  $\rho$  is the magnitude of the reflection coefficient. (7)
2.
  - a. Explain how impedance matching can be achieved using a single stub. (4)
  - b. An unknown load impedance is connected to a  $0.1\lambda$  long  $50\Omega$  lossless transmission line. The VSWR and phase of the reflection coefficient measured at the input of the line are 5 and  $40^\circ$  respectively. Determine the input and load impedances by using the Smith Chart provided. (6)
  - c. For a transmission line with a characteristic impedance of  $Z_0=50\Omega$  and terminated by a load impedance  $Z_L=(100+j40)\Omega$ , design a double stub matching network to match  $Z_L$  to  $Z_0$ . The 1<sup>st</sup> stub is located at the load, and the two stubs are separated by a distance of  $0.125\lambda$ . Find one possible solution in which the length of each stub is  $\leq 0.25\lambda$ . (10)

3. a. Explain and define briefly what Signal Flow Diagrams analysis are used to represent, and what are the two basic components of any SFD. (4)
- b. Explain briefly the difference between the available power gain and the transducer power gain. (4)
- c. Calculate the transmission (ABCD) parameters of the network shown in Figure 1.

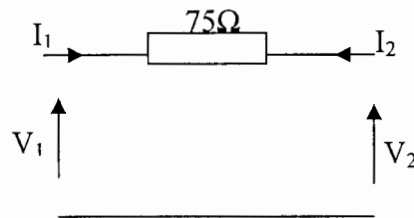


Figure 1

- d. Determine the scattering parameters,  $S_{ij}$  ( $i,j=1$  or  $2$ ), of the two-port network shown in Figure 2. Assume the characteristic impedances for the input and output ports are equal ( $Z_{01}=Z_{02}$ ). (4)

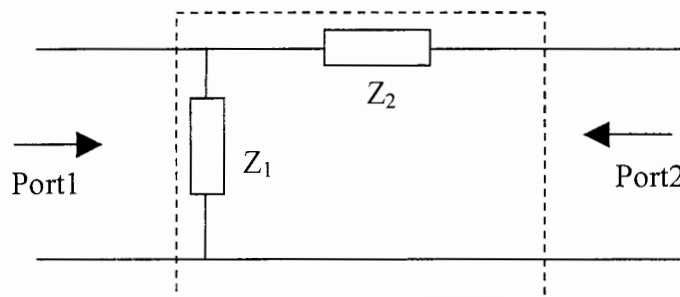


Figure 2

4. a. Explain why sometimes it is preferable to design an amplifier for less than the maximum obtainable gain, how can this be achieved? (4)
- b. A microwave transistor has the following S parameters at 10GHz:  $S_{11} = 0.45\angle 150^\circ$ ,  $S_{21} = 2.05\angle 10^\circ$ ,  $S_{12} = 0.01\angle -10^\circ$ ,  $S_{22} = 0.4\angle -150^\circ$ . The source and load impedances are  $Z_g=20\ \Omega$  and  $Z_L=30\ \Omega$ , respectively. Compute the available power gain, transducer power gain, and the operating power gain when a  $50\ \Omega$  reference impedance is assumed. (6)
- c. An amplifier has the following scattering and noise parameters

F GHz	$S_{11}$	$S_{21}$	$S_{12}$	$S_{22}$
6	$0.6\angle -60^\circ$	$2\angle 81^\circ$	0	$0.7\angle -60^\circ$

$$Z_0=50\ \Omega \quad R_N=20\ \Omega \quad NF_{\min}=2\text{dB} \quad \Gamma_{\text{opt}}=0.62\angle 100^\circ$$

Design an amplifier having a 2.5dB noise figure with the maximum gain that is compatible with this noise figure using noise figure and constant gain circles on the Smith chart provided. (10)

**You may find the following information useful:**

The constant gain and noise figure circles can be plotted using the following set of equations

$$C_s = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2}$$

$$r_s = \frac{\sqrt{1 - g_s} (1 - |S_{11}|^2)}{1 - (1 - g_s) |S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$

$$r_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$

$$C_{NF} = \frac{\Gamma_{opt}}{(N + 1)}$$

$$r_{NF} = \frac{\sqrt{N(N + 1 - |\Gamma_{opt}|^2)}}{(N + 1)}$$

**SKK**