



The
University
Of
Sheffield.

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Autumn Semester 2007-2008 (2 hours)

High Speed Electronic Circuit Design 6

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1.
 - a. Explain briefly the difference between return and insertion losses. (2)
 - b. Explain with the aid of diagrams what is meant by a quarter wavelength transformer. (4)
 - c. A lossless coaxial transmission line with a length of 3cm and a characteristic impedance of 50Ω is terminated with a complex load impedance of $50+j80\Omega$ at a frequency of 3GHz. Find the reflection coefficient at the load, the input impedance, the return loss and insertion loss of the line. (6)
 - d. Consider a 50Ω lossless transmission line with a VSWR of 3 and a load impedance of Z_L . The distance between successive minima has been measured as 2.1cm and the distance of the first voltage minimum from the load is 0.9cm. Find the load impedance. (8)
2.
 - a. Explain briefly how the Smith chart can be used for admittance transformation. (4)
 - b. Design a double stub matching network to match a load impedance of $Z_L=150+j30\Omega$ to a transmission line with a characteristic impedance of $Z_0=50\Omega$. The 1st stub is located at the load, and the two stubs are separated by a distance of 0.125λ . The length of each stub should be $\leq 0.25\lambda$. (8)
 - c. Repeat (2.b) when the first stub is located at a distance of 0.1λ from the load. (8)

Note: Find one possible solution for each design.

3.
 - a. Explain with the aid of diagrams what is meant by the ABCD network representation. (4)
 - b. Explain briefly the difference between the available power gain and the transducer power gain. (4)

- c. Find the transmission parameters for the network shown in Figure 1

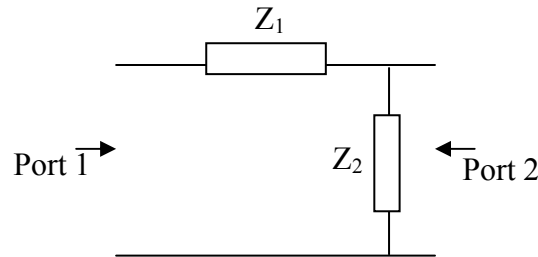


Figure 1

(6)

- d. Find the scattering parameters of the two ports network shown in Figure 2. The characteristic impedance of each port is 50Ω .

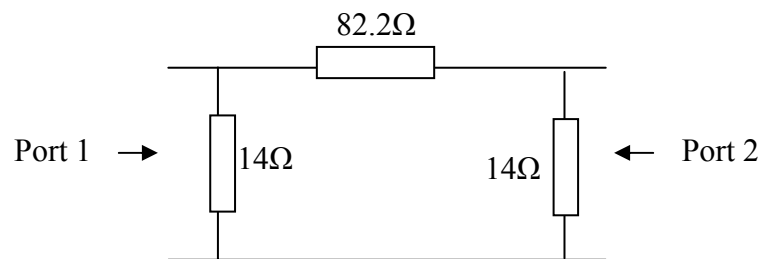


Figure 2

(6)

4. a. Explain the difference between conditional and unconditional stability (2)
- b. Explain briefly what is meant by constant gain circles. (2)
- c. An amplifier is characterised by the following S-parameters: $S_{11} = 0.72 \angle -116^\circ$, $S_{21} = 2.60 \angle 76^\circ$, $S_{12} = 0.03 \angle 57^\circ$, $S_{22} = 0.73 \angle -54^\circ$. The input side of the amplifier is connected to a source impedance of $Z_s = 75\Omega$. The output side is connected to a load of $Z_L = 100\Omega$. Assuming that the S parameters are measured with reference to a characteristic impedance of $Z_0 = 50\Omega$, find the power gains of this amplifier. (6)
- d. An amplifier has the following S-parameters measured at 4GHz with a 50Ω reference characteristics impedance: $S_{11} = 0.75 \angle -120^\circ$, $S_{21} = 2.5 \angle 80^\circ$, $S_{12} = 0.0$, $S_{22} = 0.6 \angle -70^\circ$. Design the input and output matching networks of the amplifier so that an overall gain of 11dB is achieved. Plot constant gain circles for $G_s = 2\text{dB}$ and 3dB, and $G_L = 0\text{dB}$ and 1dB. (10)

You may find the following information useful:

The constant gain circles can be plotted using the following set of equations

$$C_s = \frac{g_s S_{11}^*}{1 - (1 - g_s) |S_{11}|^2}$$

$$r_s = \frac{\sqrt{1 - g_s} (1 - |S_{11}|^2)}{1 - (1 - g_s) |S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$

$$r_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$

SKK / AT