

Richard Tozer E1356

EEE101 "Circuits + Signals"

review of course

- concept of an electrical circuit
- basic circuit elements
 - sources
 - resistors
 - capacitors + inductors

circuit analysis involves working out voltages + currents within networks consisting of sources, resistors, capacitors + inductances, reactances.

- formal analysis methods
- conventions
- power + energy
- circuit transformations

dealing with sinusoids

- concept of impedance
- impedance of inductor + capacitor
- a.c. analysis of circuits

dealing with phase

- phase diagrams
- complex numbers

- resonance
- filters

— filters

Studying

- 24 hours of lectures
 - 12 hours of problem classes
- 36

100
36
12 | 64
5

Bogart	Electric Circuits	McGraw Hill
Hayt	Engineering Circuit Analysis	"
Paul	Analysis of Linear Circuits	"
Smith R.J.	Circuits Devices + Systems	Wiley
Ciletti	Intro to circuit analysis + design	
Floyd	Principles of electric ccts	
Walls	Intro. to cct analysis	
Madhu	Linear circuit analysis	
Nilsson	Electric Circuits	
Spence R	Introductory Circuits	Wiley

Introduction

"Linear" "passive" networks.


component values are constant

interconnection of electronic circuit elements.

Voltage

- is a driving force
- drives current through a circuit

Consider a source

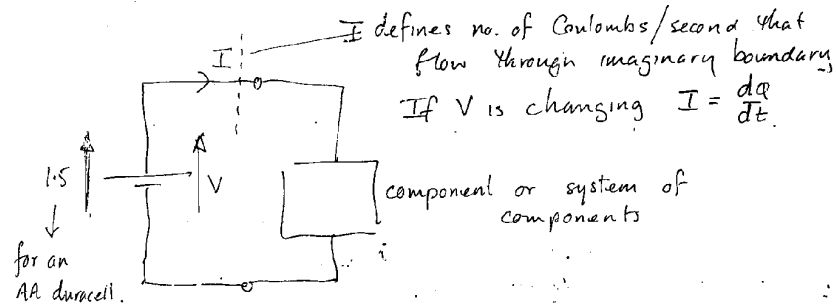

In forcing the current through the components the source is ~~do~~ doing work on the components.
— ie transferring energy to the components.

$$\text{Energy} = \int_0^{t_1} V(t) I(t) dt \quad \text{Joules (J)}.$$


$$\text{Power} = V I t_1 \quad \text{for d.c. quantities}$$

Power is rate of energy dissipation


$$\text{Joules/second} \Rightarrow \text{Watts}$$

$$\text{Power} = \frac{1}{t_1} \int_0^{t_1} V(t) I(t) dt$$

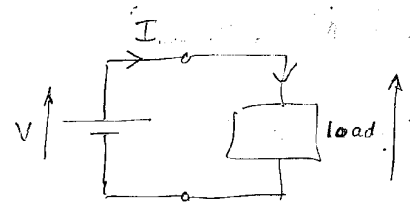
$$\text{for d.c. } P = V \cdot I \quad \text{W}$$



Source characteristic for voltage source

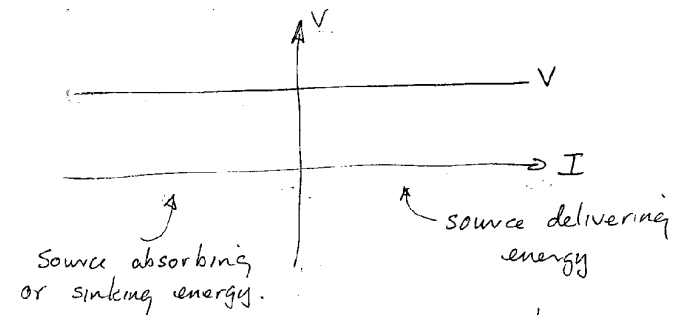

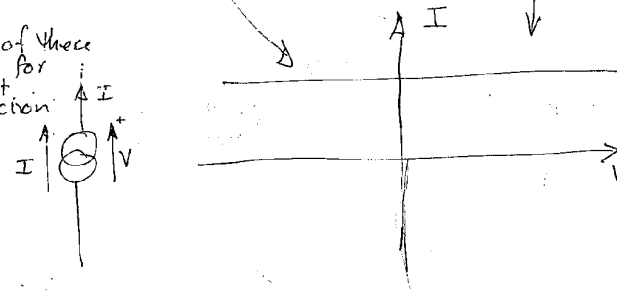
one of these labels for current direction



Resistors

— devices that obey Ohm's law

$$R = \text{resistance} = \frac{V}{I}$$

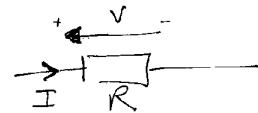

resistors are energy dissipators.

— various technologies


— wire wound for high power
(up to several kW)

— carbon, metal or oxide film for
low to medium power
0.25W to 50W.

— surface mount usually carbon or metal
film 0.1W to 0.5W (and very fiddly).

Resistors manufactured in a range of different
"tolerance series" — idea was that there
should be minimal overlap between the
tolerance bands of resistors in a given series

eg for a 10% series

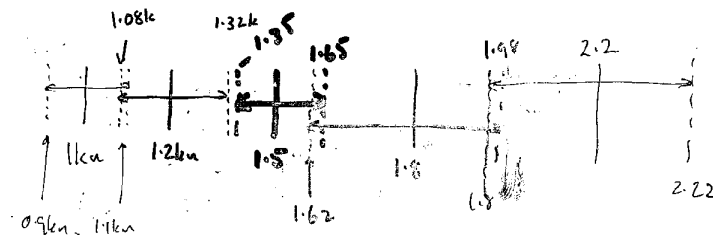


{ 1k 1.2k 1.5k 1.8k 2.2k 2.7k 3.3k 3.9k 4.7k 5.6k
6.8k 8.2k 10k
called 10% preferred values.

Power dissipation in resistors.



$$\text{Power Diss.} = VI$$

$$\text{Ohm's law } R = \frac{V}{I}$$

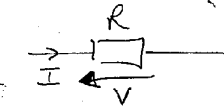


I + V are dc quantities

$$\therefore \text{Power Diss} = I^2 R \text{ or } \frac{V^2}{R}$$

basic relationship.

Resistor Combinations

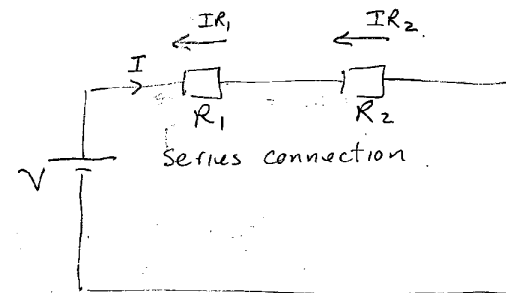


$$V = IR_1 + IR_2 = I(R_1 + R_2)$$

$$\text{or } \frac{V}{I} = R_1 + R_2$$

Resistors in series add

Other main connection is parallel

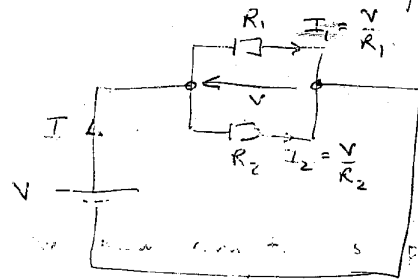

$$I = I_1 + I_2$$

$$= \frac{V}{R_1} + \frac{V}{R_2}$$

$$= V \left[\frac{1}{R_1} + \frac{1}{R_2} \right]$$


effective $R = \frac{V}{I} = \frac{V}{V \left[\frac{1}{R_1} + \frac{1}{R_2} \right]} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$

often written as $\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$

for two resistors $R = \frac{R_1 R_2}{R_1 + R_2} = \frac{3.2}{3+2} \frac{k\Omega}{k\Omega}$

Kirchoff's Laws

-- Kirchoff's current law

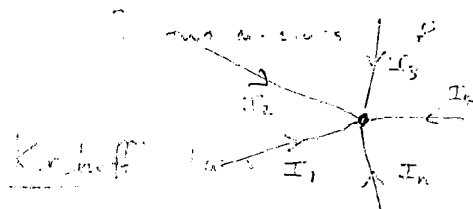


Sum of currents entering the node must equal zero.

-- Kirchoff's current law

total current entering a circuit node must equal total leaving it.

-- Kirchoff's voltage law

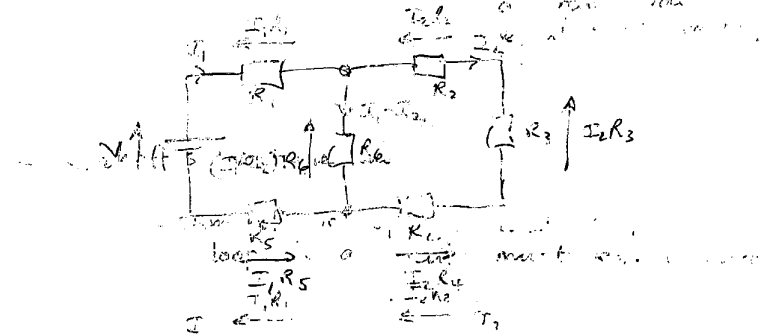-- sum of voltages around any closed loop in a circuit must equal zero



$$V - (I_1 - I_2)R_1 - (I_1 - I_2)R_6 - I_2 R_2 = 0$$

$$-(I_1 - I_2)R_6 - I_2 R_2 - I_2 R_3 - I_2 R_4 = 0$$

-- main thing to be careful of here is correct application of convention and correct directed addition of voltages around the loops, $-(I_1 - I_2)R_6 - I_2 R_2 - I_2 R_3 - I_2 R_4 = 0$


$$(I_1 - I_2)R_6 - I_2 R_2 - I_2 R_3 - I_2 R_4 = 0$$

Formal analysis methods

-- we have to be careful of


Nodal analysis: sign convention of convention

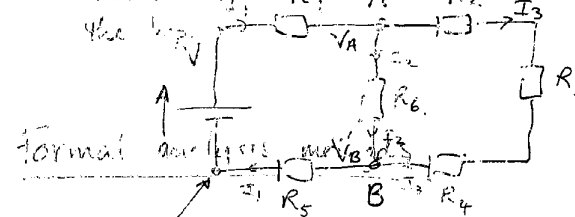correct directed addition of voltages around the loop




Formal analysis methods

node. at node A $-I_1 = I_2 + I_3$

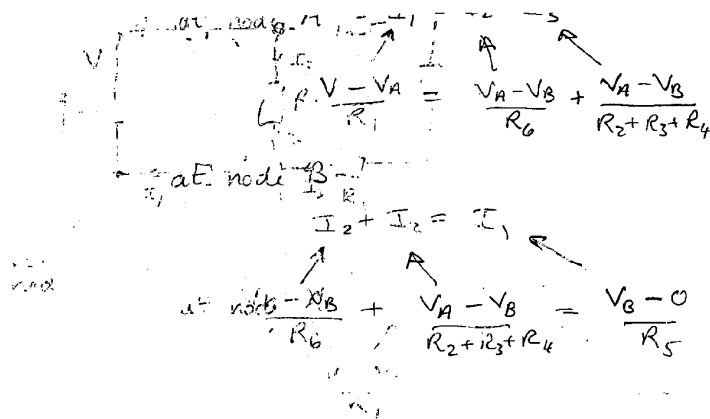

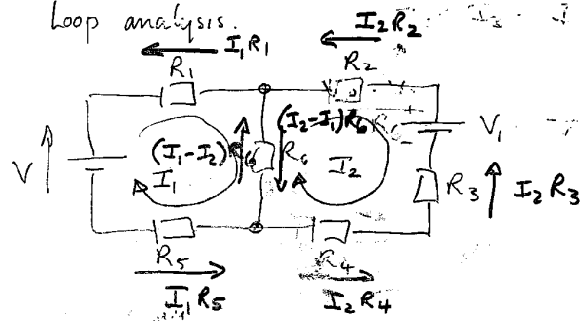Mesh analysis or Maxwell's current loops or loop analysis.



loop 1 $I_1 R_1 + (I_1 - I_2) R_6 + I_1 R_5 - V = 0$

loop 2 $I_2 R_2 + V_1 + I_2 R_3 + I_2 R_4 + (I_2 - I_1) R_6 = 0$

next step

$$I_1 (R_1 + R_6 + R_5) - I_2 R_6 = V$$

$$I_2 (R_2 + R_3 + R_4 + R_6) - I_1 R_6 = -V_1$$


$V_1 + V$ would be known.

— unknowns are $I_1 + I_2$ can be found by simultaneous solution of these two equations.




The principle of superposition.


— the response of a linear network to a number of inputs is equal to the sum of the responses to each input applied alone in turn to the network.

eg.

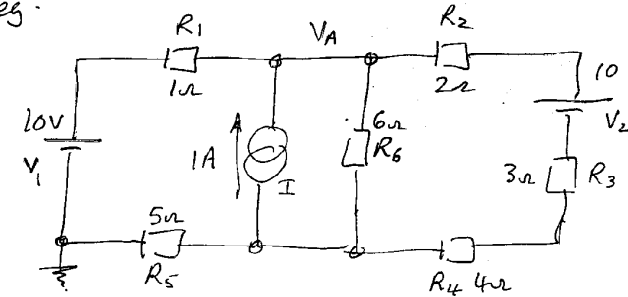




Consider V_1

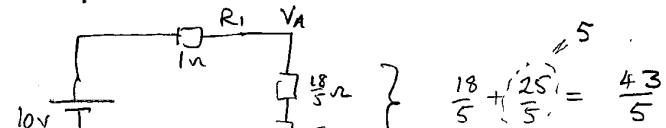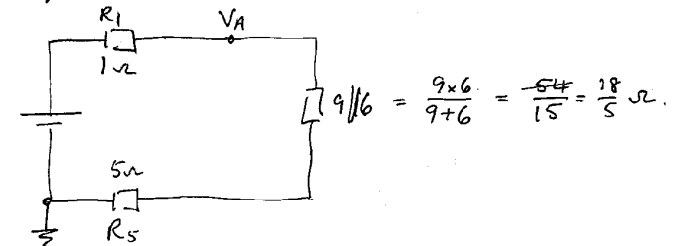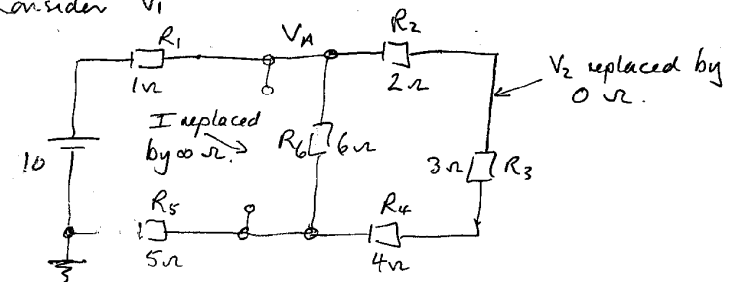

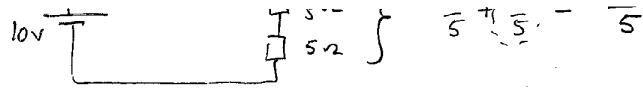


$$V_A \Big|_{\text{due to } V_1} = 10 \times \frac{43/5}{1 + 43/5} = 10 \times \frac{43}{48}$$



now consider I

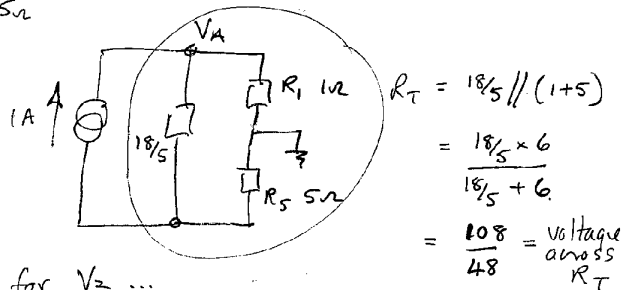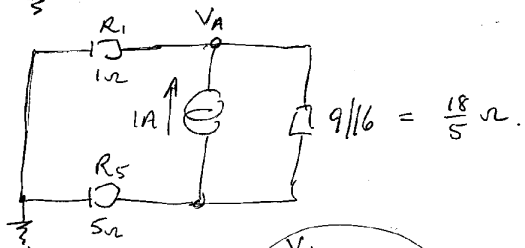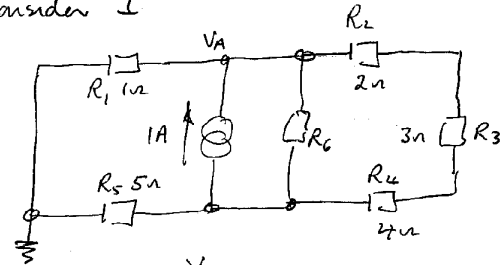

Partial ckt for V2 ...

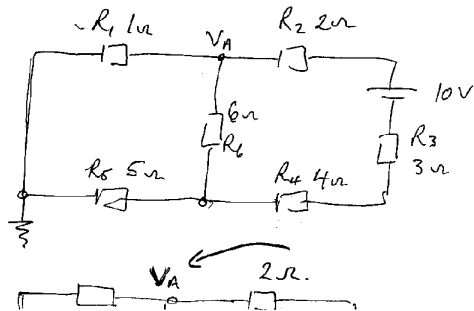
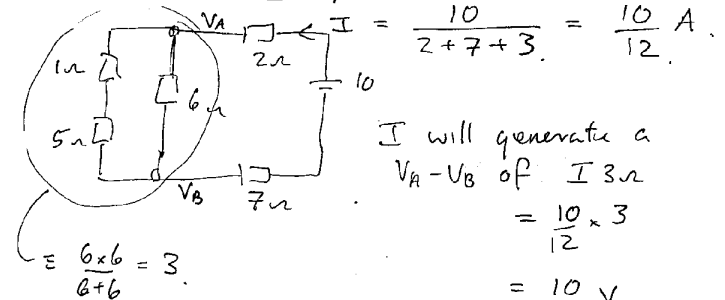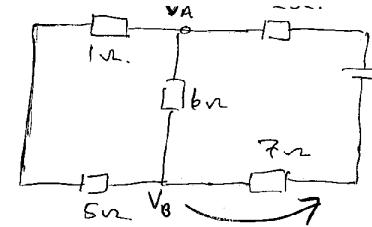
$$V_{R1} = V_A = V_{RT} \cdot \frac{1}{6}$$



I will generate a $V_A - V_B$ of $I \cdot 3\Omega$

$$= \frac{10}{12} \times 3$$

$$= \frac{10}{4} \text{ V}$$

$$= 2.5 \text{ V}$$


$$V_A - \text{ref voltage} = V_A = \frac{2.5 \times 1}{1+5} = \frac{2.5}{6} \text{ V} = \frac{5}{12} \text{ V} = \frac{20}{48}$$

$$V_A \text{ total} = V_A \Big|_{\text{due to } V_1} + V_A \Big|_{\text{due to } I} + V_A \Big|_{\text{due to } V_2}$$

$$= \frac{430}{48} + \frac{108 \cdot 1}{48 \cdot 6} + \frac{20}{48} = \frac{176}{48} \text{ V}$$

a different answer.

A nodal analysis example

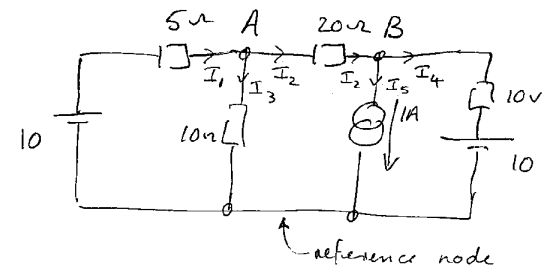

$$I_1 = I_2 + I_3$$

$$\downarrow \quad \downarrow \quad \downarrow$$

$$\frac{10 - V_A}{5\Omega} = \frac{V_A - V_B}{20\Omega} + \frac{V_A - 0}{10\Omega} \quad \text{--- (1)}$$

$$I_2 = I_4 + I_5$$

$$\downarrow \quad \downarrow \quad \downarrow$$

$$\frac{V_A - V_B}{20} = \frac{V_B - 10}{10\Omega} + 1A \quad \text{--- (2)}$$

modifying (1)

$$40 - 4V_A = V_A - V_B + 2V_A$$

$$\text{or } 40 = 7V_A - V_B \quad \text{--- (3)}$$

modifying (2)

$$V_A - V_B = 2V_B - 20 + 20$$

$$\text{or } V_A = 3V_B \quad \text{--- (4)}$$

(4) into (3)

$$40 = 7(3V_B) - V_B = 21V_B - V_B = 20V_B$$

$$V_B = \frac{40}{20} = 2V$$

$$V_A = 3V_B = 6V$$

Check

$$I_1 = \frac{10 - V_A}{5} = \frac{10 - 6}{5} = 0.8A$$


$$I_3 = \frac{V_A}{10} = \frac{6}{10} = 0.6A$$

$$I_2 = \frac{V_A - V_B}{20} = \frac{6 - 2}{20} = \frac{4}{20} = 0.2A$$

$$I_1 = I_2 + I_3 \quad (\text{first node equation})$$

$$0.8 = 0.2 + 0.6$$

loop analysis:

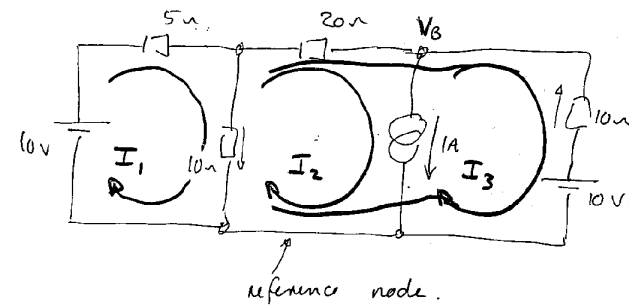

$$10 = 5I_1 + 10(I_1 - I_2) \quad \text{--- (1)}$$

$$0 = 10(I_2 - I_1) + I_2 \cdot 20 + V_B \quad \text{--- (2)}$$

$$10 + I_3 \cdot 10 = V_B \quad \text{--- (3)}$$

$$I_2 - I_3 = 1A \quad \text{--- (4)}$$

from 4+3

$$10 + (I_2 - 1)10 = V_B$$

$$10I_2 = V_B$$

eliminating V_B from (2)

$$0 = 10(I_2 - I_1) + I_2 \cdot 20 + 10I_2$$

$$= 10I_2 + 20I_2 + 10I_2 - 10I_1$$

$$= 40I_2 - 10I_1$$

$$\text{or } I_1 = 4I_2$$

4.1 2k 5mA 5V 10mA

4.2	0.75k Ω	-3.33mA	10V	-2.5mA
4.3	1.67k Ω	-4mA	6V	-6.7mA
4.4	0.67k Ω	5mA	5V	3.33mA
4.5	2.5k Ω	-2mA	2V	-5mA
4.6	0.67k Ω	-5mA	5V	-3.33mA
4.7	2.38k Ω	2.4mA	2.8V	5.7mA
4.8	1.33k Ω	2.5mA	2.5V	3.33mA
4.9	0.79k Ω	4mA	2.0V	3.16mA

Sheet 2 Q7


Q7 \rightarrow 0.53A

Q8 \rightarrow 1.91A

Q9 \rightarrow 7.65V 3.53A

Q10 \rightarrow -0.588A 3 Ω 16.57W


Thevenin Equivalent Circuits

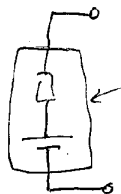

This is a standard model for a battery and is a Thevenin equivalent representation of what is inside

useful for modelling non electrical systems like batteries and certain aspects of humans + animals

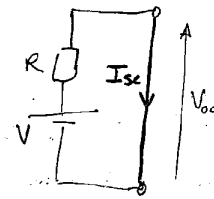useful also as a circuit transformation tool in conventional electronic circuits.




for no load connected

$$V_{oc} = V \text{ since no current flows}$$

for a short circuited output

$$I_{sc} = \frac{V}{R}$$

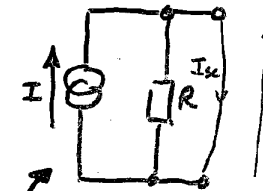


$$V_{oc} = IR \quad I_{sc} = I$$





note that if $I = \frac{V}{R}$

$$V_{oc} = V \quad I_{sc} = \frac{V}{R}$$

This is a Norton equivalent ckt.

Application to circuit problems...

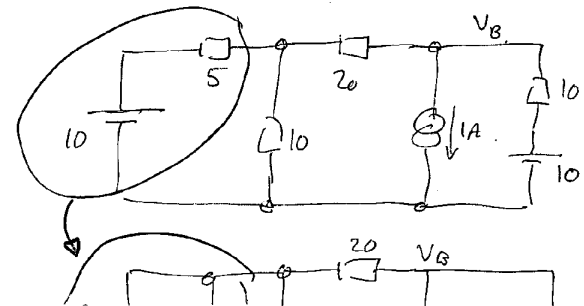

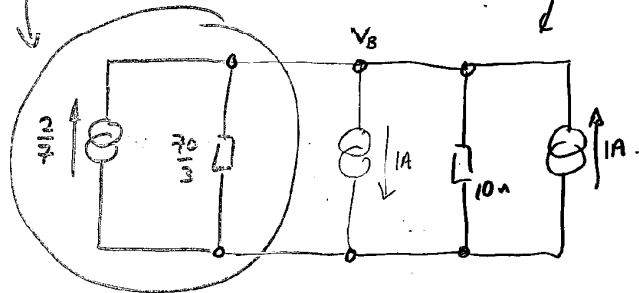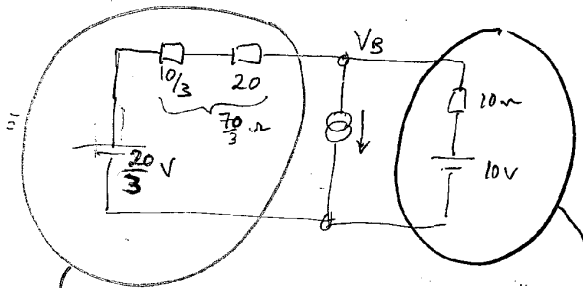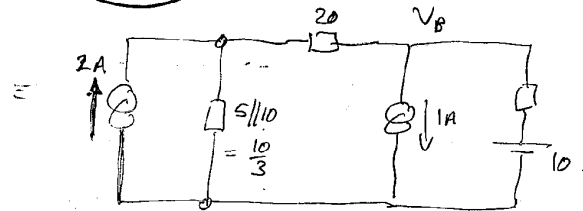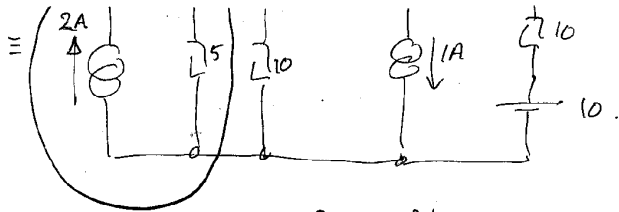


$$\begin{aligned}
 &= \frac{2}{\frac{10}{3} + 1} = \frac{20}{10 + 3} = \frac{20}{13} \\
 &= \frac{20}{13} \times 10 = \frac{200}{13} \text{ V} \\
 &= 7 \text{ V}
 \end{aligned}$$





$$\begin{aligned}
 &= \frac{100}{13} \\
 &= 7 \text{ V}
 \end{aligned}$$
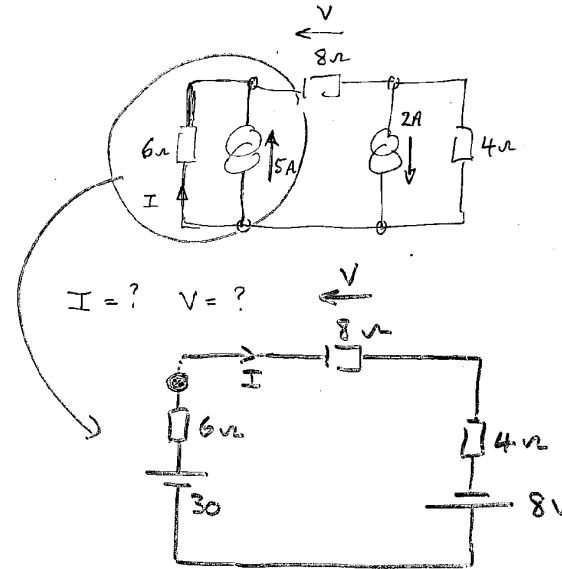
$$V_B = \frac{2}{7} \times 7 = 2 \text{ V}$$


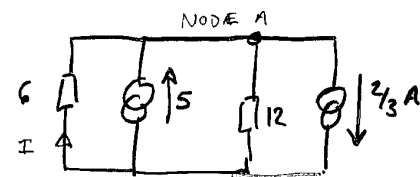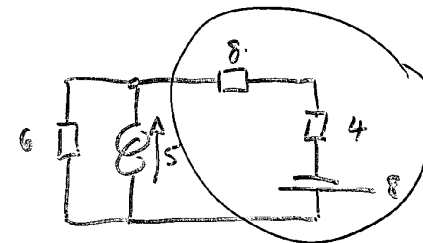
$$I = \frac{38}{18} \text{ A} \quad \therefore V = \frac{38}{18} \times 8 = \frac{38}{9} \text{ V}$$





Current entering node A = $5 - \frac{2}{3}$
 $= 4\frac{1}{3} \text{ A}$

That current flows through $6\Omega \parallel 12\Omega$
 $= \frac{72}{18} \cdot \frac{12}{3} 4\Omega$

So $V_A = 4\frac{1}{3} \times 4$
 $= 17\frac{1}{3} \text{ V}$

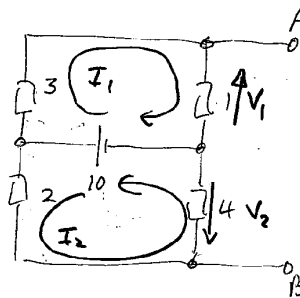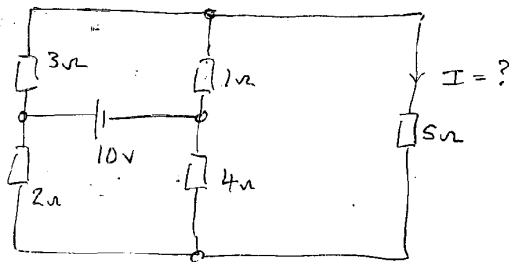$I = \frac{0 - V_A}{6} = \frac{0 - 17\frac{1}{3}}{6} = -2.89 \text{ A}$




$I_1 = \frac{10}{4} = 2.5 \text{ A}$

$V_1 = 2.5 \text{ V}$

$I_2 = \frac{10}{6} = \frac{5}{3} \text{ A}$

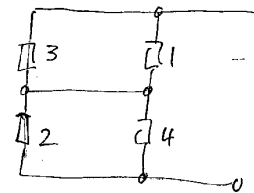
$V_2 = \frac{5}{3} \times 4 \text{ V} = \frac{20}{3} \text{ V}$



$V_2 = \frac{5}{3} \times 4 \text{ V} = \frac{20}{3} \text{ V}$
 $V_A - V_B = 2.5 \text{ V} - \frac{20}{3} \text{ V}$


$R = ? = 1 \parallel 3 + 2 \parallel 4$
 $= \frac{3}{4} + \frac{8}{6}$

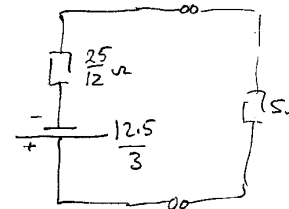$= \frac{3}{4} + \frac{4}{3} = \frac{9}{12} + \frac{16}{12}$
 $= \frac{25}{12} \Omega$




$2.5 - \frac{20}{3} = \frac{7.5 - 20}{3}$
 $= -\frac{12.5}{3}$

Thevenin and potential dividers


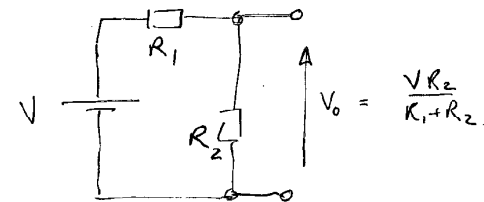


$V_0 = \frac{V R_2}{R_1 + R_2}$

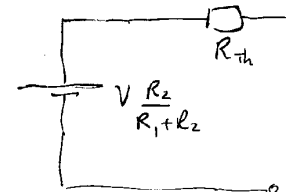


$R_{TH} = R_1 \parallel R_2$

Star - Delta transformations

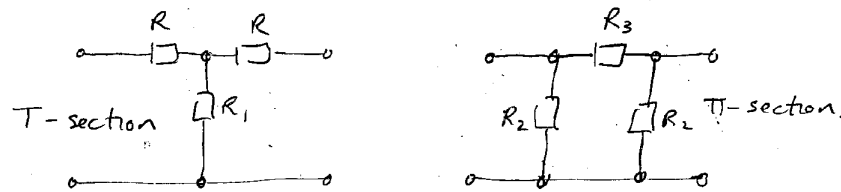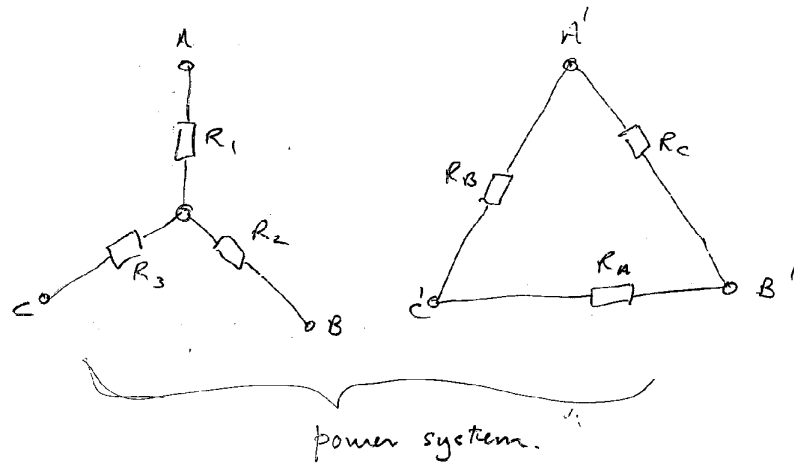

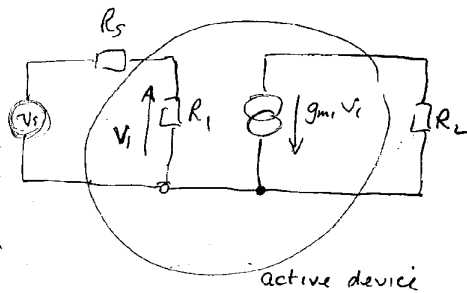HF transmission lines, attenuators + filters.



- bipolar junction transistor
- field effect transistor
- thermionic vacuum tube (valve).

$$\frac{1}{2} CV^2 = \frac{1}{2} \cdot 2500 \cdot 6.25 = \frac{15000}{2} \text{ J} = 7500 \text{ J}$$


$$\frac{1000^2 \cdot 0.5 \times 10^{-6}}{2} = 0.25 \text{ J}$$

$$400 \times 300 = 120000 \text{ J}$$

$$\frac{2.4 \times 10^6}{2} = 1.2 \text{ J}$$


Capacitors


$$I_c = C \frac{dV}{dt}$$

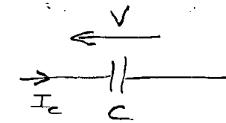

$$\text{or } V = \frac{1}{C} \int I_c dt + \text{const.}$$


Implications...

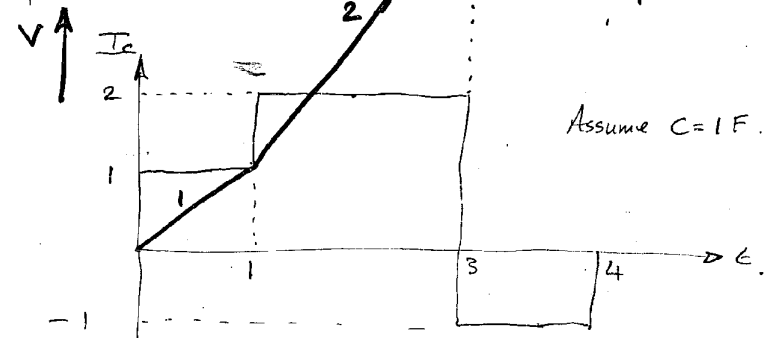

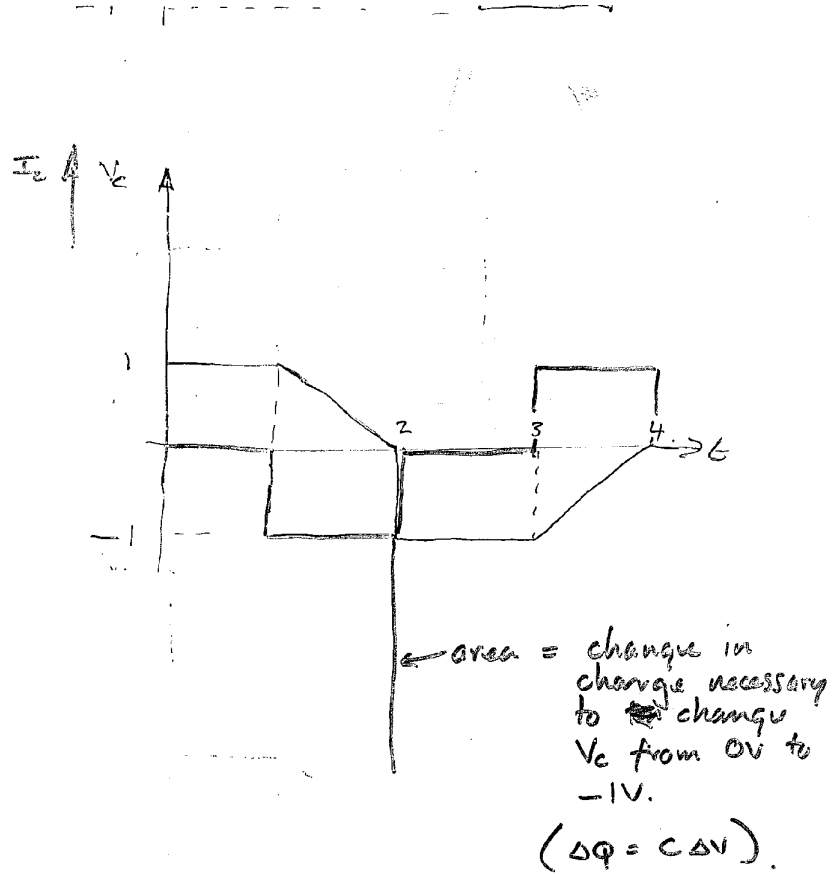



Inductance

$$V = L \frac{dI}{dt}$$

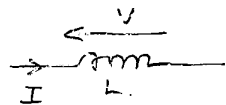

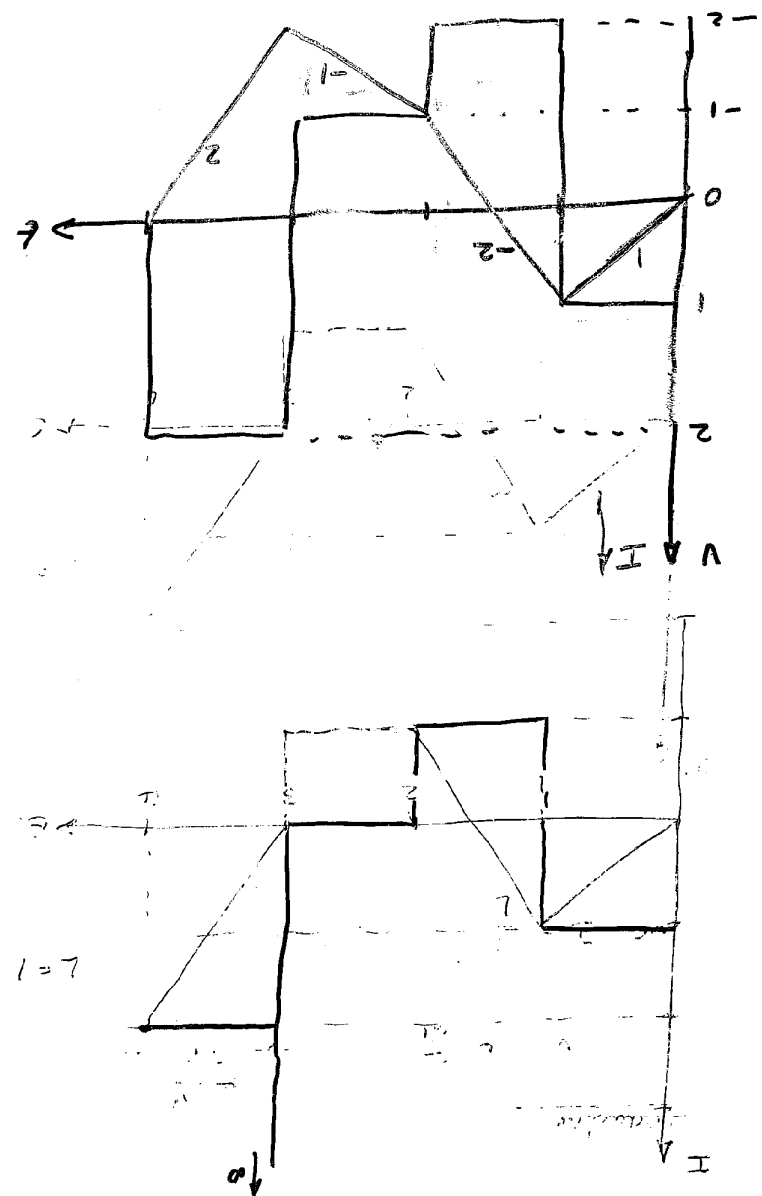
$$\text{or } I = \frac{1}{L} \int V dt + \text{const.}$$




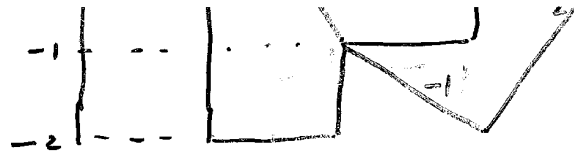

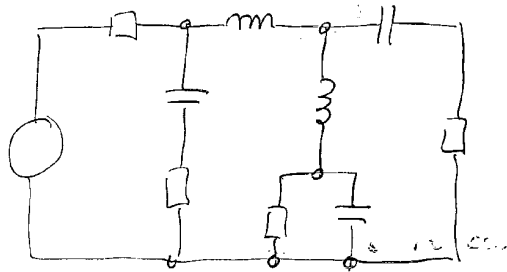At dc, inductance = short ckt.
capacitance = open ckt.




If the source is d.c.

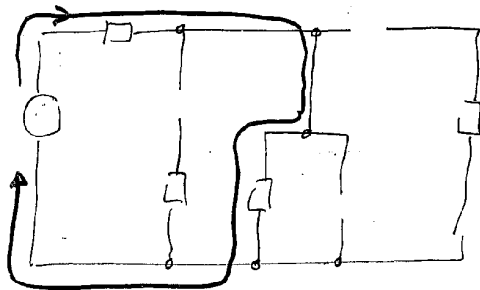


What about a.c. + capacitors + inductors?

Sinusoids

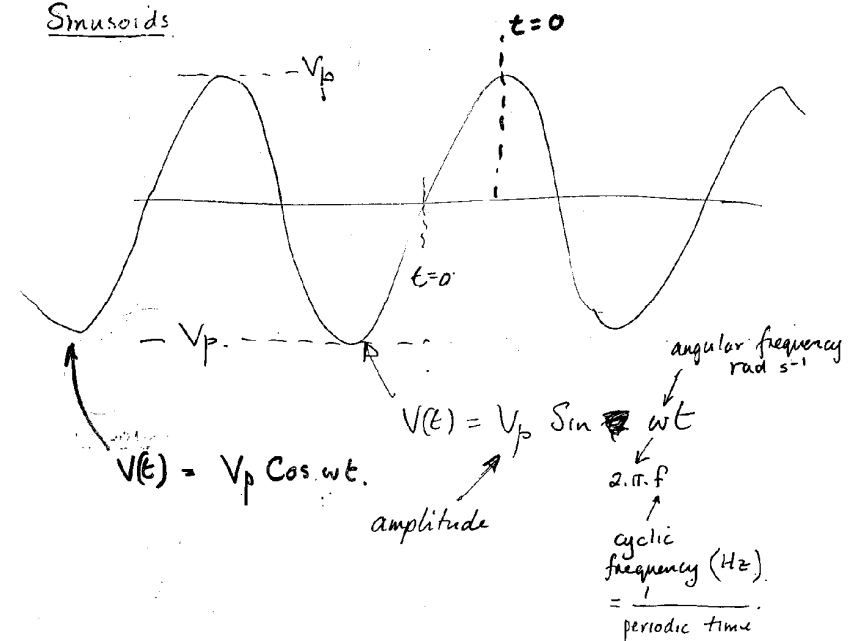

Capacitors + Sinusoids

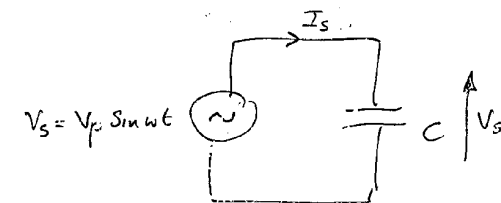

$$I_s = C \frac{dV_s}{dt} = C \frac{d(V_p \sin \omega t)}{dt}$$

$$= C \omega V_p \cos \omega t = C \omega V_p \sin \left(\omega t + \frac{\pi}{2} \right)$$


$$- \omega \sin(\omega t + \frac{\pi}{2}) = -\omega \cos \omega t$$

Impedance of the capacitance is

$$|Z_c| = \left| \frac{V_s}{I_s} \right| = \frac{V_p}{\omega C V_p} = \frac{1}{\omega C}$$

and V_s lags I_s by $\frac{\pi}{2}$ radians or 90°

For Inductors

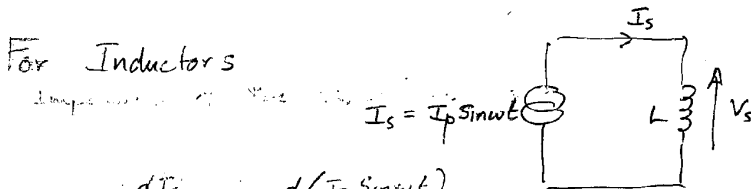



$$V_s = L \frac{dI_s}{dt} = L \frac{d(I_p \sin \omega t)}{dt}$$

$$= \omega L I_p \cos \omega t = \omega L I_p \sin(\omega t + \frac{\pi}{2})$$

$$|Z_L| = \left| \frac{V_s}{I_s} \right| = \frac{I_p \omega L}{I_p} = \omega L$$



and V_s leads I_s by $\frac{\pi}{2}$ radians or 90°

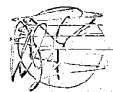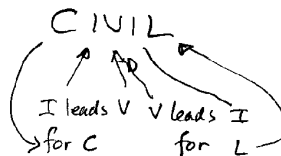To help remember what lags what in
inductors + capacitors




.T.

(I leads V for C V leads I for L)

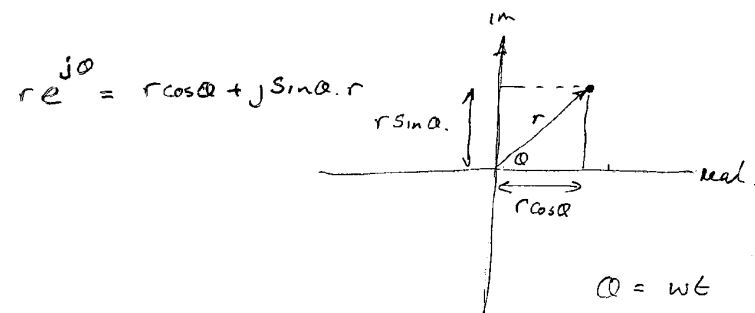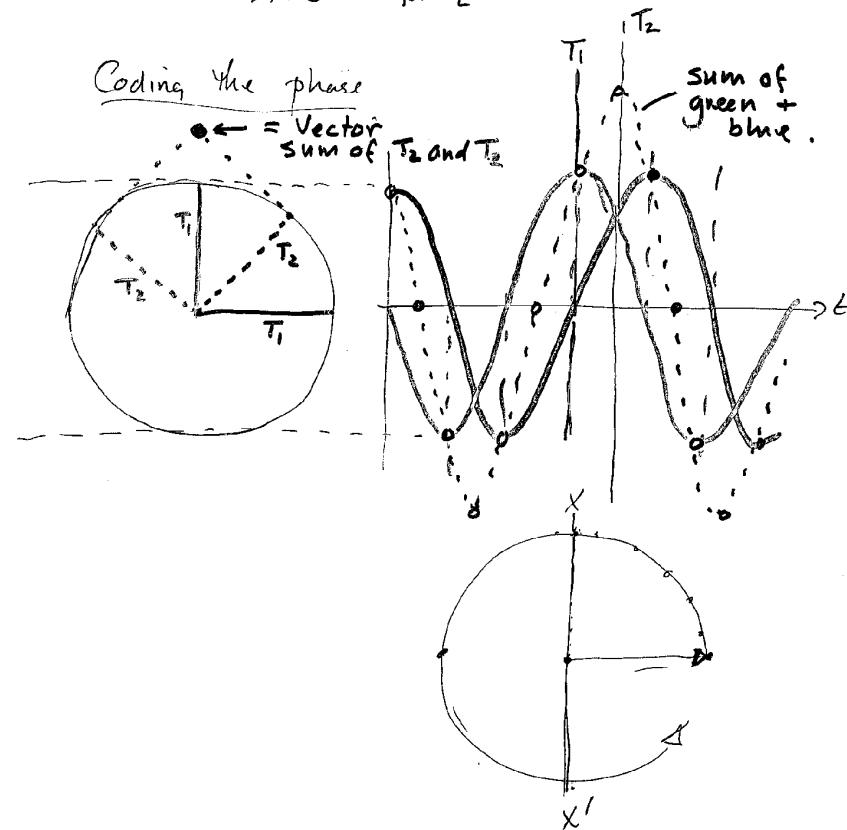


In our case.

$\phi = \omega t$
in our case.

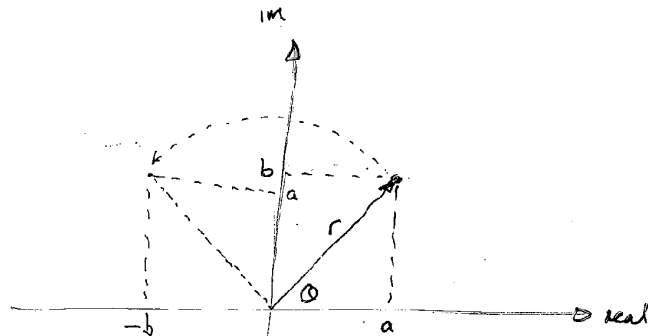

$$j(a + jb) = ja - b$$

Consider a capacitance ...

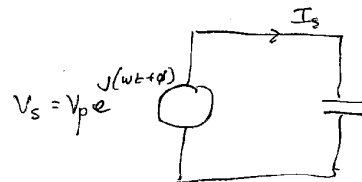

$$I_s = C \frac{dV_s}{dt} = C \frac{d(V_p e^{j(\omega t + \phi)})}{dt}$$


$$= C V_p j \omega e^{j(\omega t + \phi)}$$

$$Z_c = \frac{V_s}{I_s} = \frac{V_p e^{j(\omega t + \phi)}}{C V_p j \omega e^{j(\omega t + \phi)}}$$

$$= \frac{1}{j \omega C}$$


Some phasor + complex examinations of simple circuits

$$\bar{V}_R + \bar{V}_L = \bar{V}_s$$

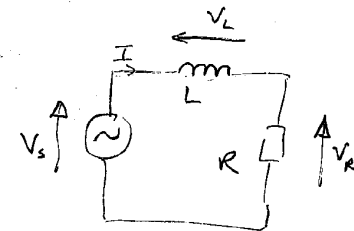

using a phasor diagram --

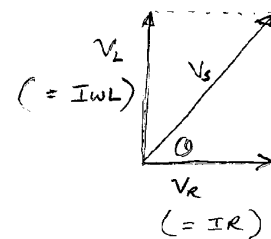use current as a reference direction because current is common to both elements.



$$V_s^2 = I^2 R^2 + I^2 \omega^2 L^2$$

$$\frac{V_s^2}{I^2} = R^2 + \omega^2 L^2$$

$$\frac{V_s}{I} = |Z| = \sqrt{R^2 + \omega^2 L^2} \text{ I direction}$$


$$\phi = \tan^{-1} \frac{I \omega L}{I R}$$

using "j" notation.

$$V_L = I \cdot Z_L = I \cdot j \omega L$$

$$V_R = I \cdot R$$

$$V_s = V_L + V_R = I j \omega L + I R$$

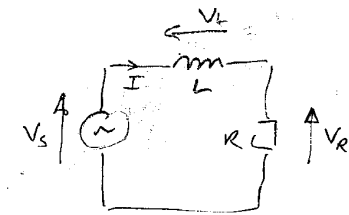

$$V_L = I \cdot Z_L = -j\omega L$$

$$V_R = I \cdot R$$


$$V_s = V_L + V_R = Ij\omega L + IR$$

$$= I(R + j\omega L)$$

$$\text{so } \frac{V_s}{I} = R + j\omega L \equiv Z$$



$$\phi = \tan^{-1} \frac{\text{Im}}{\text{Re}} = \tan^{-1} \frac{\omega L}{R}$$

$$|Z| = \sqrt{R^2 + \omega^2 L^2}$$

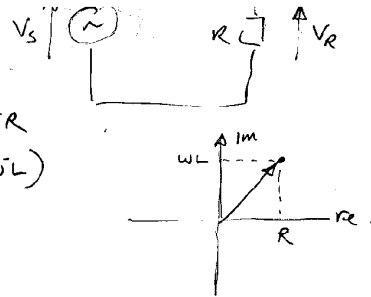


phasor...

consider the series arm

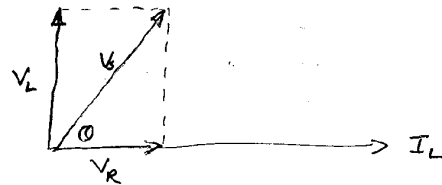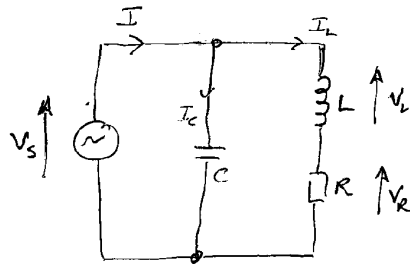

$$V_s^2 = V_L^2 + V_R^2 = I_L^2 \omega^2 L^2 + I_L^2 R^2$$
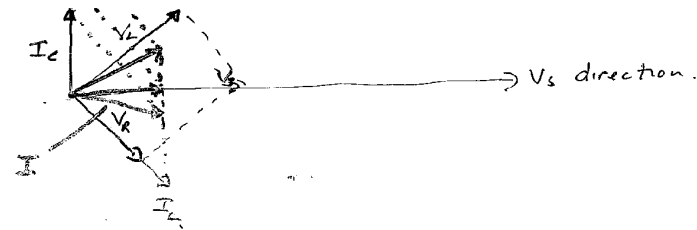
$$I_L = \frac{V_s}{\sqrt{\omega^2 L^2 + R^2}} \quad \phi = \tan^{-1} \frac{\omega L}{R}$$



j notation


$$\frac{V_s}{I} = \frac{1}{j\omega C} \parallel (R + j\omega L)$$






$$= \frac{\frac{1}{j\omega C} \cdot (R + j\omega L)}{\frac{1}{j\omega C} + R + j\omega L}$$

$$= \frac{R + j\omega L}{1 - \omega^2 LC + j\omega CR}$$

to find a condition where V_s and I are in the same phase — look for a condition that will make "j" terms disappear.


Q1

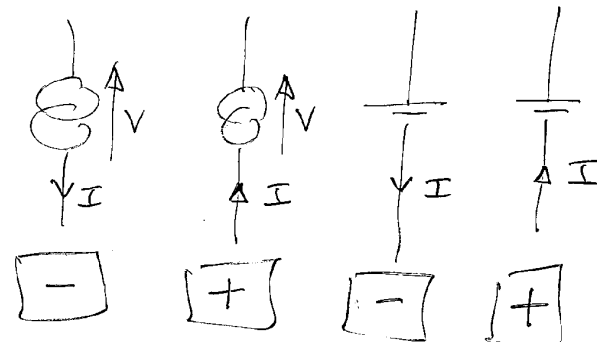

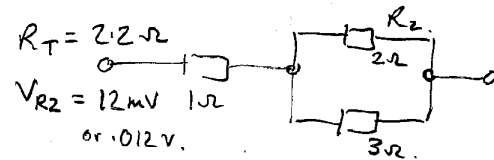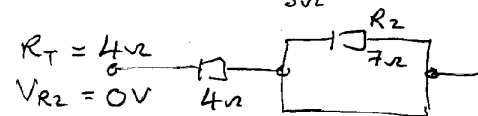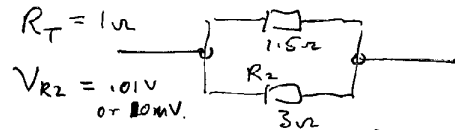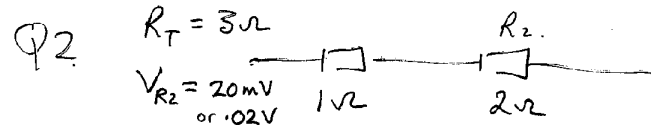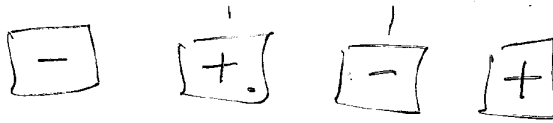

Q3.

R_3 is associated with convention error

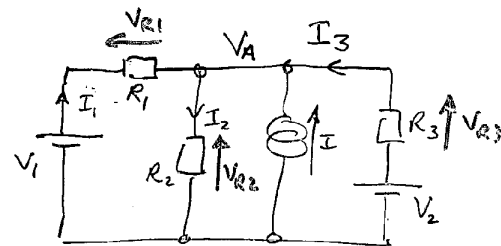


$$I_1 + I_3 + I = I_2$$


$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_3} + I = \frac{V_A}{R_2}$$

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_3} + I = \frac{V_A}{R_2}$$

Q4

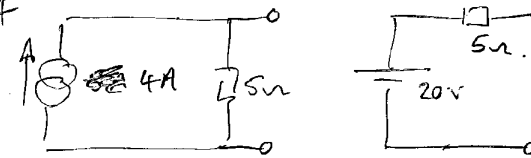


Q5

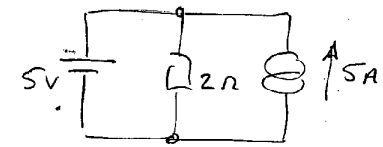

$$P_R = \frac{5^2}{2} = \frac{25}{2} = 12.5\text{W}$$

Q6.

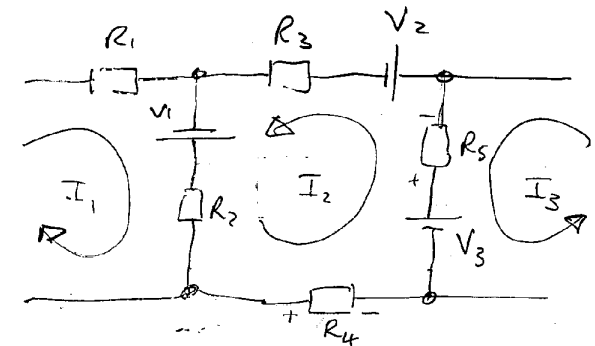


$$I_2 R_4 - V_3 + R_5 (I_2 - I_3) + V_2 + R_3 I_2 - V_1 + R_2 (I_2 + I_1) = 0$$


Q7

$$I_s = \frac{10V}{2\Omega + 6\Omega}$$

$$= \frac{10}{8} = 1.25 A$$

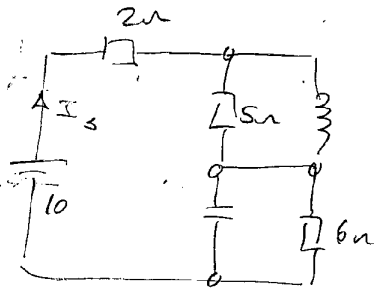


Q8.

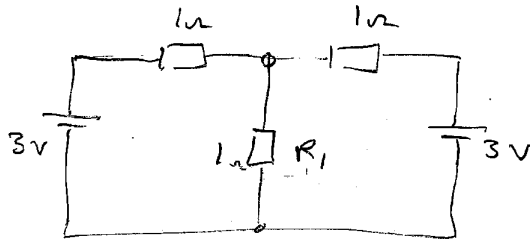

$$Ans = 4W$$

eg by superposition...

due to 3V (left.)

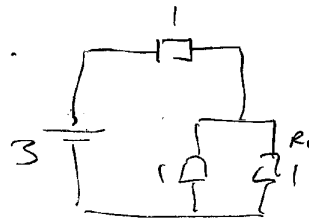

$$V_{R_1} = 1V$$

Since 3V (right) ckt is identical
it also contributes 1V.

$$\therefore V_{R_1 \text{ TOT}} = 2V$$