
# Electricity in the home

Infrastructure and Electrical safety

## Bibliography

http://www.tlc-direct.co.uk/Book/1.1.htm

# 3 phase residential distribution

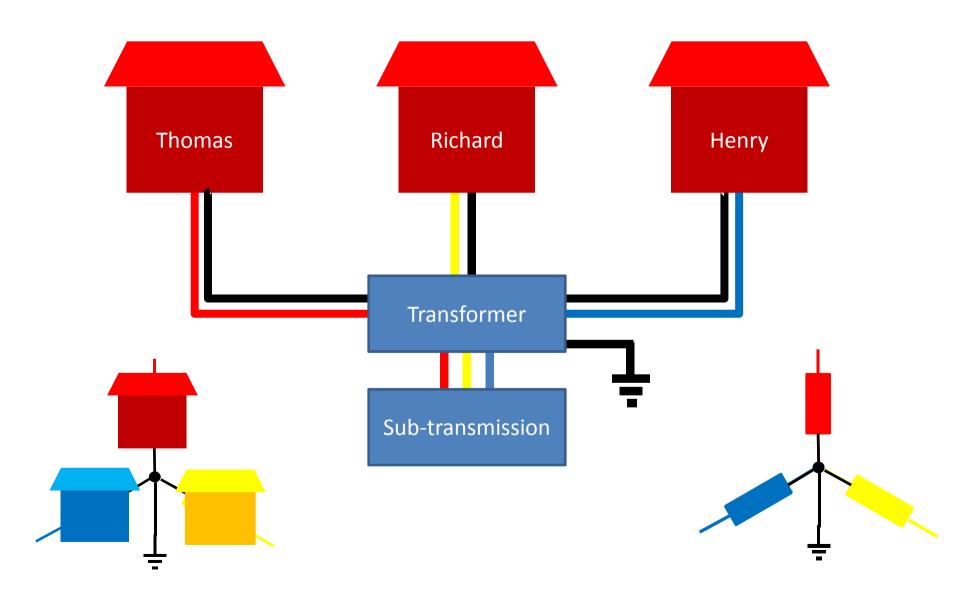

# Single Phase: Live, Neutral and Earth

- Live
  - 230/240Vac single phase
- Neutral
  - is it actually neutral? i.e. 0V
- Earth
  - Physically pinned to the electric potential of the ground









#### Earth wire (1)

- Physical contact to earth
- Safety
  - Prevent build up of static
  - Path to ground in case of insulation failure
- Measurement
  - Potential reference
  - Infinite sink source
  - Low impedence



## Earth wire (2)


- Cable
  - Overhead
    - Live and Neutral only
    - DIY Earth
  - Underground
    - Metal sheath, armoured, cable






## Earth wire (3)


 Earth loop impedance tester

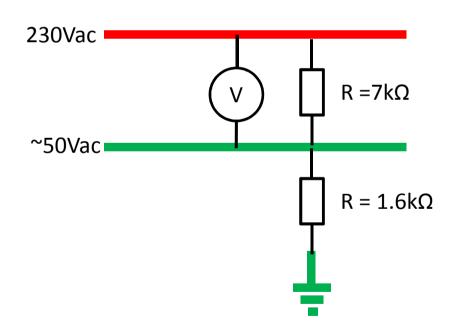

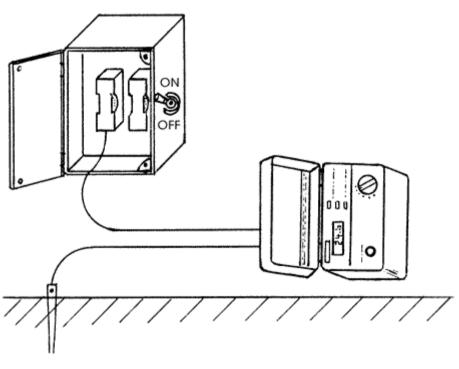

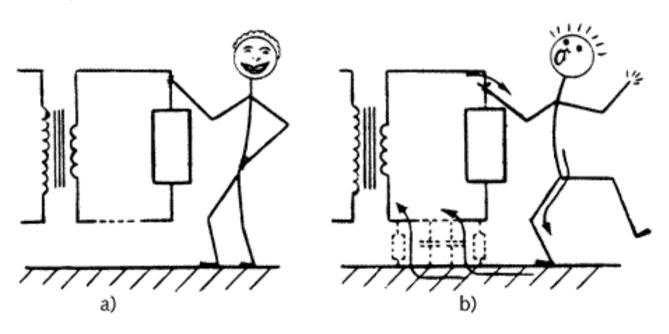
#### Earth wire (4)


- Floating vs grounded
  - Grounded: Completely define all points on a circuit
    - Expensive infrastructure
    - "Guaranteed" safety
  - Floating: Define nothing respect to anything!
    - "Complete" isolation from earth
    - Cheaper



#### Neutral wire

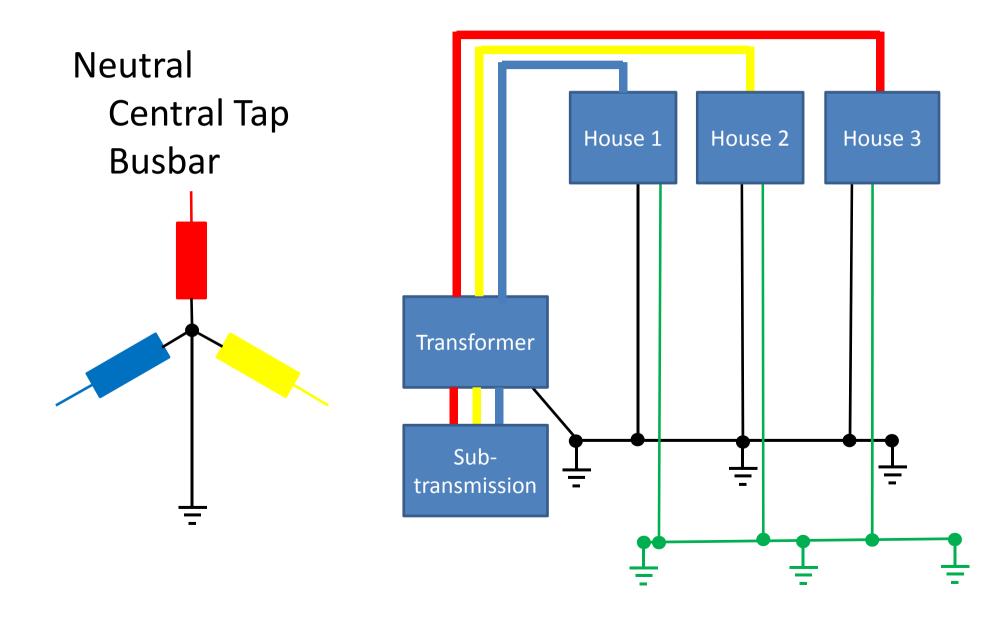


## Residential wiring

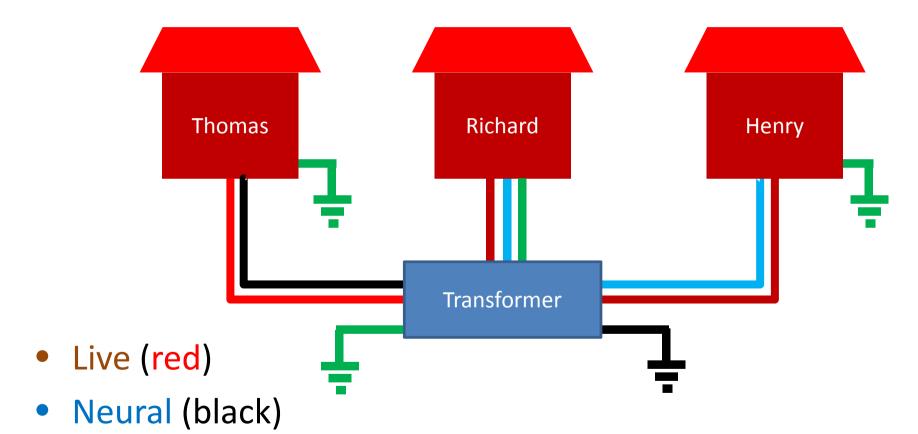

• Earth (green)

## Electricity in the home

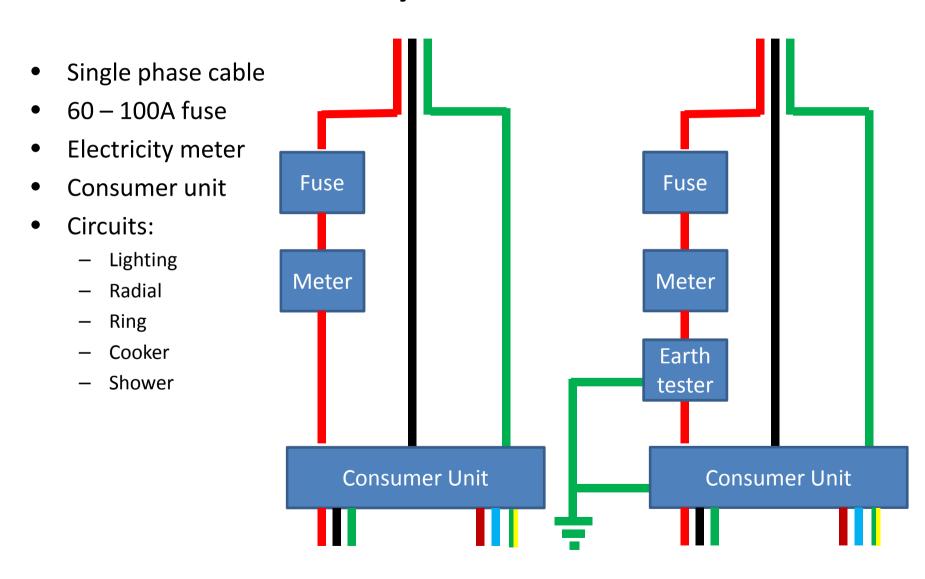

#### **Fuse**

- Fuse is a sacrificial device for over current detection
- First "fuse" proposed by Bregeut in 1847
- Modern fuse patented by Edision in 1890



- Construction
  - Wire: small cross section
  - Wire material: Zn, Cu, Al, Ag
  - Housing: Glass, ceramic, plastic, fibreglass
  - Inner medium: Air, sand (HV)
  - Variations: solder fuse, spring fuse

## Types of Fuse

- Rated current
- Rated voltage
- Speed
- I<sup>2</sup>t value
- Voltage drop
- Break capacity



#### Circuit Breaker

3 Phase 110kV oil drum circuit breaker




Mechanical (Miniature) Circuit Breaker (MCB)



Circuit breakers operate on the same principle regardless of their size

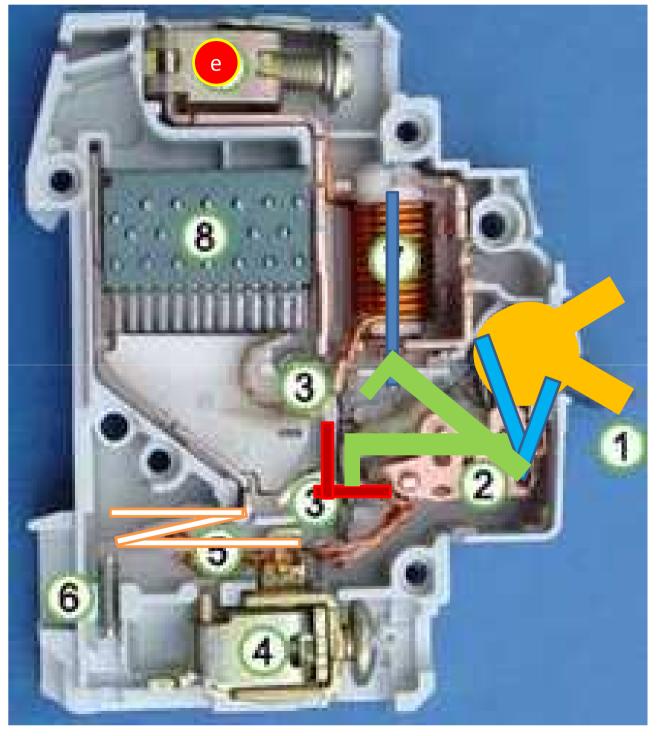- Detect fault condition
- Cut off (break) current flow
- Suppress arcs



#### MCB: How it works


- 1. Actuator lever
- Actuator mechanism
- 3. Contacts
- 4. Terminals
- 5. Bimetallic strip
- 6. Calibration screw
- 7. Solenoid
- 8. Arc divider / extinguisher

#### Residual Current Detector

- Residual current circuit breaker
- Kirschoff's first law

Trips on an imbalance between the current's

in the L and N lines

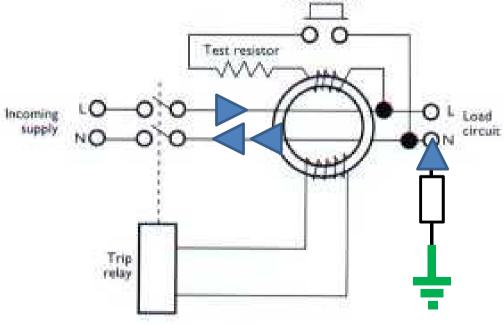

Test button

#### **Consumer Unit**

- MCB
- RCCD
- Busbar
  - Split Neutral
- WiringConsiderations



#### Wires and loops

#### **Purpose**


#### Wire rating

- Lighting
  - Ceiling rose
- Radial
- Ring
  - Spurs
- Special cases
  - Immersion heater
  - Showers
  - Cookers
  - Out buildings

	lapp / A	Imax / A	CSA / mm <sup>2</sup>
Lighting (100 W)	0.4 (4)	13.5 to 17.5	1 to 1.5
Sockets (double)	26 (18.2)	24!	2.5
Shower (8.5KW)	35	41	6
Shower (11.5KW)	48	57	10
Cooker (14KW)	29 (58)	32	4
Garage	16 – 26	24 - 32	2.5 – 4

- Diversity: Likelihood of having max demand
- X is the full load current of the largest appliance or circuit
  Y is the full load current of the second largest appliance or circuit
  Z is the full load current of the remaining appliances or circuits
- 100%X + 40%(Y+Z)

## Lighting

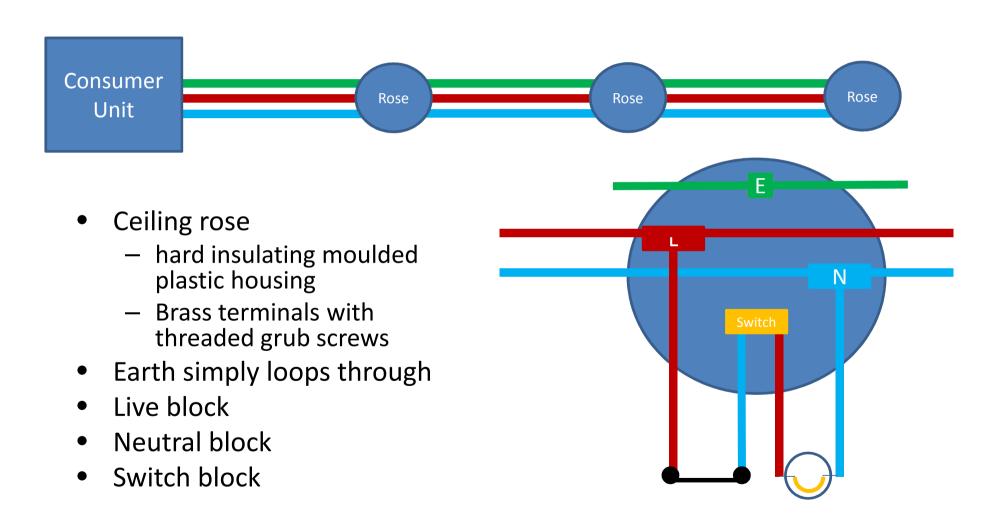

#### Radial vs Ring

Radial Circuit (20A)

Ring Circuit (32A)

