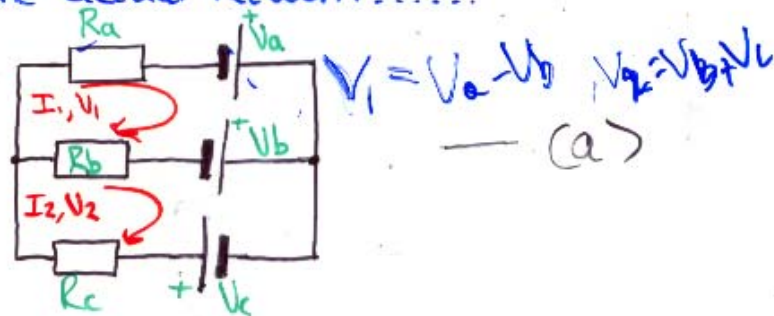



The following uses a simple electrical network to provide a physical interpretation of the C matrix utilised for active transformations.....

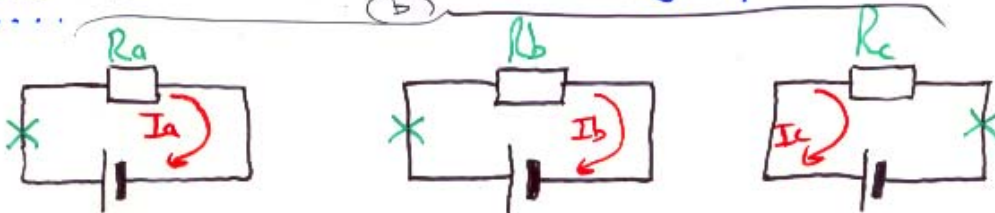Example of 'C' matrix (C.V. Jones, pg 71)

Consider the actual network.....



... which is obtain from the following 3 primitive circuits...



X - marks connection points - i.e. point where circuit is split for insertion of other circuit.

TWO IMPORTANT POINTS:-

- Currents in the individual resistors are the same in both systems (a) & (b).
 $\Rightarrow RI^2$ losses are same, both individually & in sum
 $\Rightarrow P$ dissipation is the same, i.e. Power Invariant
- Voltage sources of (b) are already in the SEPERABLE form. (C.V. Jones, pg 68)

• We have, for (b) ...

$$V_a = R_a I_a \quad V_b = R_b I_b \quad V_c = R_c I_c$$

• which can be written in matrix form

$$\begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix} = \begin{bmatrix} R_a & & \\ & R_b & \\ & & R_c \end{bmatrix} \cdot \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix}$$

N.B. Whenever a resistance or impedance matrix consists of terms on the leading diagonal only, then it represents a number of independent circuits.

• We have for (a)

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} R_a + R_b & -R_b \\ -R_b & R_b + R_c \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

• since the currents in the individual R's are the same in both systems then by inspection

$$I_a = +I_1$$

$$I_b = -I_1 + I_2$$

$$I_c = +I_2$$

which can be written in matrix form

$$\begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} +1 & & \\ -1 & +1 & \\ & +1 & \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

\Rightarrow

$$I = C I'$$