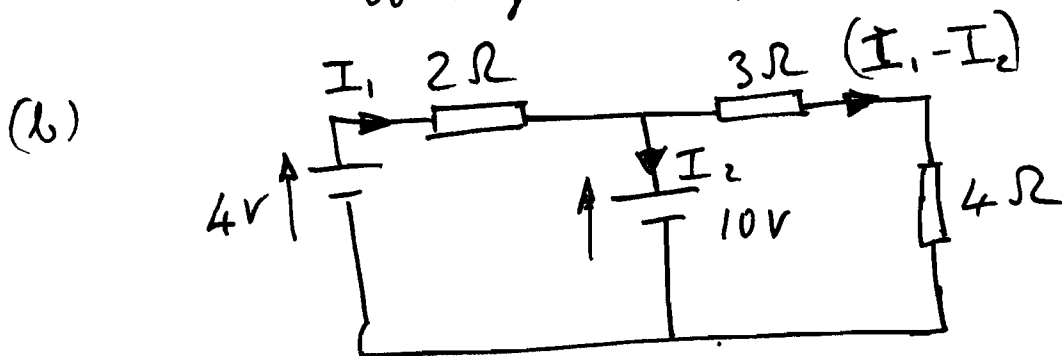


Answers.

- Q1 (a) K1 - current entering a node must equal the current leaving that node
or - the algebraic sum of the currents at a node is zero.
K2 - the algebraic sum of the voltages round a closed loop is zero.

Is it reasonable?

- K1 - if currents don't balance at a node electrons will continue to pile up or be depleted from the wire.
 K2 - if K2 is broken this implies the same point in the wire has 2 values of voltage - not possible.



Apply K1 at the nodes

K2 L.H. loop

$$4 - 2I_1 - 10 = 0 \quad \text{--- ①}$$

R.H. loop

$$10 - 3(I_1 - I_2) - 4(I_1 - I_2) = 0 \quad \text{--- ②}$$

2 equations and 2 unknowns hence can solve for I_1 and I_2

(2)

Q1 (cont.)

From ① $I_1 = -3 \text{ A}$.

Substitute into ②


$$10 - 7(-3 - I_2) = 0$$

$$\Rightarrow I_2 = -\frac{31}{7} = \underline{-4.3 \text{ A}}$$

Other branch

$$I_1 - I_2 = -3 + 4.3 \\ = \underline{1.3 \text{ A}}$$

(c)

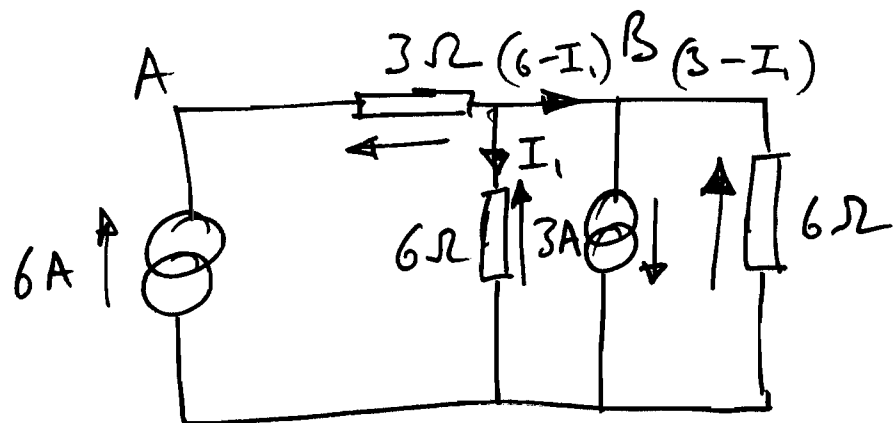

2

Apply K1 to get branch currents

Apply K2 to loop bounded by 6Ω resistors (does not include the current sources).

$$\text{i.e. } 6I_1 - 6/(3 - I_1) = 0$$

$$\therefore 6I_1 - 18 + 6I_1 = 0$$



$$\Rightarrow I_1 = \frac{18}{12} = \underline{\underline{1.5 \text{ A}}}$$

$$\text{Voltage at B} = 6(3 - I_1) = \underline{9 \text{ V}}$$

$$\text{Voltage at A} = 9 + (6 \times 3) = \underline{27}$$

Q2

(a)

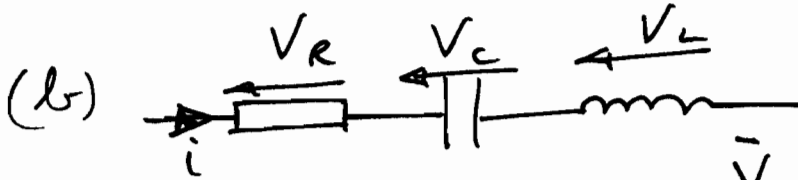
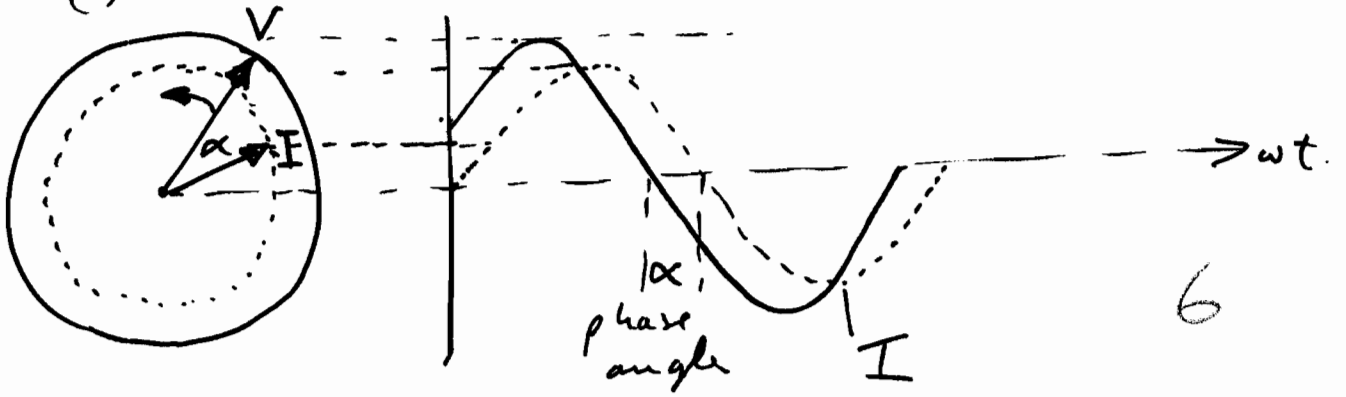


current is common

Circuit is in resonance when it becomes purely resistive.

$$\text{i.e. } \omega L = \frac{1}{\omega C}$$


$$\omega = \sqrt{\frac{1}{LC}}$$

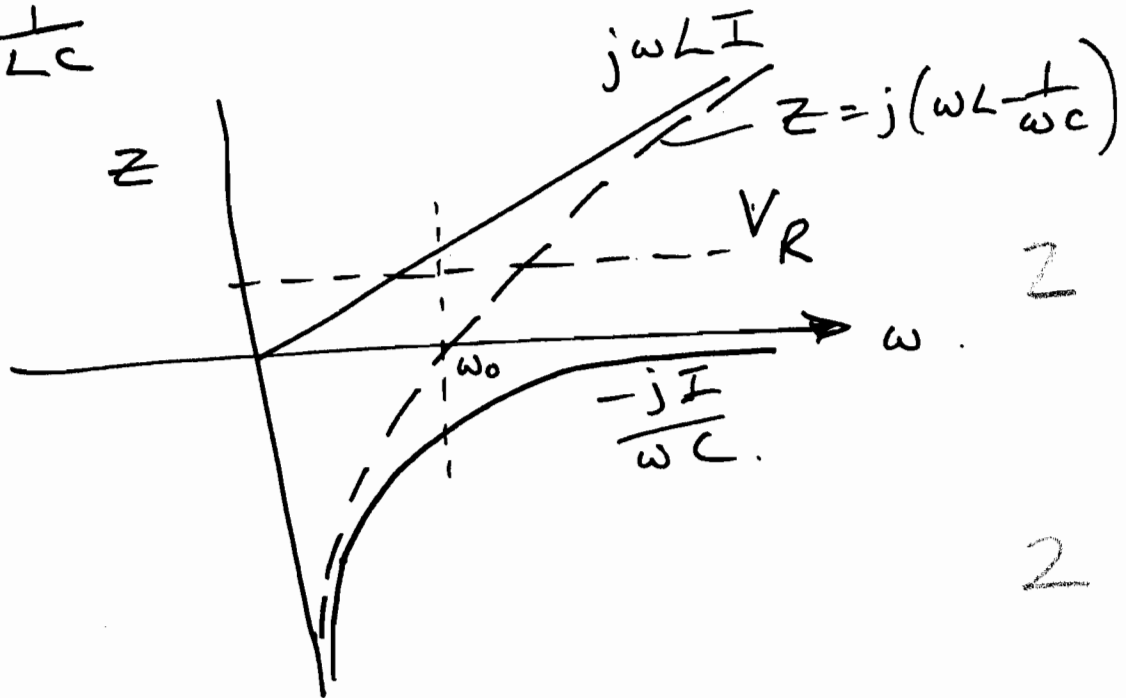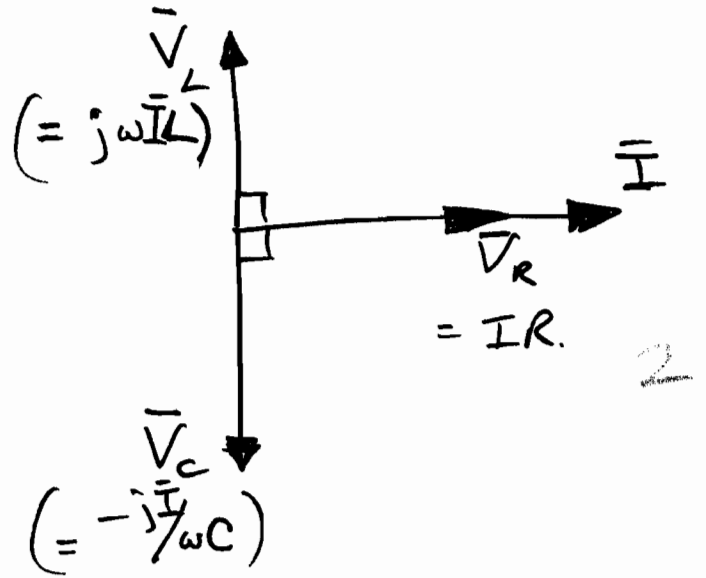

Q2(cont.)

(4)

(c)

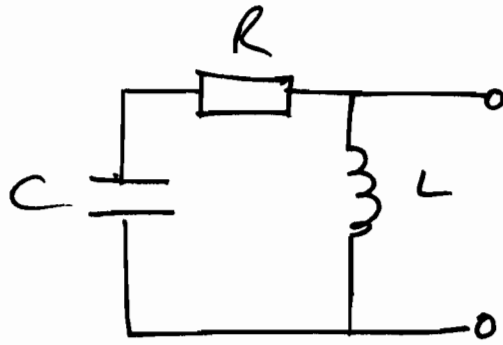

$$Z = j\omega L // (R - j/\omega C)$$

2

$$= \frac{j\omega L(R - j/\omega C)}{j\omega L + R - j/\omega C}$$

$$= \frac{j\omega LR + \frac{L}{C}}{j(\omega L - \frac{1}{\omega C}) + R}$$

$$= \frac{(j\omega LR + \frac{L}{C})(-j(\omega L - \frac{1}{\omega C}) + R)}{(\omega L - \frac{1}{\omega C})^2 + R^2}$$

2

Consider numerator only

$$j\omega LR^2 + \omega LR(\omega L - \frac{1}{\omega C}) + \frac{LR}{C} - j\frac{L}{C}(\omega L - \frac{1}{\omega C})$$

At resonance set j terms = 0

2

$$\text{ie. } \omega LR^2 - \frac{L}{C}(\omega L - \frac{1}{\omega C}) = 0$$

$$\Rightarrow \omega = \sqrt{\frac{1}{LC - C^2 R^2}}$$

2

Q 3 (a) From definition of capacitance

$$Q = CV$$

Also $i = \frac{dQ}{dt}$ (definition of current)

$$= \frac{d(CV)}{dt} = C \frac{dV}{dt} \quad (C \text{ is a constant})$$

To get voltage, separate variables and integrate

$$\int \frac{i}{C} dt = \int_{V_0}^V dV = V - V_0$$

where V_0 = initial voltage on capacitor

V = final voltage on capacitor

$$\therefore V = V_0 + \frac{1}{C} \int i dt$$

from above, if " i " is a constant then


$$V = V_0 + \frac{i}{C} t$$

ie. V will increase linearly with time.

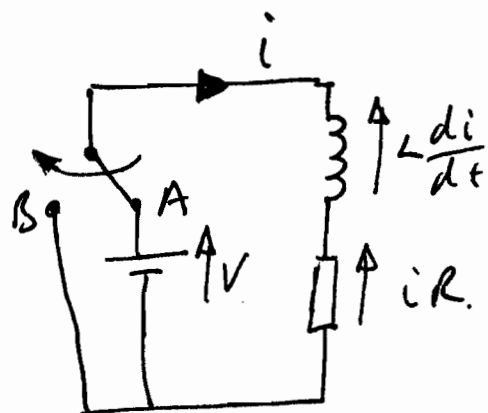(b) After switch operation i continues to flow until energy stored in the inductor is all dissipated in R

$$t < 0 \quad i = I_0 = \frac{V}{R}$$

$$t > 0 \quad \text{KVL gives } L \frac{di}{dt} + iR = 0$$



(6)

Q 3 (cont.)

separate variables and integrate

$$\int \frac{1}{i} di = -\frac{R}{L} \int dt$$

$$\Rightarrow -\frac{L}{R} \ln i = t + A$$

to get A $i = I_0$ at $t = 0$

$$\therefore -\frac{L}{R} \ln I_0 = A$$

$$\therefore -\frac{L}{R} [\ln i - \ln I_0] = t$$

$$\Rightarrow \underline{i(t) = I_0 e^{-Rt/L}} \quad 3$$

(c) current in inductor $\bar{I}_L = \frac{\bar{V}}{j8} = \frac{20}{j8} = -j2.5 \text{ A}$

current in capacitor $\bar{I}_C = \frac{20}{5-j12} = \frac{20(5+j12)}{5^2+12^2} \quad 2$

$$= \underline{0.6 + j1.44}$$

$$\therefore \text{Total current from source} = \bar{I}_L + \bar{I}_C$$

$$= -j2.5 + 0.6 + j1.44$$


$$= \underline{0.6 - j1.06 \text{ A}} \quad 2$$

Magnitude $|\bar{I}_L + \bar{I}_C| = \sqrt{0.6^2 + 1.06^2}$

$$= \underline{1.22 \text{ A}} \quad 2$$

Q 4 (a) Voltage ratio in dB = $20 \log_{10} \left(\frac{V_2}{V_1} \right)$ | ⑦
 Power ratio in dB = $10 \log_{10} \left(\frac{P_2}{P_1} \right)$ |
 dB is a log scale which allows large variations in ratio values to be illustrated graphically. 2

(b) low pass filter

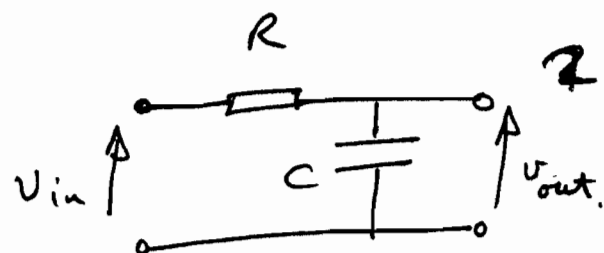

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega CR} \quad 2$$

cut-off frequency $\omega_0 = \frac{1}{CR} \quad 2$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{1}{1 + j\frac{\omega}{\omega_0}}$$

At $\omega = \omega_0$ $\left| \frac{V_{out}}{V_{in}} \right| = \left| \frac{1}{1 + j} \right| = \frac{1}{\sqrt{2}}$

At $\omega \gg \omega_0$ $\left| \frac{V_{out}}{V_{in}} \right| = \frac{\omega_0}{\omega}$ ie $\propto \frac{1}{\omega} \quad 2$

ie. ratio will reduce according to $\frac{1}{\omega}$ (not sharp)

For $\omega \gg \omega_0$ $20 \log_{10} \left(\frac{\omega_0}{\omega} \right)$ at ω

and $20 \log_{10} \frac{\omega_0}{10\omega}$ at 10ω ie. decade increase in frequency

\therefore Difference in dB = $dB_{10\omega} - dB_{\omega}$

$$= 20 \log_{10} \frac{\omega_0/10\omega}{\omega_0/\omega} = 20 \log_{10} \frac{1}{10} = -20 \text{ dB} \quad 4$$

Q4 (cont.)

(8)

ie. 20 dB/decade "roll-off"

$$(c) \quad Q = R \sqrt{\frac{C}{L}} = 5 \Rightarrow C = \frac{L}{100}$$

$$f_R = \frac{1}{2\pi \sqrt{LC}} = 3 \times 10^4 \text{ Hz}$$

$$\therefore LC = \left(\frac{1}{2\pi \times 3 \times 10^4} \right)^2 = 2.8 \times 10^{-11}$$

$$\therefore 100 C^2 = 2.8 \times 10^{-11}$$
$$\Rightarrow C = \sqrt{\frac{2.8 \times 10^{-11}}{100}} = \frac{0.53 \mu F}{2}$$

$$\therefore L = 100 C = \frac{53 \mu H}{2}$$