



The
University
Of
Sheffield.

**Data Provided: Smith Chart (3 copies),
Useful equations are given at the end
of the paper**

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Autumn Semester 2013-2014 (2 hours)

High Speed Electronic Circuit Design

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1.
 - a. Explain briefly what is meant by a matched transmission line, and what is the input impedance of this line. (2)
 - b. A lossless transmission line with a length of 2 cm and a characteristic impedance of 50Ω is terminated with a complex load impedance of $(70-j30)\Omega$ at a frequency of 2GHz. Use the required transmission line equations to calculate the input impedance, input reflection coefficient, voltage standing wave ratio, insertions and return losses. (6)
 - c. It is desired to use a section of a lossless 50Ω transmission line terminated in a short circuit to construct an equivalent inductance with a reactance of 25Ω . Assuming the guided wavelength is 75% of the free space wavelength at a frequency of 1 GHz. Determine the shortest possible line length that would exhibit the desired reactance at its input. (5)
 - d. Consider a lossless transmission line, which has a characteristic impedance of Z_0 and terminated by a load impedance of Z_L . Show that the voltage reflection coefficient at the load is given by $\Gamma = (Z_L - Z_0) / (Z_L + Z_0)$. (7)
2.
 - a. Explain the advantages of using the Smith Chart in network analysis. (4)
 - b. A lossy line with attenuation of 15 dB/m at 300 MHz, is terminated by a load with a normalized impedance of $z=3+j1$. Use the Smith chart to find the VSWR at a distance of 10cm from the load. (6)
 - c. For a transmission line with a characteristic impedance of $Z_0=50\Omega$ and terminated by a load impedance $Z_L=(150-j30)\Omega$, design a double stub matching network to match Z_L to Z_0 . The 1st stub is located at the load, and the two stubs are separated by a distance of 0.125λ .
Find one possible solution in which the length of each stub is $\leq 0.25\lambda$. (10)

3. a. Explain with aid of a diagram the difference between the input reflection coefficient and the S_{11} scattering parameter in a two ports network. (4)
- b. Explain with the aid of diagrams what is meant by the transmission matrix representation, ABCD, and why it is useful when analysing the cascade of two networks. (4)
- c. Explain briefly the interaction of the incident and reflected waves in a two port network and how it can be represented using the scattering matrix. (4)
- d. Derive expressions for the scattering parameters, S_{ij} ($i,j=1$ or 2), of the two-port network shown in Figure 1. Assume the characteristic impedances for the input and output ports are equal ($Z_{01}=Z_{02}$). (4)

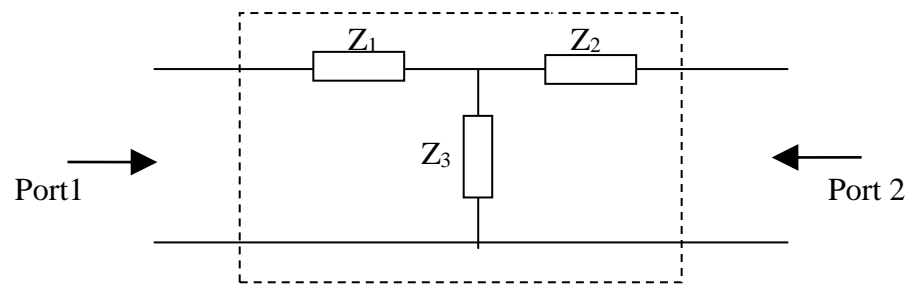


Figure 1

4. a. Explain briefly how an amplifier can be designed for a maximum gain. (2)
- b. Explain with the aid of diagrams what is meant by the unconditional stability of an amplifier. (4)
- c. Consider a two-port network with a characteristic impedance of Z_0 and with the following S parameters: $S_{11} = 0.1\angle 0^\circ$, $S_{21} = 0.8\angle 90^\circ$, $S_{12} = 0.8\angle 90^\circ$, $S_{22} = 0.2\angle 0^\circ$. What is the input reflection coefficient at port 1 when port 2 is terminated with a short circuit load? (4)
- d. Design an amplifier to have a gain of 10dB at 6GHz using a transistor with the following S parameters ($Z_0=50\ \Omega$): $S_{11} = 0.61\angle -170^\circ$, $S_{21} = 2.24\angle 32^\circ$, $S_{12} = 0.$, $S_{22} = 0.72\angle -83^\circ$. Plot, and use, constant gain circles for $G_s=0.5\text{dB}$, $G_s=1.5\text{dB}$, $G_L=1.5\text{dB}$ and $G_L=2.5\text{dB}$. (10)

You may find the following information useful:

The constant gain and noise figure circles can be plotted using the following set of equations

$$C_S = \frac{g_S S_{11}^*}{1 - (1 - g_S) |S_{11}|^2}$$

$$r_S = \frac{\sqrt{1 - g_S} (1 - |S_{11}|^2)}{1 - (1 - g_S) |S_{11}|^2}$$

$$C_L = \frac{g_L S_{22}^*}{1 - (1 - g_L) |S_{22}|^2}$$

$$r_L = \frac{\sqrt{1 - g_L} (1 - |S_{22}|^2)}{1 - (1 - g_L) |S_{22}|^2}$$

SKK