

(1)

Q1 (i)  $V_s$  sees  $R_1$  in series with the parallel combination  $R_2$  and ( $R_3$  in series with  $R_4$ )

$$\begin{aligned} \text{ie } R_{\text{eff}} &= R_1 + R_2 \parallel (R_3 + R_4) \\ &= 2 + 10 \parallel 40 = 2 + \frac{400}{50} \\ &= \underline{\underline{10 \Omega}} \end{aligned}$$

$$\therefore I_s = V_s / R_{\text{eff}} = \frac{20 \text{ V}}{10 \Omega} = \underline{\underline{2 \text{ A}}}$$

(ii) This can be done in two ways. Either

$$V_A = V_s - I_s R_1 = 20 - 2 \cdot 2 = \underline{\underline{16 \text{ V}}}$$

$$\text{or } V_A = I_s (R_2 \parallel (R_3 + R_4)) = 2 \cdot 8 = \underline{\underline{16 \text{ V}}}$$

(iii) Current sum at node A is

$$I_s = I_2 + I_3$$

(iv) Can be done two ways .... (only one needed)

(a) nodal  $I_s = I_2 + I_3$

$$\text{or } \frac{V_s - V_A}{R_1} = \frac{V_A}{R_2} + \frac{V_A}{R_3 + R_4}$$


$$\text{or } \frac{20}{2} = V_A \left[ \frac{1}{2} + \frac{1}{10} + \frac{1}{40} \right] = V_A \frac{28}{40}$$

$$\text{or } V_A = \frac{20}{2} \times \frac{8}{5} = 16 \text{ V (as before)}$$

$$\text{so } I_2 = V_A / R_2 = \underline{\underline{1.6 \text{ A}}}$$

(b) loops ....

two loops,  $I_A + I_B$ .

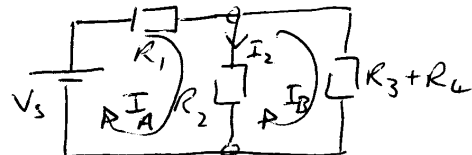

$$V_s = I_A R_1 + (I_A - I_B) R_2 \quad \text{--- (1)}$$

$$0 = (I_B - I_A) R_2 + I_B (R_3 + R_4) \quad \text{--- (2)}$$

(2)

$$\textcircled{1} \text{ gives } 20 = I_A \cdot 12 - I_B \cdot 10$$

$$\textcircled{2} \text{ gives } 0 = -I_A \cdot 10 + I_B \cdot 50 \text{ or } I_A = 5I_B$$

$$\text{sub } \textcircled{2} \text{ in } \textcircled{1} \dots 20 = 5I_B \cdot 12 - 10I_B$$

$$= 60I_B - 10I_B = 50I_B$$

$$\text{or } I_B = \frac{20}{50} = 0.4 \text{ A}$$

$$\therefore I_A = 5 \times 0.4 = 2 \text{ A (as before)}$$

$$I_2 = I_A - I_B = 2 - 0.4 = \underline{\underline{1.6 \text{ A}}}$$

(v) This can be solved most easily by nodal analysis or superposition...

(a) nodal Sum currents at A..

$$I_s + 2.5A = I_2 + I_3$$

$$\frac{20 - V_A}{2\Omega} + 2.5A = \frac{V_A}{10\Omega} + \frac{V_A}{40\Omega}$$

$$V_A \left[ \frac{1}{2} + \frac{1}{10} + \frac{1}{40} \right] = \frac{20}{2} + 2.5 = 12.5 \text{ A}$$

$$V_A = 12.5 \times \frac{40}{25} = 20 \text{ V}$$

$$\text{Thus, } I_3 = \frac{20}{40} = \underline{\underline{0.5 \text{ A}}}$$

$$P_{R_1} = I_s^2 R_1 = 0^2 \times R_1 = \underline{\underline{0 \text{ W}}}$$

(b) superposition From earlier parts,

$$I_s / \text{due to } V_s = 2 \text{ A}$$

$$I_3 / \text{due to } V_s = 0.4 \text{ A}$$

$$\text{due to current source, } V_A = 2.5 \times 40 \parallel 2 \parallel 10$$

$$= 2.5 \times 1.6\Omega = 4 \text{ V}$$

$$I_s / \text{due to } 2.5 \text{ A} = -\frac{4 \text{ V}}{2\Omega} = -2 \text{ A}$$

$$I_3 / \text{due to } 2.5 \text{ A} = \frac{4 \text{ V}}{40\Omega} = 0.1 \text{ A}$$

$$\therefore I_{s \text{ TOT}} = 2 - 2 = 0 \text{ A so } P_{R_1} = \underline{\underline{0 \text{ W}}}$$

$$I_{3 \text{ TOT}} = 0.4 \text{ A} + 0.1 \text{ A} = \underline{\underline{0.5 \text{ A}}}$$

Q2(a) For the circuits to be equivalent, open circuit output voltage from each network must be the same and the short ckt output current must also be the same.

ckt (i)  $V_{oc} \dots$

$$V_{oc} = \frac{V_s \cdot R_2}{R_1 + R_2}$$

ckt (ii)  $V_{oc} \dots$

$$V_{oc} = V_{Th}$$

$$\therefore V_{Th} = \frac{V_s R_2}{R_1 + R_2}$$

ckt (i)  $i_{sc} \dots$

$$i_{sc} = V_s / R_1$$


(since  $R_2$  is short circuited).

ckt (ii)  $i_{sc} \dots$

$$i_{sc} = \frac{V_{Th}}{R_{Th}} = \frac{V_s \frac{R_2}{R_1 + R_2}}{\frac{R_1 R_2}{R_1 + R_2}}$$

$$\text{so } V_s / R_1 = \frac{V_s \frac{R_2}{R_1 + R_2}}{R_{Th}}$$
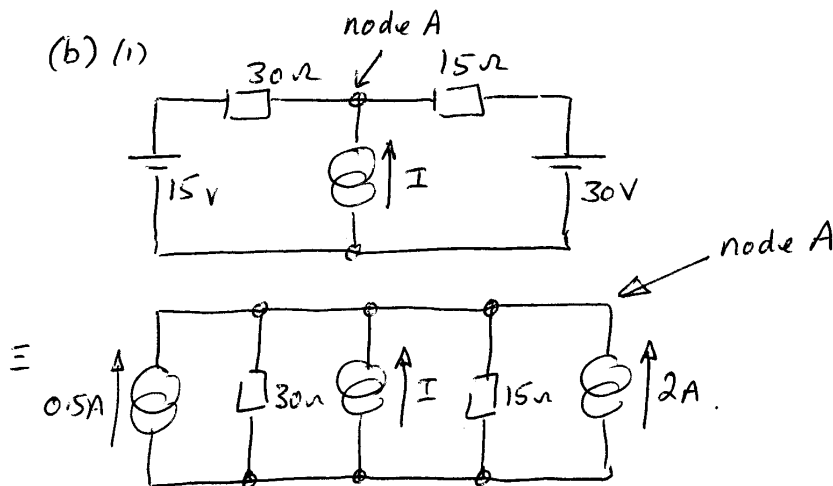
$$\text{or } R_{Th} = \frac{R_1 R_2}{R_1 + R_2} = \underline{\underline{R_1 \parallel R_2}}$$



(ii) To get  $V_A$  of zero we want zero current through the resistors.

Summing current at node A ....

$$0.5 + I + 2 = 0$$

$$\text{or } \underline{\underline{I = -2.5A}}$$

(4)

(c)(i) When switch changed to position A,

$$V_s = IR + \frac{1}{C} \int I dt + \text{const.}$$

differentiating with respect to  $t$  gives

$$0 = R \frac{dI}{dt} + \frac{1}{C} I \quad \text{or} \quad \frac{dI}{I} = -\frac{dt}{RC}$$

$$\text{thus} \quad \int \frac{1}{I} dI = -\frac{1}{RC} \int dt + C$$

$$\text{or} \quad \ln I = -\frac{t}{RC} + C$$

$$\text{when } t=0, I = V_s/R = I_0 \quad \left[ \begin{array}{l} \text{since at } t=0, V_c \\ = 0 \text{ and all } V_s \\ \text{appears across } R \end{array} \right]$$

$$\text{so } C = \ln I_0$$

$$\therefore \ln I - \ln I_0 = -t/RC$$

$$\ln \frac{I}{I_0} = -t/RC \quad \text{or} \quad I = I_0 e^{-t/RC}$$

$$= \underline{\underline{V_s/R e^{-t/RC}}}$$

$$(ii) \quad V_c = \frac{1}{C} \int I dt + C$$

$$= \frac{1}{C} \int \frac{V_s}{R} e^{-t/RC} dt + C$$


$$= \frac{V_s}{CR} \cdot (-1) \frac{1}{(\frac{1}{CR})} e^{-t/RC} + C = -V_s e^{-t/RC} + C$$

$$\text{when } t=0, V_c = 0 \quad \text{so} \quad C = V_s$$

$$\text{and } \underline{\underline{V_c(t) = V_s(1 - e^{-t/RC})}}$$

(5)

Q3(a)(i).

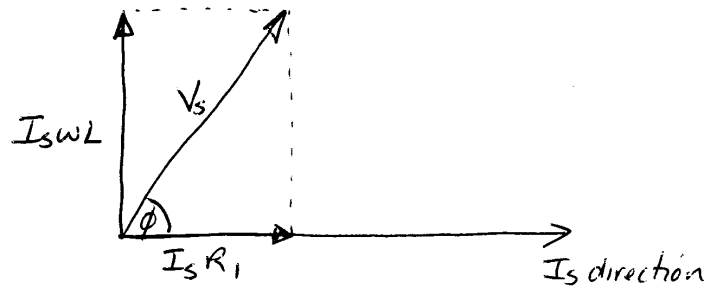

The angle between  $I_s$  &  $V_s$  is

$$\tan^{-1} \frac{\omega L}{R_1} = \tan^{-1} \frac{2\pi \cdot 500 \cdot 2.5 \times 10^{-3}}{5}$$

$$= 57.5^\circ$$


$I_s$  with respect to  $V_s$  is  $-57.5^\circ$

$$(ii) \quad \frac{V_s}{I_s} = j\omega L + R_1 = Z$$

$$Z = 5 + 2\pi \cdot 500 \cdot 2.5 \times 10^{-3} j = \underline{\underline{5 + j7.85}}$$

$$|Z| = \left[ 5^2 + 7.85^2 \right]^{1/2} = \underline{\underline{9.31 \Omega}}$$

$$(b) \quad V_Z = V_{s1} - V_{s2}$$

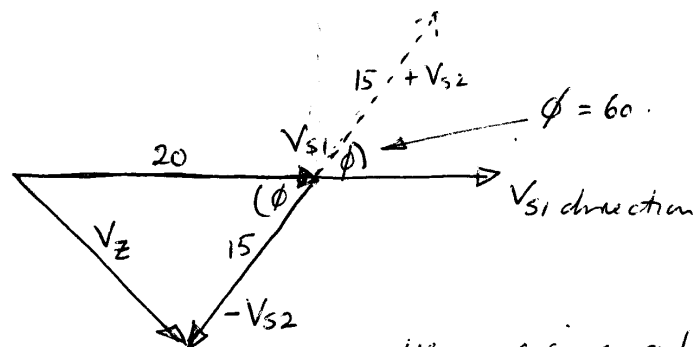

using cosine rule...

$$V_Z^2 = 20^2 + 15^2 - 2 \times 20 \times 15 \cos 60 = 400 + 225 - 300$$

$$= 325 \quad \underline{\underline{|V_Z| \approx 18 V}}$$

(6)

$$(ii) \quad V_{s1} = 20 \angle 0 = \underline{20 + j0}$$

$$\begin{aligned} V_{s2} &= 15 \angle 60 = 15 \cos 60 + j 15 \sin 60 \\ &= \underline{7.5 + j13} \end{aligned}$$

$$\begin{aligned} (iii) \quad I_z &= \frac{V_z}{Z} = \frac{20 + j0 - 7.5 - j13}{3 - j4} \\ &= \frac{12.5 - j13}{3 - j4} \\ &= \frac{(12.5 - j13)(3 + j4)}{3^2 + 4^2} \\ &= \frac{37.5 - j39 + j50 + 52}{25} \\ &= \frac{89.5 + j11}{25} = \underline{3.58 + j0.44} \end{aligned}$$

$$\therefore |I_z| = [3.58^2 + 0.44^2]^{1/2} = \underline{3.6A}$$

$$\angle I_z = \tan^{-1} \frac{11}{89.5} = \underline{7^\circ}$$

(7)

4(a) (i) A circuit is resonant when its impedance becomes purely real.

$$(ii) \quad V_s = I_s \left( j\omega L + \frac{1}{j\omega C} + R \right)$$

$$\frac{V_s}{I_s} = Z = j\left(\omega L - \frac{1}{\omega C}\right) + R.$$

At the resonant frequency, the  $j$  terms must disappear so

$$j\left(\omega L - \frac{1}{\omega C}\right) = 0$$

$$\text{or } \omega L = \frac{1}{\omega C}$$

$$\text{or } \omega^2 = \frac{1}{LC} \quad \text{or } \omega = 2\pi f = \frac{1}{\sqrt{LC}}$$

$$\therefore \underline{f = \frac{1}{2\pi\sqrt{LC}}}$$

$$(iii) \quad Q = \frac{|V_L|}{|V_R|} \text{ at resonance (ie when } \omega = \frac{1}{\sqrt{LC}}).$$

$$\text{so } Q = \frac{I_s \omega L}{I_s R} = \frac{\omega L}{R} = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R} = \underline{\underline{\frac{1}{R} \sqrt{\frac{L}{C}}}}$$

(iv) If  $f < f_r$  .....

At resonance  $X_C = X_L$ . Below resonance  $X_C$  is increased and  $X_L$  is reduced. Since the circuit is a series circuit,  $X_C$  (the larger reactance) will dominate and the circuit will look capacitive.

(8)

$$\begin{aligned}
 (b) (i) \quad V_s &= I_s (X_C \parallel (R + X_L)) \\
 &= I_s \frac{\frac{R + j\omega L}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}
 \end{aligned}$$

$$\begin{aligned}
 \frac{V_s}{I_s} = Z &= \frac{R + j\omega L}{j\omega CR + (j\omega)^2 LC + 1} \\
 &= \frac{R + j\omega L}{(1 - \omega^2 LC) + j\omega CR}
 \end{aligned}$$

(ii). Rationalise to an  $a + jb$  form ....

$$\begin{aligned}
 \frac{V_s}{I_s} &= \frac{(R + j\omega L)((1 - \omega^2 LC) - j\omega CR)}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2} \\
 &= \frac{R(1 - \omega^2 LC) + j\omega L(1 - \omega^2 LC) + \omega^2 LCR - j\omega CR^2}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2} \\
 &= \underbrace{[R(1 - \omega^2 LC) + \omega^2 LCR]}_{\text{real}} + j\omega \underbrace{[L(1 - \omega^2 LC) - CR^2]}_{\text{imaginary}}
 \end{aligned}$$

equating "j" terms to zero ....

$$L(1 - \omega_r^2 LC) = CR^2$$

$$\text{or } \omega_r^2 LC = L - CR^2$$

$$\text{or } \omega_r^2 = \frac{L}{L^2 C} - \frac{CR^2}{L^2 C}$$

$$\omega_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$