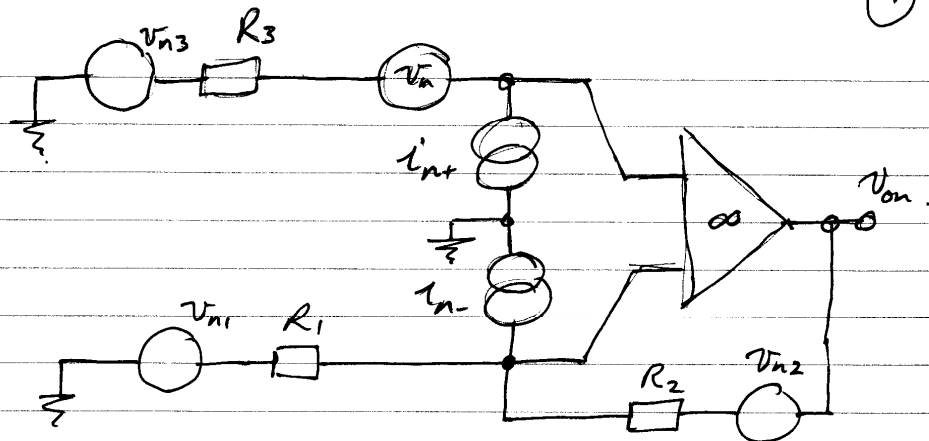


Derivation of op-amp circuit noise performance

①




① V_{on} due to V_n

$$V^+ = V_n$$

V^+ is operated on by the non-inverting amplifier gain (R_3 has no effect).

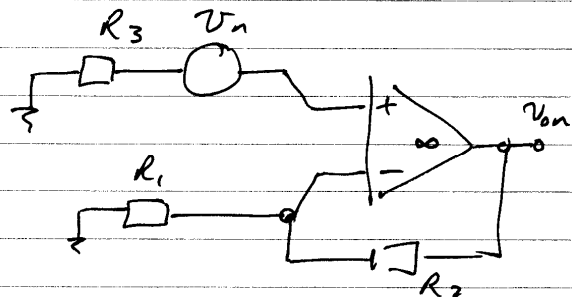
$$V_{on}/V_n = V_n \frac{R_1 + R_2}{R_1}$$



② V_{on} due to V_{n3}


V_{n3} is in the same position in the circuit as V_n to is treated in the same way.
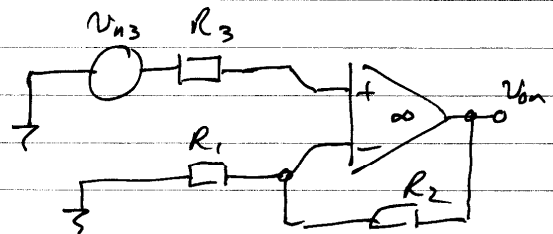
$$V_{on}/V_{n3} = V_{n3} \frac{R_1 + R_2}{R_1}$$



③ V_{on} due to i_{n+}

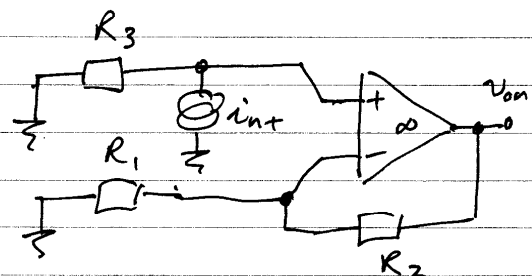i_{n+} cause a voltage $i_{n+} R_3$ across R_3 which again is operated on as for V_n . $V_{on}/i_{n+} = i_{n+} R_3 \cdot \frac{R_1 + R_2}{R_1}$.




Derivation of op-amp circuit noise performance

(2)

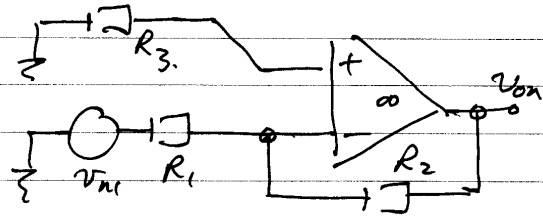(4) V_{on} due to R_1 ----


The amplifier looks like an inverting amplifier as far as R_1 is concerned.



$$V_{on} / R_1 = -V_{n1} \frac{R_2}{R_1}$$


(5) V_{on} due to R_2 ----

$$V_{on} / R_2 = V_{n2}$$

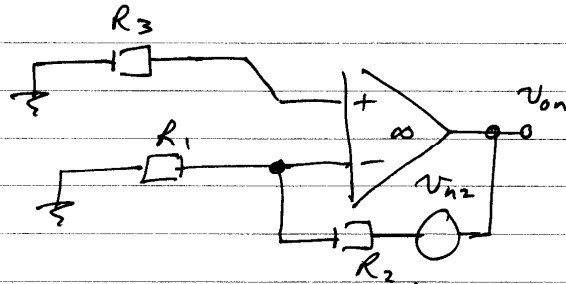

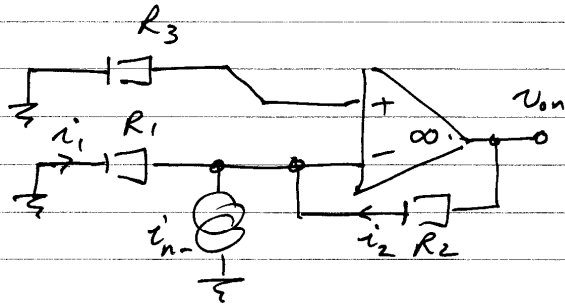(6) V_{on} due to i_n ----

i_1 must be zero because v^- is zero so there is no voltage across R_1 so $i_2 = i_n$ and a voltage $i_n R_2$ will be developed across R_2 .



Since $v^- = 0$, $V_{on} / i_n = i_n R_2$

So

$$\begin{aligned} \overline{V_{on}^2} = & \overline{V_{n1}^2} \left(\frac{R_1 + R_2}{R_1} \right)^2 + \overline{V_{n2}^2} \left(\frac{R_1 + R_2}{R_1} \right)^2 + \overline{i_{n1}^2} R_3^2 \left(\frac{R_1 + R_2}{R_1} \right)^2 \\ & + \overline{V_{n1}^2} \frac{R_2^2}{R_1^2} + \overline{V_{n2}^2} + \overline{i_{n-}^2} R_2^2 \end{aligned}$$

Derivation of op-amp circuit noise performance

3

$$= \left(\frac{R_1 + R_2}{R_1} \right)^2 \left[\overline{v_n^2} + \overline{v_{n3}^2} + \overline{i_{n+}^2} R_3^2 + \frac{R_2^2}{R_1^2} \frac{R_1^2}{(R_1 + R_2)^2} \overline{v_{n1}^2} \right. \\ \left. + \frac{R_1^2}{(R_1 + R_2)^2} \overline{v_{n2}^2} + \overline{i_{n-}^2} R_2^2 \frac{R_1^2}{(R_1 + R_2)^2} \right]$$

$$= G^2 \left[\overline{i_{n+}^2} R_3^2 + \overline{i_{n-}^2} \left(\frac{R_1 R_2}{R_1 + R_2} \right)^2 + \overline{v_n^2} + \overline{v_{n3}^2} \right. \\ \left. + \overline{v_{n1}^2} \frac{R_2^2}{(R_1 + R_2)^2} + \overline{v_{n2}^2} \frac{R_1^2}{(R_1 + R_2)^2} \right]$$

$$= G^2 \left[\overline{i_{n+}^2} R_3^2 + \overline{i_{n-}^2} \left(\frac{R_1 R_2}{R_1 + R_2} \right)^2 + \overline{v_n^2} + \overline{v_{n3}^2} \right. \\ \left. + \frac{4kTR_1 R_2^2}{(R_1 + R_2)^2} + \frac{4kTR_2 R_1^2}{(R_1 + R_2)^2} \right]$$

$$= G^2 \left[\overline{i_{n+}^2} R_3^2 + \overline{i_{n-}^2} \left(\frac{R_1 R_2}{R_1 + R_2} \right)^2 + \overline{v_n^2} + \overline{v_{n3}^2} + \overline{v_{nf}^2} \right]$$

$$\text{where } \overline{v_{nf}^2} = \frac{4kTR_1 R_2 (R_1 + R_2)}{(R_1 + R_2)^2} = \frac{4kTR_1 R_2}{R_1 + R_2}$$

= noise expected from $R_1 \parallel R_2$ where R_1 & R_2 are the feedback resistors.