

Data Provided: None



The
University
Of
Sheffield.

DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING

Spring Semester 2014-15 (2.0 hours)

EEE335 Integrated Electronics

Answer **THREE** questions. **No marks will be awarded for solutions to a fourth question.** Solutions will be considered in the order that they are presented in the answer book. Trial answers will be ignored if they are clearly crossed out. **The numbers given after each section of a question indicate the relative weighting of that section.**

1. **Figure 1** shows the schematic for a digital circuit.

 


Figure 1: Digital Circuit

- a. Derive the logic function of the circuit in **Figure 1**. (2)
- b. Draw the *transistor-level* schematic diagram for a CMOS circuit that would implement the function in **Figure 1**. There may be more than one way to implement this function: justify the way in which you have implemented the circuit. (6)
- c. Size the transistors in the circuit that you have drawn, assuming that the gate is *minimum-sized* (using the normal definition for this). (4)
- d. Assuming that the gate capacitance associated with a minimum-sized *n*-type FET is 0.5fF, estimate the capacitance associated with each of the connections (wires connecting inputs and output, and any intermediate wires between separate sub-circuits) in your *transistor-level* circuit. (2)
- e. Rather than implement the circuit in Figure 1 as a specific circuit, you decide to implement each of the individual logic gates separately as CMOS circuits. What would be the important differences between the implementation of the circuit as a whole and as separate, individual parts. (6)

2. a. A pass transistor is incorporated in a circuit as shown in **Figure 2**.

 


Figure 2: Pass Transistor Circuit

Initially (and for some time), $V_{in}=0V$, $V_G=V_{DD}$ (a voltage which is above the threshold voltage, V_T , of the transistor). You may assume that the gain of the transistor is K_N .

- i). At time, $t=0$, the input V_{in} is changed to V_{DD} . Verify that the response of V_{out} as a function of t in the period $t \geq 0$ is:

$$V_{out}(t) = (V_{DD} - V_T) - \frac{(V_{DD} - V_T)}{1 + \frac{K_N(V_{DD} - V_T)t}{2C}} \quad (4)$$

- ii). Identify the value of voltage to which V_{out} becomes asymptotic. Explain why this is the case. (2)

- b. With the capacitor, C , disconnected, what is the small signal impedance of the point labelled V_{out} to ground when:

i). $V_{in}=0$ (3)

ii). $V_{in}=V_{DD}$ (3)

Comment on the use of the transistor as an electronic switch in this circuit. (2)

- c. If you were to make a *good* electronic switch for use in a digital circuit, identify how this might be done. You do not need to do a detailed analysis of the switch's performance but you do need to relate the behaviour of the electronic switch to the behaviour of a perfect switch. (6)

3. a. i. An n-channel MOSFET has $W/L = 2\mu\text{m}/0.4\mu\text{m}$, $V_{TO}=0.6\text{V}$ and a process transconductance parameter $K_n=150\mu\text{A}/\text{V}^2$. Ignoring channel modulation and assuming the transistor is operating in saturation, calculate the values of V_{OV} and V_{GS} required for this transistor to be biased at a drain current of $100\mu\text{A}$. What is the minimum value of V_{DS} required to ensure the transistor is saturated? (2)
- ii. For the transistor in part i, and assuming operation in the saturation region, what will happen to the drain current when the following device dimensions and voltages are changed:
- The channel length is doubled,
 - V_{OV} is doubled.
- Which of these changes could lead to the transistor falling into the triode region of operation and why? (3)

- b. **Figure 3** shows a SPICE model of a source-follower, or common drain, amplifier. The transistor M1 operates at a drain current of $150\mu\text{A}$, and you can assume that its parasitic capacitances can be neglected at the frequencies under consideration. The transistor has the following parameters:

$$K_n = 200\mu\text{A}/\text{V}^2, W/L = 6\mu\text{m}/0.6\mu\text{m}, \lambda = 0.05\text{V}^{-1} \text{ and } V_{TO} = 0.5\text{V}.$$

 


Figure 3: a SPICE model of a source follower

- i. Draw the small signal model of the circuit in **Figure 3**, using the T-model for the transistor M1 and including the transistor output impedance r_o . Calculate the values of r_o , and g_m . (5)
- ii. For $R=10\text{k}\Omega$, calculate a suitable value for V_{bias} . (3)
- iii. Use your small signal model to derive an expression for the gain of the source follower (show your working). Calculate the value of the gain for $R=10\text{k}\Omega$. (4)
- iv. Sketch a graph of the output voltage, V_{out} , of the circuit in **Figure 3** over time. Assume $R=10\text{k}\Omega$ and V_{sig} is a 0.2V pk-pk sine wave at 1kHz . Include numbered axes on your graph to show the maximum, minimum and average (DC) output voltages, as well as suitable values along the time axis respectively. (3)

4. a. Give a short description of the following terms:

EEE335

- i. Current steering,
- ii. the transconductance parameter, g_m ,
- iii. channel length modulation.

(5)

b. Consider an NMOS transistor having the following parameters:

$$V_{TO}=0.4V, K_n=175\mu A/V^2, \lambda=0.1V^{-1}, W=3\mu m, L=1\mu m, C_{gs}=C_{gd}=2fF.$$

- i. Draw the small signal π model of the MOSFET described by the parameters above with the source terminal at ground. Include the dominant parasitic capacitances and the output resistance r_o . (3)

(2)

- ii. Calculate the values of r_o and g_m , assuming $V_{GS}=1V$.

- iii. The FET is attached to a circuit such that the voltage at its drain is $-25x$ that at its gate: compute the Miller equivalent capacitances and redraw your small signal model to show them. (4)

c. **Figure 4** shows a basic PMOS current mirror driven by a **5V** power supply and with the reference current set by a resistor **R**. M1 and M2 are matched transistors having $V_{TO}=-0.5V$, $K_p=200\mu A/V^2$, $\lambda=0.04V^{-1}$ and $W/L = 2\mu m/0.5\mu m$.

 


Figure 4: a PMOS current mirror

- i. Determine an appropriate value for the resistor **R** in order to set I_{ref} , the reference current through M1, at $150\mu A$. (3)
- ii. V_{DS} for M1 and M2 in **Figure 4** are initially identical. A change in the circuit to which the current mirror is attached causes V_{out} to increase by $0.5V$. What will the resultant current error be (i.e. the difference between I_{ref} and I_{out})? What feature of more advanced current mirrors minimises the current error resulting from changes such as those described? (3)

NLS/AM / Twang