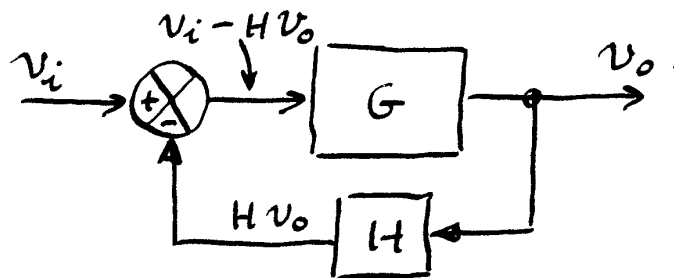


Operational Amplifiers

- most commonly used analogue building block
- been around since the 1930s (the original ones were big, heavy + power hungry)
- formed the basis of analogue computers
- designed to have
 - (i) differential input
 - (ii) very high input resistance ($> 10^9 \Omega$)
 - (iii) very low output resistance ($< 50 \Omega$)
 - (iv) very high gain. (typ 10^5)

Classical feedback system

- to understand why the op-amp is designed to have the features outlined above, consider a classical feedback system....



If the output voltage is v_o , a fraction $H v_o$ is fed back to the input stage where it is subtracted from v_i . This leaves $(v_i - H v_o)$ at the input of the gain stage G , so

$$v_o = G(v_i - H v_o).$$

$$\text{or } \frac{v_o}{v_i} = \text{system gain} = \frac{G}{1 + GH} \quad \text{--- ①}$$


If G is very large, then $GH \gg 1$

and $\frac{V_o}{V_i} \approx \frac{G}{GH} = \frac{1}{H}$. ————— (2)

This is a very useful result because it tells the designer that if G is made large enough, system gain is dependent only on the feedback fraction H . H is usually defined by well behaved components — R and C — although in this module only R will be used.


The op-amp

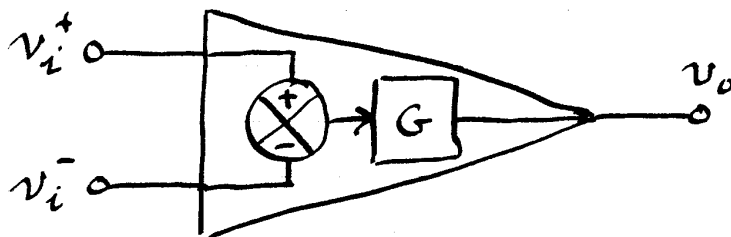- The op-amp integrates two parts of this classical feedback system....



- The input resistances must be high so that the v^- input does not affect the network that defines H and so that the v^+ input does not affect the signal source.
- The output resistance must be low so that the system can drive a load without v_o being affected and so that the system can drive the network defining H without being affected.
- The reason for the differential input and the high gain are obvious from the result (2).

- The op-amp is usually drawn as

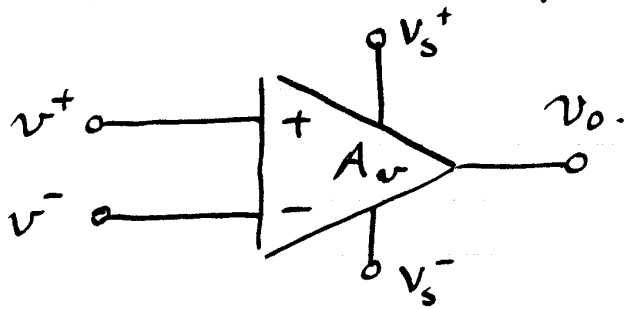

- $V_s^+ + V_s^-$ are the power supplies. They are often not included on circuit diagrams but must be connected in the real circuit. v_o cannot go outside the range $V_s^+ > v_o > V_s^-$
- v^+ is called the "non-inverting" input of the op-amp. It is identified by a "+" next to the input line, inside the op-amp triangle.
- v^- is called the "inverting input" of the op-amp and is identified by a "-".
- The output, v_o , comes from point of the amplifier symbol.
- A_v is the voltage gain (equivalent of G) which relates the output and input by the op-amp equation

$$v_o = A_v(v^+ - v^-)$$


in other words, A_v operates on the difference between $v^+ + v^-$ to produce v_o .

Op-Amp Circuits

There are many different circuits that are used with op-amps but there are two that are far more common than any others; the "non-inverting amplifier" and the "inverting amplifier".

Non-Inverting Amplifier

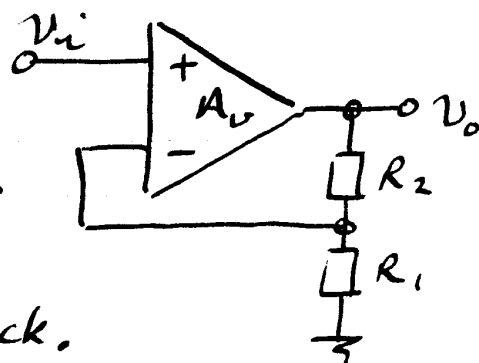When designing an op-amp circuit it is usual to assume initially that $A_v \Rightarrow \infty$. This means that its behaviour is completely controlled by the feedback.



If $A_v \Rightarrow \infty$, for finite V_o , $v^+ \approx v^-$ and this makes working out circuit behaviour quite straightforward....

$$v^- = V_o \frac{R_1}{R_1 + R_2} \quad (\text{by potential division})$$


$$v^+ = V_i \quad (\text{connected by wire})$$

$$\therefore \text{if } A_v \Rightarrow \infty, v^+ \approx v^- \text{ or } V_i \approx V_o \frac{R_1}{R_1 + R_2}$$

$$\text{or } \underline{\underline{\frac{V_o}{V_i} = \frac{R_1 + R_2}{R_1}}} \quad \text{--- (3)}$$

- notice that the feedback is returned to the v^- input.

Inverting Amplifier

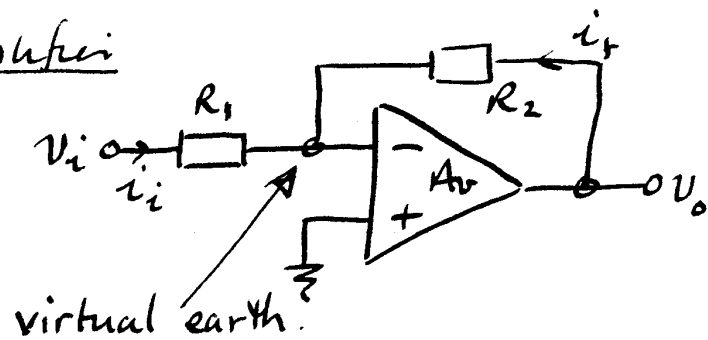

In the inverting amplifier connection, v^+ is grounded and v_i is applied to R_1 . Again if $A_v \Rightarrow \infty$, $v^+ \approx v^-$ and since v^+ is connected to zero, v^- must also be very close to zero. The v^- node in this case is sometimes called a "virtual earth" — the potential is always close to zero but the node is not actually connected to zero. To work out gain, start by summing currents at the v^- node

$$i_i + i_f = 0 \quad \text{or} \quad \frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} = 0$$

$$\text{but } v^- \approx 0 \quad \text{so} \quad \frac{v_i}{R_1} + \frac{v_o}{R_2} = 0$$

$$\text{or} \quad \underline{\underline{\frac{v_o}{v_i} = -\frac{R_2}{R_1}}} \quad \text{————— (4)}$$


— notice the "-" sign. This means that the signal is inverted (ie phase shifted by 180°) as well as amplified. Two inverting amplifiers in series would give rise to an overall non-inverting amplifier — the first stage would invert the signal and the second would invert it back to its original phase.

Effects of finite gain:

Very occasionally it may be necessary for a designer to estimate the effect of finite op-amp gain on the overall circuit gain.

Non-inverting ...

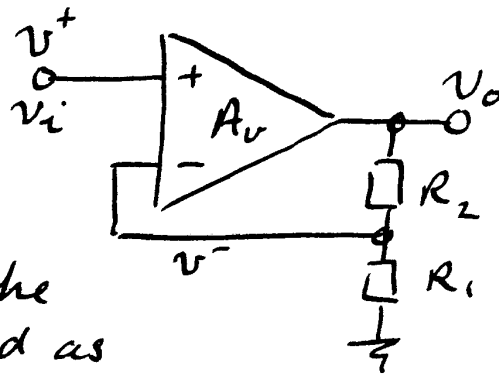When considering the effects of finite gain the $v^+ \approx v^-$ approximation cannot be used. Instead the analysis would proceed as follows:



$$v^- = v_o \frac{R_1}{R_1 + R_2} \quad (\text{as before}).$$

$$v^+ = v_i \quad (\text{as before}).$$

but now the op-amp equation must be used to relate v^+ , v^- & v_o ...

$$v_o = A_v(v^+ - v^-) = A_v\left(v_i - v_o \frac{R_1}{R_1 + R_2}\right)$$


$$\text{or } v_o \left[\frac{1}{A_v} + \frac{R_1}{R_1 + R_2} \right] = v_i$$

$$\text{or } \frac{v_o}{v_i} = \frac{1}{\frac{1}{A_v} + \frac{R_1}{R_1 + R_2}} \quad \text{--- (5)}$$

note that if $A_v \Rightarrow \infty$, $\frac{1}{A_v}$ becomes negligible and (5) becomes the same as (3).

Inverting...

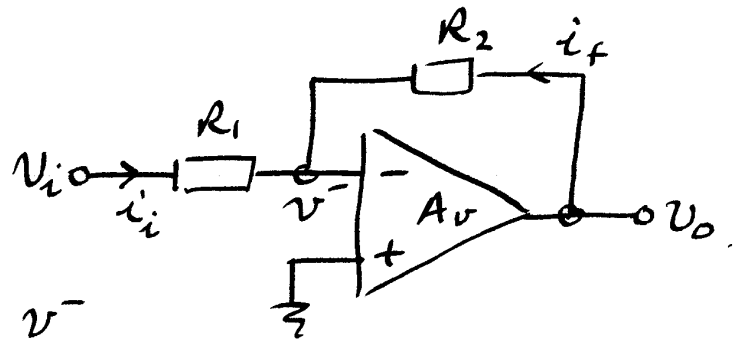Start as before
by summing
currents at the v^-
node...



$$i_i + i_f = 0 \quad \text{or} \quad \frac{V_i - v^-}{R_1} + \frac{V_o - v^-}{R_2} = 0.$$

which can be rearranged to give

$$v^- = V_i \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2}.$$

and $v^+ = 0$.

Using the op-amp equation....

$$V_o = A_v \left(0 - \left[V_i \frac{R_2}{R_1 + R_2} + V_o \frac{R_1}{R_1 + R_2} \right] \right)$$

$$\text{or } V_o \left[\frac{1}{A_v} + \frac{R_1}{R_1 + R_2} \right] = -V_i \frac{R_2}{R_1 + R_2}$$

$$\text{or } \frac{V_o}{V_i} = - \frac{\frac{R_2}{R_1 + R_2}}{\frac{1}{A_v} + \frac{R_1}{R_1 + R_2}} \quad \text{--- (6)}$$

Again, if $A_v \Rightarrow \infty$, $\frac{V_o}{V_i}$ reduces to (4).


Circuit input resistance

The input to the non-inverting circuit goes straight into the op-amp so the circuit input resistance is the same as that of the op-amp — i.e. very high.

The inverting circuit is slightly different. Taking the $A_v \Rightarrow \infty$ case, an i_i of v_i/R_i flows from the source. Input resistance is the ratio of applied signal to current drawn - ie, $v_i/i_i = R_i$. This is typically likely to be a few k Ω which makes inverting amplifiers unsuitable as amplifiers of signals derived from sources with a large Thevenin resistance.

Unity Gain Buffer.

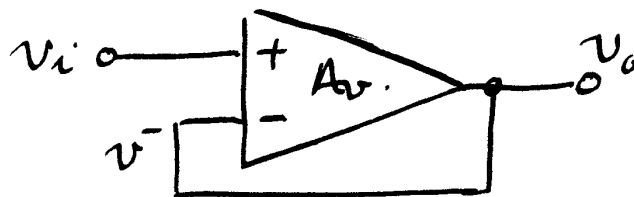- This is really a member of the non-inverting amplifier family...



Here $v^- = v_o$ so the op-amp eqn. becomes

$$v_o = A_v(v^+ - v^-) = A_v(v_i - v_o)$$


$$\text{or } \frac{v_o}{v_i} = \frac{1}{\frac{1}{A_v} + 1} = \frac{A_v}{1 + A_v}$$

If A_v is large, v_o/v_i is very close to unity.

The circuit is used to isolate high impedance sources from low impedance loads; it has a high power gain.

Circuits with multiple inputs

Summers

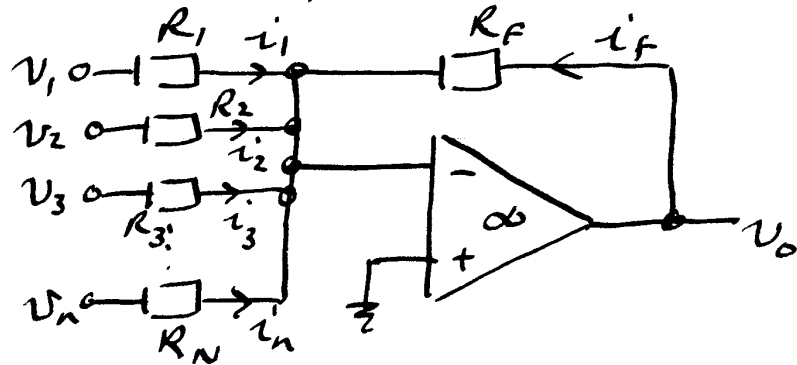

Assume $A_v \Rightarrow \infty$ so $V^- \Rightarrow$ virtual earth.
 $= 0V$.

(this assumption will always be valid in a practically sensible circuit).

then

$$i_f + i_1 + i_2 + i_3 + \dots + i_n = 0.$$

$$\text{or } \frac{V_0}{R_F} + \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \dots + \frac{V_n}{R_n} = 0.$$


$$\text{or } V_0 = - \left[V_1 \frac{R_F}{R_1} + V_2 \frac{R_F}{R_2} + \dots + V_n \frac{R_F}{R_n} \right]$$

(many analogue audio "mixers" use this circuit shape).

Subtractors

There are a couple of ways of solving a circuit like this.

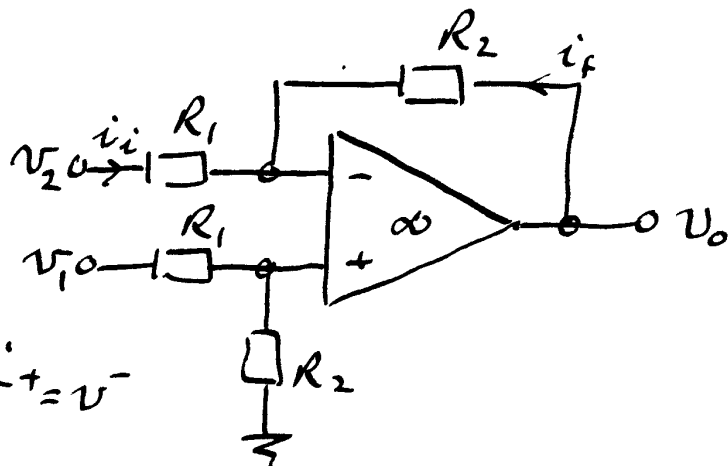Since $A_v \Rightarrow \infty$, $V^+ = V^-$



so here we will work out $v^+ + v^-$ and then equate them to get v_o in terms of $v_1 + v_2$.

summing currents at v^- node ...

$$i_i + i_f = 0 \quad \text{or} \quad \frac{v_2 - v^-}{R_1} + \frac{v_o - v^-}{R_2} = 0.$$

and this can be rearranged to give

$$v^- = v_2 \frac{R_2}{R_1 + R_2} + v_o \frac{R_1}{R_1 + R_2}.$$

v^+ is a potentially divided version of v_1 ...

$$v^+ = v_1 \frac{R_2}{R_1 + R_2}.$$

equating $v^+ + v^-$...

$$v_2 \frac{R_2}{R_1 + R_2} + v_o \frac{R_1}{R_1 + R_2} = v_1 \frac{R_2}{R_1 + R_2}.$$

$$\text{or } v_o \frac{R_1}{R_1 + R_2} = v_1 \frac{R_2}{R_1 + R_2} - v_2 \frac{R_2}{R_1 + R_2}$$


$$\text{or } \underline{v_o = \frac{R_2}{R_1} (v_1 - v_2)}.$$

Note that the accuracy of the subtraction depends upon the matching of the two R_1 s and R_2 s.

General multiple input circuit


The subtractor circuit can be generalised to allow more than two inputs. Such a circuit could be analysed by finding v^+ and v^- and equating them, or by using

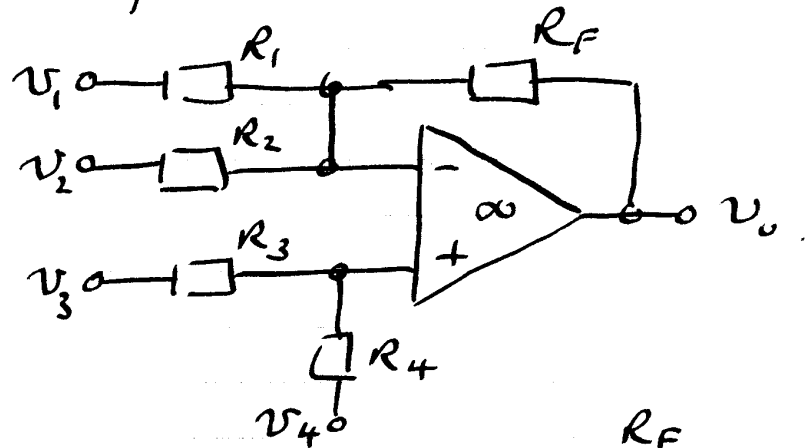The principle of superposition. Superposition has the advantage that at each stage the circuit is reduced to a relatively simple single input circuit.



Consider first the output due to v_1 . $v_2, v_3 + v_4$ are grounded.

The ckt becomes:

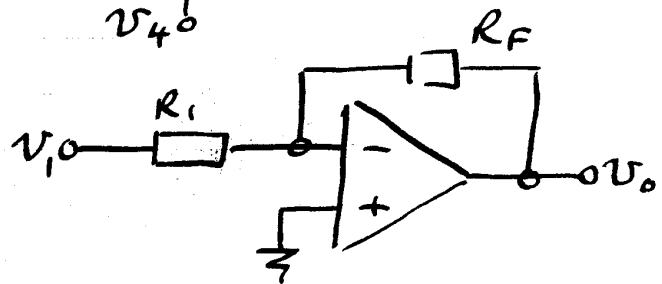


note - since both $v_3 + v_4$ are zero, v^+ is zero and v^- is a virtual 'earth'. Since v^- is a virtual earth, no current flows through R_2 so it has no effect on the circuit.

$$v_o \Big|_{\text{due to } v_1} = v_1 \left(-R_F / R_1 \right)$$

By a very similar argument (change of variable names only)

$$v_o \Big|_{\text{due to } v_2} = v_2 \left(-R_F / R_2 \right)$$

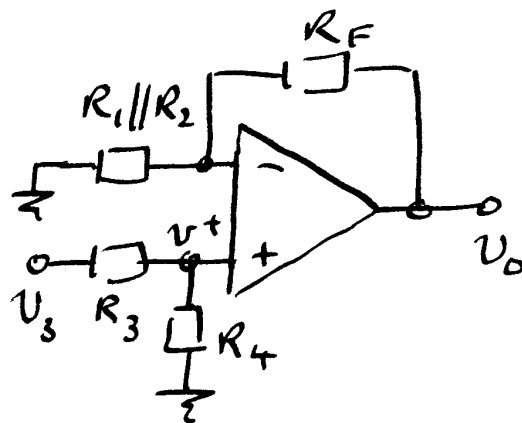The output due to V_3 leads to a more complicated circuit ...



Here, $V_1 + V_2$ are grounded so R_1 is effectively in parallel with R_2 . V^+ , the non-inverting amplifier input is a potentially divided version of V_3

$$\text{so } \frac{V_O}{V^+} = \frac{R_F + R_1 \parallel R_2}{R_1 \parallel R_2} \quad (\text{ie non-inv. amp. gain})$$

$$\text{and } \frac{V^+}{V_3} = \frac{R_4}{R_3 + R_4} \quad (\text{by pot. div.})$$

$$\therefore \frac{V_O}{V_3} = \frac{V_O}{V^+} \times \frac{V^+}{V_3} = \frac{R_4}{R_3 + R_4} \cdot \frac{R_F + R_1 \parallel R_2}{R_1 \parallel R_2}$$

$$\text{or } V_O \Big|_{\text{due to } V_3} = V_3 \frac{R_4}{R_3 + R_4} \cdot \frac{R_F + R_1 \parallel R_2}{R_1 \parallel R_2}$$

By a very similar argument....

$$V_O \Big|_{\text{due to } V_4} = V_4 \frac{R_3}{R_3 + R_4} \cdot \frac{R_F + R_1 \parallel R_2}{R_1 \parallel R_2}$$

$$V_{O \text{ TOT}} = V_O \Big|_{V_1} + V_O \Big|_{V_2} + V_O \Big|_{V_3} + V_O \Big|_{V_4}$$

And remember that if any of the V s consist of d.c. + sinusoid, those two parts can be treated separately.