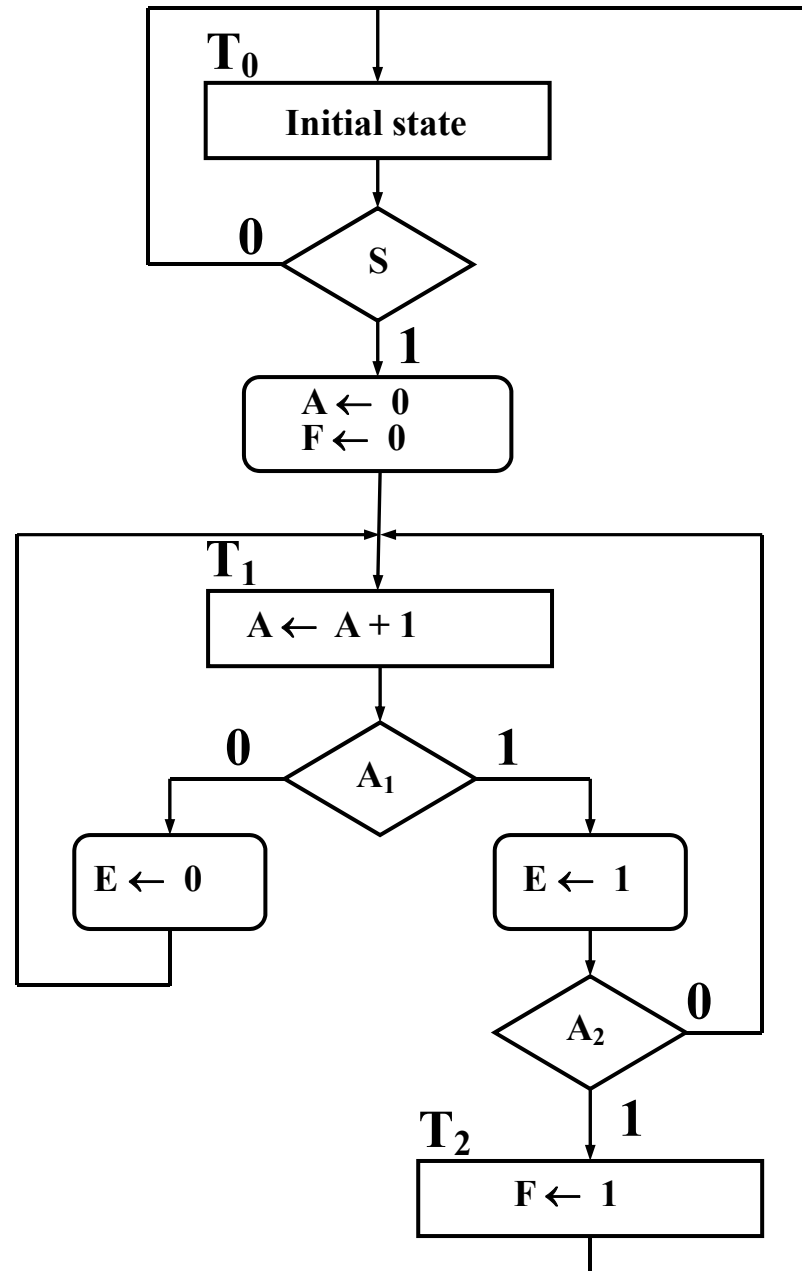


# Algorithmic State Machines (II)


- ASMD Circuit Solution
- Verilog Model of ASMD



# Data Path Components

**$(A \leftarrow A + 1)$  when state =  $T_1$**

 **$(A \leftarrow 0)$  when state =  $T_0$  and  $S = 1$**




4-bit counter with  
synchronous reset  
and chip enable

**$(E \leftarrow 1)$  when state =  $T_1$  and  $A_1 = 1$**


**$(E \leftarrow 0)$  when state =  $T_1$  and  $A_1 = 0$**

 **$(F \leftarrow 1)$  when state =  $T_2$**



D-Type flip-flop

# Controller & Data Path

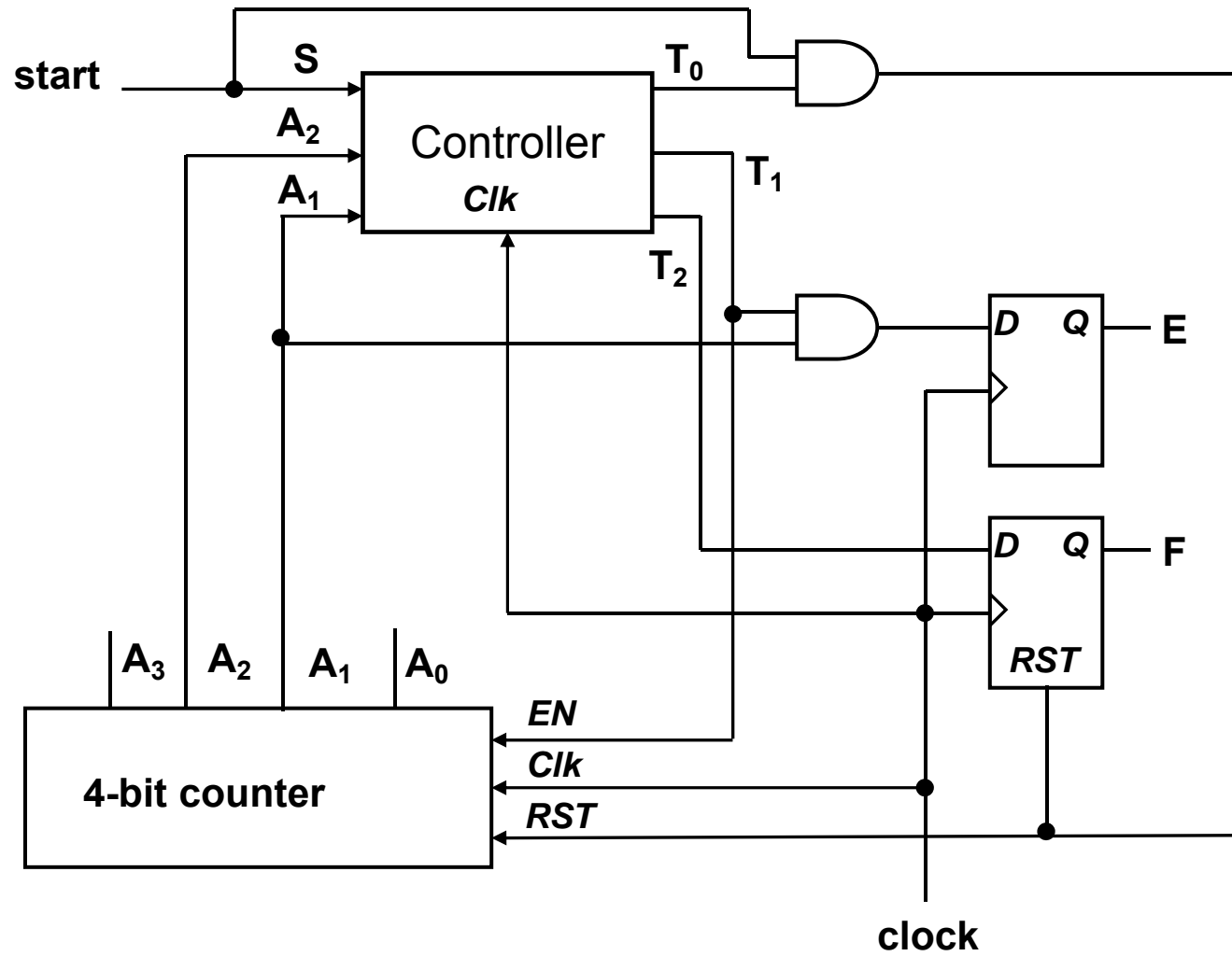

## Design Problem:

A sequential circuit is required for a counting application.


The system outputs are a four bit register  $A[3:0]$  to hold the count and two flip-flops E and F.

A signal, *Start*, initiates the system's operation by clearing the counter and status bit F.

At subsequent clock pulses the counter is incremented by 1 until the operation stops.

Counter bits  $A_2$  and  $A_3$  determine the sequence of operations.

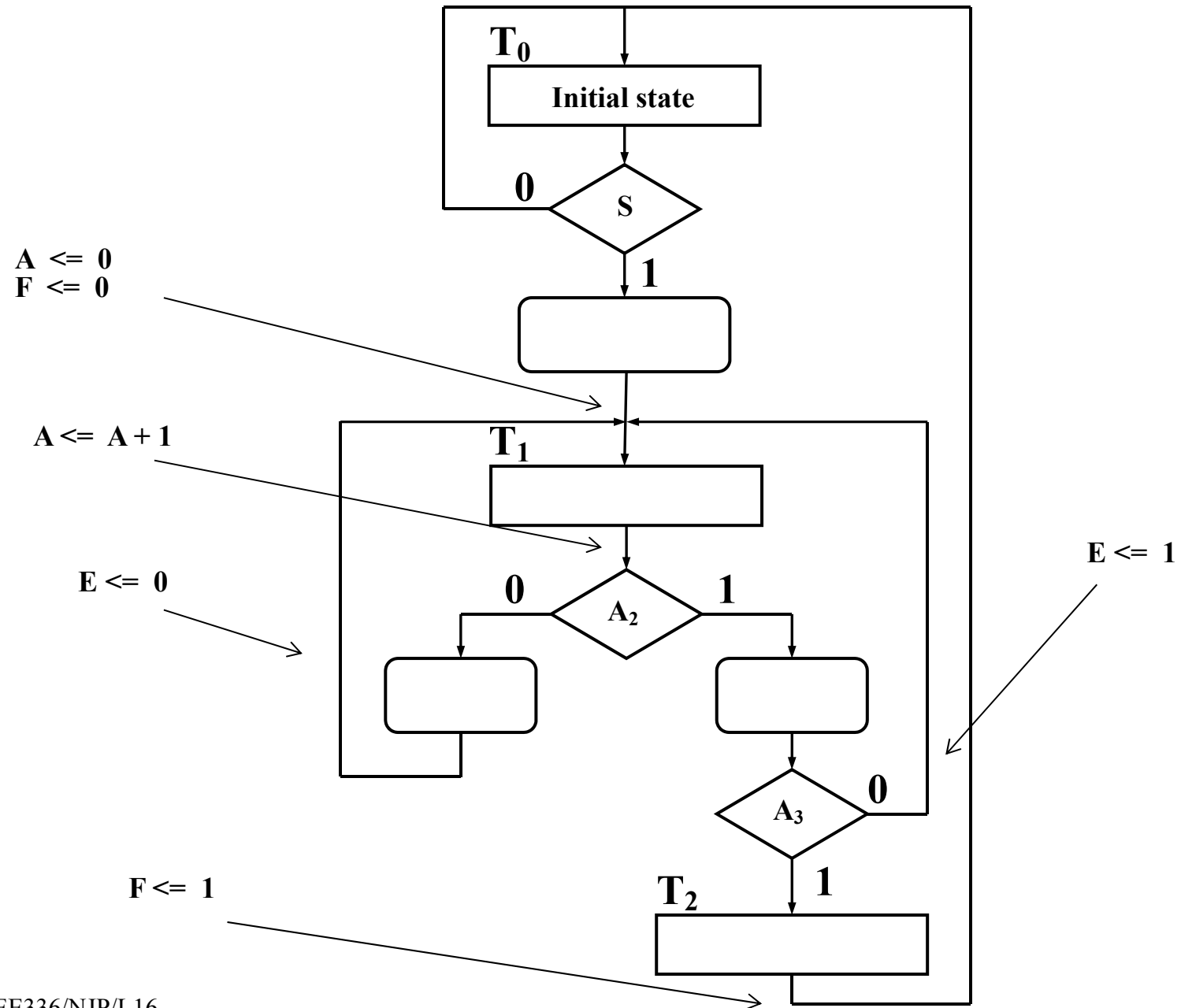Reference: Digital Design, 4e, Mano & Ciletti
---




## Sequence of operations:

If  $A_2 = 0$ , E is cleared to 0 and the count continues.

If  $A_2 = 1$ , E is set to 1; then, if  $A_3 = 0$ , the count continues, but if  $A_3 = 1$ , F is set to 1 on the next clock pulse and the system stops counting.

Then, if  $\text{Start} = 0$ , the system remains in the initial state, but if  $\text{Start} = 1$ , the operation cycle repeats.

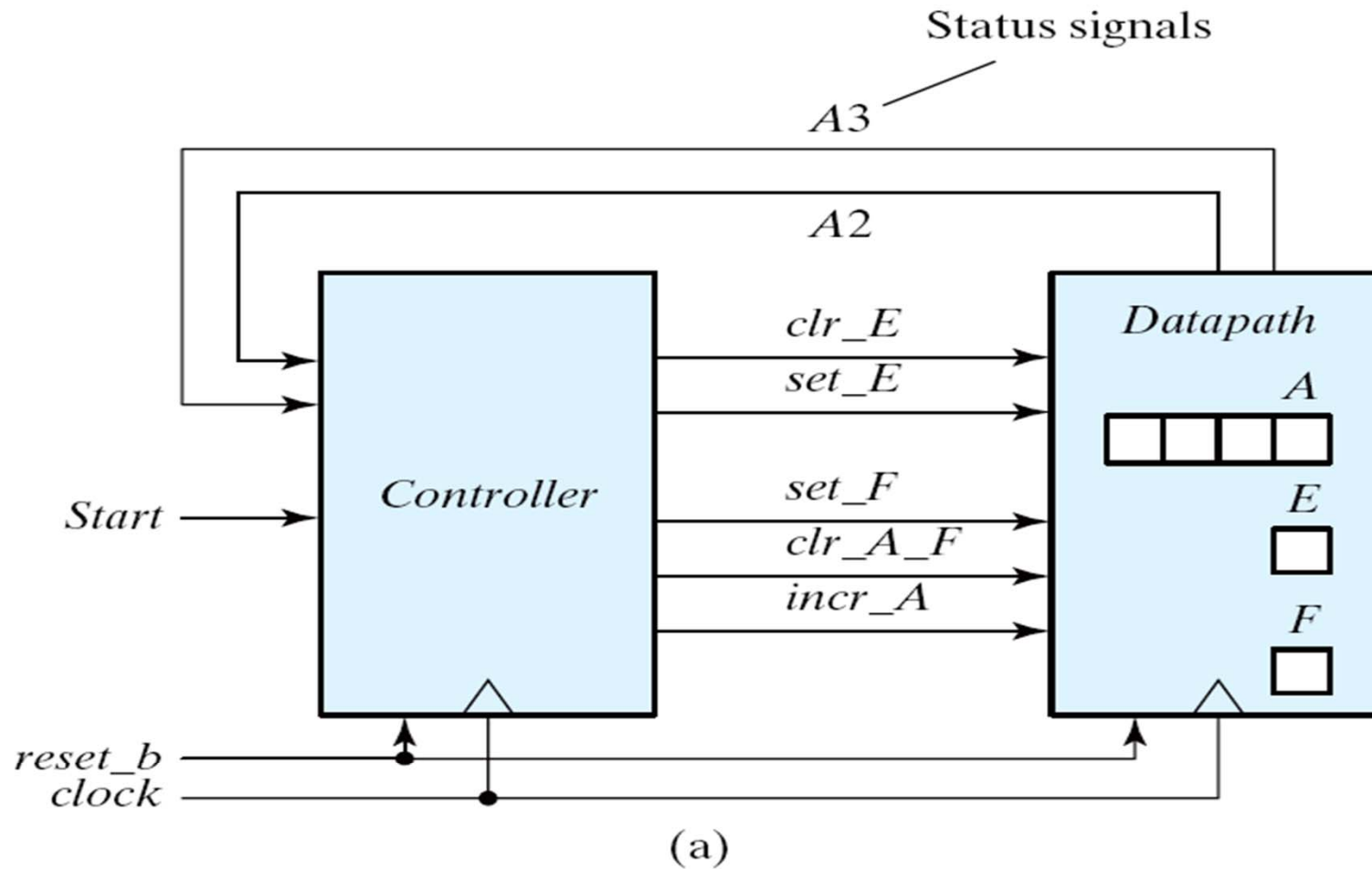(Slightly different from previous example)



Note: A3 denotes A[3],  
 A2 denotes A[2],  
 <= denotes nonblocking assignment  
 reset\_b denotes active-low reset condition



# Top Level RTL Description of Example ASMD

```
module ASMD_RTL (A, E, F, Start, clock, reset_b);  
  
    output [3:0] A;  
    output E, F;  
    input Start, clock, reset_b;  
  
    Controller_RTL  M0 (set_E, clr_E, set_F, clr_F, incr_A, A[2], A[3], Start, clock, reset_b);  
    Datapath_RTL    M1 (A, E, F, set_E, clr_E, set_F, clr_A_F, incr_A, clock);  
  
endmodule
```

# Top Level RTL Description of Example ASMD

```
module ASMD_RTL (A, E, F, Start, clock, reset_b);
```

```
  output [3:0] A;
```

```
  output E, F;
```

```
  input Start, clock, reset_b;
```

*structural top level*



```
  Controller_RTL  M0 (set_E, clr_E, set_F, clr_F, incr_A, A[2], A[3], Start, clock, reset_b);
```

```
  Datapath_RTL    M1 (A, E, F, set_E, clr_E, set_F, clr_A_F, incr_A, clock);
```

```
endmodule
```

# RTL Description of Controller

```
module Controller_RTL (set_E, clr_E, set_F, clr_A_F, incr_A, A2, A3, Start, clock, reset_b);  
  
  output reg      set_E, clr_E, set_F, clr_A_F, incr_A;  
  input           Start, A2, A3, clock, reset_b;  
  reg [1:0]        state, next_state;  
  parameter       S_idle = 2'b00, S_1 = 2'b01, S_2 = 2'b11;  
  
  always @ (posedge clock or negedge reset_b) begin  
    if (reset_b == 0) state <= S_idle;  
    else state <= next_state;  
  end
```

# RTL Description of Controller

```
module Controller_RTL (set_E, clr_E, set_F, clr_A_F, incr_A, A2, A3, Start, clock, reset_b);  
  
  output reg      set_E, clr_E, set_F, clr_A_F, incr_A;  
  input           Start, A2, A3, clock, reset_b;  
  reg [1:0]        state, next_state; ← register for state  
  parameter       S_idle = 2'b00, S_1 = 2'b01, S_2 = 2'b11;  
  
  always @ (posedge clock or negedge reset_b) begin  
    if (reset_b == 0) state <= S_idle;  
    else state <= next_state; ← define states  
  end ← Synchronous update
```

# Next State Logic

```
always @ (state, Start, A2, A3) begin  
    next_state = S_idle;  
    case (state)  
        S_idle:      if (Start) next_state = S_1; else next_state = S_idle;  
        S_1:         if (A2 & A3) next_state = S_2; else next_state = S_1;  
        S_2:         next_state = S_idle;  
        default:     next_state = S_idle;  
    endcase  
end
```

# Next State Logic

```
always @ (state, Start, A2, A3) begin
```

```
    next_state = S_idle;
```

```
    case (state)
```

```
        S_idle:      if (Start) next_state = S_1; else next_state = S_idle;
```

```
        S_1:         if (A2 & A3) next_state = S_2; else next_state = S_1;
```

```
        S_2:         next_state = S_idle;
```

```
        default:     next_state = S_idle;
```

```
    endcase
```

```
end
```



*combinational logic using  
blocking assignments*

# Output Logic

```
always @ (state, Start, A2) begin  
    set_E    = 0;  
    clr_E    = 0;  
    set_F    = 0;  
    clr_A_F  = 0;  
    incr_A   = 0;  
    case (state)  
        S_idle:    if (Start) clr_A_F = 1;  
        S_1:       begin incr_A = 1; if (A2) set_E = 1; else clr_E = 1; end  
        S_2:       set_F = 1;  
    endcase  
end  
endmodule
```

# Datapath Logic

```
module Datapath_RTL (A, E, F, set_E, clr_E, set_F, clr_A_F, incr_A, clock);  
  
  output reg [3:0] A;  
  output reg      E, F;  
  input          set_E, clr_E, set_F, clr_A_F, incr_A, clock;  
  
  always @ (posedge clock) begin  
    if (set_E)      E <= 1;  
    if (clr_E)      E <= 0;  
    if (set_F)      F <= 1;  
    if (clr_A_F)    begin A <= 0; F <= 0; end  
    if (incr_A)     A <= A + 1;  
  end  
endmodule
```



# Datapath Logic

```
module Datapath_RTL (A, E, F, set_E, clr_E, set_F, clr_A_F, incr_A, clock);
```

```
    output reg [3:0] A;
```

```
    output reg      E, F;
```

```
    input          set_E, clr_E, set_F, clr_A_F, incr_A, clock;
```

```
    always @ (posedge clock) begin
```

```
        if (set_E)      E <= 1;
```

```
        if (clr_E)      E <= 0;
```

```
        if (set_F)      F <= 1;
```

```
        if (clr_A_F)    begin A <= 0; F <= 0; end
```

```
        if (incr_A)     A <= A + 1;
```

```
    end
```

```
endmodule
```

*sequential logic using  
nonblocking assignments*

