

EEE 117.Electrical Circuits and Networks.First half (that's TOZER)

- basic ideas of circuits and components and key ckt laws.
- d.c. circuits
- a.c. circuits
 - phasor representation
 - complex number representation.
- power


Ken Mitchell.

- magnetic circuits
- inductance
- power.
- real + reactive power
- three phase.


Networks.

- usually described by circuit diagrams (or schematic diag.) (or ~~sch~~ schematics)
- represents the connectivity of an assembly of electrical




electronic components.

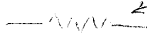
each different component has a symbol  ← old UK symbol?

 resistor

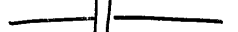 capacitor


 inductor

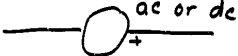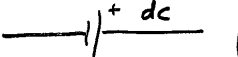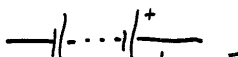 ac or dc
 dc
 dc
 } voltage or e.m.f. sources.

 current source.

Components connected together by ideal wires

eg

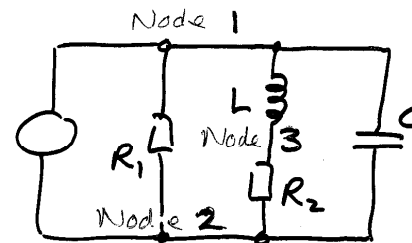


- a circuit "node" is where two or more components are connected together



Node 1 has 4 connections

{ Node 2 has 4 connections
 { Node 3 has 2 connections.
 { Simple node because it only has 2 connections
 { Major nodes because they have 3 or more connections.


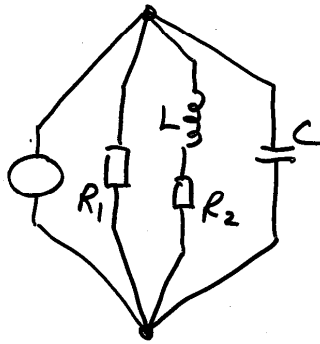
cct can be redrawn to make the nodes more obvious



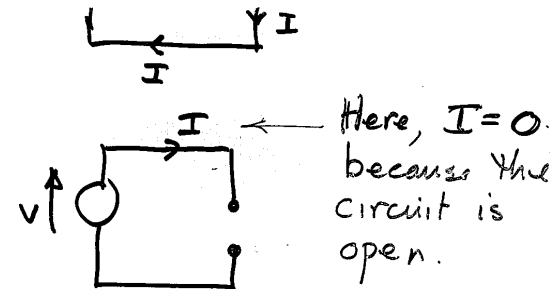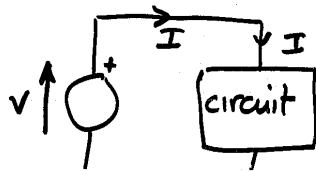Current flows around a circuit
 — it is driven by "electromotive force" or e.m.f. The emf provides a potential difference which makes the electrons move.



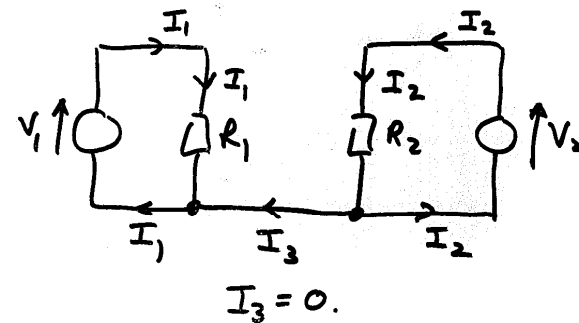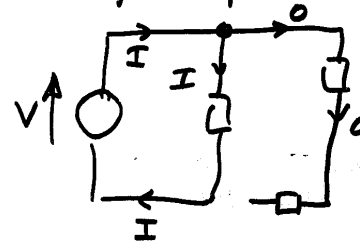If part of the circuit is open, no current will flow through the open part




— Objective is to understand how circuits work so that one can be inventive in achieving design


units.

Current

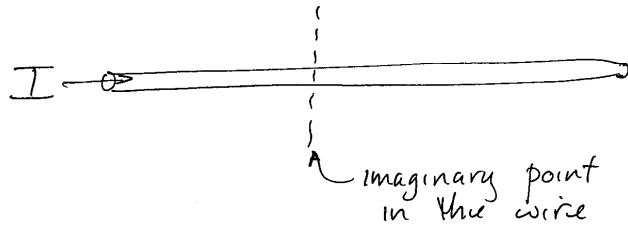— rate of passage of charge through an imaginary point in a cct



$$I = \frac{dq}{dt} \text{ at the imaginary point.}$$

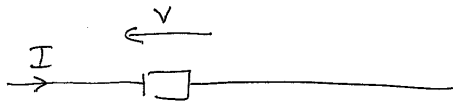Power & Energy:

$$\begin{aligned} \text{work done} = \text{energy used} &= \int_0^t V \cdot I \cdot dt \\ &= V \cdot I \cdot t \text{ at dc.} \end{aligned}$$


power = rate of energy use

$$= \frac{1}{t} \int_0^t V I \cdot dt = V I \text{ at dc.}$$

If V & I are functions of time,
ie $V \Rightarrow V(t)$ $I \Rightarrow I(t)$





$$E = \int_0^t V(t) I(t) dt.$$
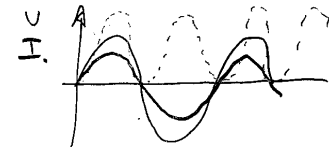
$$\text{Power} = \frac{1}{T} \int_0^T V(t) I(t) dt.$$



$$P = \frac{1}{T} \int_0^{T/2} V(t) I(t) dt.$$





bottom half has been chopped off.

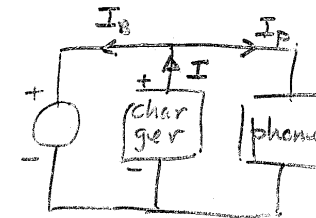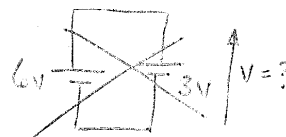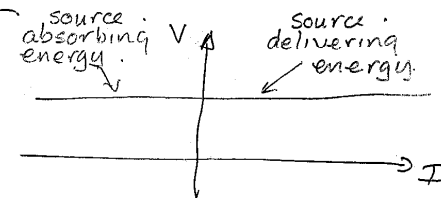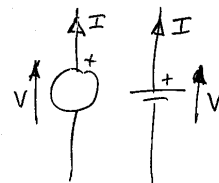Voltage Sources

Current Sources

- usually exist as electronic ccts with internal feedback designed to maintain a constant I .

- usually operate over a limited range of terminal voltage.

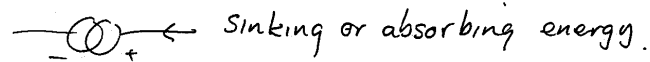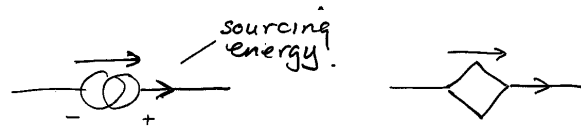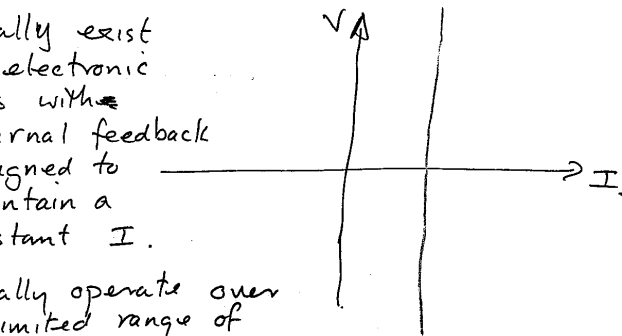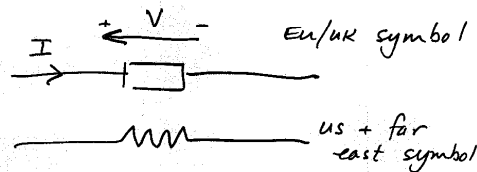Resistors

$$V = IR$$

R is an energy sink and it dissipates the energy it sinks

Size (physical) of the resistor determines its ability to dissipate

heat.

Power in resistive circuits

$$P_{at\ dc} = VI \text{ J s}^{-1} \text{ or } \boxed{W - \text{Watts}}$$

$$V = IR$$

$$P = VI = V\left(\frac{V}{R}\right) = \frac{V^2}{R} \text{ W (if } V = \text{volts)} \\ \left(= \frac{V}{R}\right)$$

$$P = (IR)I = I^2R \text{ W (if } I = \text{amps)}$$

Preferred resistor values


— preferred value series

E6 \rightarrow 20% tolerance.


E12 \rightarrow 10% tolerance

E24 \rightarrow 5% tolerance.

look at E12.

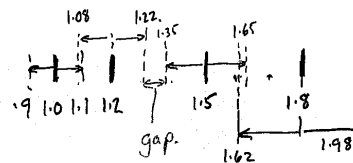

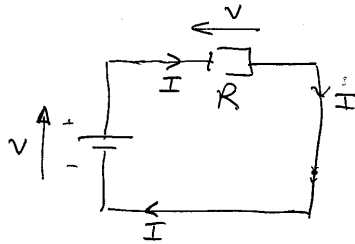E12 series 1, 1.2, 1.5, 1.8, 2.2, 2.7, 3.3, 3.9,
4.7, 5.6, 6.8, 8.2




Sum of directed voltages around any closed loop in a ckt must be zero

Current entering a point in the circuit must equal current leaving that point.

Kirchoff's laws

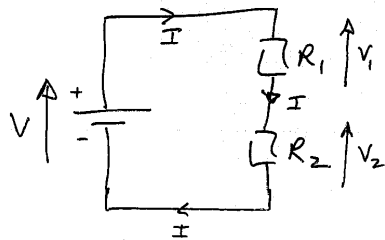If there is more than one resistor in the circuit...




R_1 & R_2 are in series because the same current must flow through them.

$$V_1 = IR_1 \quad V_2 = IR_2$$

$$V + (-V_1) + (-V_2) = 0$$

$$\text{or } V = V_1 + V_2 = IR_1 + IR_2 = I(R_1 + R_2) \quad \text{--- (1)}$$


want to make

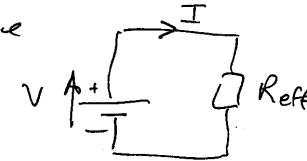

$$R_{\text{eff}} = \frac{V}{I} = R_1 + R_2 \quad (\text{from eq (1)})$$

If more than two resistors are connected in series

R_{eff} = sum of values.

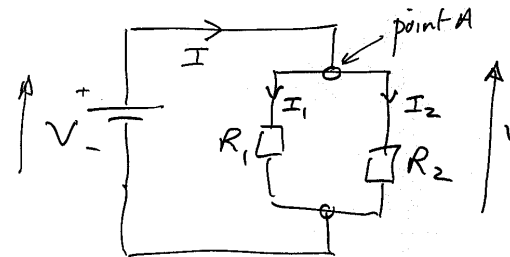

$$I_1 = \frac{V}{R_1} \quad I_2 = \frac{V}{R_2}$$

using Kirchhoff's current law.


$$I = I_1 + I_2$$

↑
current entering
↑
current leaving point A.

point A

$$I = \frac{V}{R_1} + \frac{V}{R_2} = V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \quad \text{--- (2)}$$

to model this as

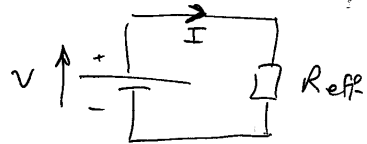



$$R_{\text{eff}} = \frac{V}{I} = \frac{V}{V \left(\frac{1}{R_1} + \frac{1}{R_2} \right)} \quad \text{(using eqn. (2))}$$

$$\therefore R_{\text{eff}} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$\text{or } \frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2}$$


if there are more than two resistors in parallel
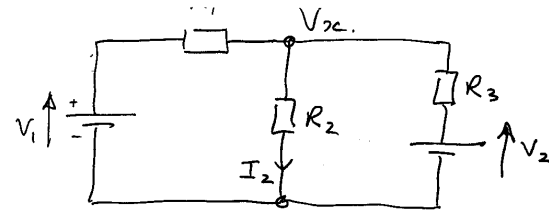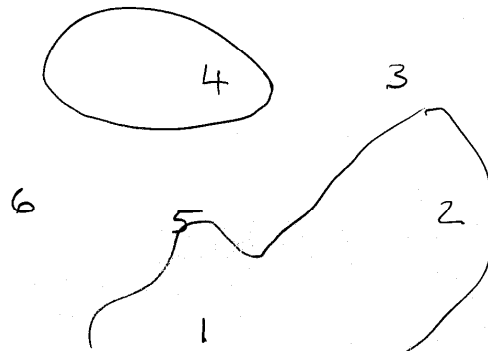
$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$



Methods of solution

(i) Application of Kirchhoff's laws.

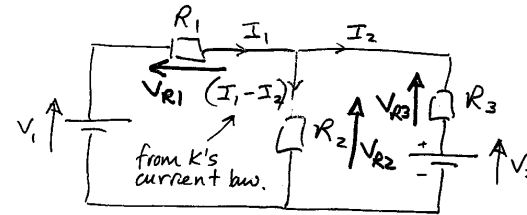

use Kirchhoff's current law at each node to avoid creating redundant variables

use K's voltage law to sum voltages around the two loops.

$$V_1 - V_{R1} - V_{R2} = 0 \quad \text{--- loop 1}$$

$$V_2 + V_{R3} - V_{R2} = 0 \quad \text{--- loop 2.}$$

expanding loop 1

$$V_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0 \quad \text{--- l1}$$

expanding loop 2

$$V_2 + I_2 R_3 - (I_1 - I_2) R_2 = 0 \quad \text{--- l2}$$

collecting terms

collecting terms

$$V_1 - I_1(R_1 + R_2) + I_2 R_2 = 0 \quad \text{11.}$$

$$V_2 + I_2(R_3 + R_2) - I_1 R_2 = 0 \quad \text{12.}$$

using the substitution approach.

$$\text{from 11 } I_2 = \frac{I_1(R_1 + R_2) - V_1}{R_2}$$

$$\therefore \text{ using 12 } V_2 + \frac{I_1(R_1 + R_2) - V_1}{R_2}(R_3 + R_2) - I_1 R_2 = 0$$

$$V_2 R_2 + (I_1(R_1 + R_2) - V_1)(R_3 + R_2) - I_1 R_2^2 = 0.$$

$$V_2 R_2 + I_1(R_1 + R_2)(R_3 + R_2) - V_1(R_3 + R_2) - I_1 R_2^2 = 0.$$


$$V_2 R_2 + I_1(R_1 R_3 + R_2 R_3 + R_2 R_1 + R_2^2) - V_1(R_3 + R_2) - I_1 R_2^2 = 0.$$

$$\therefore I_1 = \frac{V_1(R_3 + R_2) - V_2 R_2}{R_1 R_3 + R_2 R_3 + R_2 R_1}$$

— substitute back in one of the loop equations to find I_2

Nodal Analysis

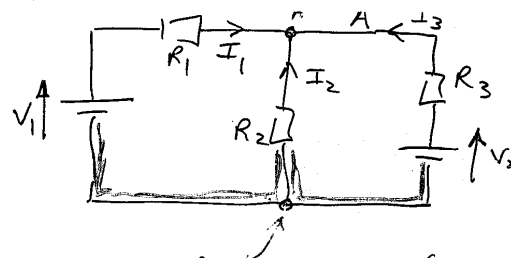— aims to find node voltage w.r.t a reference node.



reference node (all the green stuff is reference node.)

let voltage at A w.r.t. reference node be V_A

— label currents entering (or leaving) the node.

— do a current sum at the node

$$I_1 + I_2 + I_3 = 0$$

$$\frac{V_1 - V_A}{R_1} + \frac{0 - V_A}{R_2} + \frac{V_2 - V_A}{R_3} = 0$$

collect terms together to end up in this case with.


$$V_A = (\text{a function of } V_1, V_2 \text{ + } R_s)$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_3} = V_A \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$V_A = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

then all the other unknowns can be found easily once V_A is known.

LOOP ANALYSIS

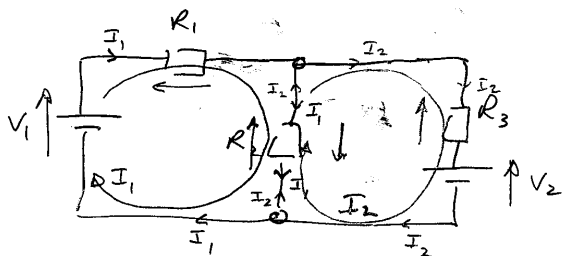

- define a current flowing ~~in~~ around each loop of the circuit
- add up directed voltage drops around each loop.

$$\text{— loop 1 } V_1 - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$\text{or } V_1 = I_1 (R_1 + R_2) - I_2 R_2$$

$$\text{— loop 2 } (I_2 - I_1) R_2 + I_2 R_3 + V_2 = 0$$


$$\text{or } -V_2 = -I_1 R_2 + I_2 (R_2 + R_3)$$

Principle of superposition


The current in any branch of a circuit is linearly proportional to each of the sources driving the circuit

this means that each source can be considered in turn with all the

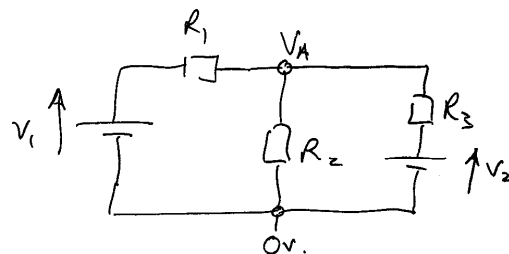other sources replaced by their internal impedance (0Ω for a voltage source or $\infty\Omega$ (ie open ckt) for current source)




eg find V_A using superposition

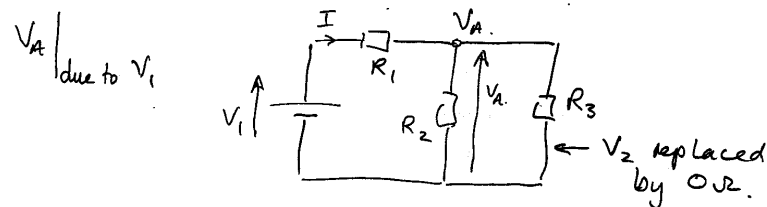

$$I = \frac{V_1}{R_1 + R_2 \parallel R_3}$$
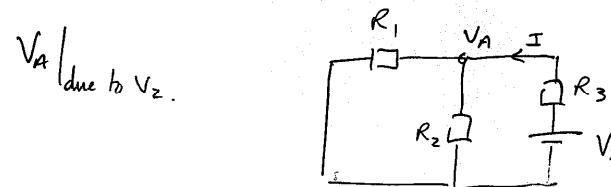
$$V_A = I (R_2 \parallel R_3) = V_1 \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3}$$



$$I = \frac{V_2}{R_3 + (R_1 \parallel R_2)}$$


$$V_A = I (R_1 \parallel R_2) = \frac{V_2 \times (R_1 \parallel R_2)}{R_3 + (R_1 \parallel R_2)}$$

$$V_{A_{TOT}} = V_A|_{\text{due to } V_1} + V_A|_{\text{due to } V_2}$$


$$= V_1 \frac{R_2 || R_3}{R_1 + (R_2 || R_3)} + V_2 \frac{R_1 || R_2}{R_3 + (R_1 || R_2)}$$

Thevenin and Norton Equivalent Ccts.

Thevenin

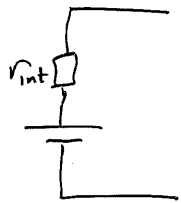

this would model a battery.

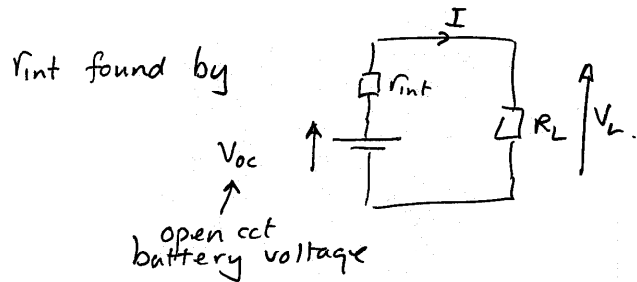


$$I = \frac{V_{oc}}{r_{int} + R_L}$$

$$V_L = I R_L = \frac{V_{oc} R_L}{r_{int} + R_L}$$

r_{int} is the only unknown.

Let I have a ccc

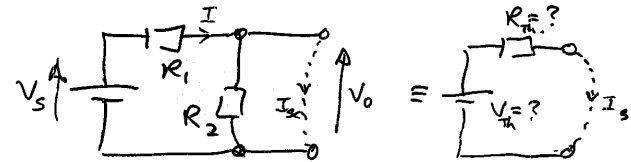

what is V_o with no external load?

$$V_o = V_s \frac{R_2}{R_1 + R_2}$$

$$I = \frac{V_s}{R_1 + R_2} \quad V_o = I R_2 = \frac{V_s R_2}{R_1 + R_2}$$


$$V_{TH} = V_o = V_s \frac{R_2}{R_1 + R_2}$$



$$I_{sc} = \frac{V_s}{R_1} \quad I_{sc} = \frac{V_{TH}}{R_{TH}}$$

$$= \frac{V_s R_2}{R_{TH} (R_1 + R_2)}$$

$$\therefore \frac{V_s}{R_1} = \frac{V_s R_2}{R_{TH} (R_1 + R_2)}$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$

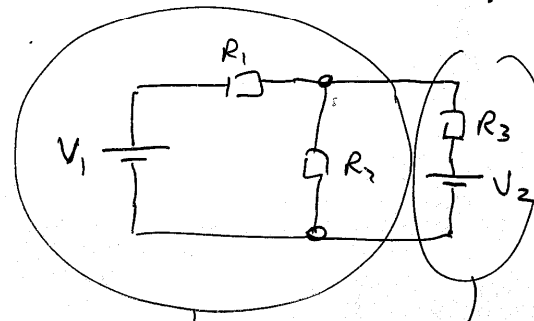

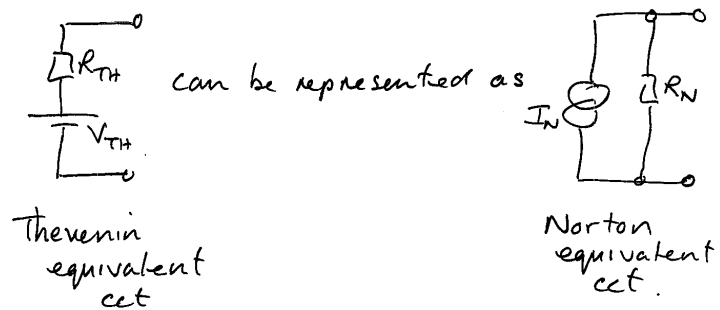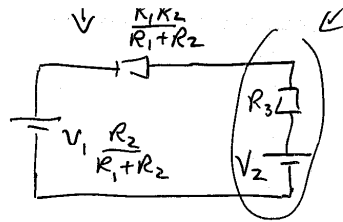


$$\text{short ckt o/p } I = \frac{V_{th}}{R_{th}} \quad \text{short ckt o/p } I = I_N$$

$$\therefore I_N = \frac{V_{th}}{R_{th}} \text{ for equivalence}$$

$$\text{open ckt o/p } V = V_{th} \quad \text{open ckt o/p voltage} \\ = I_N R_N \\ = \frac{V_{th}}{R_{th}} \cdot R_N$$

$$V_{th} = \frac{V_{th} R_N}{R_{th}} \text{ for equivalence} \\ \text{so } R_{th} = R_N$$

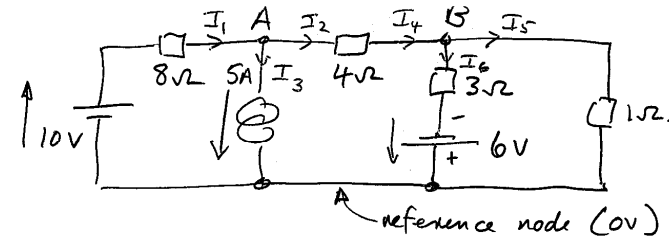A more complicated ckt with ^a current source.



A nodal approach.

sum currents at node A

$$I_1 = I_2 + I_3$$

entering leaving

$$\frac{10 - V_A}{8} = \frac{V_A - V_B}{4} + 5 \quad \text{--- (1)}$$

sum currents at node B.

$$I_4 = I_5 + I_6$$

$$\frac{V_A - V_B}{4} = \frac{V_B - 0}{1} + \frac{V_B - (-6)}{3} \quad \text{--- (2)}$$

rearrange (1)

$$10 - V_A = 2V_A - 2V_B + 8.5 \\ = 2V_A - 2V_B + 40$$

$$-30 = 3V_A - 2V_B \quad \text{--- (1a)}$$

rearrange (2)

$$3V_A - 3V_B = 12V_B + 4V_B + 24$$

$$3V_A - 2V_B = 16V_B \quad \text{--- (2a)}$$

$$24 = 3V_A - 19V_B \quad \text{--- (2a)}$$

$$\begin{aligned} (-30 &= 3V_A - 2V_B) \\ +(-24 &= -3V_A + 19V_B) \end{aligned}$$

$$-54 = 0 + 17V_B$$

$$V_B = -\frac{54}{17} = -3.18 \text{ V}$$

sub V_B in 1a.

$$-30 = 3V_A - \left(-\frac{108}{17}\right)$$



$$-30 - \frac{108}{17} = 3V_A$$

$$V_A = -\frac{510 + 108}{17 \times 3} = -\frac{618}{51} \text{ V}$$

$$= -12.1 \text{ V}$$

check ... using 2a.
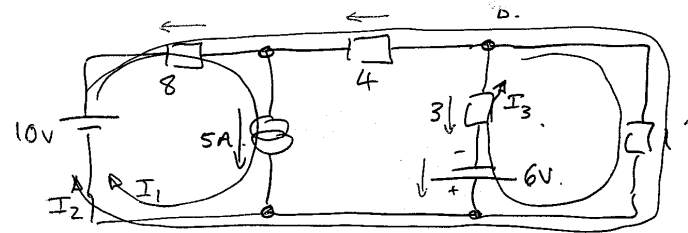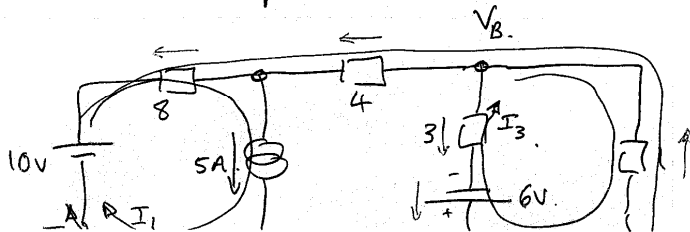
$$\begin{aligned} 24 &= 3 \times (-12.1) - 19 \times (-3.18) \\ &= -36.3 + 60.4 \\ &\approx 24 \end{aligned}$$



Loop ① $I_1 = 5 \text{ A}$

loop ② $10 = 8(I_1 + I_2) + 4I_2 + 1(I_2 + I_3)$

loop ③ $3I_3 + 6 + (I_2 + I_3)1 = 0$

rearrange loop ②

$$10 = 40 + 13I_2 + I_3$$

$$-30 = 13I_2 + I_3$$

rearrange loop 3.

$$-6 = I_2 + 4I_3$$

multiply loop 2 by (-4) and add to loop 3

$$120 = -52I_2 - 4I_3$$

$$-6 = I_2 + 4I_3$$

$$114 = -51I_2 + 0$$

$$I_2 = -\frac{114}{51} = -2.24 \text{ A}$$

sub. in loop 3

$$-6 = -\frac{114}{51} + 4I_3$$

$$-6 = -\frac{114}{51} + 4I_3$$

$$\frac{-306 + 114}{51 \times 4} = I_3 = \frac{-192}{4 \times 51} = -0.941 \text{ A}$$

$$V_B = (I_2 + I_3)1$$


$$= (-2.24 - 0.941)$$

$$= -3.18 \text{ V.}$$

A brief review of homework.

main points

— Not showing working.

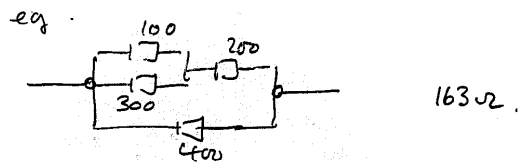

$$R_{\text{eff}} = 400 \parallel (200 + (100 \parallel 300))$$

$$= 163.$$

— Not finding voltage across or current through the resistor of interest to calculate power.


— Abusing current sharing rules.

Calculation

$$\uparrow I$$

$$V = I(R_1 \parallel R_2)$$

$$= I \frac{R_1 R_2}{R_1 + R_2}$$

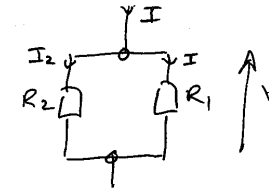


$$I_2 = \frac{V}{R_2} = I \frac{R_1 R_2}{R_1 + R_2} \times \frac{1}{R_2}$$

$$= I \frac{R_1}{R_1 + R_2}$$

$$V = I R_1 \parallel (R_2 \parallel R_3)$$
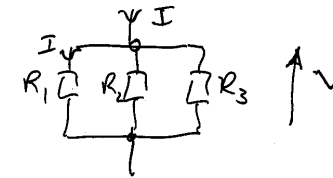
$$= I \frac{R_1 (R_2 \parallel R_3)}{R_1 + (R_2 \parallel R_3)}$$



$$I_1 = \frac{V}{R_1} = I \frac{R_1 (R_2 \parallel R_3)}{R_1 + (R_2 \parallel R_3)} \times \frac{1}{R_1}$$

$$= I \frac{R_2 \parallel R_3}{R_1 + (R_2 \parallel R_3)}$$

$$= I \frac{R_2 R_3}{R_1 R_3 + R_1 R_2 + R_2 R_3}$$

* — Rounding

$$0.03 \text{ A} \rightarrow 30 \text{ mA or } 30 \times 10^{-3} \text{ A.}$$


$$1894 \text{ V} \rightarrow 1.89 \times 10^3 \text{ V or } 1.89 \text{ kV}$$

$$3 \mu\text{A} = (0.000003 \text{ A}) \text{ not a good idea}$$

significance figures is sufficient

If the answer is 2 it should be written as 2.00

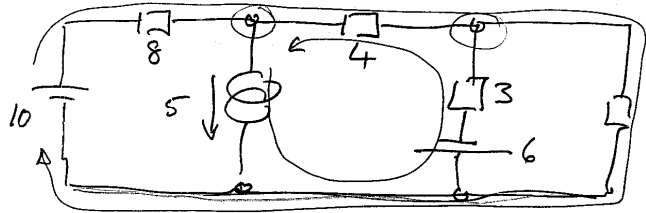- must draw a circuit if you are going to use algebraic variables like I_1, I_2, V_3 , etc.



- need as many equations as there are simple closed loops (3 in this case)



number of nodes, $n = 3$.

number of branches, $b = 5$



minimum number of loops required

$$= (b - n) + 1$$

$$= (5 - 3) + 1 = 3$$

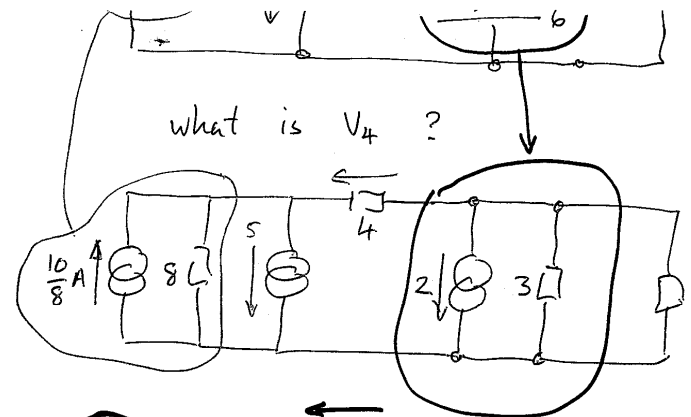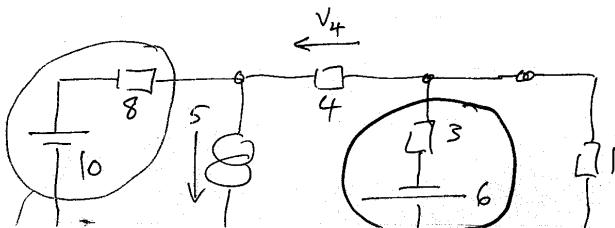

what is V_4 ?

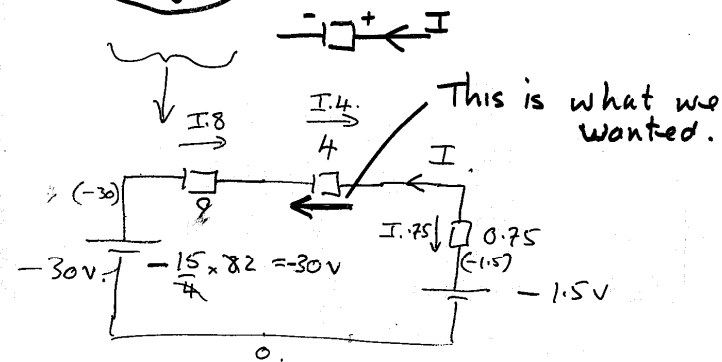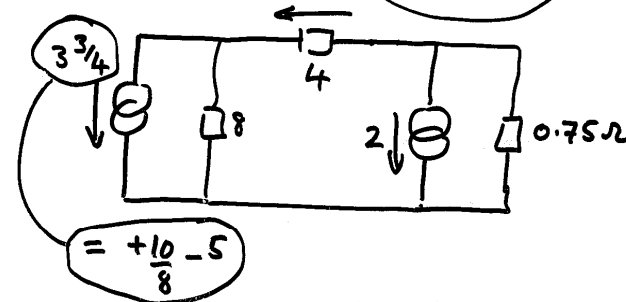

$$-1.5 - I(0.75) - I_4 - I_8 = -30$$


$$28.5 = I(12.75)$$

$$I = 2.235$$

$$I = \frac{28.5}{12.75}$$

$$V_{4\mu} = -I \cdot 4 = -\frac{28.5}{12.75} \times 4.$$

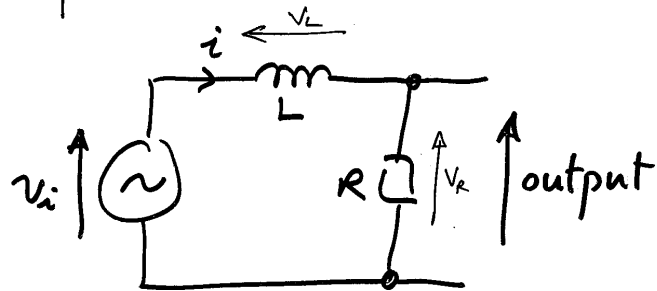
A quick background to the passive circuits lab.



inductor governed by

$$V = L \frac{dI}{dt}$$

let I be a sinusoidal forced current


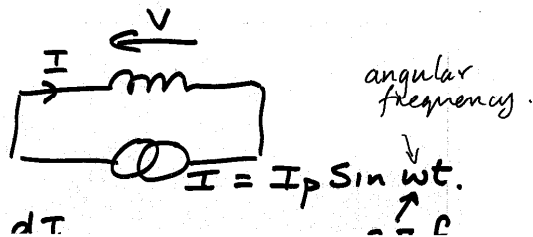


$$V = L \frac{dI}{dt}$$

$$V = L \frac{d(I_p \sin \omega t)}{dt}$$

$$= L I_p \omega \cos \omega t$$

I lags V by 90°

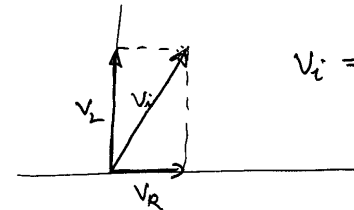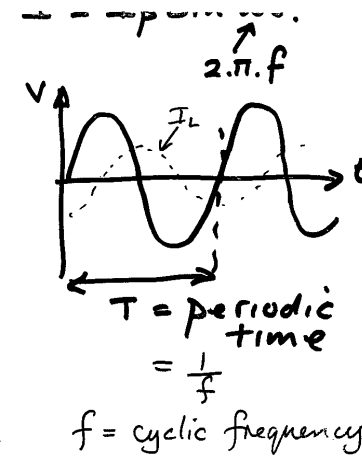



$$V_i = \sqrt{V_L^2 + V_R^2}$$

for a sinusoid the "impedance" of an inductor is

$$Z_L = \omega L = X_L$$

inductive impedance inductive reactance

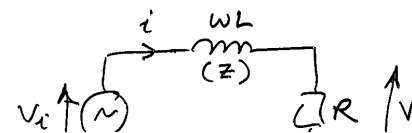

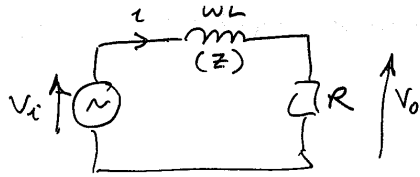

$$i = \frac{v_i}{Z_L + R} = \frac{v_i}{\sqrt{Z_L^2 + R^2}}$$




$$= \frac{v_i}{\sqrt{w^2 L^2 + R^2}}$$

$$\frac{v}{i} = Z_{cct} = \sqrt{w^2 L^2 + R^2}$$



$$v_o = iR = v_i \frac{R}{\sqrt{w^2 L^2 + R^2}}$$

Circuits containing C

$$I = C \frac{dv}{dt}$$

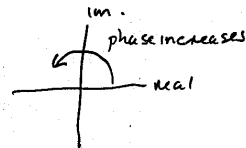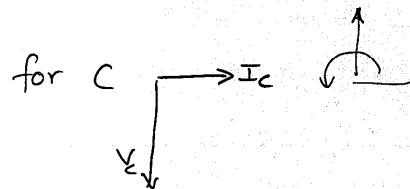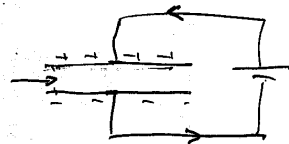
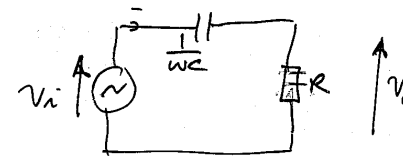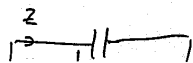
$$\text{Capacitive reactance} = \frac{1}{wc}$$






$$Z = \sqrt{R^2 + \left(\frac{1}{wc}\right)^2}$$

$$v_o = i_Z R$$

$$i_Z = \frac{v_i}{Z}$$
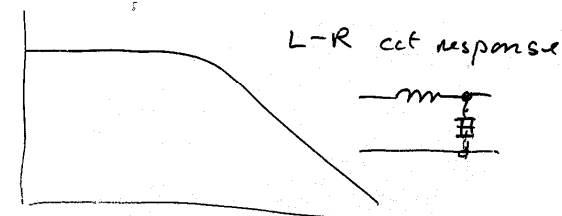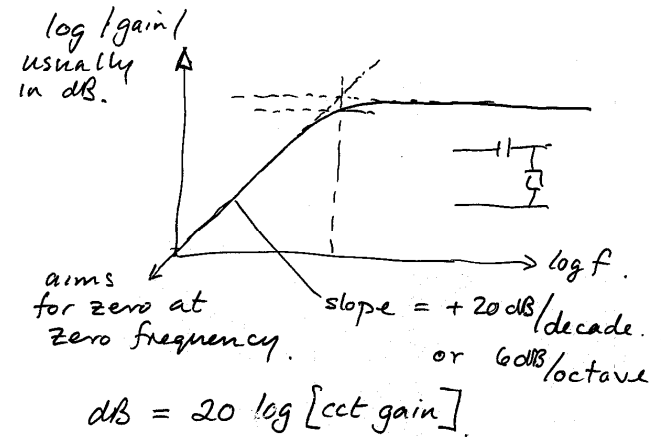
$$v_o = \frac{v_i}{\sqrt{R^2 + \left(\frac{1}{wc}\right)^2}} \cdot R = \frac{v_i R wc}{\sqrt{1 + R^2 w^2 c^2}}$$



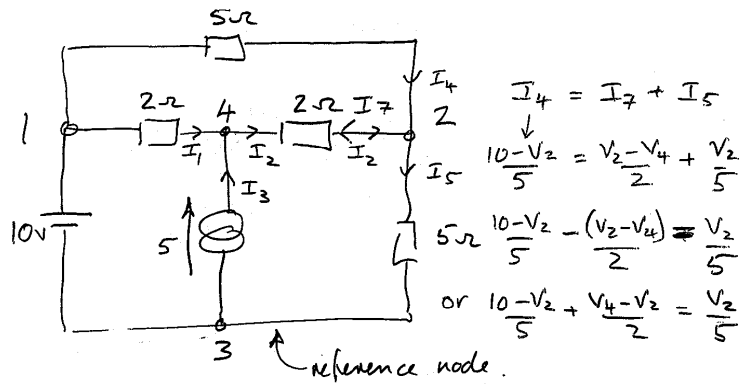

$V_{\text{node 1}} = 10\text{V}$ by inspection.

— need node equations to find $V_4 + V_2$

Sum currents at node 4: $I_1 + I_3 = I_2$

$$\frac{10-V_4}{2} + 5 = \frac{V_4-V_2}{2}$$

$$\text{or } 10 - V_4 + 10 = V_4 - V_2$$

$$\text{or } 20 = 2V_4 - V_2 \quad \text{--- (1)}$$

Sum currents at node 2: $I_4 + I_2 = I_5$

$$\frac{10-V_2}{5} + \frac{V_4-V_2}{2} = \frac{V_2}{5}$$

$$20 - 2V_2 + 5V_4 - 5V_2 = 2V_2$$

$$20 = -5V_4 + 9V_2 \quad \text{--- (2)}$$

Sub V_2 from eqn. (1) into (2)

$$20 = -5V_4 + 9(2V_4 - 20)$$

$$20 = 13V_4 - 180$$

$$\text{or } V_4 = \frac{200}{13} = 15.4\text{V}$$

Using (1) $20 = \frac{2 \times 200}{13} - V_2$

$$260 = 400 - 13V_2$$

$$-140 = -13V_2$$

$$V_2 = \frac{140}{13} = 10 \text{ and a bit.}$$

I_1 is the current through top 5Ω from left to right. (I_4 in the cct diag above.)


$$I_1 (= I_4) = \frac{10 - V_2}{5}$$

$$= 10 - \frac{140}{13}$$

$$\quad \quad \quad \frac{5}{13}$$

$$= \frac{130 - 140}{5 \cdot 13} = -\frac{2}{13}$$

$$= -0.154\text{A}$$

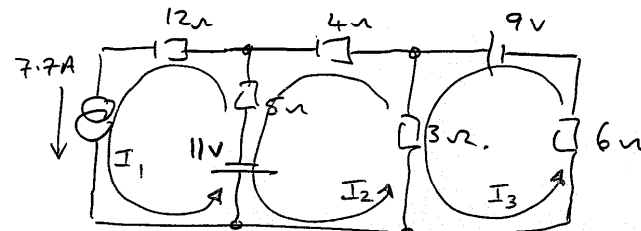

$$I_1 = 7.7\text{A}$$

Sum voltages around loop I_2 .

$$11 - (I_2 - I_3)3 - I_2 4 - (I_2 - I_1)5$$

$$\text{or } 11 - 12I_2 + 3I_3 + 38.5 = 0$$

$$\text{or } 11 - 12I_2 + 3I_3 + 38.5 = 0.$$

Sum voltages around loop I_3

$$9 - (I_3 - I_2)3 - I_3 6 = 0$$

$$9 - 9I_3 + 3I_2 - 6I_3 = 0$$

$$3 - 3I_3 + I_2 = 0$$