

EEE123 Problem Sheet Solutions

Diode Conduction State

Q1 Solutions are only provided for those problems that are given with a numerical answer.

(a) -

(b) - make an assumption; here it will be assumed that the diode is not conducting so diode must be replaced by an open circuit....

must find V_A and V_C w.r.t. reference....

$$V_A = 6V$$

$$V_C = 4V \text{ (no volts are dropped across } R)$$



$\therefore V_A - V_C = 2V \Rightarrow$ diode conducts; assumption wrong.

- now must recalculate to find forward bias current....

since this is a series loop, simplest way to proceed is add up voltage around loop....

$$4V + I_D R + 0.7V - 6V = 0$$

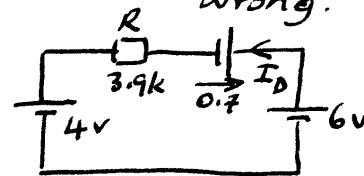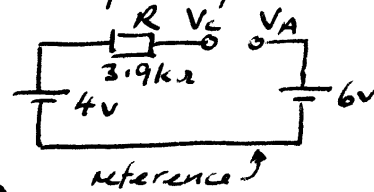
$$\text{or } I_D = \frac{6 - 4 - 0.7}{3.9k\Omega} = \underline{\underline{0.33mA}}$$



(c) -

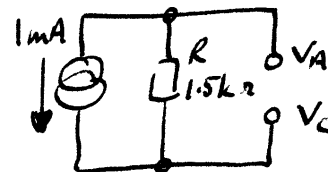(d) - assume diode not conducting as in (b)

$$\begin{aligned} V_A - V_C &= \text{volts across } R \\ &= -1mA \times 1.5k\Omega \\ &= \underline{\underline{-1.5V}} \end{aligned}$$




\therefore diode reverse biased by 1.5V \Rightarrow assumption is correct.

(e) - assume diode not conducting

$$V_A = 2\text{mA} \times 12\text{k}\Omega = 24\text{V}$$

$$V_C = 9\text{mA} \times 2.2\text{k}\Omega = 19.8\text{V}$$
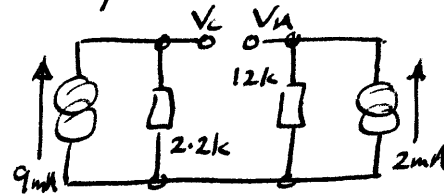
$$V_A - V_C = 24 - 19.8 = \underline{\underline{4.2\text{V}}}$$



\therefore assumption wrong; diode conducts.

- now replace diode by a 0.7V source...


using superposition...

$$I_D(0.7\text{V}) = -0.7 / 14.2\text{k}\Omega$$

$$I_D(9\text{mA}) = - \frac{9\text{mA} \cdot 2.2\text{k}}{14.2\text{k}}$$

$$I_D(2\text{mA}) = + \frac{2\text{mA} \cdot 12\text{k}}{14.2\text{k}}$$
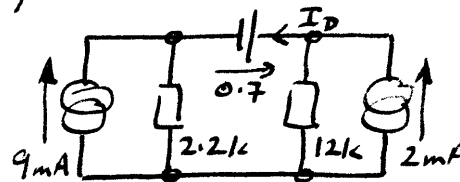
$$I_{\text{TOT}} = \frac{1}{14.2\text{k}} [-0.7 - 19.8 + 24] = \frac{3.5\text{V}}{14.2\text{k}\Omega} = \underline{\underline{246\mu\text{A}}}$$



Note that converting the combinations (9mA, 2.2k Ω) and (2mA, 12k Ω) into Thevenin equivalents yields a single loop that can be solved easily as in (b).

(f) -

(g) -

Q2 In all the examples of Q2, the condition $V_D = 0.7\text{V}$, $I_D = 0$ is required so assume a conducting diode, find I_D in terms of variable source then put $I_D = 0$.


Alternatively replace diode by an open circuit and find out the value of source that will give $V_A - V_C = 0.7\text{V}$.

(a) - The loop equation for this circuit is ...

$$0.7V + V + I_D 1k\Omega = 0$$

if $I_D = 0$,
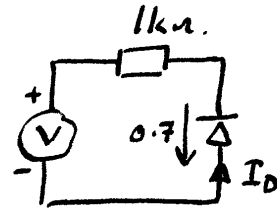
$$0.7 + V = 0 \text{ or } \underline{\underline{V = -0.7V}}$$




(b) - The loop equation for this circuit is ...

$$V + I_D 3.9k\Omega + 0.7 - 6 = 0$$

and if $I_D = 0$,
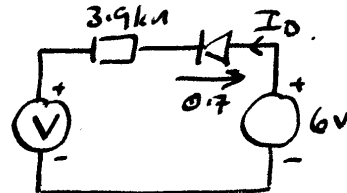
$$V = 6 - 0.7 = \underline{\underline{5.3V}}$$



(c) - voltage across $1k\Omega$ is $0.7V$ so...

$$I_R = 0.7 / 1k\Omega = 0.7mA.$$


summing currents at diode's anode node....

$$I_T = I_R + I_D = \frac{V - 0.7}{3.3k\Omega}.$$

and putting $I_D = 0$...

$$I_R = 0.7 / 1k\Omega = \frac{V - 0.7}{3.3k\Omega}$$
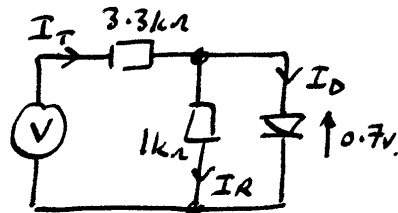
$$\text{or } V = \frac{0.7 \times 3.3}{1} + 0.7 = \underline{\underline{3.01V}}$$



(d) - voltage across $1.5k\Omega$ is $0.7V$ so...


$$I_R = 0.7 / 1.5k\Omega.$$

summing currents at diode anode node...

$$I + I_R + I_D = 0 = I + 0.7 / 1.5k\Omega + I_D$$

if $I_D = 0$,
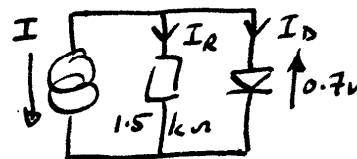
$$I + 0.7 / 1.5k\Omega = 0 \text{ or } I = -\frac{0.7}{1.5k\Omega} = \underline{\underline{-0.467mA}}$$



(e) - using loops ...

$$0.7V + (I_D - I_2)2.2k\Omega + (I_D - I)12k\Omega = 0$$


$$\text{but } I_2 = -9mA$$

$$\therefore 0.7V + 2.2k\Omega I_D + 12k\Omega I_D + 19.8V - I \cdot 12k\Omega = 0$$

$$\text{and if } I_D = 0$$

$$0.7V + 19.8V - 12k\Omega I = 0$$
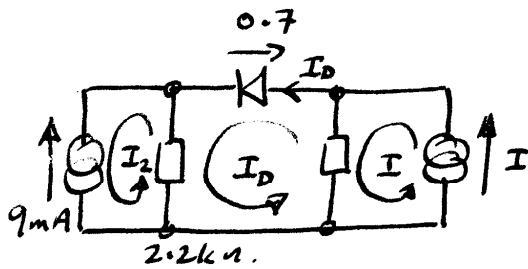
$$\text{or } I = \frac{0.7V + 19.8V}{12k\Omega} = + \frac{20.5}{12k\Omega} = + \underline{\underline{1.71mA}}$$




(f) - using loops

$$-V + 0.7 + (I_D + 0.6) \cdot 12 = 0$$


$$\text{if } I_D = 0 \dots$$

$$-V + 0.7 + 7.2 = 0$$
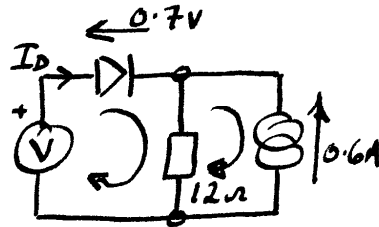
$$\text{or } \underline{\underline{V = 7.9V}}$$



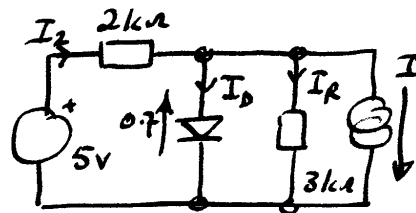(g) - since volts across
3kΩ is 0.7V,
 $I_R = 0.7/3k\Omega$.



Summing current at
diode anode node...

$$I_2 = I_D + I_R + I$$

$$\text{or } \frac{5 - 0.7}{2k\Omega} = I_D + \frac{0.7}{3k\Omega} + I$$

$$\text{and if } I_D = 0,$$

$$\frac{4.3}{2k\Omega} - \frac{0.7}{3k\Omega} = I = \underline{\underline{1.92mA}}$$