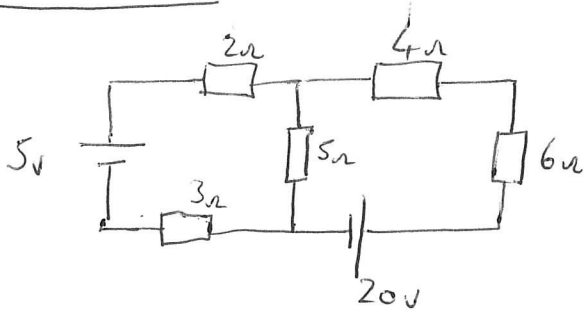




QUESTION 1

1

(a)



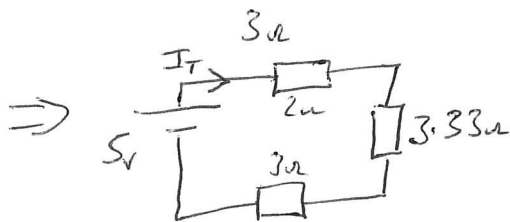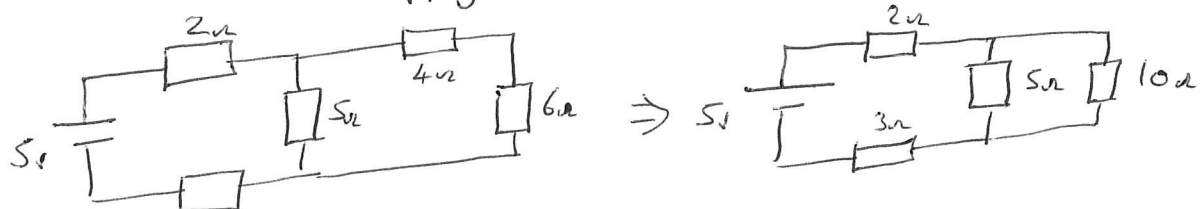First consider the 5V supply - short out the 20V battery




$$\therefore I_T = \frac{5}{2+3+3.33} = 0.6A$$

and hence the current through the 5Ω resistor is

$$I_{5\Omega} = \frac{10}{5+10} \cdot I_T = \frac{10}{15} \times 0.6 = 0.4A \downarrow$$

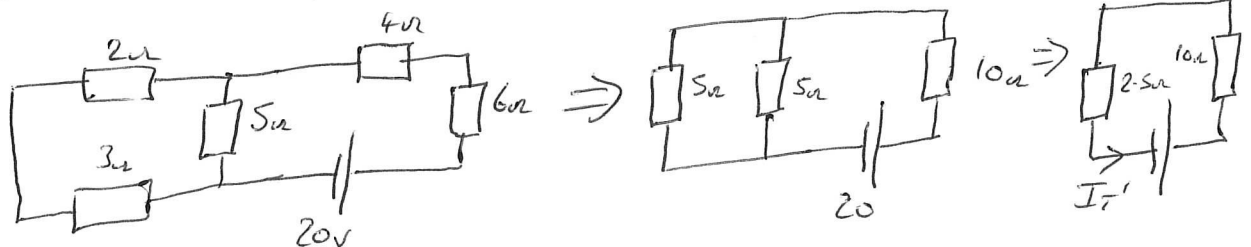Now consider the 20V supply and short out the 5V battery.



$$I_T' = \frac{20}{12.5} = 1.6A$$

and the current through the 5Ω resistor is

$$I_{5\Omega}' = \frac{5}{5+5} \cdot 1.6 = 0.8A \downarrow$$


By superposition the total current through the 5Ω resistor is:

$$I_{5\Omega \text{ TOTAL}} = 0.4\downarrow + 0.8\downarrow = \underline{\underline{1.2\downarrow}}$$

QUESTION 1 (CONTINUED)

2

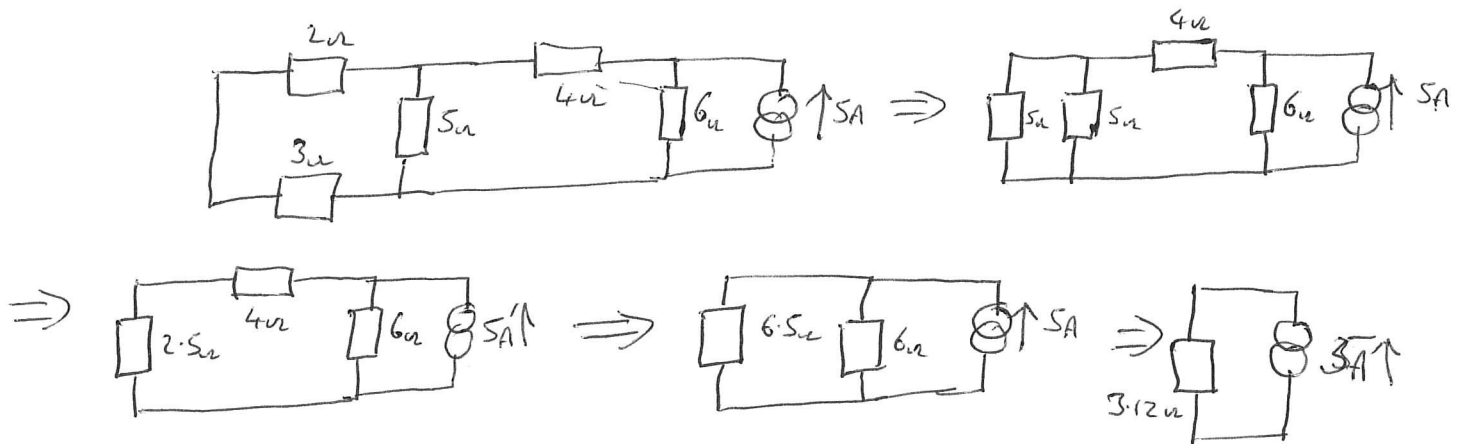- (b) We can use the analysis from part (a), but now need to consider the effect of the $5A$ current source alone:



\therefore Voltage across 3.12Ω resistor $= I \cdot R = 5 \times 3.12 = 15.6V$

Hence the current through the 6.5Ω resistor is $15.6/6.5 = 2.4A$.
This is the same current flowing through the 2.5Ω resistor. Hence the current flowing through the 5Ω resistor is $1.2A \downarrow$.

By superposition the total current flowing through the 5Ω resistor is now:

$$I_{5\Omega \text{ TOTAL}} = 1.2 \downarrow + 1.2 \downarrow = \underline{\underline{2.4A \downarrow}}$$

(from (a))

- (c) For Thevenin we need the open circuit voltage which is equal to the voltage across the 6Ω resistor. Using the working from part (a) - for the $5V$ source current through 6Ω resistor (for branch in network) is:

$$I_{6\Omega} = I_T \times \frac{S}{S+10} = 0.6 \times \frac{5}{15} = 0.2A \downarrow$$


For the $20V$ source the current through the 6Ω resistor is equal to $I_T' = 1.6A \uparrow$

Hence total current through 6Ω resistor is $1.6 \uparrow + 0.2 \downarrow = 1.4A \uparrow$
and the Thevenin voltage is $1.4 \times 6 = 8.4V \downarrow$


QUESTION 1 (CONTINUED)

3

Resistance of the network:

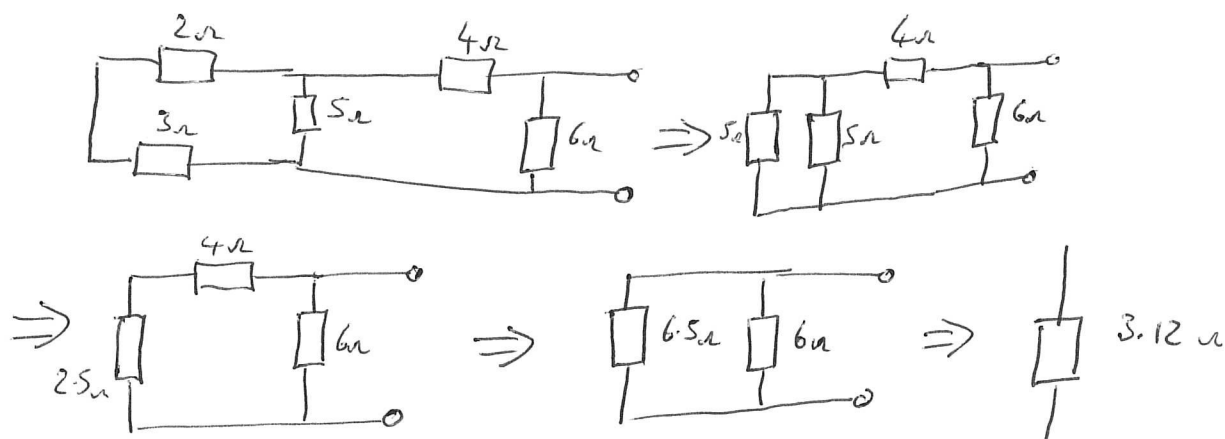


Hence the Thevenin circuit is:

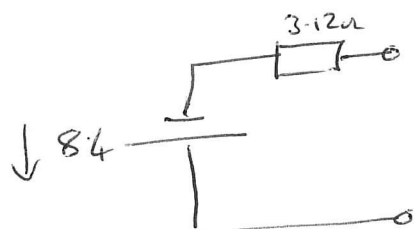

When the load is connected $I = \frac{8.4}{(10 + 3.12)} = 0.64A \uparrow$ and the

power dissipated $= I^2 R = 0.64^2 \cdot 10 = \underline{\underline{4.096W}}$

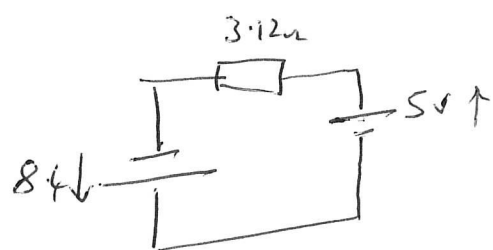d. When the rechargeable battery is connected:




Applying K's voltage law $8.4 + 5 - 3.12I = 0$
 $\therefore I = 4.29A$

The battery will act as a source.

(e) The Norton current can be found directly from Thevenin.

$$I_N = \frac{V_{TH}}{R_{TH}} = \frac{8.4}{3.12} = 2.69A$$

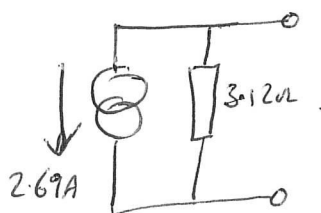

QUESTION 2

4

(a)(i) The impedance of the circuit is:

$$Z = R + j\omega L + \frac{1}{j\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

At resonance the imaginary terms cancel and the impedance becomes purely resistive:


Therefore

$$\omega L = \frac{1}{\omega C} \quad \text{at resonance}$$


$$\omega^2 = \frac{1}{LC} \Rightarrow \omega = \frac{1}{\sqrt{LC}}$$

Now $\omega = 2\pi f$ hence
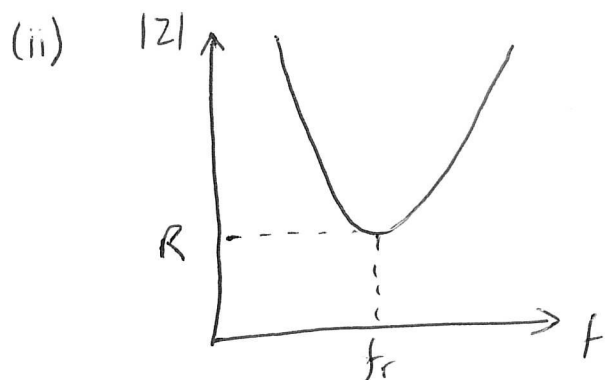
$$\underline{\underline{f_r = \frac{1}{2\pi\sqrt{LC}}}}$$



(iii)

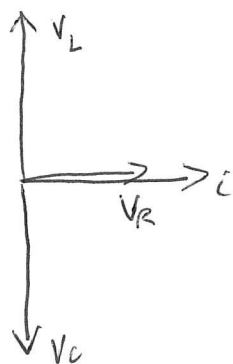

$|V_L| = |V_C|$ at resonance.

QUESTION 2 (CONTINUED)

5

(iv)

$$Q = \left| \frac{V_L}{V_R} \right| \text{ at resonance}$$

$$Q = \frac{I_s \omega L}{I_s R} = \frac{\omega L}{R}$$

however at resonance $\omega = \frac{1}{\sqrt{LC}}$

$$\therefore Q = \frac{1}{\sqrt{LC}} \cdot \frac{L}{R} = \underline{\underline{\frac{1}{R} \sqrt{\frac{L}{C}}}}$$

(v)

Using $Q = 6.86$ then since:

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \Rightarrow 6.86 = \frac{1}{100} \sqrt{\frac{L}{C}}$$

$$\therefore 686^2 = \frac{L}{C} \Rightarrow 470596 C = L \quad - (1)$$

Now:

$$f_r = 23200 = \frac{1}{2\pi\sqrt{LC}} \Rightarrow LC = 4.706 \times 10^{-11} \quad (2)$$

Substituting for L in (2) from (1):

$$470596 C^2 = 4.706 \times 10^{-11}$$

$$\therefore C = 0.01 \mu F$$

Then back substituting:

$$L = 4.7 mH.$$

(These are the values used in the Passive Networks lab).

QUESTION 2 (CONTINUED)

6

(b) (i) Impedance of the RL branch is:

$$Z_{RL} = R + j\omega L$$

but this is then in parallel with the capacitor:

$$\therefore \frac{1}{Z} = \frac{1}{Z_{RL}} + \frac{1}{1/j\omega C} = \frac{1}{R + j\omega L} + j\omega C = \frac{1 + j\omega CR - \omega^2 LC}{R + j\omega L}$$

$$\therefore Z = \frac{R + j\omega L}{1 + j\omega CR - \omega^2 LC}$$

(ii) Rationalise to the form $a + jb$ by multiplying through by the complex conjugate of the denominator $(1 - \omega^2 LC - j\omega CR)$

$$\therefore Z = \frac{R + j\omega L (1 - \omega^2 LC - j\omega CR)}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2}$$

The denominator is now real so we need to set the imaginary terms in the numerator to zero.

Multiplying out the numerator:

$$\text{Num} = R - \omega^2 RLC - \underline{j\omega CR^2} + \underline{j\omega L} - \underline{j\omega^3 L^2 C} + \omega^2 LCR$$

Setting the imaginary terms to zero:

$$- \omega CR^2 + \omega L - \omega^3 L^2 C = 0$$

$$\therefore \omega^2 L^2 C = L - CR^2$$


$$\therefore \omega^2 = \frac{L - CR^2}{L^2 C} = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\therefore \omega = \underline{\underline{\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}}$$

QUESTION 3

7

(a)

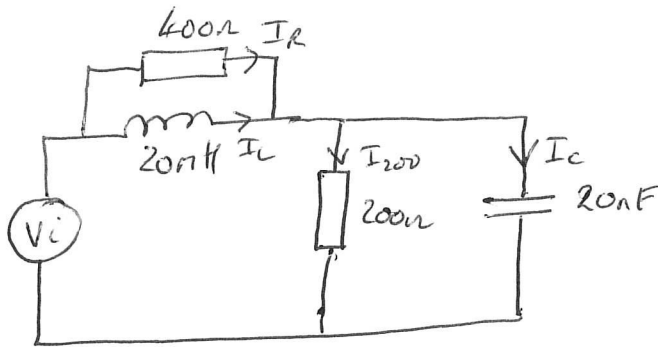

At $t = 0^-$ $V_i = -10V$ DC So:

$$\underline{I_R = 0} \quad (\text{since there is no } V \text{ across inductor})$$

$$\underline{I_c = 0} \quad (\text{since } V_i \text{ is dc for } t < 0)$$

$$I_L = \frac{V_i}{200} = \frac{-10}{200} = \underline{\underline{-50mA}}$$

At $t = 0^+$ $V_i = 20V$ so:

$$I_L \text{ is unchanged at } \underline{\underline{-50mA}}$$

V_c will remain unchanged at $-10V$ at $t = 0^+$ so

$$I_R = \frac{20 - (-10)}{400} = \underline{\underline{75mA}}$$

$$I_c = I_L + I_R - I_{200} = -50 + 75 + 50 = \underline{\underline{75mA}}$$

(b)

Before the switch is closed:

$$Q_1 = C_1 V_1 \quad \& \quad Q_2 = 0$$

Then the energy in C_1 is:

$$E_{C_1} = \frac{1}{2} C_1 V_1^2 = \frac{1}{2} \times 3 \times 10^{-6} \times 100^2 = \underline{\underline{15mJ}}$$

(No energy stored in C_2)

After closing the switch the capacitors will share the charge equally and the voltages will be equal.

QUESTION 3 (CONTINUED)

8

$$\text{i.e. } Q_1 = Q_{1A} + Q_{2A} \Rightarrow C_1 V_1 = C_1 V_{1A} + C_2 V_{2A}$$

and since $V_{1A} = V_{2A}$ then:

$$3 \times 10^{-6} \times 100 = 3 \times 10^{-6} V_{1A} + 2 \times 10^{-6} V_{1A}$$

$$\therefore V_{1A} = V_{2A} = 60V$$

$$\begin{aligned} \therefore E_1 = E_{1A} + E_{2A} &= \frac{1}{2} C_1 V_{1A}^2 + \frac{1}{2} C_2 V_{1A}^2 = \frac{1}{2} \times 3 \times 10^{-6} \times 60^2 + \frac{1}{2} \times 2 \times 10^{-6} \times 60^2 \\ &= \underline{\underline{9mJ}} \end{aligned}$$

Energy lost as heat dissipated in the resistor.

- (c) Before the switch is closed there is no voltage across the resistor or capacitor and the current is zero. When the switch is closed V_s appears across R and C , however the voltage across C cannot change instantaneously.

$$V_s = V_R + V_C \text{ at all times}$$

$$V_s = iR + \frac{1}{C} \int_0^t i \, dt$$

$$\text{differentiating: } \frac{dV_s}{dt} = \frac{di}{dt} R + \frac{i}{C}$$

$$\text{However } V_s \text{ is constant so } \frac{dV_s}{dt} = 0$$

$$\therefore \frac{di}{i} = -\frac{1}{RC} dt$$

$$\text{integrating: } \ln(i) = -\frac{1}{RC} t + A \quad (A = \text{constant of integration})$$

Now when $t = 0^+$ (immediately after the switch is closed) let the current be I_0 where:

$$I_0 = \frac{V_s}{R}$$

QUESTION 3 (CONTINUED)

9

Therefore

$$A = \ln I_0$$

Hence

$$\ln(i) - \ln(I_0) = -\frac{1}{RC} t$$

Rearranging and taking antilogs:

$$i = I_0 e^{-t/RC}$$

Voltage across the capacitor is:

$$V_C = \frac{1}{C} \int_0^t I_0 e^{-t/RC} dt = -\frac{RC}{C} I_0 \left[e^{-t/RC} \right]_0^t$$

$$V_C = -I_0 R \left[e^{-t/RC} - 1 \right] = I_0 R \left[1 - e^{-t/RC} \right]$$

$$\therefore \underline{\underline{V_C = V_s \left[1 - e^{-t/RC} \right]}}$$


(d) Substituting values in the above equation yields:

$$V_C = 10 \left(1 - e^{\frac{-2}{10^{-5} \cdot 10^{-5}}} \right) = 10 \left(1 - e^{-2} \right) = \underline{\underline{8.65V}}$$

QUESTION 4

10

(a)(i) Assuming an ideal transformer:

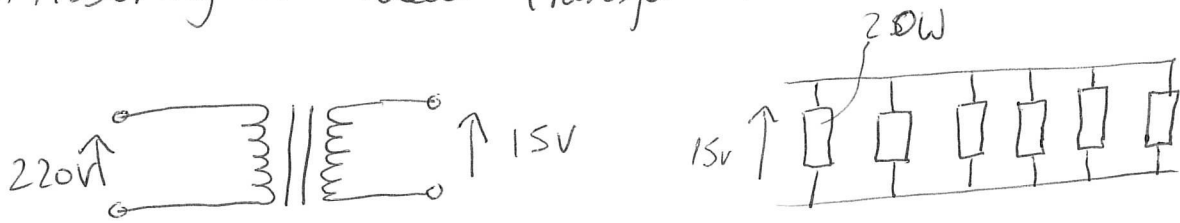

For six 20W bulbs the total load will be $6 \times 20 = 120W$.
Since the bulbs are purely resistive then the power-factor is unity and this is also the VA rating.

$$\text{Transformer rating} = \underline{\underline{120VA}}$$

$$\text{The turns ratio is given by } \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{220}{15} = \underline{\underline{14.67}}$$


(ii) Since the power-factor = 1 and the transformer is ideal:

$$I_P \cdot V_P = I_S V_S = VA$$

$$\text{Hence } I_P = \frac{VA}{V_P} = \frac{120}{220} = \underline{\underline{0.545A}}$$

$$I_S = \frac{VA}{V_S} = \frac{120}{15} = \underline{\underline{8A}}$$

(b)(i)

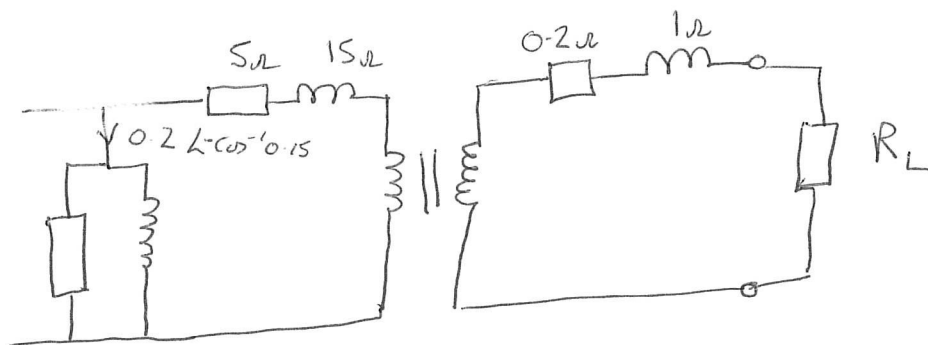

First find R_L (the effective resistance of all 6 bulbs):

$$P_L = 120W \quad V_S = 15$$

$$\therefore R_L = \frac{V_S^2}{P_L} = \frac{15^2}{120} = 1.875\Omega$$

QUESTION 4 (CONTINUED)

11


Referring all secondary quantities to the primary side:

$$R_2' = \left(\frac{N_1}{N_2}\right)^2 \cdot R_2 = 14.67^2 \times 0.2 = 43.04 \Omega$$

$$X_2' = \left(\frac{N_1}{N_2}\right)^2 \cdot X_2 = 14.67^2 \times 1 = 215.2 \Omega$$

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 \cdot R_L = 14.67^2 \times 1.875 = 403.52 \Omega$$

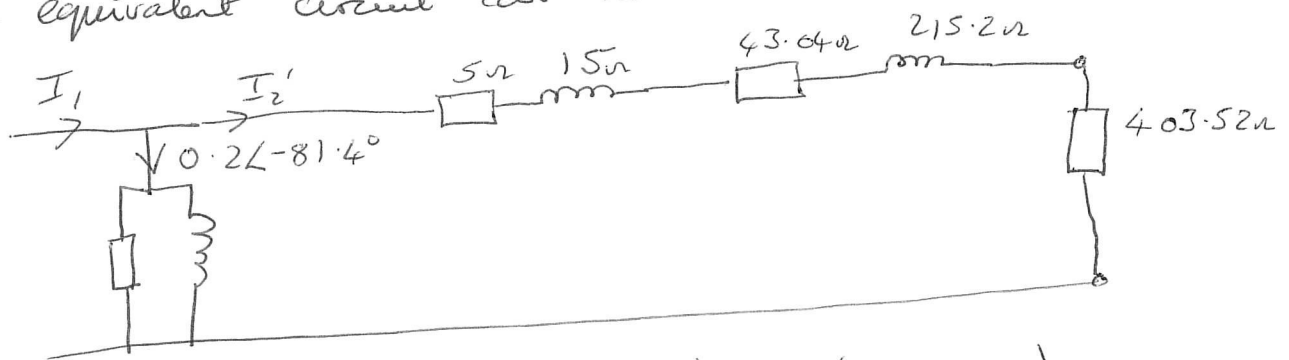The equivalent circuit can now be drawn as:



(ii)

$$\begin{aligned} \therefore Z_2' &= (5 + 43.04 + 403.52) + j(15 + 215.2) \\ &= 451.56 + j230.2 = 506.85 \angle 27^\circ \Omega \end{aligned}$$

$$\therefore I_2' = \frac{220 \angle 0^\circ}{506.85 \angle 27^\circ} = 0.434 \angle -27^\circ \text{ A}_{\text{rms}}$$

$$\begin{aligned} I_M &= 0.2 \text{ A} \text{ at } 0.15 \text{ pf lagging} \\ &= 0.2 \angle -81.4^\circ \text{ A}_{\text{rms}} \end{aligned}$$

$$\begin{aligned} \therefore I_1 &= I_M + I_2' = 0.2 \angle -81.4^\circ + 0.434 \angle -27^\circ \\ &= 0.574 \angle -43.46^\circ \text{ A} \end{aligned}$$

The total input current to the transformer is:

$$\underline{\underline{0.574 \angle -43.46^\circ \text{ A}_{\text{rms}}}}$$

(iii) The output power of the whole lighting system is:

$$P_L = I_2'^2 R_L' = 0.434^2 \times 403.52 = 76 \text{ W}$$

\therefore Power output from each bulb is $\frac{76}{6} = \underline{\underline{12.67 \text{ W}}}$

Voltage across bulbs (referred to primary side) is:

$$V_B' = I_2' \cdot R_L' = 0.434 \times 403.52 = 175.13 \text{ V}$$

\therefore Actual voltage across each bulb is:

$$V_B = \frac{N_2 \times V_1}{N_1} = \frac{175.13}{14.67} = \underline{\underline{11.94 \text{ V}_{\text{rms}}}}$$

(iv) Copper losses in transformer:

$$P_{\text{loss}} = I_2'^2 (R_1 + R_2') = 0.434^2 (5 + 43.04) = \underline{\underline{9.05 \text{ W}}}$$

(v) Core losses:

$$V_p \cdot I_m \cos \phi_m = 220 \times 0.2 \times 0.15 = 6.6 \text{ W}$$

$$\text{(Check } P_{\text{in}} = V_p I_1 \cos \phi = 220 \times 0.574 \times \cos(-43.46) = 91.66 \text{ W)}$$

$$P_{\text{in}} = P_{\text{out}} + P_{\text{loss}} = 76 + 9.05 + 6.6 = 91.65 \text{ W}$$

$$\text{Efficiency} = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\% = \frac{76}{91.66} = \underline{\underline{82.9\%}}$$

C. Using $V_{\text{rms}} = 4.44 f N \phi_{\text{rms}}$

$$N_p = \frac{220}{4.44 \times 50 \times 2 \times 10^{-3}} = \underline{\underline{495 \text{ TURNS}}}$$

$$N_2 = \frac{15}{4.44 \times 50 \times 2 \times 10^{-3}} = \underline{\underline{34 \text{ TURNS}}}$$

QUESTION 5

13

- (a) Calculate the current drawn by a single induction motor:

$$I_{ph} = I_{Line} = \frac{VL0^\circ}{Z\angle\phi^\circ} = \frac{400\angle 0^\circ/\sqrt{3}}{(3.6+j1.2)} \\ = 60.86\angle -18.4^\circ A$$

The power drawn by each motor is:

$$P = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \cdot 400 \cdot 60.86 \cos(-18.4^\circ) \\ = 40 \text{ kW}$$

Therefore total power drawn by the refrigeration system during opening hours is:

$$P_{TOT} = 2 \times 40 = \underline{\underline{80 \text{ kW}}}$$

$$P.f. = \cos 18.4^\circ = \underline{\underline{0.949 \text{ (lagging)}}}$$

- (b) Calculate the real and reactive power of all loads:

Lighting: $P = 30000 \text{ kW}$ $Q = 0 \text{ kVAR}$

Refrigeration $P = 80000 \text{ kW}$ (part (a))

$$Q = \frac{P}{\cos \phi} \sin \phi = \frac{80000}{0.949} \sin 18.4^\circ \\ = 26.6 \text{ kVAR}$$

Miscellaneous:

$$P = S \cos \phi = 20000 \times 0.6 = 12 \text{ kW}$$

$$Q = S \sin \phi = 20000 \times 0.8 = 16 \text{ kVAR}$$

(i) The total real power is:

$$P_{TOT} = 30000 + 80000 + 12000 = \underline{\underline{122 \text{ kW}}}$$

(ii) The total reactive power is:

$$Q_{TOT} = 0 + 26.67 + 16.0 = \underline{\underline{42.67 \text{ kVAR}}}$$

(iii) The total apparent power:

$$S_{TOT} = \sqrt{P_{TOT}^2 + Q_{TOT}^2} = \sqrt{122^2 + 42.67^2} = \underline{\underline{129.2 \text{ kVA}}}$$

(iv) The overall power factor:

$$\text{P.f.} = \frac{P_{TOT}}{S_{TOT}} = \frac{122}{129.2} = \underline{\underline{0.944}}$$

(c) During closing hours:

Lighting: $P = 4000 \text{ W}$ $Q = 0 \text{ VAR}$

Refrigeration $P = 40 \text{ kW}$ $Q = 13.3 \text{ kVAR}$

Miscellaneous $P = 8000 \times 0.6 = 4800 \text{ W}$
 $Q = 8000 \times 0.8 = 6400 \text{ VAR}$

$$\therefore P_{TOT_CLOSED} = 4 + 40 + 4.8 = 48.8 \text{ kW}$$

$$\therefore Q_{TOT_CLOSED} = 0 + 13.3 + 6.4 = 19.7 \text{ kVAR}$$

Hence the total kVA when closed is:

$$S_{TOT_CLOSED} = \sqrt{48.8^2 + 19.7^2} = \underline{\underline{52.63 \text{ kVA}}}$$

$$\text{Power factor} = \frac{P_{TOT}}{S_{TOT}} = \frac{48.8}{52.63} = \underline{\underline{0.927 \text{ (lagging)}}}$$


(d) During opening hrs:

$$P_{TOT} = 122 \text{ kW}$$

$$Q_{TOT} = 42.67 \text{ kVAR}$$

$$S_{TOT} = 129.2 \text{ kVA}$$

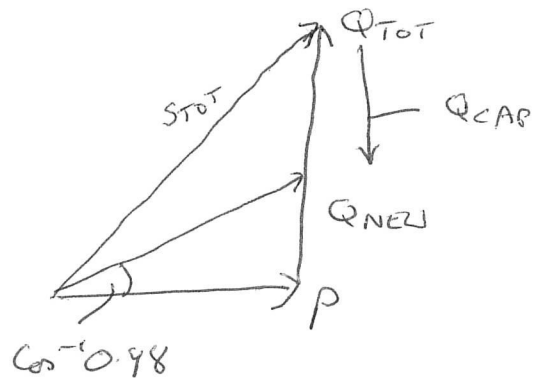Adding power-factor correction capacitors will not alter the real power drawn, but will effect Q and S .



After the capacitors are added:

$$Q_{NEW} = P \tan \phi = P \tan (\cos^{-1} 0.98) \\ = 122 \tan (\cos^{-1} 0.98) = 24.8 \text{ kVAR}$$

Hence the capacitors must provide:

$$Q_{CAP} = 42.67 - 24.8 = 17.87 \text{ kVAR} \\ \text{or } \frac{17.87}{3} = 5.96 \text{ kVAR / phase.}$$

Since the capacitors are star connected.

$$Q_{CAP-PH} = \frac{V_{PH}^2}{X_C} \Rightarrow X_C = \frac{400^2}{3 \times 5960} = 8.95 \Omega$$

$$\text{Hence } C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \cdot 50 \cdot 8.95} = \underline{\underline{356 \mu F}}$$

(a) (i) Using the equation:

$$NI = S\phi = S \cdot B \cdot A$$

then we first need to find the reluctance, S :

$$S_T = S_{\text{IRON}} + S_{\text{AIR}}$$

$$= \frac{L_{\text{iron}}}{\mu_0 \mu_r A} + \frac{L_{\text{air}}}{\mu_0 A} = \frac{0.478}{\mu_0 \cdot 800 \times 900 \times 10^{-6}} + \frac{0.002}{\mu_0 \cdot 900 \times 10^{-6}}$$

$$= 0.528 \times 10^6 + 1.768 \times 10^6 = 2.296 \times 10^6 \text{ H}^{-1}$$

$$\text{Now } I = \frac{S_T \times B \times A}{N} = \frac{2.296 \times 10^6 \times 1.4 \times 900 \times 10^{-6}}{500} = \underline{\underline{5.785 \text{ A}}}$$

(ii) The self-inductance is given by:

$$L = \frac{N^2}{S_T} = \frac{500^2}{2.296 \times 10^6} = \underline{\underline{0.109 \text{ H}}}$$

(b)(i). At a frequency of 100 kHz the reactance of the inductor is:

$$X = 2\pi f \cdot L = 2\pi \cdot 100 \cdot 0.109 = 68.5 \Omega$$

Hence the impedance, Z is:

$$Z = R + jX = 30 + j68.5 = 74.78 \angle 66.35^\circ \Omega$$

and the current is 5.785 (max value)

$$\therefore V_{\text{PK}} = I \cdot Z = 5.785 \times 74.78 = 432.6 \text{ V}_{\text{PK}} \\ \equiv \underline{\underline{305.9 \text{ V}_{\text{RMS}}}}$$

QUESTION 6 (CONTINUED)

17

(ii) The average power dissipated in the coil is

$$P = I_{\text{RMS}}^2 \cdot R = \frac{I_{\text{PK}}^2}{2} \cdot R = \frac{5.785^2}{2} \times 30 = \underline{\underline{502\text{W}}}$$

(iii) Peak energy stored in the inductor is:

$$E = \frac{1}{2} L I_{\text{PK}}^2 = \frac{1}{2} \times 0.109 \times 5.785^2 = \underline{\underline{1.824\text{J}}}$$

(c)(i) If the peak current is 8A and the flux density remains at 1.4 T then

$$S_{\text{NEW}} = \frac{NI}{B \cdot A} = \frac{500 \times 8}{1.4 \times 900 \times 10^{-6}} = 3.174 \times 10^6 \text{ H}^{-1}$$

$$\therefore S_{\text{IRONNEW}} + S_{\text{AIRNEW}} = S_{\text{NEW}}$$

Let the gap length be g :

$$\frac{1}{\mu_0 A} \left(\frac{0.48 - g}{800} + g \right) = 3.174 \times 10^6$$

$$\therefore 799g = (3.174 \times 10^6 \times \mu_0 \times 900 \times 10^{-6} \times 800) - 0.48$$

$$\therefore \underline{\underline{g = 3\text{mm}}}$$

(ii) The new self inductance is:

$$L_{\text{NEW}} = \frac{N^2}{S_{\text{NEW}}} = \frac{500^2}{3.174 \times 10^6} = \underline{\underline{78.8\text{mH}}}$$

QUESTION 6 (CONTINUED)

18

(iii) If the resistance of the coil is neglected then:

$$V_{rms} = 4.44 \cdot f \cdot N \cdot \phi_{max} = 4.44 f N B \cdot A$$

$$= 4.44 \times 100 \times 500 \times 1.4 \times 900 \times 10^{-6}$$

$$= \underline{\underline{279.7 V_{rms}}}$$