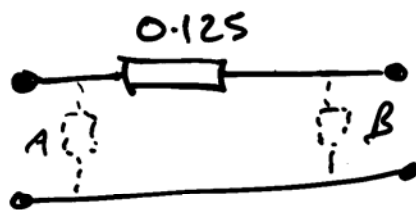


EXAMPLE Q4 part (c) & (d). 2003

A 60 MVA 132/33 kV STAR-DELTA TRANSFORMER WITH THE STAR WINDING SOLIDLY EARTHED, HAS A NOMINAL TAP IMPEDANCE ( $Z_{HL}$ ) OF 12.5%. THE TAP CHANGER IS ASSUMED TO BE ON THE 132 kV WINDING. DRAW THE EQUIVALENT CIRCUITS FOR NOMINAL TAP AND  $\pm 10\%$  TAP. (ASSUME IMPEDANCES  $Z_H$  &  $Z_L$  ARE PROPORTIONAL TO THE SQUARE OF THE NUMBER OF TURNS ON THE WINDING CONCERNED)

SOLUTION

a) ON NOMINAL TAP  $Z_{HL} = j0.125 \text{ pu} \text{ at } k=1$



$$A = \frac{Z}{1-k}$$

$$B = \frac{Z}{R(R-1)}$$


b) ON THE  $+10\%$  TAP

$$Z_{HL} = R_H^2 Z_{HL \text{ Nom}} = (1.1)^2 \cdot 0.125 = j0.1513$$

$$A = \frac{Z}{1-k} = \frac{j0.1513}{1-1.1} = -j1.513$$

$$B = \frac{Z}{R(R-1)} = \frac{j0.1513}{1.1(1.1-1)} = j1.375$$
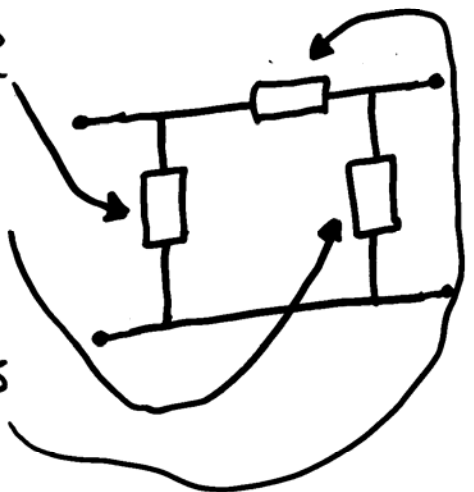
$$C = \frac{Z}{k} = \frac{j0.1513}{1.1} = j0.1375$$




-10%  $A = j1.0125$   $B = -j1.125$   $C = j0.1125$

CALCULATE THE 3- $\phi$  SYMMETRICAL FAULT CURRENT FOR EACH TRANSFORMER TAP FOR A FAULT ON THE LV SIDE. ASSUME THE FAULT LEVEL ON THE HV SIDE IS 1500 MVA.

FROM FAULT LEVELS GIVEN WE CAN CALCULATE THE SYSTEM IMPEDANCE:

$$Z_{SYS} = \frac{60}{1500} = j0.04 \text{ pu}$$

ON NOMINAL TAP THE CIRCUIT BECOMES:-

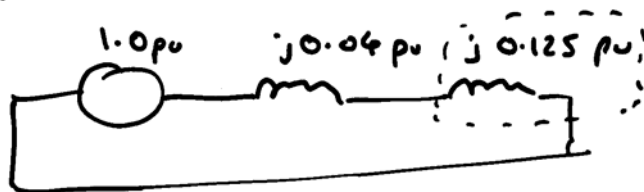



$$I_{fpu} = \frac{1}{j(0.04 + 0.125)} = -j6.06 \text{ pu}$$

$$\text{BUT } I_{BASE} = \frac{60 \times 10^6}{\sqrt{3} \times 33000} = \underline{1049.7 \text{ A} \approx 1050 \text{ A}}$$

$$|I_f| = 6.06 \times 1050 = \underline{\underline{6363 \text{ A}}}$$

FOR +10% TAP

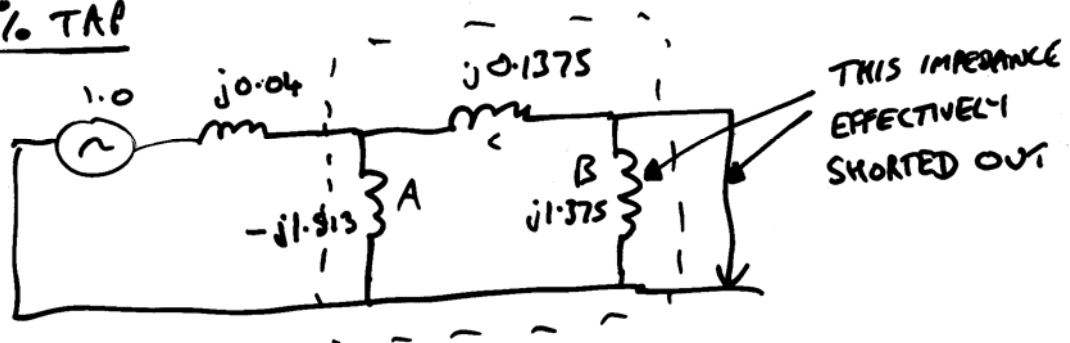

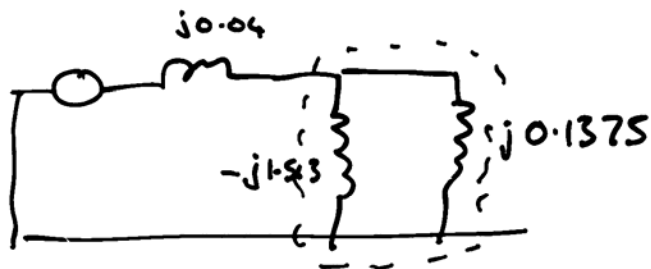

|| COMBINATION

$$\frac{1}{\frac{1}{-j1.513} + \frac{1}{j0.1375}}$$

$$= \frac{1}{\frac{j0.1375 - j1.513}{1.513 \times 0.1375}}$$

$$= \frac{1}{\frac{-j1.3755}{0.208}} = \frac{1}{-j6.61}$$

$$= \underline{j0.151}$$

$$I_F = \frac{1}{j(0.04 + 0.151)} = \underline{-j5.236 \text{ pu}}$$

$$|I_F| = I_{\text{BASE}} \times I_{\text{pu}} = 1050 \times 5.236 \\ = \underline{5497 \text{ A}}$$

for -10%

$$I_F = \underline{7430 \text{ A}}$$