

## EEE331 Analogue Electronics

### 3<sup>rd</sup> lecture:

- common emitter with feedback resistance
- 2 transistor circuit elements:
  - Darlington pair
  - Cascode pair
  - differential pair (introduction)


## EEE331 Analogue Electronics

### summary of last lecture: single BJTs and their voltage gains

- common emitter:  $G = -g_m(r_{CE} || R_L) \approx -g_m R_L$   
used as inverting amplifier
- common base:  $G = g_m R_L$   
used as fast switch
- emitter follower:  $G = \frac{(\beta+1)R_L}{(r_{BE} + \beta+1)R_L}$   
 $\approx g_m R_L / (1 + g_m R_L) \approx 1$   
used as buffer

## EEE331 Analogue Electronics
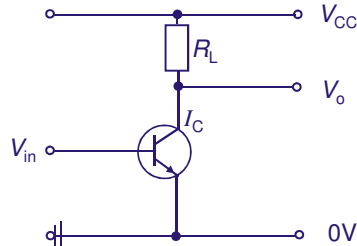
### common emitter (CE) BJT: situation without bias



$r_{CB}$  varies from device to device

$g_m$  depends on bias & temperature

transconductance:

consider input voltage:

gives collector current:

changes collector voltage:

$$g_m = \Delta I_C / \Delta V_{in}$$

$$V_{in} = V_{BE \text{ bias}} \pm \Delta V_{BE} / 2$$

$$I_C = I_{CB} \pm g_m \Delta V_{BE} / 2$$

$$V_o = V_{CC} - I_C R_L$$

$$= V_{CC} - I_{CB} R_L \pm g_m R_L \Delta V_{BE} / 2$$

$$V_{o, \text{bias}} = \text{const. } \Delta V_o \text{ varying}$$

hence voltage gain:


$$\Delta V_o / \Delta V_{in} = -g_m R_L$$

note:

$g_m < 0$  inverts signal and is a function of  $V_{BE \text{ bias}}$

## EEE331 Analogue Electronics

### common emitter (CE) BJT: biasing

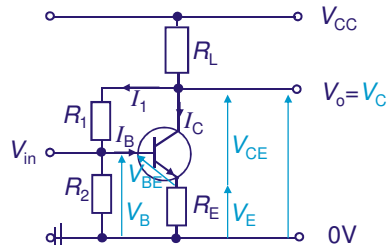

aim: use resistors to establish **constant bias conditions** & control  $I_C$

principle: large  $R_E \rightarrow$  large  $V_E \rightarrow V_B = V_E + V_{BE} \approx V_E = R_E I_E = \text{const.}$

and **negative feedback** by  $R_1, R_2$ :

increase of  $I_C \rightarrow$  smaller  $V_C = V_{CC} - (I_1 + I_C) R_L$


$\rightarrow$  smaller  $V_B = V_{CC} - (I_1 + I_C) R_L - I_1 R_1$

$\rightarrow$  reduces  $I_C$  by  $\Delta I_C = g_m \Delta V_B$

$\rightarrow$  **stabilises**  $I_C$

## EEE331 Analogue Electronics

### common emitter (CE) BJT: biasing

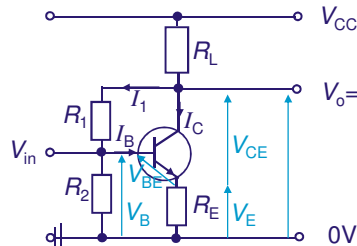

note for max. symmetrical swing of output voltage:  
 $V_C = V_B (R_1=0) \dots V_{CC} (R_L=0)$   
 $= \frac{1}{2} (V_{CC} + V_E + 0.7V)$


aim: calculation of output  $I_C$

assume:  $I_B$  negligibly small,  $V_{BE} \approx 0.7V$ ,  $h_{FE} \gg 1$  (i.e.  $I_C \approx I_E$ )

Kirchhoff's Voltage Law:  $V_{CC} = I_1 R_2 + I_1 R_1 + (I_1 + I_C) R_L$   
 $= I_C R_L + I_1 (R_1 + R_2 + R_L)$  (i)  
 and also:  $I_1 R_2 = V_B = V_E + V_{BE} = I_C R_E + 0.7V$  (ii)  
 insert (ii) into (i) gives:  $V_{CC} = I_C R_L + [I_C R_E + 0.7V] / R_2 (R_1 + R_2 + R_L)$   
 and solve for  $I_C$ :  $I_C = \frac{V_{CC} R_2 - 0.7V (R_1 + R_2 + R_L)}{R_2 R_L + R_E (R_1 + R_2 + R_L)} \approx \text{constant}$

## EEE331 Analogue Electronics

### common emitter (CE) BJT: coupling

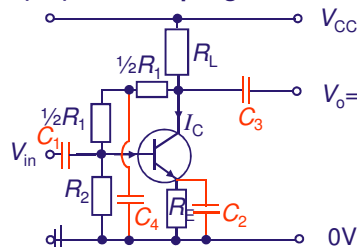

note on  $C_2$  and  $C_4$ :  
 shorten small a.c. signals to ground and so remove negative feedback by  $R_1$  and  $R_E$  on circuit gain

aim: getting mid-frequency signals in and out

use: capacitors for **coupling** (signal transfer) and **decoupling** (removal)

roles:  $C_1$  couples signal from source to BJT base without allowing source to affect bias (or vice versa)


$C_2$  decouples emitter BJNode (shortens emitter node to ground as far as small signals re concerned, prevents  $R_E$  has same stabilisation effect on the signal as on DC bias conditions)

$C_3$  couples signal from output at collector node to the load

$C_4$  decouples mid-point of  $R_1$

## EEE331 Analogue Electronics
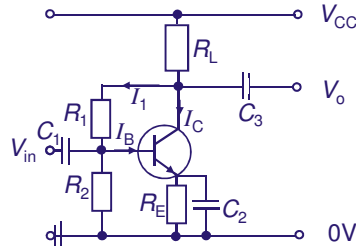
### common emitter (CE) BJT: voltage gain with bias




- aim: draw small signal circuit by replacing
- all d.c. voltage sources by short circuits ( $0\Omega$ )
  - all d.c. current source by open circuits ( $\infty$  resistance)
  - all capacitors by short circuits
  - $V_{CC}$  by direct connection to ground from signal's point of view

## EEE331 Analogue Electronics
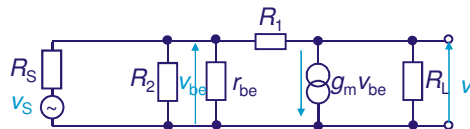
### common emitter (CE) BJT: voltage gain with bias

$$\text{sum currents at output node: } v_o/R_L + (v_o - v_{be})/R_1 + g_m v_{be} = 0 \quad (i)$$

$$\text{sum currents at input node: } (v_s - v_{be})/R_S + (v_o - v_{be})/R_1 - v_{be}/R_2 - v_{be}/r_{be} = 0 \quad (ii)$$




- aim: draw small signal circuit by replacing
- all d.c. voltage sources by short circuits ( $0\Omega$ )
  - all d.c. current source by open circuits ( $\infty$  resistance)
  - all capacitors by short circuits ( $C_4$  ignored here)
  - $V_{CC}$  by direct connection to ground from signal's point of view

## EEE331 Analogue Electronics
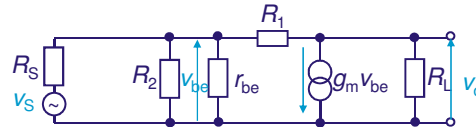
### common emitter (CE) BJT: voltage gain with bias

$$\text{sum currents at output node: } v_o/R_L + (v_o - v_{be})/R_1 + g_m v_{be} = 0 \quad (i)$$

$$\text{sum currents at input node: } (v_s - v_{be})/R_S + (v_o - v_{be})/R_1 - v_{be}/R_2 - v_{be}/r_{be} = 0 \quad (ii)$$



solve (i) and (ii) for  $v_{be}$ , then equate to eliminate  $v_{be}$ :

$$\begin{aligned} -v_o/[g_m(R_1 \parallel R_L)] &\approx -v_o(R_1 + R_L)/(g_m R_1 R_L - R_L) = v_{be} \\ &= (v_s/R_S + v_o/R_1)(R_1 \parallel R_2 \parallel R_S \parallel r_{be}) \\ &= v_s(R_1 \parallel R_2 \parallel R_S \parallel r_{be})/R_S + v_o(R_1 \parallel R_2 \parallel R_S \parallel r_{be})/R_1 \end{aligned}$$

gives voltage gain

$$G = v_o/v_s = -R_1/R_S \{1 + R_1/[(g_m R_1 \parallel R_L)(R_1 \parallel R_2 \parallel R_S \parallel r_{be})]\}^{-1}$$


$$\approx -R_1/R_S \cdot 1/(1 + g_m R_1) \text{ mostly independent from BJT for } R_1 \ll R_2, R_S, r_{be}$$

$$\lim_{R_1 \rightarrow \infty} G = -R_1/R_S \{1 + R_1/[(g_m R_1)(R_2 \parallel R_S \parallel r_{be})]\}^{-1}$$

$$\approx -g_m R_L (R_2 \parallel r_{be})/(R_S + R_2 \parallel r_{be}) \text{ independent of } R_1 \text{ (no feedback)}$$

## EEE331 Analogue Electronics
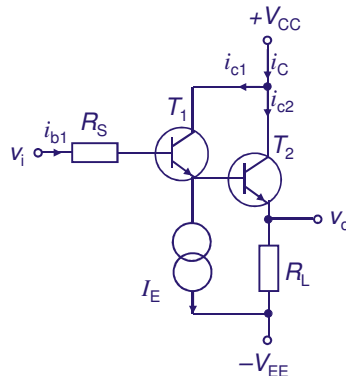
### 2 transistor circuit elements: The Darlington pair



- definition: two transistors  $T_1$  and  $T_2$  in CC mode with **collectors connected**
- current source (or resistor) establishes DC bias current  $I_E$  for  $T_1$  to ensure  $\beta_1$  is large enough (not needed for s.s. circuit)
- for the composite transistor element:

$$i_C = i_{C1} + i_{C2}$$

$$i_{C1} = \beta_1 i_{B1}$$

$$i_{C2} = \beta_2 i_{B2}$$

$$i_{B2} = i_{B1} + i_{C1} = (\beta_1 + 1) i_{B1}$$

$$\rightarrow i_{C2} = \beta_2 (\beta_1 + 1) i_{B1}$$

$$\rightarrow \text{current gain: } \beta_{101} = i_C/i_{B1} = \beta_2 (\beta_1 + 1) + \beta_1 \approx \beta_1 \beta_2$$

symmetrical in  $i=1,2$


voltage gain:

$$v_o/v_i = \frac{R_L}{R_L + r_{be2} + [r_{be1} + R_S/(\beta_1 + 1)]/(\beta_2 + 1)}$$

is  $\approx 1$  for large  $R_L$  and  $\beta_1, \beta_2 \gg 1$

## EEE331 Analogue Electronics
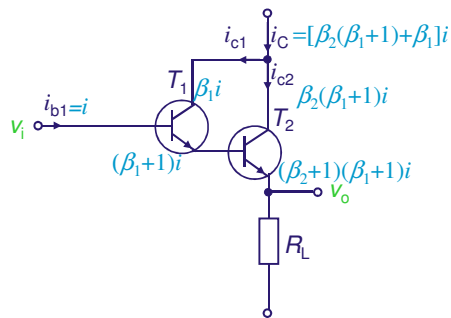
### 2 transistor circuit elements: The Darlington pair



- work out small signal **currents** and **voltages** to determine the input resistance
- at output:  


$$V_o = R_L (\beta_2 + 1)(\beta_1 + 1)i$$
 and also:  

$$V_o = V_i - (\beta_1 + 1)i r_{be1} - (\beta_2 + 1)(\beta_1 + 1)i r_{be2}$$
- equate and get  

$$r_i = V_i / i \dots$$

## EEE331 Analogue Electronics
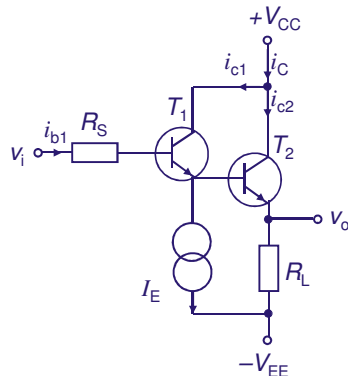
### 2 transistor circuit elements: The Darlington pair



- definition: two transistors  $T_1$  and  $T_2$  in CC mode with **collectors connected**
- input resistance:  

$$r_i = (\beta_1 + 1)[r_{be1} + (\beta_2 + 1)(r_{be2} + R_L)]$$


$$\approx (\beta_1 + 1)(\beta_2 + 1)(r_{be2} + R_L) \text{ is large}$$
- output resistance:  

$$r_o = R_L \parallel \{r_{be2} + [r_{be1} + R_S / (\beta_1 + 1)] / (\beta_2 + 1)\}$$

$$\approx r_{be2} \text{ is small}$$
- Both, input resistance and current gain are improved (enlarged)** compared to single transistor, which is very useful for BJTs (but not for MOSFETs for which both quantities are infinite anyway.)

## EEE331 Analogue Electronics

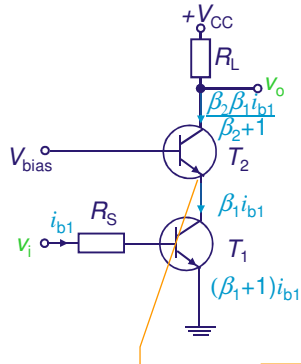
### 2 transistor circuit elements: The Cascode pair



- definition: two transistors with  $T_1$  in CE mode driving  $T_2$  in CB mode so that **emitter** of  $T_2$  connected to **collector** of  $T_1$
- consider output current:  
 $i_o = i_{C2} = \beta_2 \beta_1 i_{b1} / (\beta_2 + 1) \approx \beta_1 i_{b1}$ , hence current gain:  
 $i_o / i_{b1} = \beta_2 \beta_1 / (\beta_2 + 1) \approx \beta_1$  is rather small
- consider output voltage:  
 $v_o = -i_o R_L = -\beta_2 \beta_1 i_{b1} R_L / (\beta_2 + 1)$   
consider input voltage:  
 $v_i = [R_S + (\beta_1 + 1)r_{be1}] i_{b1}$ , hence voltage gain:  
 $v_o / v_i = -\beta_2 \beta_1 R_L / \{ [R_S + (\beta_1 + 1)r_{be1}] [\beta_2 + 1] \}$   
 $\approx -\beta_1 R_L / (R_S + \beta_1 r_{be1})$  can be high
- CE stage of  $T_1$  sees only load of  $r_{be2} \ll R_L$** , hence gain ( $=g_m R_L$ ) and associated Miller effect are much smaller for cascode compared to normal CE circuit: good high-f amplification!
- use also as level shifter in MOSFETs

## EEE331 Analogue Electronics

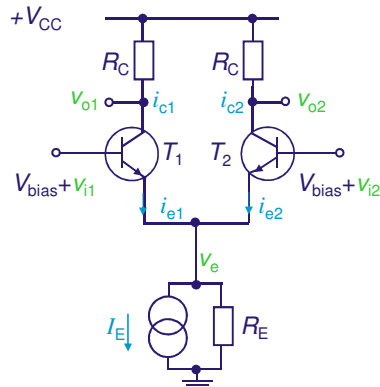
### 2 transistor circuit elements: The differential pair (emitter coupled pair)



- definition: **two transistors with joined emitters** and biased by constant current source
- operation principle:  
consider  $v_{i1} = v_{i2} + \Delta v$ , this increases  $i_{e1}$  by some  $\Delta i$ , hence, as  $i_{e1} + i_{e2} = I_E = \text{const.}$ :  $i_{e2}$  must decrease by same  $\Delta i$ , thus output for  $i_c \approx i_e$ :  
$$v_o^{\text{diff}} = v_{o1} - v_{o2} = [V_{CC} - (i_c + \Delta i)R_C] - [V_{CC} - (i_c - \Delta i)R_C] = -2\Delta i R_C$$
 is proportional to **current difference** through  $T_1$  and  $T_2$
- problem: for BJTs this is usually not proportional to **voltage difference**

## EEE331 Analogue Electronics

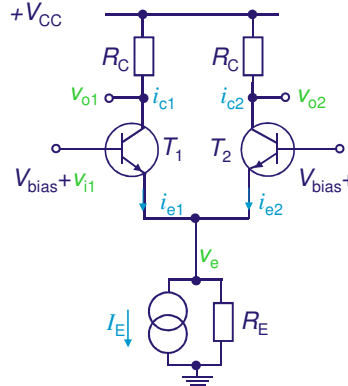
### 2 transistor circuit elements: The differential pair (emitter coupled pair)



- assume  $R_E, r_{ce} \rightarrow \infty, r_b = 0$
- use Ebers-Moll equations for  $i_c(v_{be})$ :  
 $i_c = i_s \exp(v_{be}/V_{to})$   
 with turn-on voltage of  $V_{to} \approx 0.7\text{eV}$  for a Si BJT and some characteristic current  $i_s$ , hence  
 $i_{c1}/i_{c2} = \exp(v_{i1} - v_{i2})/V_{to} = \exp(v_i^{\text{diff}}/V_{to})$
- also  $v_{i1} - v_{be1} + v_{be2} - v_{i2} = 0$   
 and  $i_{e1} + i_{e2} = I_E = (i_{c1} + i_{c2})/\alpha$   
 where  $\alpha = i_c/i_e = \beta/(\beta+1)$ , hence:  
 $i_{c1}/I_E = \alpha i_{c1}/(i_{c1} + i_{c2})$   
 $= \alpha / (1 + i_{c2}/i_{c1})$   
 $= \alpha / [1 + \exp(-v_i^{\text{diff}}/V_{to})]$   
 and  
 $i_{c2}/I_E = \alpha / [1 + \exp(+v_i^{\text{diff}}/V_{to})]$


## EEE331 Analogue Electronics
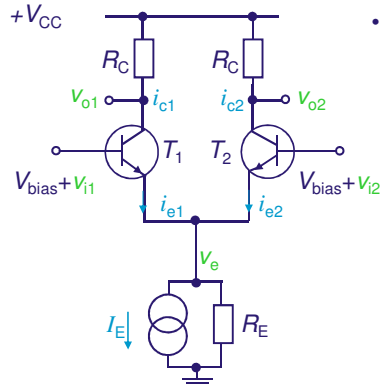
### 2 transistor circuit elements: The differential pair (emitter coupled pair)



$$\begin{aligned}
 v_o^{\text{diff}} &= v_{o1} - v_{o2} \\
 &= -2 \frac{1}{2} (i_{c1} - i_{c2}) R_C \\
 &= (i_{c2} - i_{c1}) R_C \\
 &= \alpha I_E R_C \left\{ \frac{1}{1 + \exp(+v_i^{\text{diff}}/V_{to})} - \frac{1}{1 + \exp(-v_i^{\text{diff}}/V_{to})} \right\} \\
 &= \alpha I_E R_C \tanh(-v_i^{\text{diff}}/2V_{to})
 \end{aligned}$$

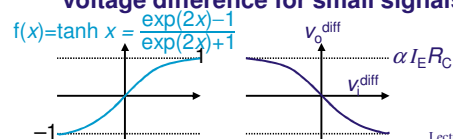
where  $\tanh x$  is a function that is symmetrical about the origin and converges to unity for  $x \rightarrow \infty$ , i.e. we have a **linear relationship between output voltage difference and input voltage difference for small signals!**





## EEE331 Analogue Electronics
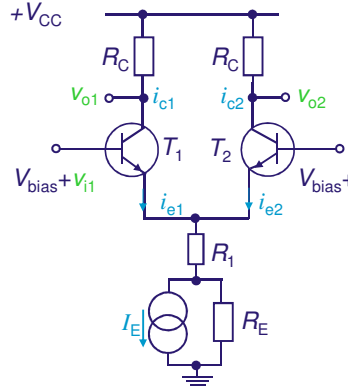
### 2 transistor circuit elements: The differential pair (emitter coupled pair)



- **note on emitter degeneration:** add  $R_1$  to the joint emitters provides negative feedback: if  $i_c$  rises,  $i_e$  increases, thus also the voltage drop across  $R_1$ , which reduces the bias and thus drives  $i_b$  and  $i_c$  back.
- in detail: look at Ebers-Moll equation:  

$$v_{be} = V_{to} \ln(i_c/i_s)$$
 If one must provide higher base voltages to  $T_1$  and  $T_2$  to get the same  $i_c$  with  $R_1$  present, then this also means the non-linear  $i_c(v_{be})$  regime begins only at higher voltage; i.e.  $R_1$  effectively extends the linear region!

## EEE331 Analogue Electronics

### 2 transistor circuit elements: The differential pair (emitter coupled pair)

#### calculation of differential mode gain $A_{dm}$ :

- consider  
 $v_{o1} \rightarrow v_{o1} + \Delta v$ ,  $i_{c1} \rightarrow i_{c1} + \Delta i$ , hence also  
 $v_{o2} \rightarrow v_{o2} - \Delta v$ ,  $i_{c2} \rightarrow i_{c2} - \Delta i$
- As total current  $I_E$  into current source and resistor  $R_E$  stays constant, no changes occur below the emitters of  $T_1$  and  $T_2$  and we can replace this part with a short circuit and only need to consider  $T_1$  (no need to worry about  $T_2$  since  $T_1$ 's emitter is tied to ground from small signal point of view). Thus get the differential mode half-circuit:



$$v_{o1} = -g_m v_{be} R_C = -g_m v_{11} R_C$$


with  $v_{11} = -v_{12} = v_{11}^{diff}/2$  and  $v_{o1} = -v_{o2} = v_o^{diff}/2$ ,  
 hence  $A_{dm} = v_o^{diff}/v_{11}^{diff} = 2v_{o1}/2v_{11} = -g_m R_C$

## EEE331 Analogue Electronics

### 2 transistor circuit elements: The differential pair (emitter coupled pair)
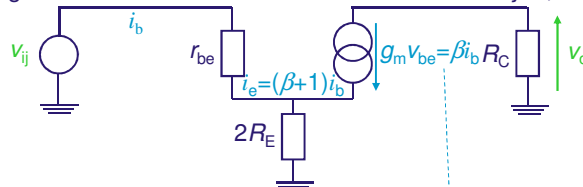
#### calculation of common mode gain $A_{cm}$ :

- replace single  $R_E$  with two parallel branches, each with resistance  $2R_E$
- As left and right halves of circuit are completely identical and the drives signals to both sides also, no large signal current will flow between emitters between  $T_1$  and  $T_2$ . As there is no interaction between both halves, we can split circuit down the middle and consider just one half. Thus get the common mode half-circuit for each side  $j=1,2$ :



Kirchhoff's Law:  $v_{ij} - i_b r_{be} - i_b (\beta + 1) 2R_E = 0$ , thus  $i_b = v_{ij} / [r_{be} + 2R_E (\beta + 1)]$

Also:  $v_{oj} = -\beta i_b R_C$

Put together:  $A_{cm} = v_{oj} / v_{ij} = -\beta R_C / [r_{be} + 2R_E (\beta + 1)] = \frac{-g_m R_C}{1 + 2g_m R_E (1 + 1/\beta)}$

## EEE331 Analogue Electronics

### 2 transistor circuit elements: The differential pair (emitter coupled pair)

#### common mode rejection ratio (CMRR):

- aim: for differential amplifier, maximise gain  $A_{dm}$  in differential mode (= gain for opposite voltage signals) and simultaneously, minimise gain  $A_{cm}$  for identical input voltages applied to both inputs
- use as a quality factor the common mode rejection ratio (CMRR)

defined as the dimensionless ratio

$$CMRR = |A_{dm} / A_{cm}| = 1 + 2g_m R_E (\beta + 1) / \beta$$

- CMRR increases with  $g_m$ , and as  $g_m v_{be} = \beta i_b$  it is best to use BJTs with large  $\beta$  and operate them at high current.
- at high frequencies:  $Z = 1 / (j\omega C_{cb}) \parallel R_C$  decreases  $R_C^{eff}$  for small signals, which thus reduces  $A_{dm}$  (not  $A_{cm}$ !) and thereby CMRR.
- notes on differential amplifiers using FETs:
  - ~ JFETs are better than MOSFETs for this as they have lower noise.
  - Differential gain of FETs is lower than for differential amps based on BJTs, due to smaller  $g_m$ .
  - + FETs give much wider linear operation than BJTs as current varies only like the square rather than exponentially with voltage.