

EEE331 Analogue Electronics


8th lecture:

- operational amplifiers (Op-Amps), part II
 - frequency behaviour of 2-stage MOS Op-Amps
 - multi-stage Op-Amps
 - feedback theory

EEE331 Analogue Electronics

2-stage MOS operational amplifier: frequency behaviour, I

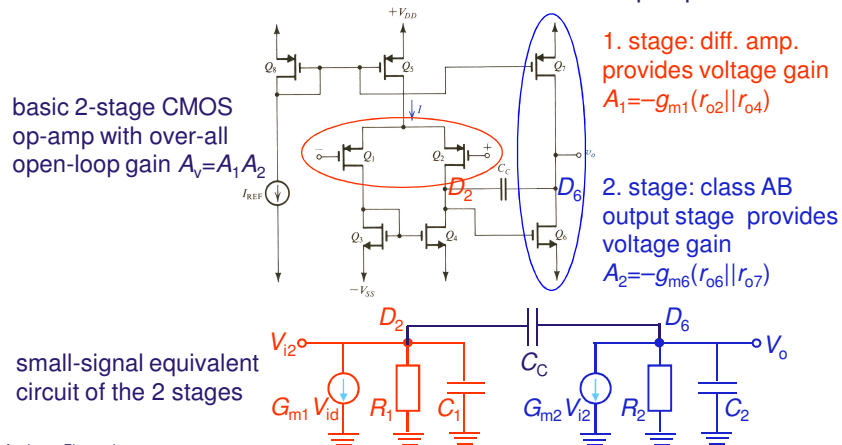Calculation of the frequency behaviour, in particular ω_{p1} , ω_{p2} , ω_1 and ω_2




EEE331 Analogue Electronics

2-stage MOS operational amplifier: frequency behaviour, II

Calculation of the frequency behaviour, in particular ω_{p1} , ω_{p2} , ω_1 and ω_2

1. stage: transconductance: $G_{m1}=g_{m1}=g_{m2}$
 output resistance: $R_1=r_{o2}||r_{o4}$
 capacitance: $C_1=C_{DG2}+C_{DB2}+C_{DG4}+C_{DB4}+C_{GS6}$
 This is the total capacitance at the interface between the two stages.
2. stage: transconductance: $G_{m2}=g_{m6}$
 output resistance: $R_2=r_{o6}||r_{o7}$
 capacitance: $C_2=C_{DG6}+C_{DB6}+C_{DG7}+C_{DB7}+C_L$
 This is the total capacitance at the output node of the Op Amp and usually dominated by the load capacitance C_L , while $C_{DG6} \ll C_C$.

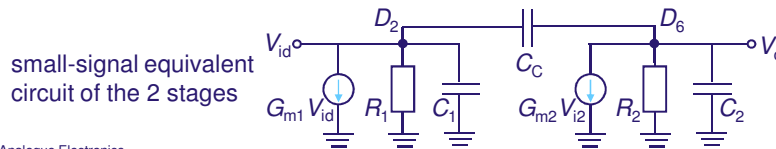

EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

2-stage MOS operational amplifier: frequency behaviour, III

Calculation of the frequency behaviour, in particular ω_{p1} , ω_{p2} , ω_1 and ω_2

equation for currents at node D_2 : $G_{m1} V_{id} + V_{i2}/R_1 + sC_1 V_{i2} + sC_C (V_{i2} - V_o) = 0$

equation for currents at node D_6 : $G_{m2} V_{i2} + V_o/R_2 + sC_2 V_o + sC_C (V_o - V_{i2}) = 0$

solve 2nd equation for V_{i2} : $V_{i2} = V_o (1/R_2 + sC_2 + sC_C) / (sC_C - G_{m2})$

insert V_{i2} into 1st equation to get: $V_{id}/V_o = \{sC_C/G_{m1} - [(1/R_2 + sC_2 + sC_C) \times (1/R_1 + sC_1 + sC_C)] / [(sC_C - G_{m2}) G_{m1}]\}$

then re-arrange to get voltage gain and sort according to powers of s :

$$V_o/V_{id} = [G_{m1}(G_{m2} - sC_C)R_1R_2] / \{1 + s[C_1R_1 + C_2R_2 + C_C(R_1 + R_2 + G_{m2}R_1R_2)] + s^2 R_1R_2 [C_1C_2 + C_C(C_1 + C_2)]\}$$

is a transfer function with $A_{DC} = \lim_{s \rightarrow 0} V_o/V_{id} = (G_{m1}R_1)(G_{m2}R_2)$, as expected,

one transmission zero (zero of the nominator) for $\omega_z = s_z = G_{m2}/C_C$,

two poles ω_{p1} and ω_{p2} (roots of denominator) that we get from writing it as

$$D(s) = (1 + s/\omega_{p1})(1 + s/\omega_{p2}) = 1 + s(1/\omega_{p1} + 1/\omega_{p2}) + s^2/(\omega_{p1}\omega_{p2}) \approx 1 + s/\omega_{p1} + s^2/(\omega_{p1}\omega_{p2})$$

dominant pole: $\omega_{p1} = \{R_1[C_1 + C_C(1 + G_{m2}R_2)] + R_2(C_2 + C_C)\}^{-1} \approx 1/(R_1C_CG_{m2}R_2)$

note Miller enlargement of $C_C \gg C_1$ in neg. feedback of 2nd stage whose gain is $G_{m2}R_2$


and second pole: $\omega_{p2} = (G_{m2}C_C)/[C_1C_2 + C_C(C_1 + C_2)] \approx G_{m2}/(C_1 + C_2)$

EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

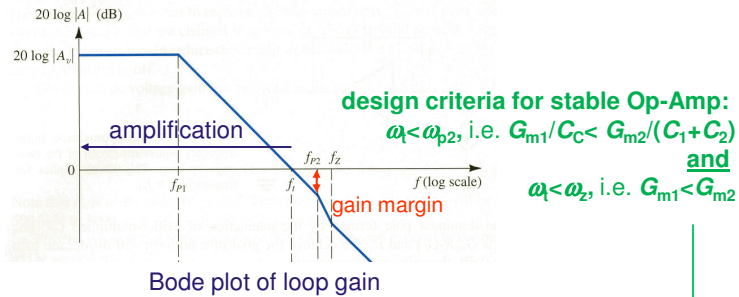
2-stage MOS operational amplifier: frequency behaviour, IV



one transmission zero (zero of the nominator) for $\omega_z = s_z = G_{m2}/C_C$,
 two poles ω_{p1} and ω_{p2} (roots of denominator) that we get from writing it as
 $D(s) = (1 + s/\omega_{p1})(1 + s/\omega_{p2}) = 1 + s(1/\omega_{p1} + 1/\omega_{p2}) + s^2/(\omega_{p1}\omega_{p2}) \approx 1 + s/\omega_{p1} + s^2/(\omega_{p1}\omega_{p2})$
 dominant pole: $\omega_{p1} = \{R_1[C_1 + C_C(1 + G_{m2}R_2)] + R_2(C_2 + C_C)\}^{-1} \approx 1/(R_1C_CG_{m2}R_2)$
 uniform gain roll-off down to 0dB if C_C is selected so that $\omega_1 = \omega_{p1} \lim_{s \rightarrow 0} V_o/V_{id} \approx G_{m1}/C_C < \omega_{p2}, \omega_z$
 and second pole: $\omega_{p2} = (G_{m2}C_C)/[C_1C_2 + C_C(C_1 + C_2)] \approx G_{m2}/(C_1 + C_2)$

EEE331 Analogue Electronics

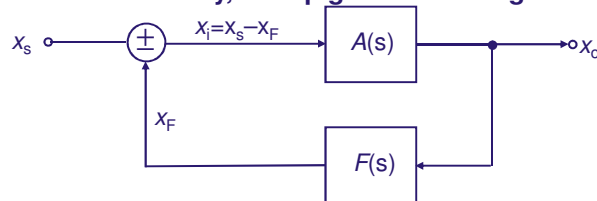formal feedback theory, I: loop gain and total gain



Consider a **non-inverting amplifier** where x_s can be either a voltage or a current signal to be amplified. $A(s)$ denotes the -frequency dependent- amplification factor and $F(s)$ the feedback. Then we have:


$$\left. \begin{aligned} x_i &= x_s - x_f \\ x_o &= A(s) x_i \\ x_f &= F(s) x_o \end{aligned} \right\} \begin{aligned} x_o &= A(s) [x_s - F(s) x_o] \\ \text{hence gain: } G(s) &= x_o/x_s = A(s) / [1 \pm A(s)F(s)] \end{aligned}$$

loop gain

for large loop gain $A(s)F(s) \gg 1$: $G \approx A/(AF) = 1/F(s)$ depends on feedback, rather than on the actual amplifier. This is a useful concept for all systems with finite input and zero output resistance (i.e. no load effects).

EEE331 Analogue Electronics

formal feedback theory, II

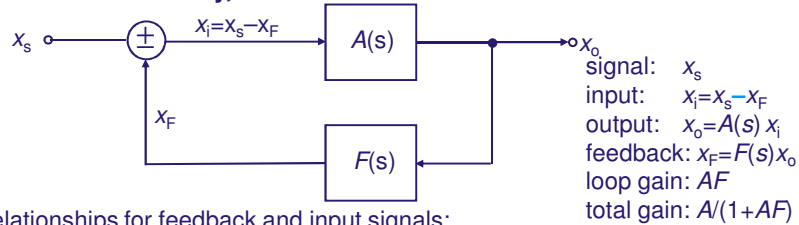

Relationships for feedback and input signals:


$$x_F = F(s)A(s)(x_s - x_F) \rightarrow x_F = AF/(1+AF) x_s$$

$$x_i = x_s - F(s)A(s) x_i \rightarrow x_i = 1/(1+AF) x_s$$

is reduced in the amplifier with negative feedback (to almost zero for large negative feedback)

EEE331 Analogue Electronics

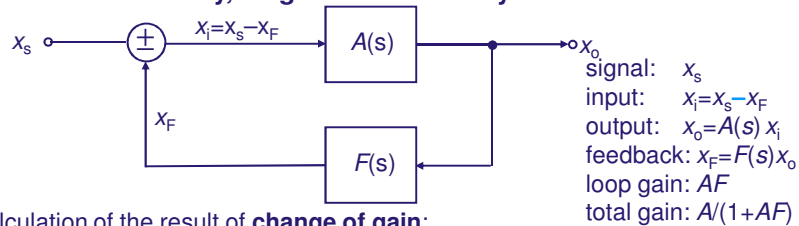formal feedback theory, III: gain de-sensitivity factor



calculation of the result of **change of gain**:

$$G = A/(1+AF)$$

$$\rightarrow dG/dA = [1+AF - A(F+AdF/dA)] / (1+AF)^2 = 1/(1+AF)^2$$

=0 for constant F


$$\rightarrow 1/G dG/dA = 1/(1+AF)^2 (1+AF)/A = 1/(1+AF) 1/A$$

$$\rightarrow dG/G = [1/(1+AF)] dA/A$$

The percentage change in total gain G due to variations in some circuit parameter is thus smaller than the percentage change in A by a factor of $(1+AF)$. This is known as the **de-sensitivity factor**.

EEE331 Analogue Electronics

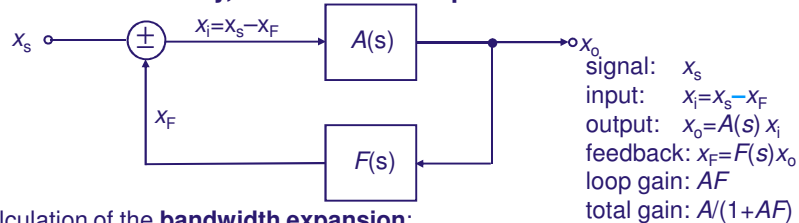formal feedback theory, IV: bandwidth expansion



calculation of the **bandwidth expansion**:

Consider an amplifier whose high-frequency response is characterised by a single pole and whose mid-band gain is A_m . Then the high-frequency gain is $A(s) = A_m / (1 + s/\omega_H)$ where ω_H denotes the upper 3dB-frequency.

With negative feedback, with a frequency-independent factor F , this becomes $G(s) = A(s) / [1 + FA(s)]$

$$= A_m / \{ [1 + s/\omega_H] [1 + FA_m / (1 + s/\omega_H)] \}$$

$$= A_m / [1 + s/\omega_H + FA_m]$$

$$= A_m / (1 + FA_m) \times 1 / \{ 1 + s / [\omega_H (1 + FA_m)] \}$$

gain \times bandwidth = constant


reduced mid-band gain increased upper 3-dB frequency $\omega_{Hf} = \omega_H (1 + FA_m)$

EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

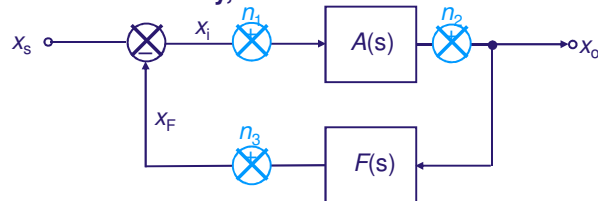formal feedback theory, V: influence of disturbances



consider influence of disturbances due to **additive noise**:

The **effect will depend on where in the circuit the noise is added**:

output due to n_1 : $x_o = A(x_s - x_F + n_1) = A(x_s - Fx_o + n_1) = A/(1+AF) x_s + A/(1+AF) n_1$

output due to n_2 : $x_o = A(x_s - x_F) + n_2 = A(x_s - Fx_o) + n_2 = A/(1+AF) x_s + 1/(1+AF) n_2$

output due to n_3 : $x_o = A(x_s - x_F) = A(x_s - Fx_o - n_3) = \underbrace{A/(1+AF) x_s}_{\text{signal}} - \underbrace{A/(1+AF) n_3}_{\text{noise}}$


Disturbance at the input and in the feedback loop are amplified by the same amount as the signal, **disturbances at the output end are suppressed**.

EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

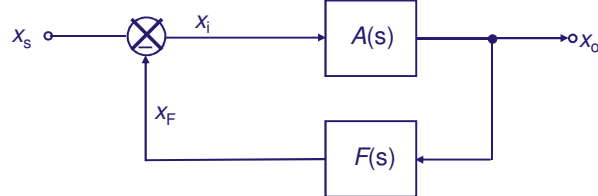formal feedback theory, VI: stability vs. oscillation



The closed-loop transfer function $G(s) = A(s)/[1 + A(s)F(s)]$ is a complex function for physical frequencies $s = j\omega$. $G(j\omega) = A(j\omega)/[1 + A(j\omega)F(j\omega)]$, and so is the loop gain $A(j\omega)F(j\omega) = |A(j\omega)F(j\omega)| \exp j\phi(\omega)$

If the loop gain $|AF| \geq 1$ for any frequency where the phase shift around the loop (i.e. between x_i and x_s) is 0° or 360° , then the system will become unstable.


The **inverting summer** which subtracts x_F from x_s at the input (i.e. negative feedback) **already introduces a 180° phase shift** between these signals.

Another 180° phase shift will make the feedback positive, and the circuit will start to oscillate. Hence, the **phase lag for stable amplification must be**

$0 < |\phi(\omega)| < 180^\circ$ for all frequencies with $|A(\omega)F(\omega)| \geq 1$, i.e. magnitude ≥ 0 dB.

EEE331 Analogue Electronics

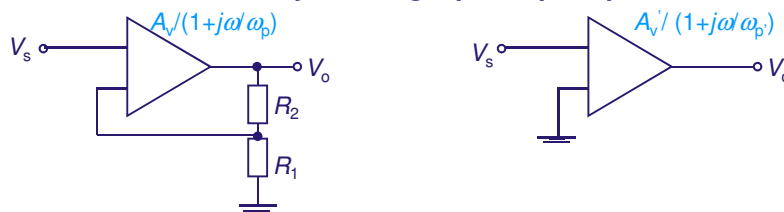formal feedback theory, VII: single-pole Op-Amps




voltage gain:

$$\begin{aligned}
 G = V_o/V_s &= \frac{A_v'/(1+j\omega\omega_p)}{1 + [A_v'/(1+j\omega\omega_p)] R_1/(R_1+R_2)} \equiv A_v'/(1+j\omega\omega_p) \quad \text{where} \\
 &= A_v'/[1+j\omega\omega_p + A_v'R_1/(R_1+R_2)] \\
 &= A_v'/[1 + A_v'R_1/(R_1+R_2) + j\omega\omega_p] \\
 &= \frac{A_v'/(1 + A_v'R_1/(R_1+R_2))}{1 + j\omega\omega_p \{1 + A_v'R_1/(R_1+R_2)\}} \\
 &= \{A/(1+AF)\} / \{1 + j\omega[\omega_p(1+AF)]\} \\
 &= A / \{(1+AF)(1 + j\omega[\omega_p(1+AF)])\}
 \end{aligned}$$

$A_v' = A_v/[1 + A_vR_1/(R_1+R_2)] \approx (R_1+R_2)/R_1$
 for $A_vR_1/(R_1+R_2) \gg 1$
 and
 $\omega_p' = \omega_p[1 + A_vR_1/(R_1+R_2)]$
 Note again $A_v'\omega_p = A_v\omega_p = \text{constant}$


EEE331 Analogue Electronics

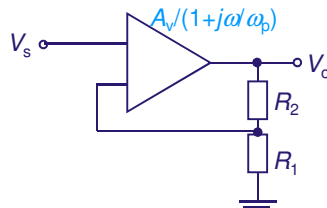formal feedback theory, VII: single-pole Op-Amps



voltage gain:
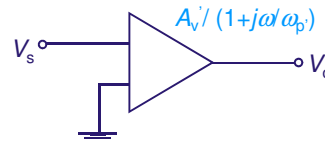
$$\begin{aligned} G = V_o/V_s &= \frac{A_v/(1+j\omega\omega_p)}{1+[A_v/(1+j\omega\omega_p)] R_1/(R_1+R_2)} \\ &= A_v/[1+j\omega\omega_p + A_v R_1/(R_1+R_2)] \\ &= A_v/[1+A_v R_1/(R_1+R_2) + j\omega\omega_p] \\ &= \frac{A_v/[1+A_v R_1/(R_1+R_2)]}{1+j\omega\omega_p [1+A_v R_1/(R_1+R_2)]} \\ &= \{A/(1+AF)\}/\{1+j\omega[\omega_p(1+AF)]\} \\ &= A/\{(1+AF)(1+j\omega[\omega_p(1+AF)])\} \end{aligned}$$



advantages:


- yields max. phase shift of 90°, i.e. single-pole Op-Amps with resistive feedback cannot oscillate and are always stable!
- hence easy to use

disadvantages:


- low unity gain bandwidth (few MHz)
- poor slewing rates

EEE331 Analogue Electronics

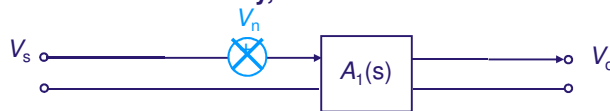formal feedback theory, VIII: noise reduction in 2-stage Op-Amps



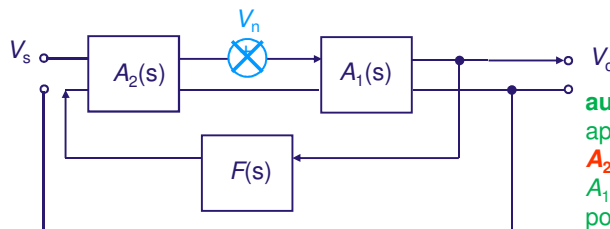signal-to-noise ratio of amplifier with input noise but without feedback: $S/N = V_s/V_n$




audio amplifier as an application example:
 A_2 =noise-free pre-amp.
 A_1 = power amp. with power-supply hum

signal-to-noise ratio of 2-stage amplifier with feedback where another noise-free stage precedes the noisy stage:

$$V_o = V_s A_1 A_2 / (1 + A_1 A_2 F) + V_n A_1 / (1 + A_1 A_2 F) \rightarrow S/N = V_s A_2 / V_n \text{ is } A_2\text{-times larger}$$

EEE331 Analogue Electronics

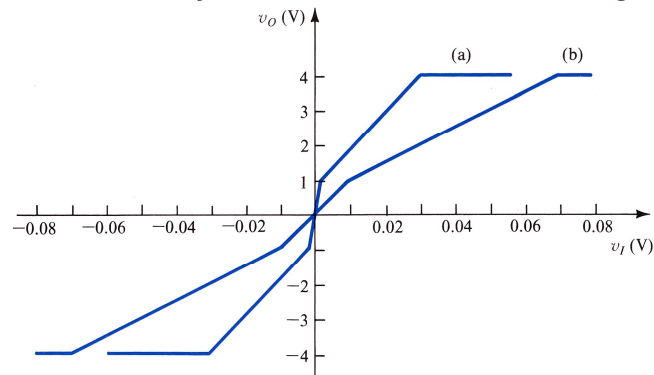formal feedback theory, IX: distortion reduction in 2-stage Op-Amps





(a): class B amplifier with large cross-over distortion where the voltage gain A_v is piecewise linear but changes from 1000 to 100 and then 0.
 (b): the gain is reduced to $G=A/(1+AF)$ by negative feedback with $F=0.01$:
 $A_{v1}=1000/(1+1000 \times 0.01)=90.9$, $A_{v2}=100/(1+100 \times 0.01)=50$ is much better

EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

multi-stage Op-amps: feedback theory

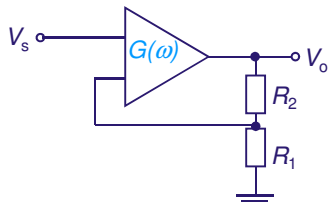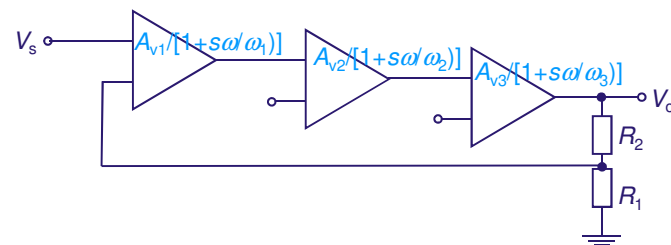

gain: $G(\omega)=A_v/[(1+s/\omega_1)(1+s/\omega_2)(1+s/\omega_3)]$
 where $A_v=A_{v1} A_{v2} A_{v3}$
 if ω_1 , ω_2 and ω_3 are all well separated


note: - most Op-Amps have 2 or 3 poles
 - extra poles can be introduced by feedback loops

EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

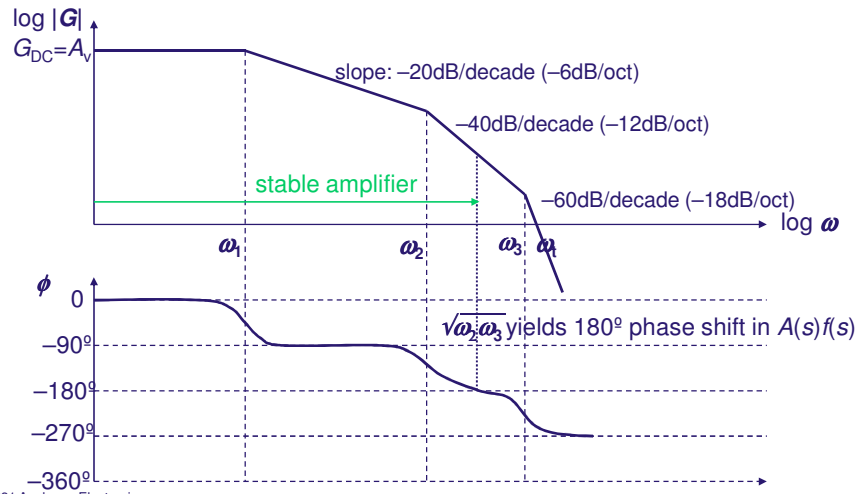multi-stage Op-amps: Bode plot of a bad 3-stage Op-Amp. design




EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

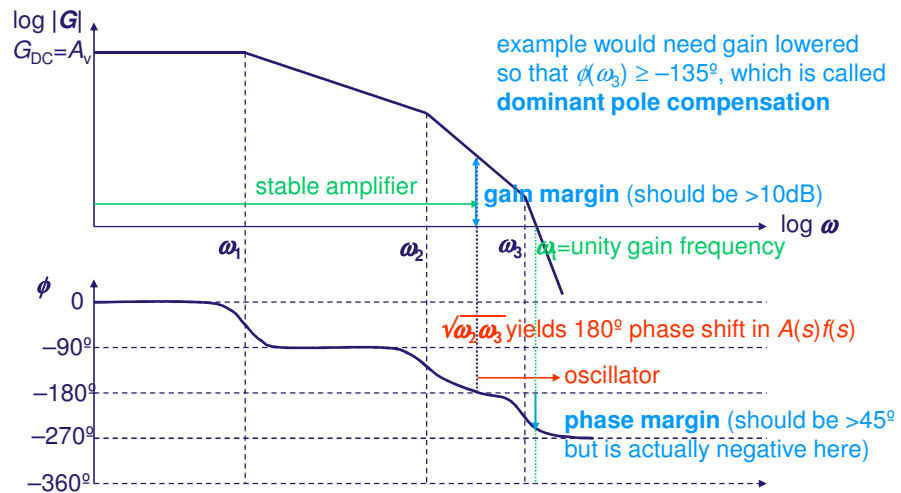multi-stage Op-amps: Bode plot of a bad 3-stage Op-Amp. design




EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

multi-stage Op-Amps: the 741 Op-Amp

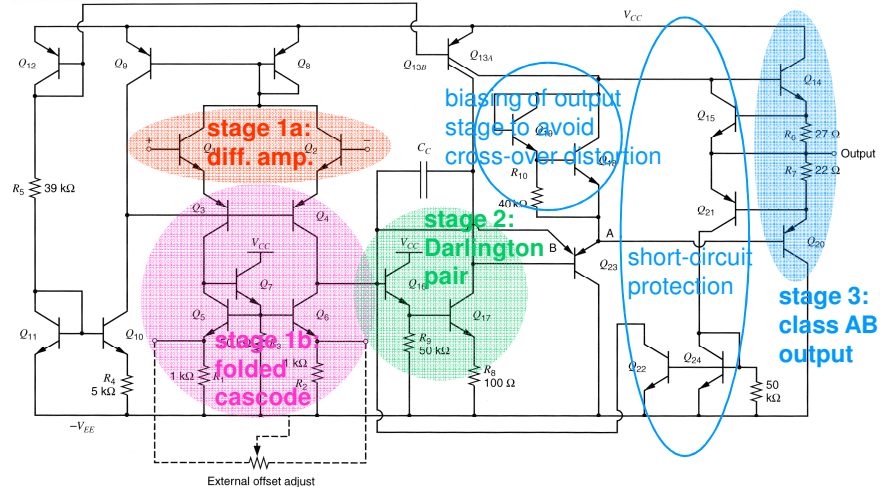


EEE331 Analogue Electronics

Lecture 8

EEE331 Analogue Electronics

multi-stage Op-Amps: the 741 Op-Amp

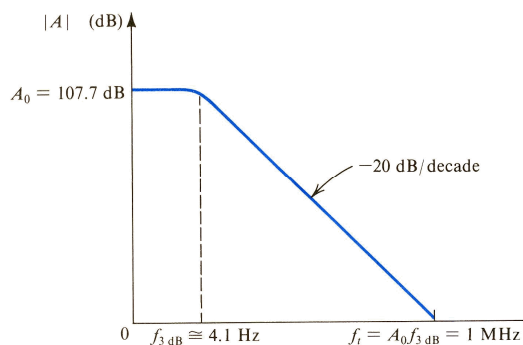

small-signal voltage gain:

$$G = v_o/v_i = (v_{i2}/v_i) (v_{o2}/v_{i2}) (v_o/v_{o2})$$

$$= -G_{m1} (R_{o1} || R_{i2}) \times (-G_{m2} R_{o2}) G_{v03} R_L / (R_L + R_{out})$$

$$= (-483) \times (-527) \times 0.964$$

$$= 2.44 \times 10^5 \text{ V/V} = \mathbf{107.7\text{dB}}$$

for $G_{m1} = 0.19 \text{ mA/V}$,
 $G_{m2} = 6.5 \text{ mA/V}$, $G_{v03} \approx 1$,
 $R_{o1} = 6.7 \text{ M}\Omega$, $R_{i2} = 4.1 \text{ M}\Omega$,
 $R_{o2} = 81 \text{ k}\Omega$, $R_{out} \approx 75 \Omega$, $R_L = 2 \text{ k}\Omega$

dominant pole frequency:

$$f_p = 1/(2\pi C_{in} R_i) = \mathbf{4.1\text{Hz}}$$

where $C_{in} = C_C(1 + G_{m2}) = 15.5 \text{ nF}$
and $R_i = (R_{o1} || R_{i2}) = 2.54 \text{ M}\Omega$

unit-gain bandwidth:

$$f_t = G f_p = \mathbf{1.0\text{MHz}}$$

EEE331 Analogue Electronics

Lecture 8