

EEE225: Analogue and Digital Electronics

Lecture VIII

James E. Green

Department of Electronic Engineering
University of Sheffield
j.e.green@sheffield.ac.uk

1 / 16

EEE225: Lecture 8

This Lecture

- 1 Non-Linear Effects
 - Slew Rate Limiting
 - Slew Rate Limiting: Square
 - Slew Rate Limiting: Sine
 - Slew Rate Limiting: Triangle
- 2 Opamps with Frequency Dependent Feedback
 - Integrator
 - Integrator: Frequency Domain
 - Integrator: Time Domain
 - Problems with Integrators
 - Differentiator
- 3 Review
- 4 Bear

2 / 16

EEE225: Lecture 8

Non-Linear Effects
Slew Rate Limiting


Slew Rate Limiting

- Slew rate limiting is *non-linear*, the ratio of v_o and v_i depends on the magnitude of v_i . It is a limit on the maximum rate of change of output voltage.
- It is particularly prevalent in problems where large signals and high frequencies are in use.
- It is often caused by the differential pair and VAS current source's inability to charge or discharge the compensation capacitor sufficiently quickly.
- Manufacturers specify in $V/\mu s$. (TL081 8 $V/\mu s$). Specific opamps can manage 5000 $V/\mu s$.
- Opamp manufacturers artificially increase the value of c_{cb} to obtain stability and a first order response. But increasing c_{cb} increases the current needed from the differential stage and VAS current source. It's a *compromise*, greater stability (esp. at lower closed loop gain) comes at the expense of lower slew rate.

3 / 16

EEE225: Lecture 8

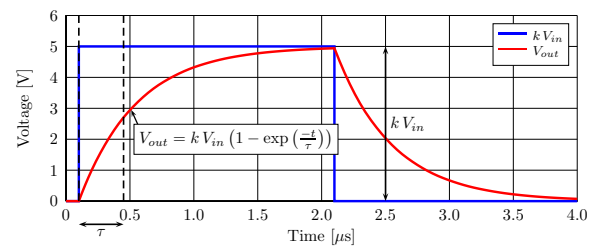Non-Linear Effects
Slew Rate Limiting: Square




The square input signal interacts with the (low pass) opamp as if the opamp was an RC network. The result is an exponential rise to maximum of the form $V_o = k V_{in} (1 - \exp t/\tau)$ where $t = 0$ is the rising edge of the square signal, k is the system gain and τ is the time-constant of the opamp. Max rate of change = $(k V_{in})/\tau$. If the initial rate of change was maintained the output waveform would cross the setpoint at τ .

4 / 16

EEE225: Lecture 8

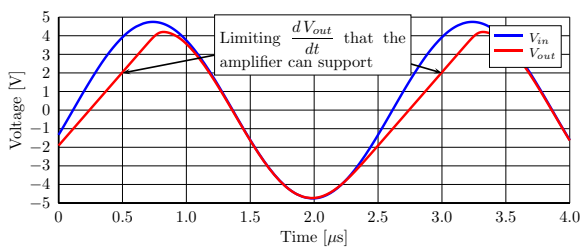Non-Linear Effects
Slew Rate Limiting: Sine



Max rate of change of a sinusoid,


$$V_{in} \sin(\omega t) = \frac{d(V_{in} \sin(\omega t))}{dt} \Big|_{\max} = V_{in} \omega \cos(\omega t) \Big|_{\max} \quad (1)$$

Max when $\cos(\omega t) = 1$. Max dV/dt for sinusoid is $V_{in} \omega$.

5 / 16

EEE225: Lecture 8

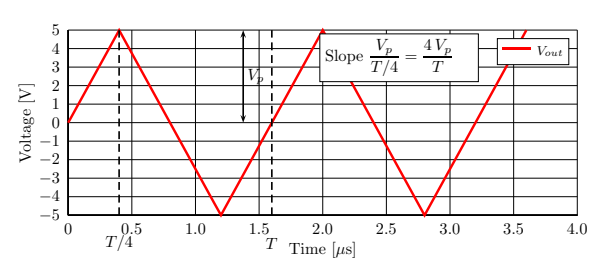Non-Linear Effects
Slew Rate Limiting: Triangle



For the triangle the rate of change of voltage is constant. In the graph above the amplifier must change its output voltage by V_p in a time, $T/4$ where T is the period. For example if $V_p = 5V$ and $T = 1.6 \mu s$ the slew rate must be $\geq \frac{4 \times 5}{1.6 \times 10^{-6}} V/s$ or $12.5 V/\mu s$

6 / 16


Opamps with Frequency Dependent Feedback

Part II of the second section of the course...

- Introduction of simple general opamp amplifier (Z_1 , Z_2 , not R_1 , R_2)
- An analogue integrator
 - Freq domain analysis
 - Time domain analysis
 - Problems with integrators
 - Analogue circuit to solve 1st order differential equation (printed notes)
- An analogue differentiator
 - Freq domain analysis
 - Time domain analysis
 - Problems with differentiators
- Pole-Zero Circuits.
 - Description of first order circuits (HP, LP, PZ)
 - Example with defined components
 - Example of intrinsic freq response type problem

7 / 16

Some Standard opamp circuits

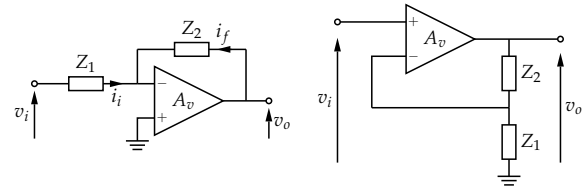

Inverting design gain...

$$\frac{v_o}{v_i} = -\frac{Z_2}{Z_1} \quad (2)$$


Non-inverting design gain...

$$\frac{v_o}{v_i} = \frac{Z_1 + Z_2}{Z_1} \quad (3)$$

Provided closed loop gain is not dependent on open loop gain (i.e. if $A_v \rightarrow \infty$). Z_n is an arbitrary impedance (could be R, L and C).

8 / 16

Opamp Integrator

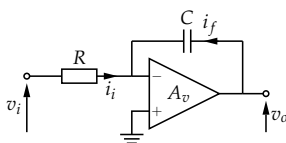

In the frequency domain.

$$\frac{v_o}{v_i} = -\frac{Z_2}{Z_1} \quad (4)$$


$$\frac{v_o}{v_i} = -\frac{\left(\frac{1}{j\omega C}\right)}{R} = -\frac{1}{j\omega C R} \quad (5)$$

- Integrators used in filters, instrumentation circuits and in control systems, but not often implemented using an opamp.

- Often $j\omega = s$ where 's' is the same as appears in the Laplace transform. So (5) becomes $1/(s C R)$.


- As ω approached 0 (i.e. DC) the gain $\rightarrow \infty$. This can not actually happen as the gain can not rise above A_v

9 / 16

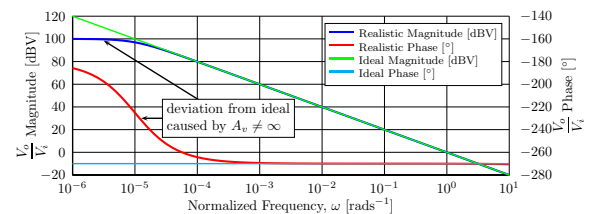

The finite A_v affects performance by moving the pole up from zero frequency to some finite frequency. The graph above is normalised i.e. $C R = 10^0$. The usable range of the integrator is about $10^{-3} \rightarrow 10^1$ Hz normalised but it depends on the value of A_v to some extent. Care should be taken to avoid phase errors as well as magnitude errors.

10 / 16

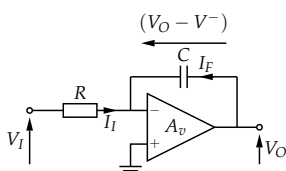

In the time domain (notice upper case letters)

$$I_I + I_F = \frac{V_I - V^-}{R} + \frac{C d(V_O - V^-)}{dt} = 0 \quad (6)$$

Assuming $V^- \approx 0$

$$\frac{V_I}{R C} = -\frac{dV_O}{dt} \quad (7)$$

integrating both sides,


$$V_O = -\frac{1}{R C} \int V_I dt + A \quad (8)$$

A is a constant proportional to the voltage across the capacitor prior to the start of the integration. Integrators have a major problem however, called "wind-up".

11 / 16

- There is no DC feedback between output and input.
- Any small voltage (offset of the opamp or offset of the signal source) is integrated over time.
- Eventually the integrator output will saturate against one of the power supply rails.

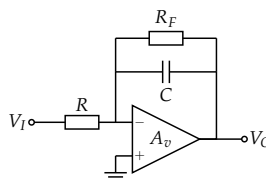
This can be avoided by providing DC feedback either as part of a larger system or more directly using a resistor.



The result of the DC pathway (R_F) is to change the gain of the circuit from $-A_0$ at DC to $-R_F/R$. This moves the pole up in frequency, decreasing the useful frequency range of the integrator.

12 / 16

Opamp Differentiator

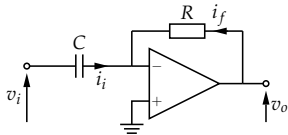

In the frequency domain.


$$\frac{v_o}{v_i} = -j\omega CR = -sCR \quad (9)$$

In the time domain,

$$V_O = CR \frac{dV_I}{dt} \quad (10)$$

- Key components interchanged. Same assumptions as for integrator. Same style of analysis.
- The capacitance and intrinsic frequency response of the opamp (A_V) interact with each-other forming (in the case of first order opamp assumptions) a second order circuit. This makes the differentiator unusable for a few decades of frequency around resonance.

13/ 16

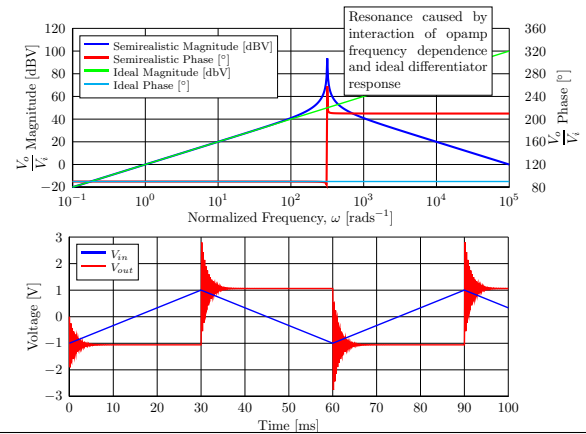

14/ 16

Review

- Discussed **slew rate limiting**, a non-linear effect which depends on signal magnitude. Examples for square, sine and triangle given.
- Introduced two opamp circuits for integration and differentiation of signals using resistors and capacitors as gain setting components.
- Considered some limitations and impracticalities of both circuits including the interaction between the intrinsic frequency response of the opamp and the frequency dependent feedback.

15/ 16



16/ 16