

QUESTION 1

11

(i) Star - Delta transformation:

$$Z_{AB} = Z_A + Z_B + \frac{Z_A Z_B}{Z_C}$$

$$Z_{BC} = Z_B + Z_C + \frac{Z_B Z_C}{Z_A}$$

$$Z_{CA} = Z_C + Z_A + \frac{Z_C Z_A}{Z_B}$$

Now from the star connected network:

$$Z_A = (25 + j60) \quad Z_B = (15 + j20) \quad Z_C = (40 - j25)$$

$$\begin{aligned} \therefore Z_{AB} &= (25 + j60) + (15 + j20) + \frac{(25 + j60)(15 + j20)}{(40 - j25)} \\ &= 96.36 \angle 84.38^\circ \Omega \end{aligned}$$

$$\begin{aligned} \therefore Z_{BC} &= (15 + j20) + (40 - j25) + \frac{(15 + j20)(40 - j25)}{(25 + j60)} \\ &= 69.93 \angle -15^\circ \Omega \end{aligned}$$

$$\begin{aligned} \therefore Z_{CA} &= (40 - j25) + (25 + j60) + \frac{(40 - j25)(25 + j60)}{(15 + j20)} \\ &= 181.82 \angle -0.76^\circ \Omega \end{aligned}$$


The effective phase currents in the equivalent delta can now be calculated: (V_{AB} is reference)

$$I_{AB} = \frac{6600 \angle 0^\circ}{96.36 \angle 84.38^\circ} = 68.49 \angle -84.38^\circ$$

$$I_{BC} = \frac{6600 \angle -120^\circ}{69.93 \angle 15^\circ} = 94.38 \angle -105^\circ \text{ A}$$

$$I_{CA} = \frac{6600 \angle -240^\circ}{181.82 \angle -0.76^\circ} = 36.30 \angle 120.76^\circ \text{ (or } 36.30 \angle -239.24^\circ \text{)}$$

Find the line currents:

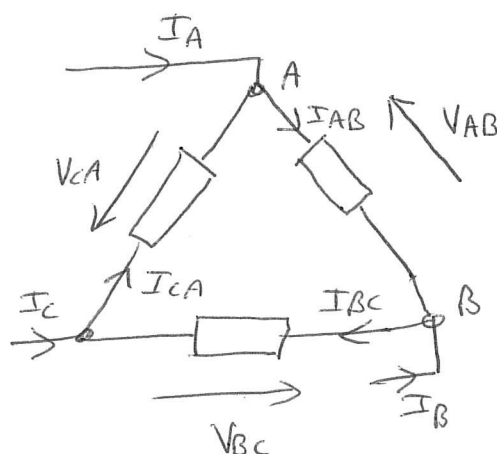

$$\therefore I_A = I_{AB} - I_{CA} = \underline{\underline{102.52 \angle -75.73^\circ \text{ A}}}$$

$$I_B = I_{BC} - I_{AB} = \underline{\underline{38.71 \angle -143.545^\circ \text{ A}}}$$

$$I_C = I_{CA} - I_{BC} = \underline{\underline{122.5 \angle 87.26^\circ \text{ A}}}$$


(ii) Voltage across each phase of the load:

$$V_{AO} = I_A Z_A = 102.52 \angle -75.73^\circ \times (25 + j60) = \underline{\underline{6663.8 \angle -8.35^\circ \text{ V}}}$$

$$V_{BO} = I_B Z_B = 38.71 \angle -143.545^\circ \times (15 + j20) = \underline{\underline{967.775 \angle -90.415^\circ \text{ V}}}$$

$$V_{CO} = I_C Z_C = 122.5 \angle 87.26^\circ \times (40 - j25) = \underline{\underline{5778.3 \angle 55.25^\circ \text{ V}}}$$

(b)(i) Phasor diagram

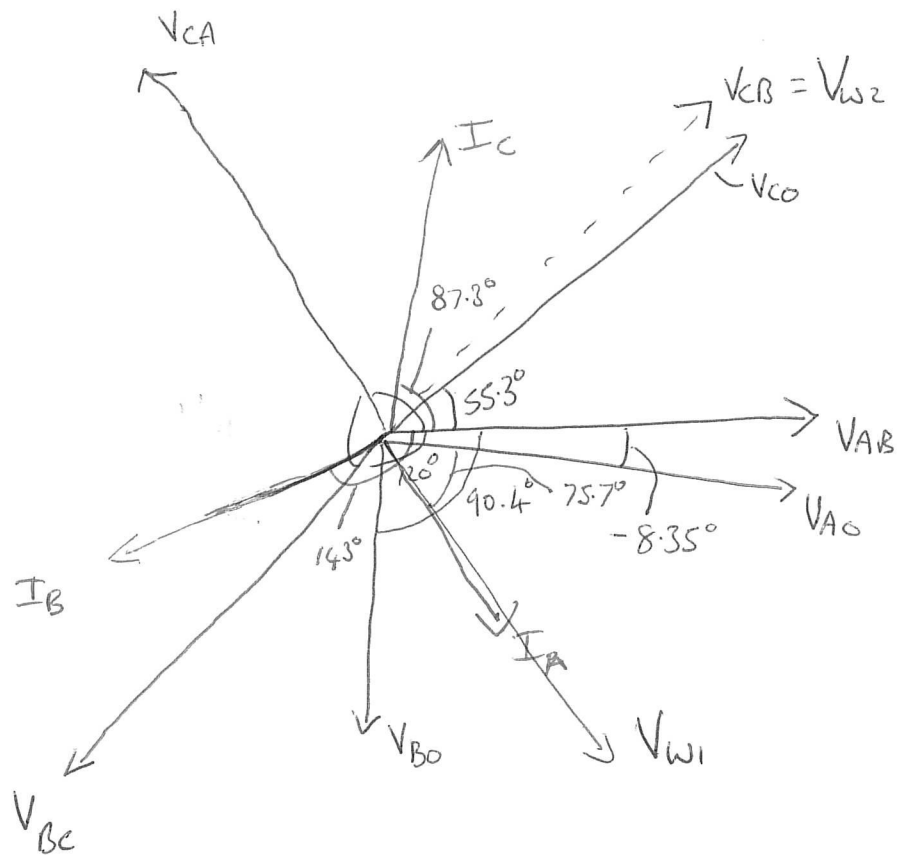

The voltage across the coil of $W_2 = V_{CB} = 6600 \angle 60^\circ$

The voltage across the coil of W_1 is the voltage across the 25Ω resistor in phase A:

$$V_{W1} = I_A \cdot 25 = 2563 \angle -75.73^\circ \text{ V}$$

(ii) Wattmeter W_1 reads:

$$W_1 = V_{W1} \cdot I_A \cdot \cos \phi_1$$

where ϕ_1 is the angle between V_{W1} and $I_A = 0^\circ$

$$\therefore W_1 = 2563 \times 102.52 = 262.7 \text{ kW}$$

Wattmeter W_2 reads:

$$W_2 = V_{CB} \cdot I_C \cdot \cos \phi_2$$

where $\phi_2 = \text{angle between } V_{CB} \text{ and } I_C = 27.3^\circ$

QUESTION 1 (CONTINUED)

14

$$W_2 = 6600 \times 122.5 \cos 27.3^\circ = \underline{\underline{718.4 \text{ kW}}}$$

If W_1 was correctly connected $W_1 + W_2$ would measure the total power, but neither reading would mean anything by itself. With this incorrect connection W_1 actually measures the power in phase A. ($W_1 + W_2 = 981.1 \text{ kW}$)

(c)(i). The voltage coil of W_1 should be removed from the midrail of the load on phase A and reconnected to phase B to measure V_{AB} .

$$W_1 \text{ now reads } V_{AB} \times I_A \times \cos \phi_3$$

where ϕ_3 is the angle between V_{AB} and $I_A = 75.7^\circ$

$$\therefore W_1 = 6600 \times 102.52 \times \cos 75.7^\circ = 167.1 \text{ kW}$$

$$\text{Hence now } W_1 + W_2 = 167.1 + 718.4 = \underline{\underline{885.7 \text{ kW}}}$$

(c)(ii) Power dissipated:


$$P_T = I_A^2 R_A + I_B^2 R_B + I_C^2 R_C$$

$$\begin{aligned} &= 102.52^2 \times 25 + 38.71^2 \times 15 + 122.5^2 \times 40 \\ &= \underline{\underline{885.5 \text{ kW}}} \end{aligned}$$

(iii) This is clearly an unbalanced system so when the star point is connected to the neutral point of the supply a current will flow in the neutral conductor. Hence the wattmeters will give incorrect readings.

(a) Plain air-break circuit breakers

Arc chute

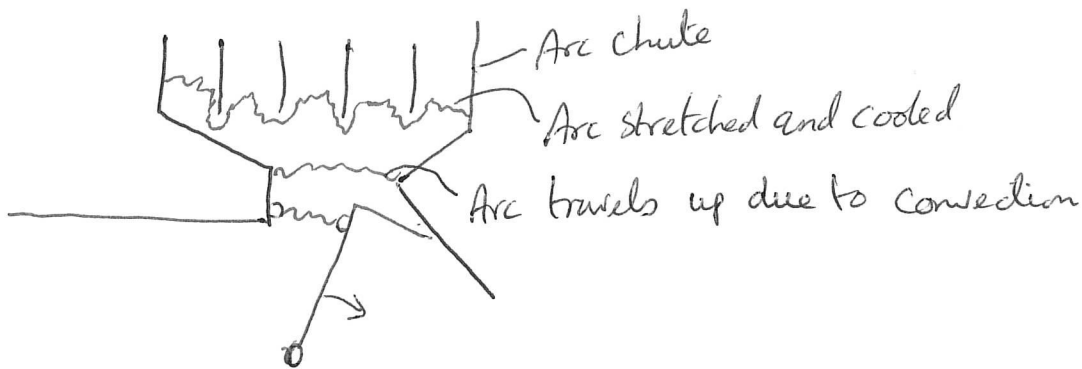

- Used at bottom end of system
- Use of convection due to heating to move arc upwards into arc-chutes which stretch and split the arc (arc chute type)
- Blow out coil uses magnetic field to move arc (blow out coil)

(b) Per-Unit is the value of any quantity, expressed as a ratio or fraction of an arbitrary base value of the same quantity. In power systems the base values selected are normally the rated values of a particular piece of equipment specified - normally rated MVA and line-voltage.

QUESTION 2 (CONTINUED)

6

(c) (i). Before the link is connected choose a base value of 50 MVA.

G2 is unchanged at 0.1 pu

$$T2 = 0.12 \times \frac{50}{60} = 0.1 \text{ pu}$$



$$X_T = 0.2 \text{ pu}$$

$$MVA_{F10} = \frac{1}{X_T} = \underline{\underline{5 \text{ pu}}}$$

Therefore the fault level at busbar B before the link is connected is:

$$MVA_F = MVA_B \times MVA_{F10} = 50 \times 5 = \underline{\underline{250 \text{ MVA}}}$$

(ii) After the link is added, refer all quantities to the same MVA base:-

$$G1 = 0.11 \times \frac{50}{90} = 0.0611 \text{ pu}$$

$$T1 = 0.15 \times \frac{50}{120} = 0.0625 \text{ pu}$$

$$T3 = 0.08 \times \frac{50}{100} = 0.04 \text{ pu}$$


$$\text{Grid Infeed} = 1.0 \times \frac{50}{300} = 0.167 \text{ pu}$$

$$Z_{\text{Base (line)}} = \frac{V_B^2}{MVA_B} = \frac{(132000)^2}{50 \times 10^6} = 348 \Omega$$


$$\therefore X_{\text{pu line}} = \frac{20}{348} = 0.0575 \text{ pu.}$$

QUESTION 2 (CONTINUED)

7

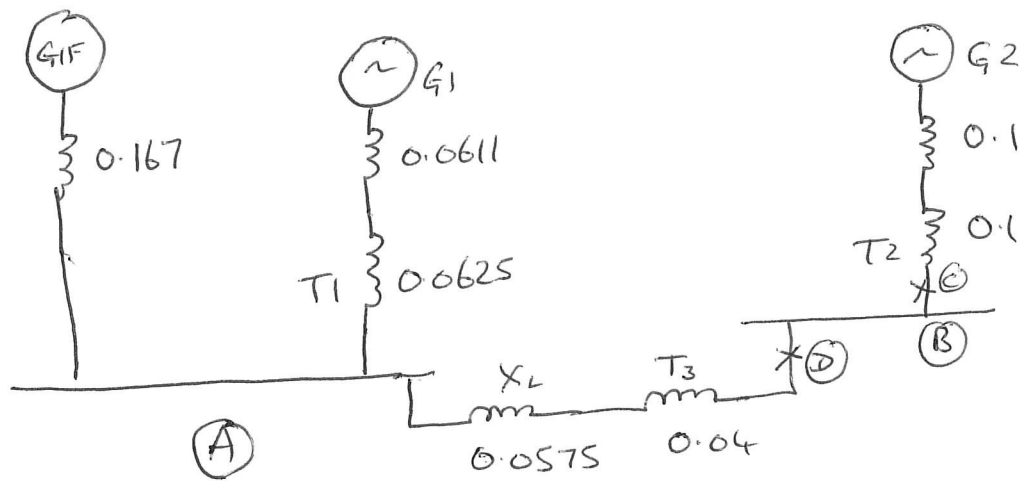

Simplifying:

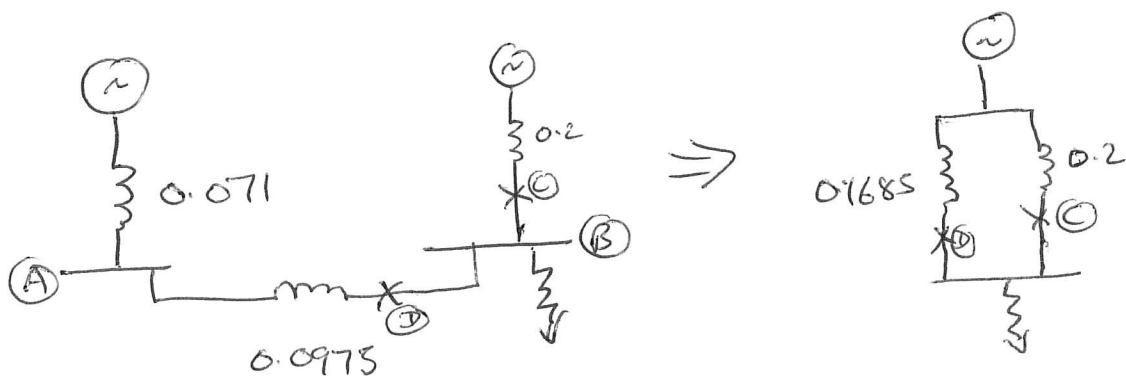

$$\therefore X_T = 0.09145 \text{ pu} \quad \therefore \text{MVA}_{\text{FPU}} = \frac{1}{0.09145} \times 50 = \underline{\underline{546.7 \text{ MVA}}}$$

$$\text{MVA through breaker C} = \frac{1}{0.2} \times 50 = 250 \text{ MVA}$$

$$\text{MVA through breaker D} = \frac{1}{0.1685} \times 50 = 296.7 \text{ MVA}$$

$$\text{Fault current through breaker C} = \frac{\text{MVA}}{\sqrt{3} V_b} = \frac{250 \times 10^6}{\sqrt{3} \times 66000} = \underline{\underline{2.19 \text{ kA}}}$$

$$\text{Fault current through breaker D} = \frac{\text{MVA}}{\sqrt{3} V_b} = \frac{296.7 \times 10^6}{\sqrt{3} \times 66000} = \underline{\underline{2.59 \text{ kA}}}$$

(iii) Referring back to earlier diagrams the p.u. fault current through the 132 kV branch is:

$$I_{\text{pu}} = \frac{1}{0.1685} = 5.93 \text{ pu}$$

$$\text{Hence pu current in G1 is } \frac{0.167}{0.167 + 0.0611 + 0.0625} \times 5.93 = 3.41 \text{ pu}$$

QUESTION 2 (CONTINUED)

8

$$I_B \text{ at G1 is } \frac{50 \times 10^6}{\sqrt{3} \times 25000} = 1155A$$

$$\text{Hence fault current at G1 is } \underline{\underline{3938A}}$$

(iv). If the fault level at B is to be limited to 500MVA then the fault level from the 132kV line must be limited to :

$$500 - 250 = 250 \text{ MVA}$$

$$\text{Since } MVA_F = \frac{1}{X_T} \times MVA_B \Rightarrow X_T = 0.2 \text{ pu}$$


The current reactance of the 132kV system is 0.1685 then the additional reactance required is :

$$X_{\text{add}} = 0.2 - 0.1685 = \underline{\underline{0.0315 \text{ pu}}}$$

QUESTION 3

9

(a) (i)

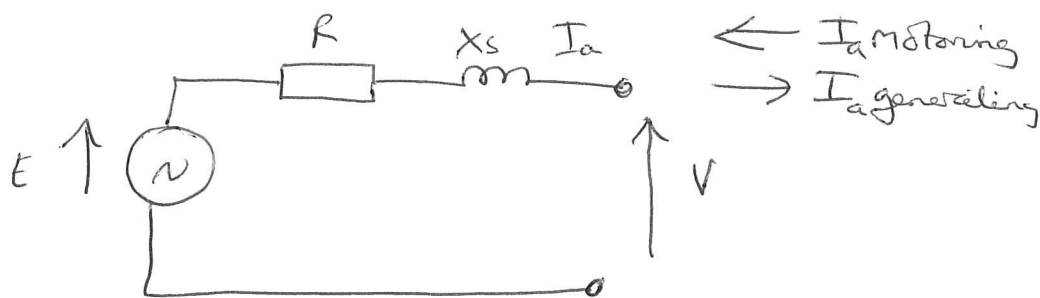

I_a - Input / output stator phase current (A)

V - Supply (or terminal) voltage per phase (V)


E - Induced emf per phase due to the dc excited field on the rotor (V)

R - Stator winding resistance per phase (Ω)

X_s - Synchronous reactance - effective reactance due to the self-, mutual-, and leakage fluxes produced by the stator winding.


(ii) Perform an open-circuit and short-circuit test.

Open-circuit test / EMF test.

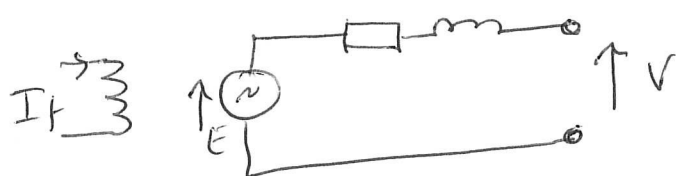

Rotate the machine at synchronous speed and pass DC current through the field winding.

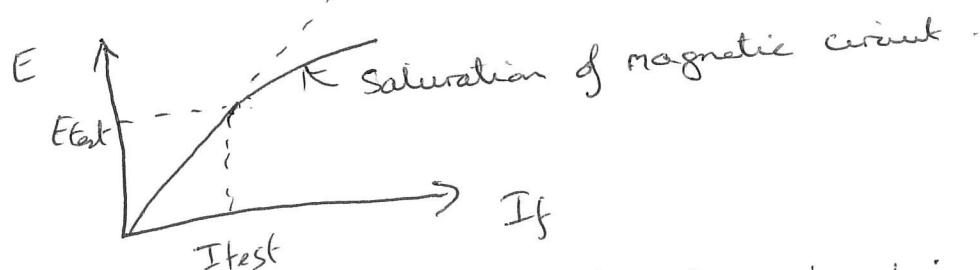On open-circuit $I_a = 0 \therefore V = E$





Increase I_f and measure V . Initially E varies linearly with I_f as the reactance of the magnetic circuit is dominated by the airgap. If I_f increases further saturation occurs and reluctance of the iron circuit becomes significant.

QUESTION 3 (CONTINUED)

10

(ii) Short circuit test.

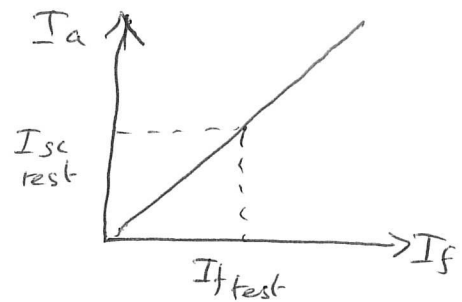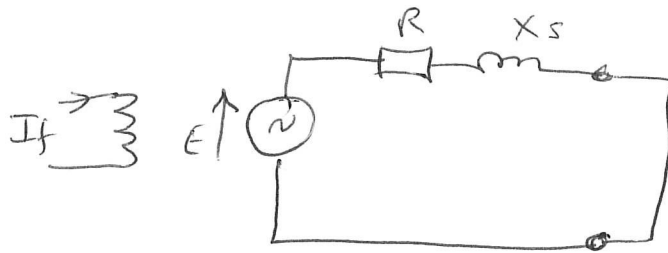

Perform test at $I_{sc} = I_{rated}$ (ie. non-saturated region) by spinning the machine at synchronous speed and adjusting I_f .

$$Z = R + jX_s = \frac{E_{test}}{I_{test}}$$


R can be obtained by direct resistance measurement then

$$X_s = \sqrt{Z^2 - R^2}$$

(iii) For a machine acting as a motor:

$$\bar{E} = \bar{V} - \bar{I}_a R - j\bar{I}_a X_s$$


leading p.f.

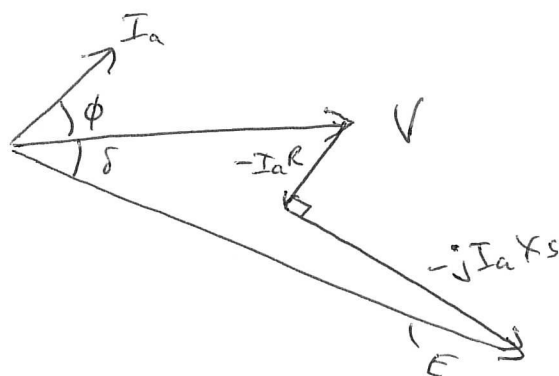


QUESTION 3 (CONTINUED)

11

lagging power factor:

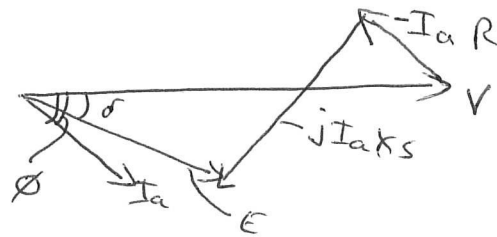

Unity power factor:

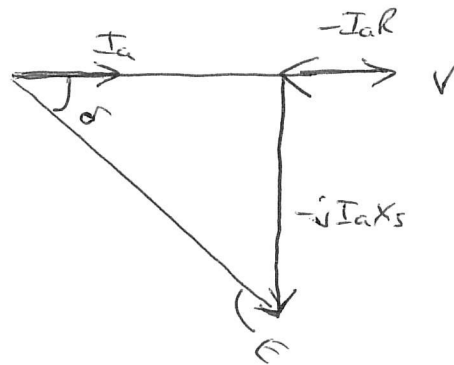

(b)(i) Since $V_A = \sqrt{3} V_L I_L$

$$\therefore I_L = \frac{V_A}{\sqrt{3} V_L} = 92.4 \text{ A}$$

at a power-factor of 0.75 lagging ($= -41.4^\circ$)

For a generator:

$$E \angle \delta = V \angle 0^\circ + j \bar{I}_a X_s$$

$$= \frac{50000}{\sqrt{3}} \angle 0^\circ + 92.4 \angle -41.4^\circ \times 8 \angle 90^\circ$$

$$= 28868 \angle 0^\circ + 739.2 \angle 48.6^\circ = 29362 \angle 1.08^\circ$$


\therefore Excitation voltage is 29362 V ($= 50856 \text{ line}$).

$$\text{Percentage regulation} = \left(\frac{E - V}{V} \right) \times 100 = \frac{29362 - 28868}{28868} \times 100 = \underline{\underline{1.7\%}}$$

QUESTION 3 (CONTINUED)

12

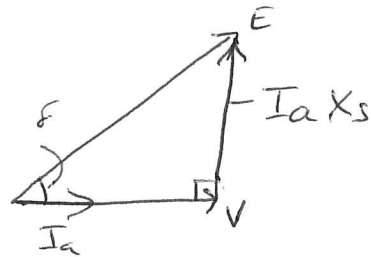- (ii) If the excitation remains unchanged at 29362 V and the input power is increased, the load angle will increase until I_a is in phase with V :



$$(I_a X_s)^2 = E^2 - V^2$$

$$= 29362^2 - 28868^2$$

$$\therefore I_a = \underline{\underline{670.4 \text{ A}}}$$

and the load angle δ is $\cos^{-1}\left(\frac{28868}{29362}\right) = \underline{\underline{10.5^\circ}}$

- (iii) The power input to the generator remains at 8 MVA \times p.f. = 6 MW

But total power = $\frac{3 V_{ph} E_{ph} \sin \delta}{X_s}$

Now excitation is decreased by 12%

$$\therefore E_{ph\text{-new}} = 29362 \times 0.88 = 25839 \text{ V}$$

$$\therefore 6 \times 10^6 = \frac{3 \times 28868 \times 25839 \sin \delta}{8}$$

$$\therefore \sin \delta = \frac{6 \times 10^6 \times 8}{3 \times 28868 \times 25839} = 0.0215$$

$$\therefore \delta = 1.23^\circ$$

Since $E \angle \delta = V \angle 0^\circ + I \angle \phi \cdot 8 \angle 90^\circ$

$$\text{then } I \angle \phi = \frac{E \angle \delta - V \angle 0^\circ}{8 \angle 90^\circ} = \frac{25839 \angle 1.23^\circ - 28868 \angle 0^\circ}{8 \angle 90^\circ}$$

$$= \underline{\underline{385.6 \angle 79.6^\circ \text{ A}}} \quad (\text{p.f.} = 0.18 \text{ leading})$$




QUESTION 4

13

(a) Conditions preferred when operating transformers in parallel:

- Same no-load voltage ratios - small differences will lead to circulating currents even on no-load, and incorrect load sharing
- Same per unit impedance - magnitude only would lead to correct sharing of MVA, but not at the same power factors. Difference will lead to unbalanced sharing
- Ideally same R/X ratio as well as above to ensure loads shared at the same power-factor.
- Must have the same phase sequence / same phase group.




(b) Dy11 Delta-star connection

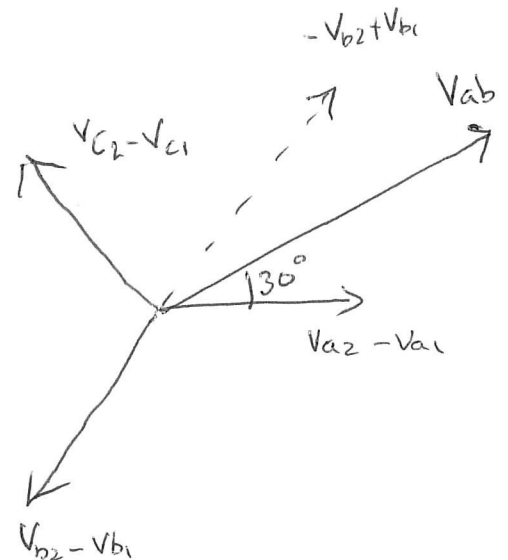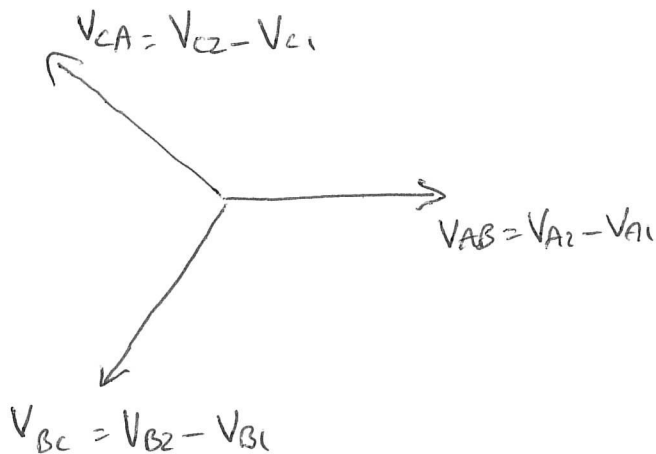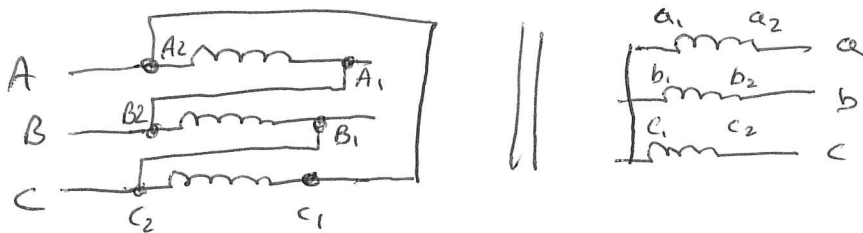

Primary voltage is in phase with respective secondary voltage but scaled by the turns ratio. Consequently for the Dy11 there is a 30° forward phase shift between secondary and primary terminals.

QUESTION 4 (CONTINUED)

14

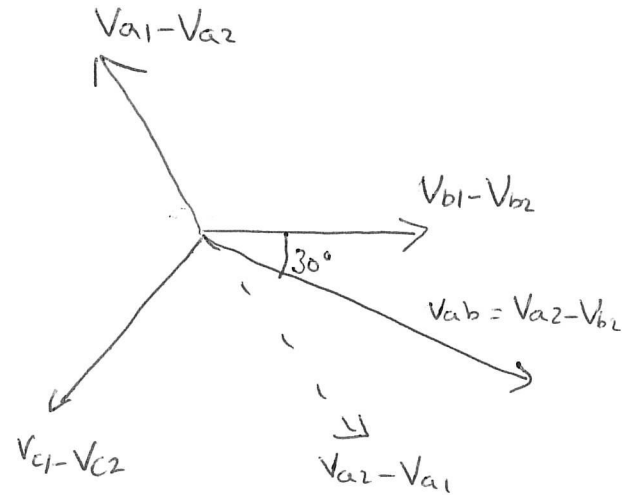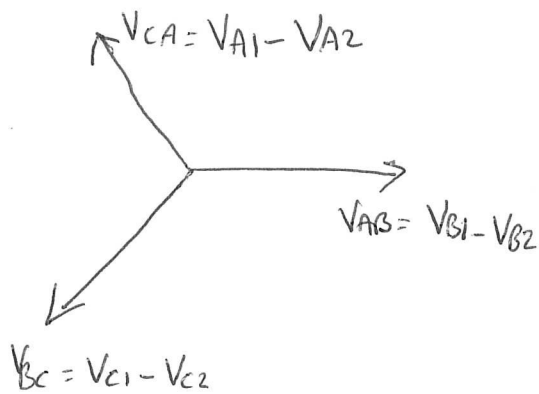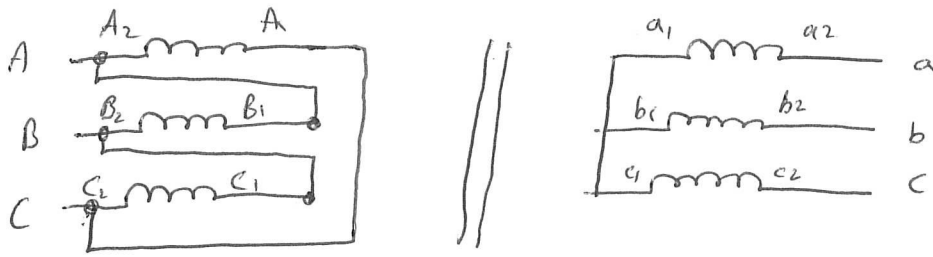

For Dy1 there is a 30° lagging phase shift between the secondary and primary terminals.

(c)(i) Choose a base of 8 MVA:-

$$Z_{pu1} = 0.03 + j0.06 = 0.0671 \angle 63.4^\circ$$

$$Z_{pu2} = (0.05 + j0.15) \cdot \frac{8}{4} = 0.1 + j0.3 = 0.3162 \angle 71.6^\circ$$

$$Z_{puT} = Z_{pu1} + Z_{pu2} = 0.13 + j0.36 = 0.383 \angle 70.14^\circ$$

$$VA_1 = 10 \angle 45.6^\circ \times \left(\frac{0.3162 \angle 71.6^\circ}{0.383 \angle 70.14^\circ} \right)^* = 10 \angle 45.6^\circ \times (0.826 \angle 1.46^\circ)^* = \underline{\underline{8.26 \angle 44.14^\circ \text{ MVA}}}$$

(p.f. = 0.918)

$$VA_2 = 10 \angle 45.6^\circ \times \left(\frac{0.0671 \angle 63.4^\circ}{0.383 \angle 70.14^\circ} \right)^* = 10 \angle 45.6^\circ \times (0.175 \angle -6.74^\circ)^* = \underline{\underline{1.75 \angle 52.34^\circ \text{ MVA}}}$$

(p.f. = 0.611 lag)

QUESTION 4 (CONTINUED)

15

(c)(ii) Transformer 1 (8MVA unit) operates at $\frac{8.26}{8} \times 100 = 103\%$ of its full load rating (i.e. overloaded)

Transformer 2 (4MVA unit) operates at $\frac{1.75}{4} \times 100 = 43.8\%$ of its full load rating (i.e. underloaded)

(d)(i) For the transformers to share the load correctly the per unit impedances, relative to the transformers own MVA rating must be equal. +

Unit 1 ($0.03 + j0.06$) on an 8MVA base

Unit 2 ($0.05 + j0.15$) on a 4MVA base

Since unit 1 is overloaded the reactor must be placed in series with this unit

\therefore The size of the reactor is $(0.05 + j0.15) - (0.03 + j0.06) = \underline{\underline{0.02 + j0.09}}$ and its rating is 8MVA

$$\therefore Z_{pu} + \text{reactor} = 0.05 + j0.15 = 0.158 \angle 71.6^\circ$$

$$(ii) \text{ New } Z_{puT} = (0.05 + j0.15) + (0.1 + j0.3) = 0.15 + j0.45 = 0.474 \angle 71.6^\circ$$

$$\text{Hence } VA_1 = 10 \angle 45.6^\circ \times \left(\frac{0.3162 \angle 71.6^\circ}{0.474 \angle 71.6^\circ} \right)^* = \underline{\underline{6.67 \angle 45.6^\circ \text{ MVA}}}$$

$$VA_2 = 10 \angle 45.6^\circ \times \left(\frac{0.158 \angle 71.6^\circ}{0.474 \angle 71.6^\circ} \right)^* = \underline{\underline{3.33 \angle 45.6^\circ \text{ MVA}}}$$

i.e. both units operate at 83% of their full load capacity

$$(e) \text{ Existing demand} = 10 \text{ MVA} @ 0.7 \text{ lag} = 7 \text{ MW} + 7.14 \text{ MVAR}$$

$$\text{Synchronous machine} = 4 \text{ MVA} @ 0.8 \text{ lead} = 3.2 \text{ MW} - 2.4 \text{ MVAR}$$

$$\therefore \text{New demand is } 10.2 \text{ MW} + 4.74 \text{ MVAR} = \underline{\underline{11.23 \angle 24.9^\circ \text{ MVA}}}$$

$$\therefore \text{Since at full load the transformers could supply } \frac{10}{0.83} = 12.04 \text{ MVA}$$

then they should be able to cope with the addition of the synchronous machine