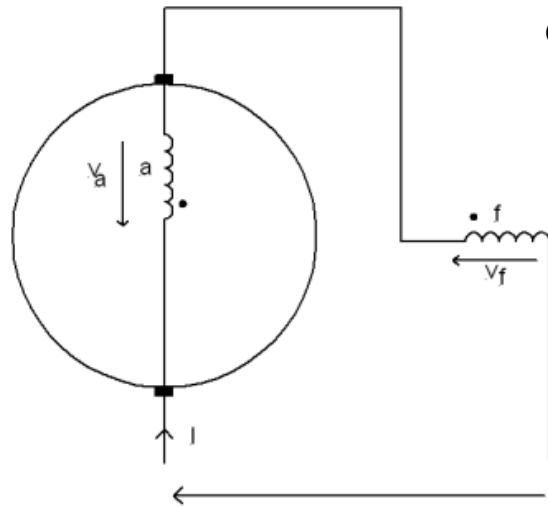


Modelling of Machines

Section 7

Universal series motor

Kron primitive



Rotor coil (on q-axis) often called armature coil
- Hence subscript 'a'

- Same current passes through the stator and rotor coil
- Reversing the current does not affect direction of rotation and so can be used on both DC and AC supplies – hence the term universal
- Speed on AC supply not restricted by mains frequency (e.g. 2-pole induction machine with is <3000rpm)
- Widely used in mass-market, cost-sensitive applications such domestic appliances, main power tools and kitchen gadgets as low-cost, high-speed machine

BUT – has several performance drawbacks so only used up to <1kW (often cited as being fractional horsepower machines)

Analysis

$$\begin{array}{c|c|c|c|c|c}
 \begin{array}{c} v_a \\ v_f \end{array} & = & \begin{array}{cc} R_a + L_a p & \omega_r M \\ 0 & R_f + L_f p \end{array} & \begin{array}{c} i_a \\ i_f \end{array} & \begin{array}{l} \text{Constraining equations:} \\ V = V_a + V_f \\ I = I_a = I_f \end{array}
 \end{array}$$

DC operation

On DC the equations reduce to

$$\begin{array}{c|c|c|c|c|c}
 \begin{array}{c} v_a \\ v_f \end{array} & = & \begin{array}{cc} R_a & \omega_r M \\ 0 & R_f \end{array} & \begin{array}{c} i_a \\ i_f \end{array} & &
 \end{array}$$


Applying the constraining equations yields:

$$V = I (R_a + R_f + \omega_r M)$$

$$T = \frac{\text{Output power}}{\omega_{r_{mech}}} = \frac{\text{Output power}}{\omega_{r_{elec}}} \times \text{pole pairs}$$

$$\text{Electrical power input} = VI = \underbrace{I^2 R}_{\text{Losses}} + \underbrace{\omega_r M I^2}_{\text{Mech. out}}$$
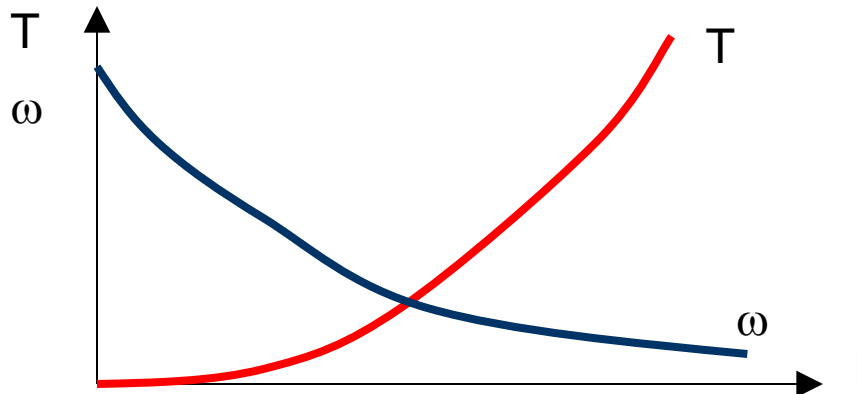
$$T = \frac{\text{pole pairs}(\omega_r M) I^2}{\omega_r} = \text{pole pairs} \times M I^2$$



Typical form of torque-speed curve on fixed voltage supply

In practice, square law torque behaviour limited by saturation