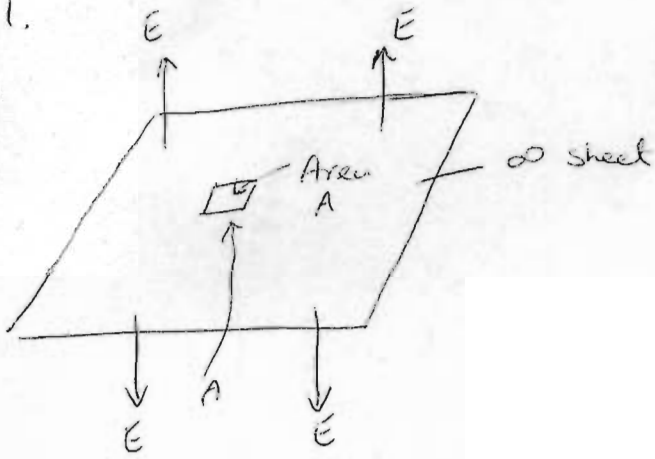


Q1.

a)



(charge density / unit area = q_s)

By symmetry E is perpendicular to the sheet and independent of the lateral position and has the same value on either side of the sheet.

Gauss' Law $\oint_s E dA = \frac{q_s A}{\epsilon_0} \leftarrow \text{Enclosed charge}$


$$\therefore E \times 2A = \frac{q_s A}{\epsilon_0}$$

Contribution from
top and bottom
surfaces

$$\therefore E = \frac{q_s}{2\epsilon_0}$$

⑤

b)

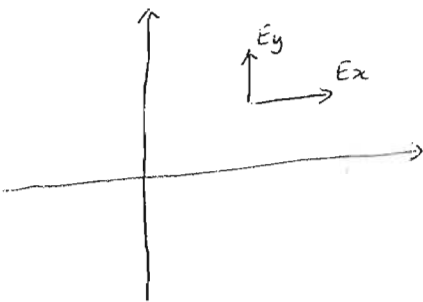

$E_y = E_x = \text{field due to infinite sheet.}$

$$= \frac{q_s}{2\epsilon_0}$$

$$\frac{q_s}{2\epsilon_0} = \frac{5 \times 10^{-6}}{2 \times 8.854 \times 10^{-12}} = 2.82 \times 10^5 \text{ V/m}$$

(2)

E field at :-

$$A = (2.82, 2.82, 0) \times 10^5 \text{ V/m}$$

$$B = (2.82, 2.82, 0) \times 10^5 \text{ V/m}$$

$$C = (2.82, -2.82, 0) \times 10^5 \text{ V/m}$$

(5)

- c) Ampere's Law states that the line integral of the B-field around a closed path is equal to μ_0 times the current linking the path:

$$\oint B \cos \theta \, dL = \mu_0 I$$

Applying this to a circular path around an infinitely long wire, then at each point on the path $\theta = 0$ (i.e. $\cos \theta = 1$), and by symmetry B is constant. θ is the angle between the B-field and the direction of the path.

$$\therefore B \cdot 2\pi r = \mu_0 I$$

$$\text{or } B = \frac{\mu_0 I}{2\pi r}$$

(4)

- d) Since the field at a distance r from the wire M is

$$B = \frac{\mu_0 I}{2\pi r}$$

The flux linking the circuit can be found by integration

$$\phi = \int B(r) \, da = \int_{z_1}^{z_2} \int_{r_1}^{r_2} B \, dr \, dz = \int_{z_1}^{z_2} \int_{r_1}^{r_2} \frac{\mu_0 I}{2\pi r} \, dr \, dz$$

$$= (z_2 - z_1) \cdot \frac{\mu_0 I}{2\pi} \ln \left(\frac{r_2}{r_1} \right)$$

(3)

The Induced emf $E = \frac{d\phi}{dt}$

$$E = (z_2 - z_1) \frac{\mu_0}{2\pi} \ln\left(\frac{r_2}{r_1}\right) \frac{dI}{dt}$$

$$z_2 - z_1 = 80 \times 10^{-3} \text{ m}$$

$$\ln\left(\frac{r_2}{r_1}\right) = \ln 3 = 1.099$$

$$\begin{aligned} \frac{dI}{dt} &= \frac{d}{dt} I_0 \sin \omega t = \omega I_0 \cos \omega t \\ &= 2\pi \cdot 50.4 \text{ A s}^{-1} \text{ rms} \end{aligned}$$

$$\therefore E = 80 \times 10^{-3} \times \frac{4\pi \times 10^{-7}}{2\pi} \times 1.099 \times 400\pi$$

$$= \underline{\underline{22 \mu\text{V}}} \text{ rms}$$

(6)

Q2

④

a) (i) Initially the reluctance of the magnetic circuit may be calculated from:-

$$S = \frac{l}{\mu_0 \mu_r A} = \frac{\pi D}{\mu_0 \mu_r A} = \frac{\pi \cdot 0.2}{4\pi \times 10^{-7} \times 1000 \times 10 \times 10^{-4}} = \underline{\underline{5 \times 10^5 \text{ H}^{-1}}} \quad (2)$$

(ii) The flux in the core is related to the flux density by:

$$\phi = B \cdot A$$

But $N I = \phi S$

$$\therefore I = \frac{B \cdot A \cdot S}{N} = \frac{1 \times 10 \times 10^{-4} \times 5 \times 10^5}{1000}$$

$$= \underline{\underline{0.5 \text{ A}}} \quad (2)$$

(iii) Self-inductance of the coil may be obtained from:

$$L = \frac{N^2}{S} = \frac{1000^2}{5 \times 10^5} = \underline{\underline{2 \text{ H}}} \quad (2)$$

(iv) After the slot is cut the new reluctance of the magnetic circuit is given by:-


$$S_{\text{new}} = \frac{l_{\text{core}}}{\mu_0 \mu_r A} + \frac{l_{\text{gap}}}{\mu_0 A} = \frac{1}{4\pi \times 10^{-7} \times 10 \times 10^{-4}} \times \left(\frac{\pi \cdot 0.2 - 0.01}{1000} + 0.01 \right)$$

$$= 8.45 \times 10^6 \text{ H}^{-1}$$

and the new self inductance of the coil is:

$$L_{\text{new}} = \frac{1000^2}{8.45 \times 10^6} = \underline{\underline{0.118 \text{ H}}} \quad (3)$$

(5)

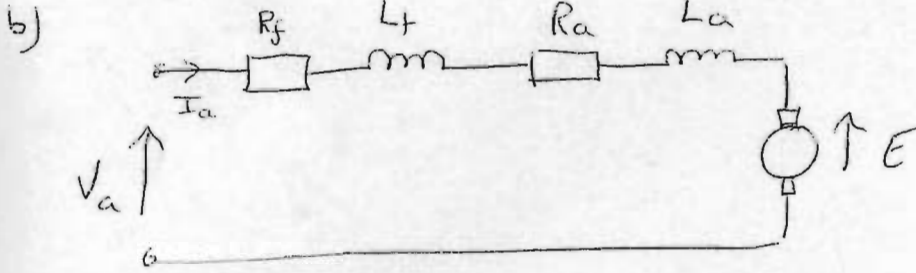

For wound field

$$I_f = I_a$$

In steady-state (i.e. D.C.) L_a and L_f can be omitted.

$$V = I_a(R_f + R_a) + E$$

$$T = M \cdot I_f \cdot I_a = M I_a^2$$

$$E = M \cdot I_f \cdot \omega = M I_a \omega$$

I_f = Field current

$= I_a$ = Armature current

ω = rotational speed (rad/s)

M = Mutual coupling between windings.


Ignoring voltage drops across R_f and R_a

$$E \approx V_a \approx M I_a \omega$$

$$V_a \approx M \sqrt{\frac{T}{M}} \omega$$

$$\therefore \omega \approx \frac{V_a}{\sqrt{T M}}$$

$$T \propto I_a^2$$

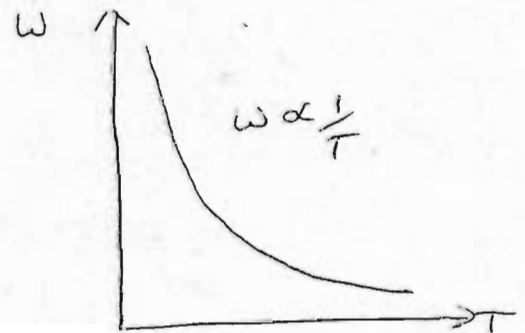

(5)

c) (i) $R_f = 1\Omega$ $R_a = 0.2\Omega$ $M = 1\text{V/rad/s}$

$$T_{\text{LOAD}} = 0.01 \omega^2$$

$$T_{\text{MOTOR}} = M I_a^2 = 1 \cdot I_a^2$$

At steady-state $T_{\text{LOAD}} = T_{\text{MOTOR}}$

$$\therefore 0.01 \omega^2 = I_a^2 \Rightarrow \omega = 10 I_a$$

(6)

Now $V = I_a (R_a + R_f) + M I_a \omega$

$$\therefore 12 = I_a (R_a + R_f) + 1 \cdot I_a \cdot 10 I_a$$

$$12 = 1.2 I_a + 10 I_a^2$$

$$\underline{\underline{I_a = 1.037 A}}$$

$$T = M I_a^2 = 1 \cdot 1.037^2 = 0.01 \text{ W}$$

$$\therefore \omega = \sqrt{\frac{1.037^2}{0.01}} = 10.37 \text{ rad/s} = \underline{\underline{99 \text{ rpm}}}$$

(4)

(ii)

For 10V Supply

$$10 = 1.2 I_a + 10 I_a^2$$

$$\therefore I_a = 0.942 A$$

$$\omega_{\text{new}} = \sqrt{\frac{0.942^2}{0.01}} = 9.42 \text{ rad/s} = 90 \text{ rpm}$$

ie. Motor slows down by 9 rpm.

3a.

p-type has resistivity $\rho = 2.5 \times 10^{-3}$

$$\rho = \frac{1}{e p \mu_h + e n \mu_n}$$

$\downarrow \rightarrow 0$

$$\rho = \frac{1}{e p \mu}$$

$$p = 5 \times 10^{22} = N_A \quad n \cdot p = n_i^2 \quad n = 2 \times 10^9$$

For compensated region

$$n \cdot p = n_i^2 \quad N_A + p = p + N_D$$

$$N_A - N_D = p - n$$

$$p = \frac{n_i^2}{n} \quad N_A - N_D = \frac{n_i^2}{n} - n$$

$$n^2 + (N_A - N_D)n - \frac{n_i^2}{2} = 0$$

Solution

$$n = \frac{N_D - N_A}{2} \pm \sqrt{\frac{(N_A - N_D)^2 - 4n_i^2}{2}}$$

$$1 \text{ solution } \frac{N_D - N_A}{2} + \frac{N_A - N_D}{2} = 0$$


$$\text{other } n = N_D - N_A = 5 \times 10^{22} \text{ cm}^{-3}$$

$$p = 2 \times 10^9$$


in significant

82

(3b) (i) Equilibrium.

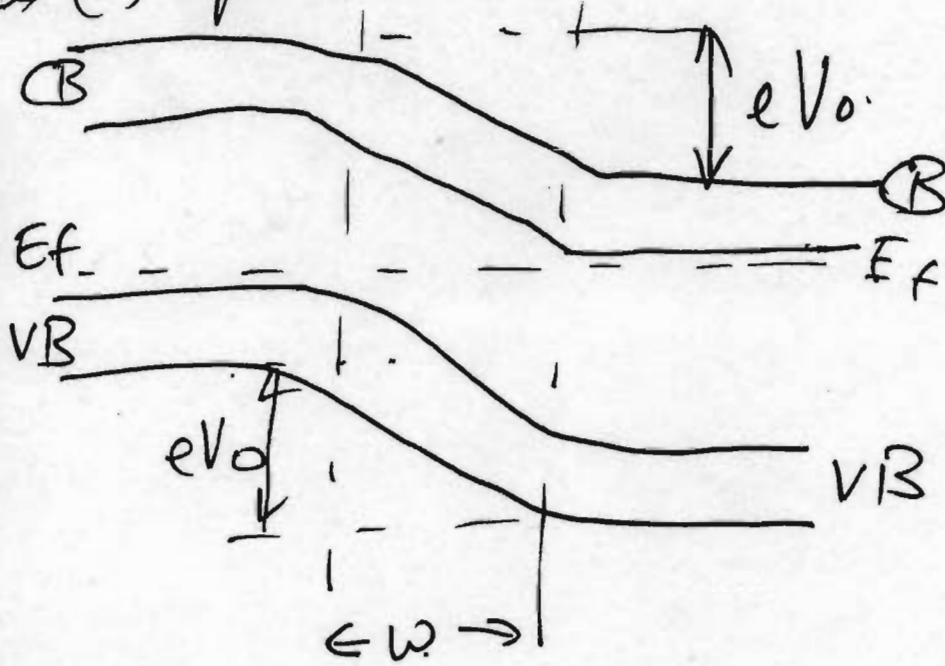

(ii) Forward Bias

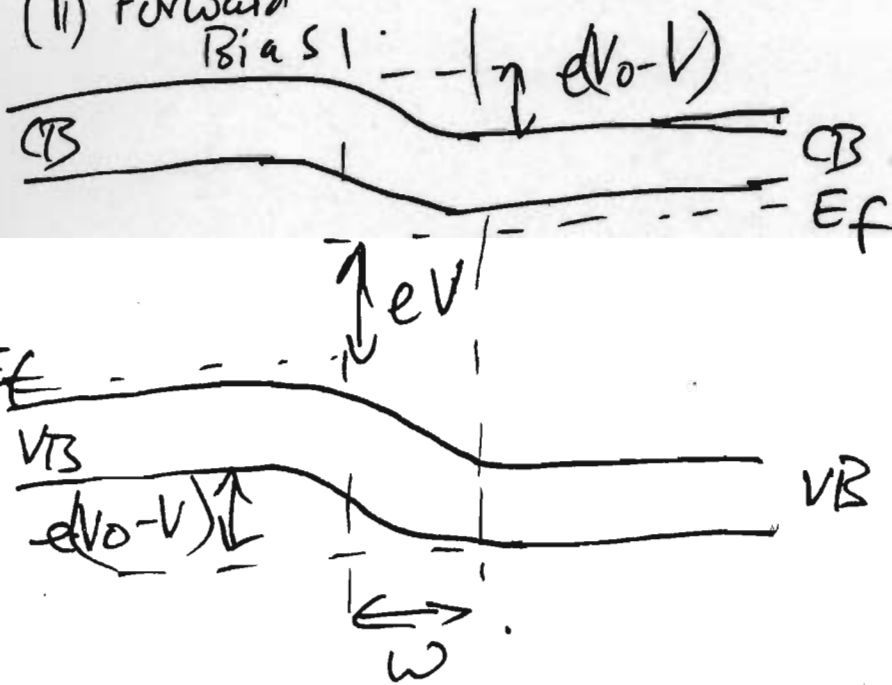

$$(3c) \quad I = I_0 \left(e^{\frac{eV}{kT}} - 1 \right)$$

↑
Saturation
current = I_0

$$T = 298 \text{ K}$$

$$I = 1 \times 10^{-9} (e^{19.44} - 1)$$

$$= 277 \text{ mA}$$

3d.

$$i = \eta \frac{eP}{h\nu}$$

$$E = 2.2 \text{ eV}$$

but $E = h\nu$

and $\frac{h\nu}{e} =$

E in eV

$$= \eta \frac{P}{E(\text{eV})}$$

$$= 227 \mu\text{A}$$


$$E = 0.8 \text{ eV} \quad E < E_g (1.1 \text{ eV})$$




No photocurrent.

$$I \rightarrow I_0 (1 \times 10^{-9} \text{ A})$$

4. $\phi_{Al} = 5.4 \text{ eV} \quad \phi_{semi} = 4.5$

$\phi_m > \phi_{semi}$ Schottky.

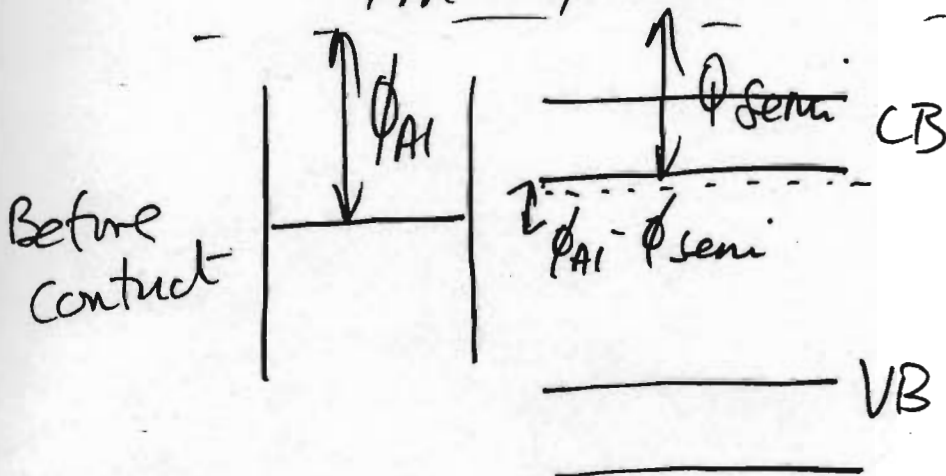

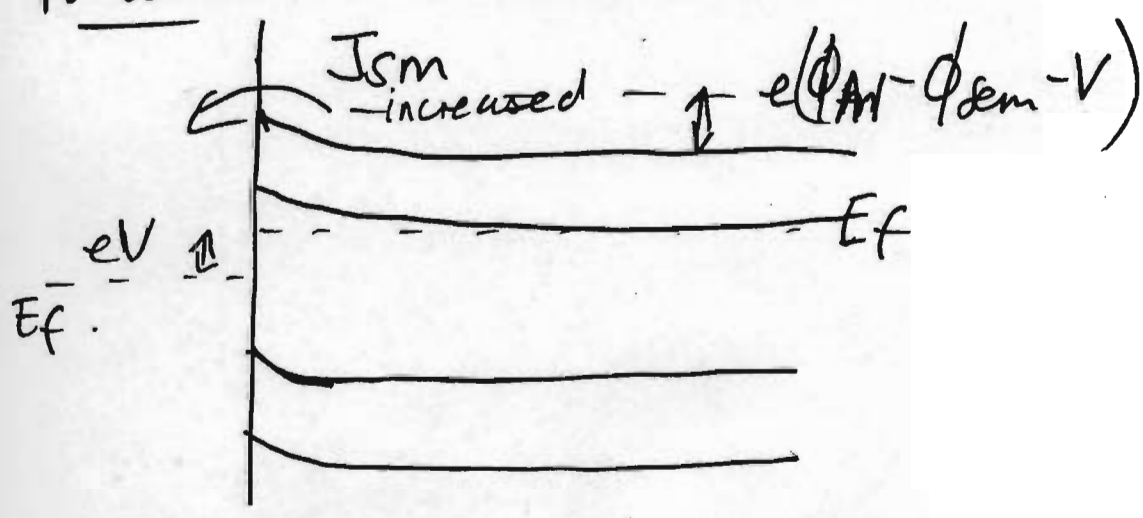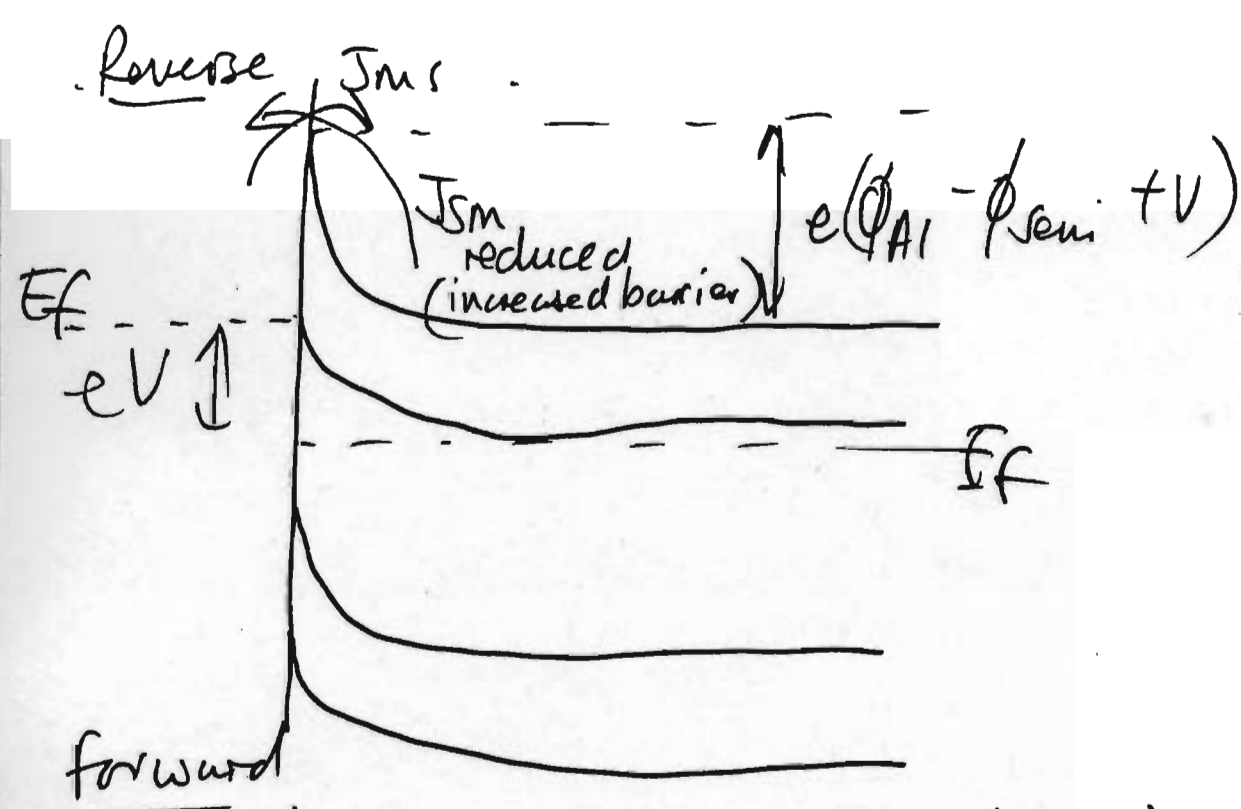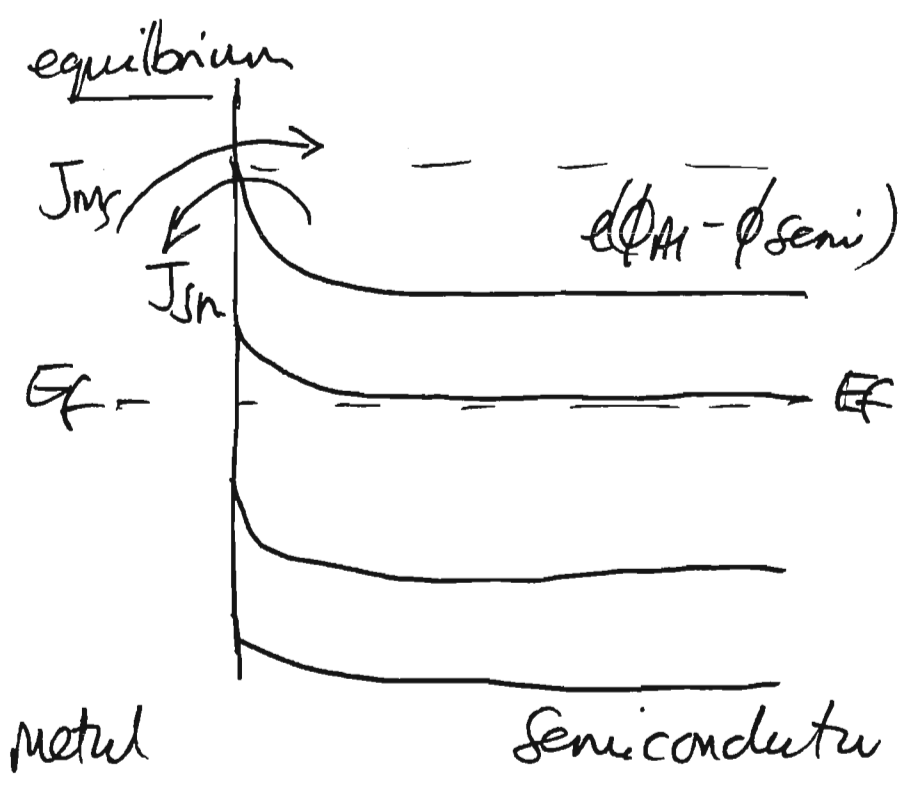

4b $I_d = \frac{\mu_e C_g}{l^2} \left[V_g - V_T - \frac{V_d}{2} \right] V_d.$ (11)

Saturation condition $V_d = V_g - V_t.$

$$[] \rightarrow \left[V_g - V_T - \frac{V_g}{2} + \frac{V_t}{2} \right] (V_g - V_t)$$

$$\frac{V_g - V_t}{2} (V_g - V_t)$$

$$\frac{(V_g - V_t)^2}{2}.$$

$$\frac{\mu_e C_g}{l^2} = 60.$$

(i) $V_g = 1.0 \text{ V}$ $V_g - V_T = 0.2 \text{ V}$ $\frac{(V_g - V_t)^2}{2} = 0.02$

(ii) " 2.0 V $V_g - V_T = 1.2 \text{ V}$ " = 0.72

(iii) " 3.0 V $V_g - V_T = 2.2 \text{ V}$ " = 2.42

(i) So $I_{ds} = 1.2$

(ii) $I_{ds} = 43.2$

(iii) $I_{ds} = 145.2$

4C

(12)

$$\text{Transconductance} = \frac{dI_d}{dV_{dsat}}$$

$$I_{ds} = \frac{\mu_e C_g}{2} (V_g - V_t)^2$$

Differentiate but $V_g - V_t = V_{dsat}$.


$$dI_{ds} = \frac{\mu_e C_g}{2} V_{dsat} \cdot dV_{dsat} \quad (dI_s)$$

$$g_m = \frac{dI_{ds}}{dV_{ds}} = \left(\frac{\mu_e C_g}{2} \right) V_{ds}$$

= 60 (from before)

- | | | |
|-------|-----------------------------|-------------|
| (i) | $V_g - V_t = V_{ds} = 0.2V$ | $g_m = 12$ |
| (ii) | " " " " $1.2V$ | $g_m = 72$ |
| (iii) | " " " " $2.2V$ | $g_m = 132$ |

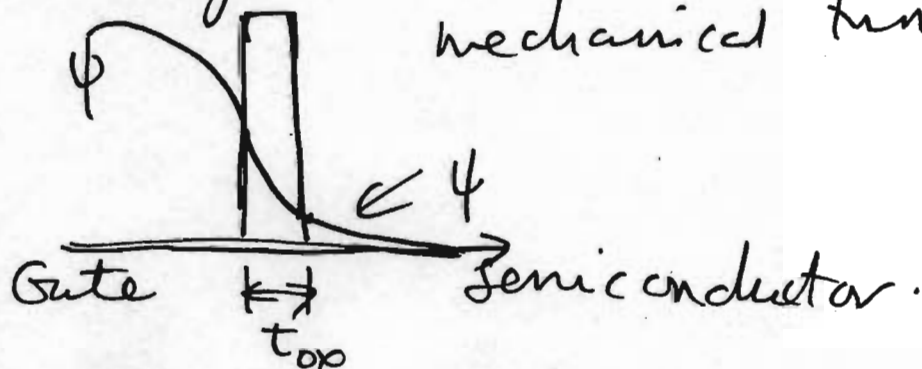4d. Electrons will tunnel through gate oxide if thin enough. Mechanism is Quantum mechanical tunneling.




(13) ~~14~~

wavefunction within the gate oxide will take the form of an exponential decay

$$\psi(x) = A e^{-\alpha x}$$

↑
constant

Other type of device is a Zener diode

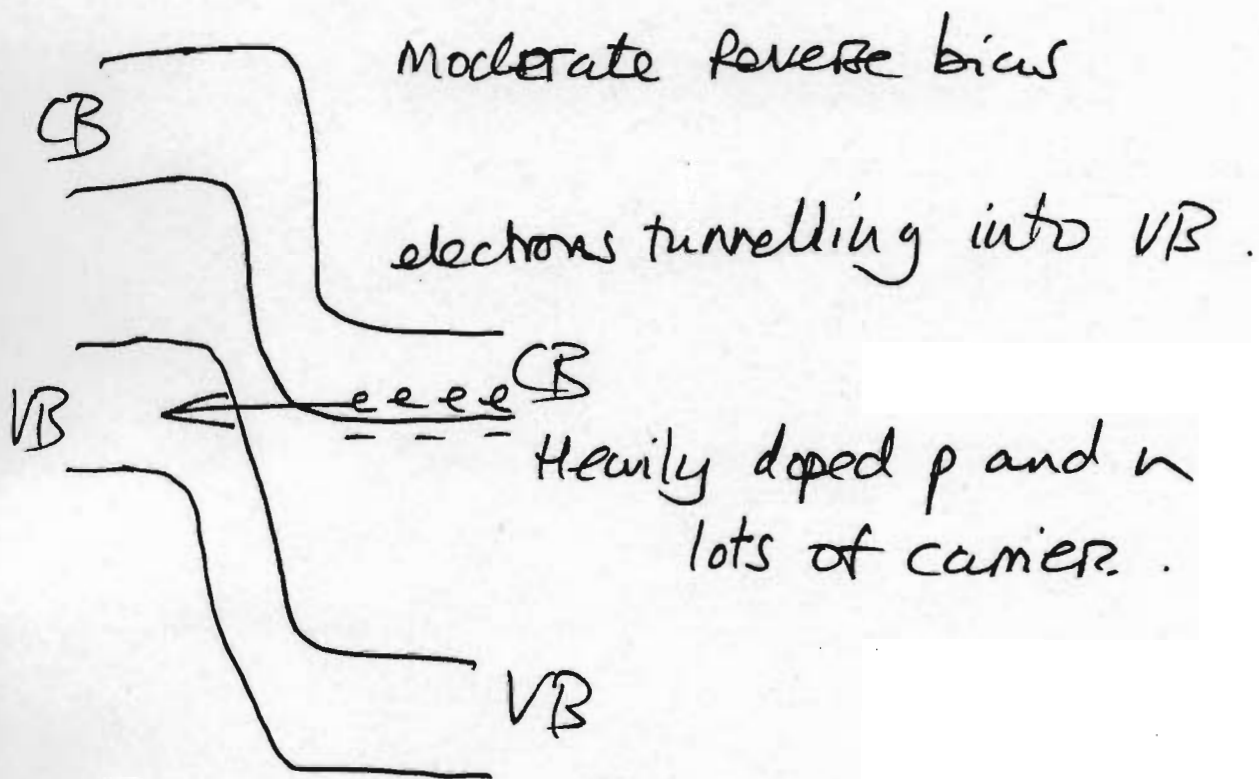

Application is as a voltage reference
Tunnelling current holds device at a certain reverse bias.

5.

- a. (i) The relationship between collector current, I_C , and base emitter voltage, V_{BE} , for a bipolar junction transistor is given by:

$$I_C = I_{CO} \left(\exp\left(\frac{eV_{BE}}{kT}\right) - 1 \right)$$

where I_{CO} , e , k and T are constants. Show that the mutual conductance, g_m , of the transistor is given by:

$$g_m = \frac{eI_C}{kT} \quad (6)$$

$$g_m = \frac{dI_C}{dV_{BE}} = \frac{d}{dV_{BE}} \left[I_{CO} \left(\exp\left(\frac{eV_{BE}}{kT}\right) - 1 \right) \right] = \frac{eI_{CO}}{kT} \exp\left(\frac{eV_{BE}}{kT}\right)$$

$$\text{For forward bias, } I_C = I_{CO} \left(\exp\left(\frac{eV_{BE}}{kT}\right) - 1 \right) \approx I_{CO} \exp\left(\frac{eV_{BE}}{kT}\right)$$

$$\therefore \frac{eI_{CO}}{kT} \exp\left(\frac{eV_{BE}}{kT}\right) \approx \frac{eI_C}{kT}$$

- (ii) Show how the g_m may be expressed as $g_m = \frac{\beta}{r_{be}}$. (3)

$$r_{be} = \frac{\partial V_{BE}}{\partial I_B} \quad \text{and} \quad \beta = \frac{\partial I_C}{\partial I_B}$$

$$\therefore g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{\partial I_C}{\partial I_B} \times \frac{\partial I_B}{\partial V_{BE}} = \frac{\beta}{r_{be}}$$

- b. (i) For the common emitter amplifier circuit of figure 5, assuming I_B is negligible, calculate the d.c. bias conditions, V_B , V_E , V_C and I_C , and hence the small signal parameters g_m and r_{be} .

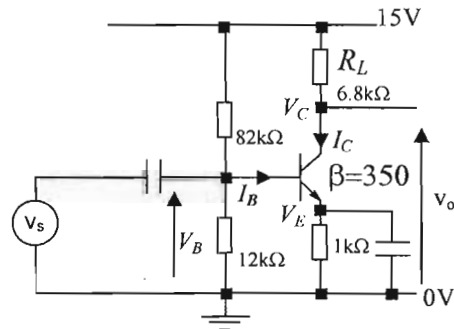


Figure 5

(6)

$$V_B = 15 \times \frac{12\text{k}\Omega}{12\text{k}\Omega + 82\text{k}\Omega} = 1.91\text{ V}$$

$$V_E = V_B - 0.7 = 1.21\text{ V}$$

$$I_E = \frac{V_E}{1\text{k}\Omega} = 1.21\text{ mA}$$

If $I_C \approx I_E$ (I_C assumed negligible): $I_C \approx 1.21\text{ mA}$

$$V_C = 15 - I_C R_L = 15 - 1.62\text{ mA} \times 6.8\text{k}\Omega = 6.74\text{ V}$$

$$g_m = \frac{eI_C}{kT} = \frac{1.21\text{ mA}}{0.026} = 46.5 \times 10^{-3}\text{ A/V}$$

$$r_{be} = \frac{350}{46.5 \times 10^{-3}} = 7521 = 7.52\text{ k}\Omega$$

- (ii) Draw a small signal equivalent circuit of the transistor and the surrounding circuitry and determine the voltage gain v_o/v_s of the amplifier.


(5)

$$R_T = 12\text{k}\Omega // 82\text{k}\Omega = 10.47\text{ k}\Omega$$

$$v_o = -g_m v_{be} \times R_L$$

$$\frac{v_o}{v_s} = -46.5 \times 10^{-3} \times 6.8\text{k}\Omega$$
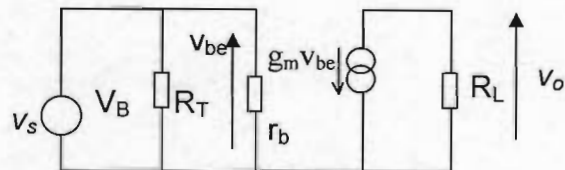
$$\frac{v_o}{v_s} = -46.5 \times 10^{-3} \times 6.8\text{k}\Omega = 316\text{ V/V}$$



You should assume that $V_{BE} = 0.7\text{ V}$, that $kT/e = 0.026$ and that all capacitors are short circuit to a.c. signals.

6.

- a. (i) Figure 6a shows a network consisting of noisy resistors, a noise voltage source and a noise current source.

Find the noise free resistance R_{Th} and the mean - square noise voltage v_{nTh}^2 (in terms of $V^2 \text{ Hz}^{-1}$) which form the Thevenin equivalent of the noisy network.

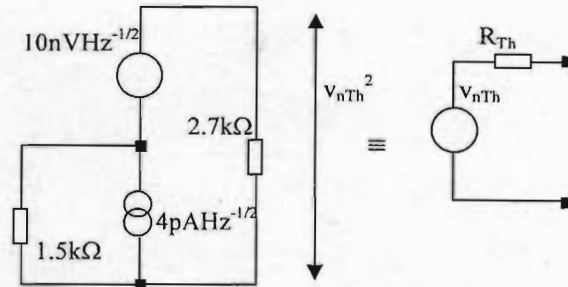


Figure 6a

(8)

$$R_{Th}, \text{ by inspection, is } 1.5\text{k}\Omega // 2.7\text{k}\Omega = \frac{1.5\text{k}\Omega \times 2.7\text{k}\Omega}{1.5\text{k}\Omega + 2.7\text{k}\Omega} = 964\Omega.$$

Using superposition to find the contribution of each noise source:

$$\text{Due to } 10\text{nV: } \overline{v_{n(1)}^2} = (10\text{nV})^2 \times \left(\frac{2.7\text{k}\Omega}{2.7\text{k}\Omega + 1.5\text{k}\Omega} \right)^2 = 4.133 \times 10^{-17} \text{ V}^2 \text{ Hz}^{-1}$$

$$\text{Due to } 4\text{pA: } \overline{v_{n(2)}^2} = (4\text{pA})^2 \times \left(\frac{2.7\text{k}\Omega \times 1.5\text{k}\Omega}{2.7\text{k}\Omega + 1.5\text{k}\Omega} \right)^2 = 1.488 \times 10^{-17} \text{ V}^2 \text{ Hz}^{-1}$$

$$\text{Due to } 1.5\text{k}\Omega: \overline{v_{n(3)}^2} = 4kT(1.5\text{k}\Omega) \times \left(\frac{2.7\text{k}\Omega}{2.7\text{k}\Omega + 1.5\text{k}\Omega} \right)^2 = 1.027 \times 10^{-17} \text{ V}^2 \text{ Hz}^{-1}$$

$$\text{Due to } 2.7\text{k}\Omega: \overline{v_{n(4)}^2} = 4kT(2.7\text{k}\Omega) \times \left(\frac{1.5\text{k}\Omega}{2.7\text{k}\Omega + 1.5\text{k}\Omega} \right)^2 = 5.707 \times 10^{-18} \text{ V}^2 \text{ Hz}^{-1}$$

$$\text{Total noise, } \overline{v_{nTh}^2} = \overline{v_{n(1)}^2} + \overline{v_{n(2)}^2} + \overline{v_{n(3)}^2} + \overline{v_{n(4)}^2} = 7.22 \times 10^{-17} \text{ V}^2 \text{ Hz}^{-1}$$

$$\sqrt{\overline{v_{nTh}^2}} = 8.5 \times 10^{-9} \text{ V Hz}^{-1/2} = 8.5 \text{ nV Hz}^{-1/2}$$

- (ii) If v_{nTh}^2 is assumed to be thermal noise generated by a noisy R_{Th} , what is the effective noise temperature of R_{Th} ?

$$4kR_{Th}T_E = 7.22 \times 10^{-17} \text{ V}^2 \text{ Hz}^{-1}$$


$$\therefore T_E = \frac{7.22 \times 10^{-17}}{4 \times k \times 964} = 1356 \text{ K}$$

(3)

The mean square thermal noise voltage generated by a resistor R is $4kTR \text{ V}^2 \text{ Hz}^{-1}$ where $k = 1.38 \times 10^{-23}$. The ambient temperature, T , is 300K throughout the question.

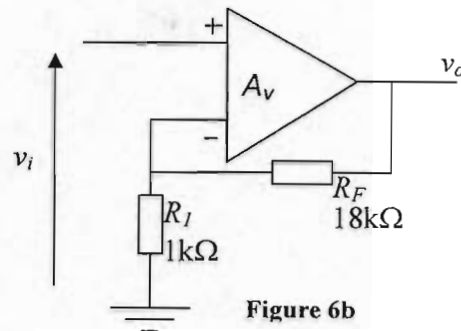- b. (i) The manufacturer's data for the single pole operational amplifier in the circuit of figure 6b specifies a gain bandwidth product of 150MHz, a slew rate of $300\text{V}\mu\text{s}^{-1}$.

What is the small signal upper -3dB frequency of the circuit of figure 6b?



(3)

Assuming $A_v \gg 1$:

$$\text{Gain, } k = 1 + \frac{R_F}{R_i} = 19$$

GBP = 150MHz, therefore:

$$\text{-3dB bandwidth is } \frac{150\text{MHz}}{19} = 7.89\text{MHz}$$

- (ii) What is the maximum frequency that can be amplified by the circuit of figure 1 if a 20V peak to peak sinusoidal output signal is to remain unaffected by slew rate effects? (4)

Slew rate effects occur if maximum rate of change of output voltage exceeds the slew rate.

$$\text{If } v(t) = \hat{V} \sin \omega t, \text{ then } \frac{dv}{dt} = \hat{V} \omega \cos \omega t$$

Max rate of change occurs when $\cos \omega t = 1$.

If peak to peak voltage is 20V, $\hat{V} = 10$.

$$\hat{V} \omega = \text{slew rate, SR} = 300 \times 10^6 = 2\pi \hat{V} f$$

$$\therefore f = \frac{\text{SR}}{2\pi \hat{V}} = \frac{300 \times 10^6}{2\pi \times 10} = 4.77 \times 10^6$$

- (iii) Find the gain magnitude at a frequency of 5MHz (2)

Circuit is first order, so transfer function can be written as:

$$\frac{v_o}{v_i} = \frac{19}{1 + \frac{jf}{7.89\text{MHz}}}$$

$$\text{Therefore at 5MHz, gain magnitude is } \left| \frac{v_o}{v_i} \right| = \left| \frac{19}{1 + \frac{j5\text{MHz}}{7.89\text{MHz}}} \right| = \frac{19}{\sqrt{1 + (0.634)^2}} = 16$$


Section D

Q7
a.

The outputs of a Moore machine depend solely on the current state. Therefore, more states are required, and there will be at least one cycle latency between inputs and outputs.

The outputs of a Mealy machine depend on the current state and the inputs. Therefore, fewer states are required, and there is no latency between inputs and outputs.

2

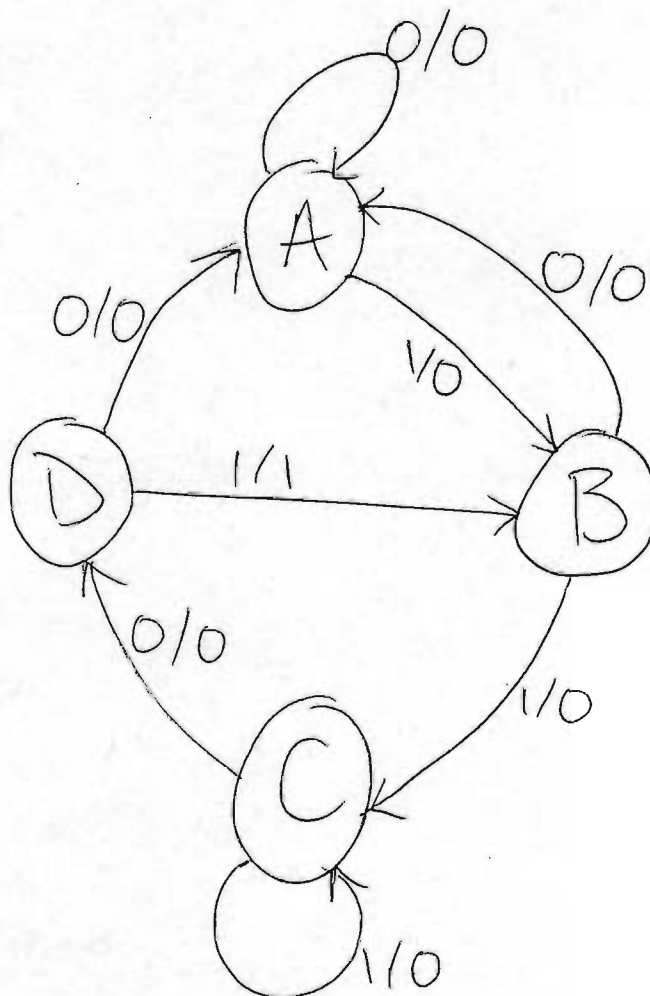b.
(i)

3

Q7

b continued.


(ii)

Present State		Next State				Output	
		Input = 0		Input = 1		Input = 0	Input = 1
Q1	Q0	Q1	Q0	Q1	Q0	Z	Z
0	0	0	0	0	1	0	0
0	1	0	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	0	1	0	1

3

C.

(ii)

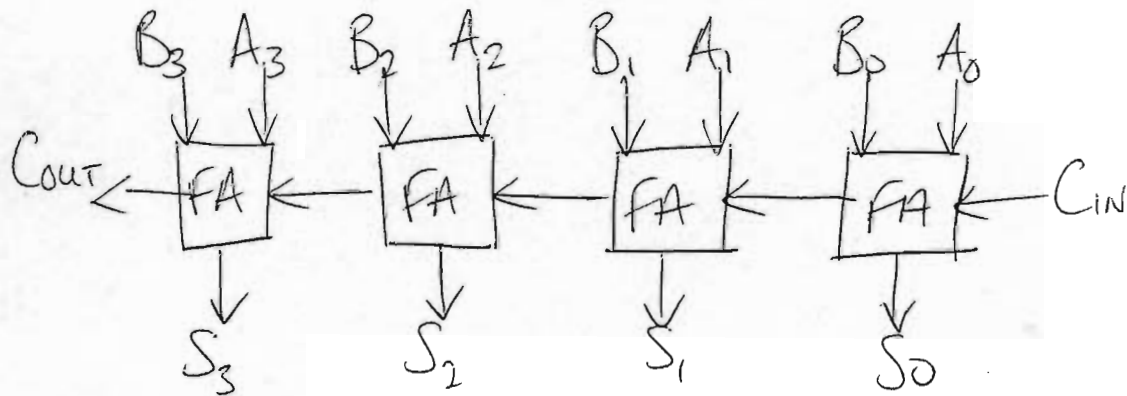

2

(ii) The max propagation delay is from B₀ or A₀ to S₃:

$$\begin{aligned}
 & T_{XOR} + 3(T_{AND} + T_{OR}) + T_{XOR} \\
 &= 0.1 + 3(0.2) + 0.1 \\
 &= 0.8 \text{ ns}
 \end{aligned}$$

2

Q7

C continued.


- (iii) This is known as a ripple carry adder because of the way the carry signal is passed along, or ripples from one adder to the next.

The disadvantage of this is that it has a long propagation delay. This can be overcome by employing a carry lookahead adder.

The carry look ahead adder would not necessarily be of benefit in FPGA technology, as many FPGAs have dedicated support for ripple carry adders.

3

(iv)

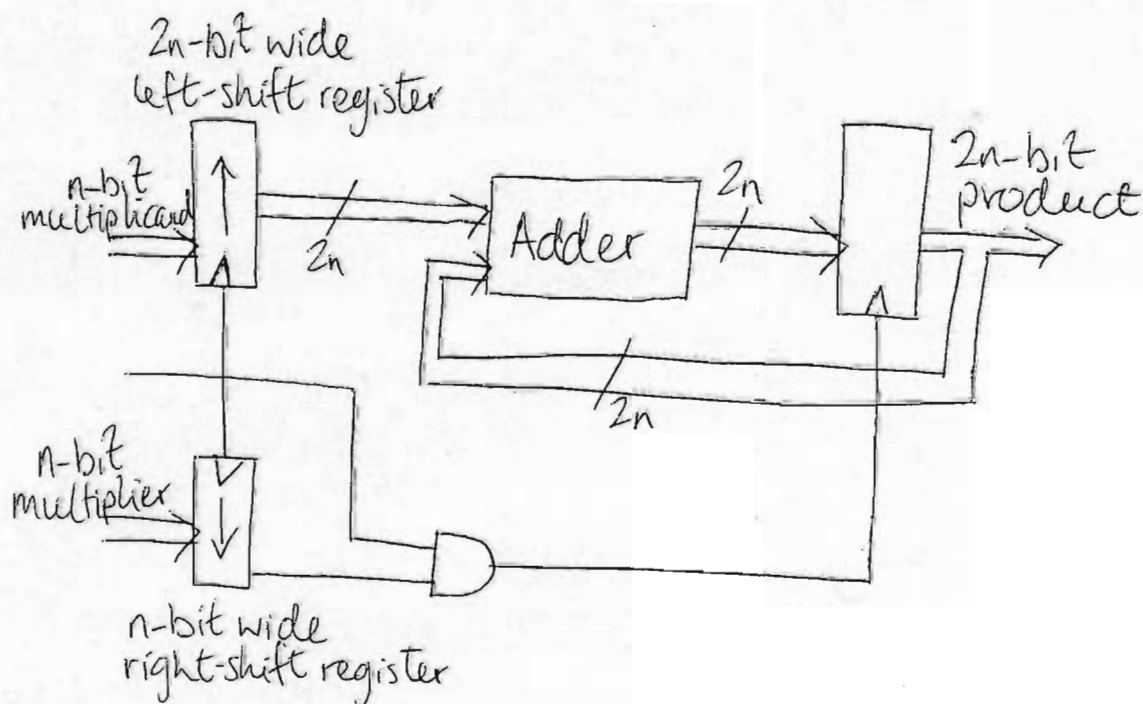

Q7

C (iv) continued.


Initialisation:

- the n -bit multiplicand is loaded into the bottom n bits of the upper shift register, and the top n -bits are loaded with zeros.
 - The n -bit multiplier is loaded into the lower shift register.
 - The output register is loaded with zeros.
- At each stage the current LSB of the multiplier determines whether the current multiplicand value is added to the total.
 - The process takes n clock cycles, excluding initialisation.

5

Q8.

a.

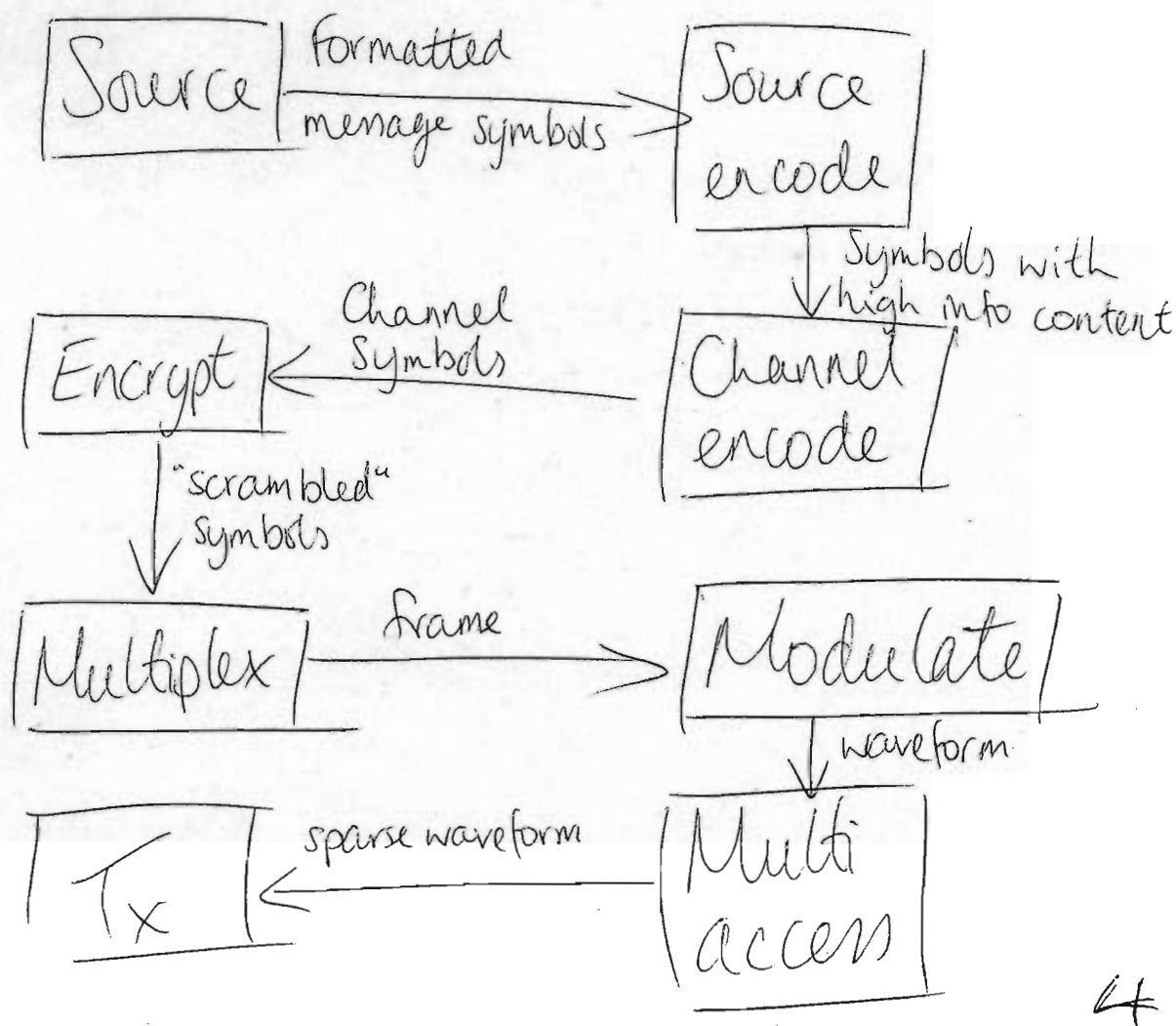

b. (i) Average Codeword Length

$$\begin{aligned}\bar{L} &= 0.4 \times 1 + 0.25 \times 2 + 0.2 \times 3 + 0.1 \times 4 \\ &\quad + 0.05 \times 4 \\ &= 2.1\end{aligned}$$

Compression Ratio

$$CR = 3 / 2.1 = 10/7 \quad 2$$

(ii) Entropy: $\sum_{j=1}^5 P(m_j) \log_2 P(m_j) = 2.041$

$$\text{Coding efficiency} = \frac{2.041}{2.1} \times 100 = 97.2\%$$

Q8.

23

b continued.

(iii)


If the average codeword length is less than the entropy, some of the information will be lost.

Such coding techniques are called "lossy" coding.

2


c.

(i) ASK output for the sequence "101".

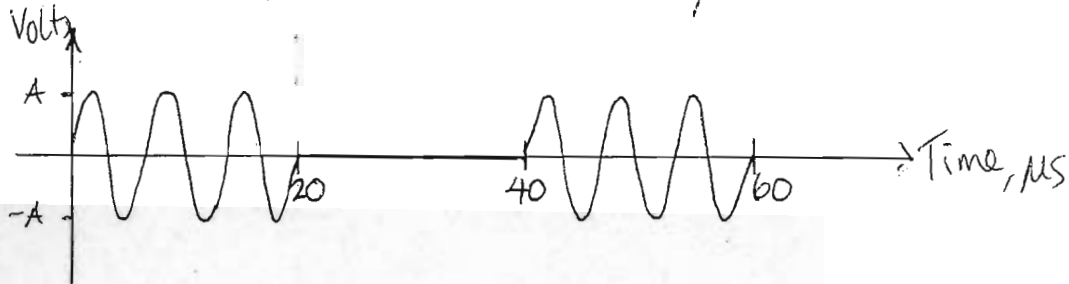


2

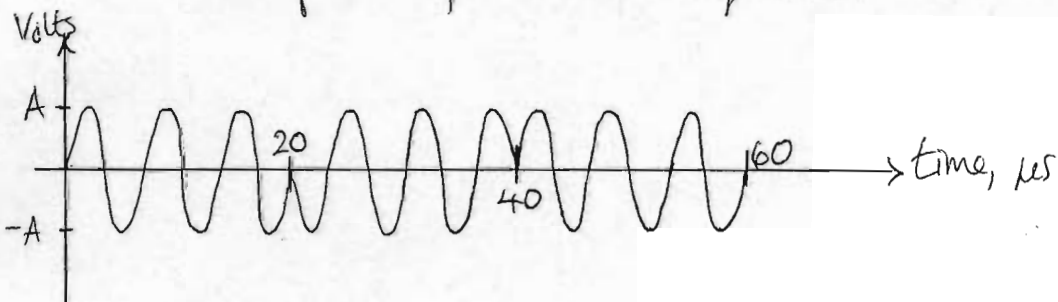(ii) BPSK output for the sequence ~~"101"~~ "101".



2

(iii)

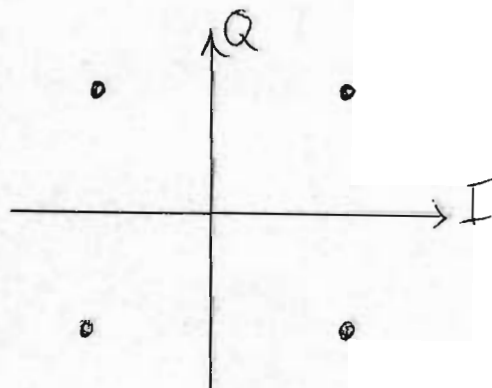

QPSK
Constellation
Diagram


3

Q8.

C continued.

(iv)

QAM16 will achieve higher data rates than 8-PSK.

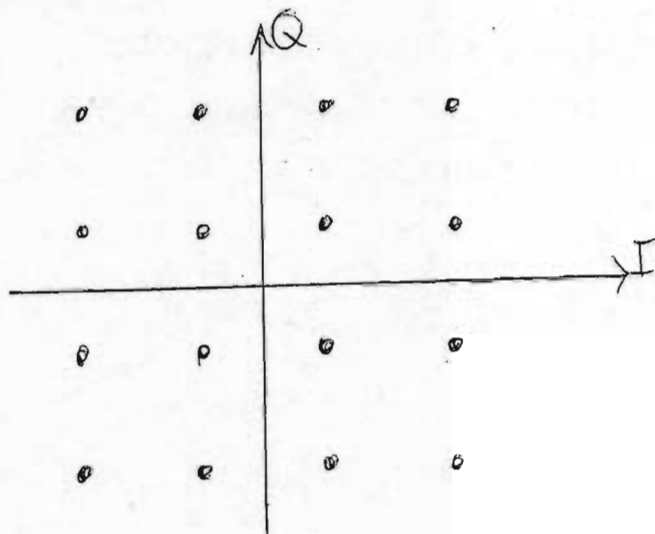

QAM16
Constellation
Diagram

QAM16 is used in modems and digital TV.

3