


## EEE331/EEE6037 exam 2013: exam questions and model solutions

### 1. single BJT circuits

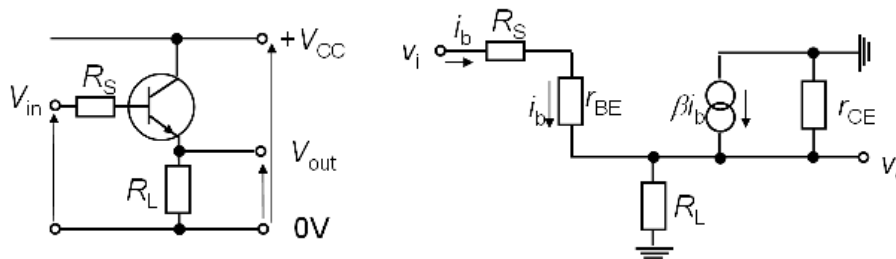- a. Draw the small-signal equivalent circuit for an emitter follower with load resistor  $R_L$  and signal resistor  $R_S$ . Derive an expression for the voltage gain  $v_o/v_i$ , taking into account the resistance of the base-emitter junction,  $r_{BE}$ , and the resistance of the collector-emitter junction,  $r_{CE}$ . Under what conditions does the gain approximate to unity?

Solution:

The small-signal circuit is on the right. As  $r_{CE}$  looks like a connection to ground from a small signal point of view, this means it appears in parallel to the load resistor. The currents are also marked.  $i_b$  denotes the base current.



2 points

output voltage calculation:  $v_o = (r_{CE} \parallel R_L) (\beta + 1) i_b$

input voltage calculation:  $v_i = (R_S + r_{BE}) i_b + (r_{CE} \parallel R_L) (\beta + 1) i_b$

Hence, the voltage gain:  $v_o/v_i = [(\beta + 1) (r_{CE} \parallel R_L)] / [R_S + r_{BE} + (\beta + 1) (r_{CE} \parallel R_L)]$

Here the sign  $\parallel$  stands for parallel connection of resistors according to Kirchoff's Law. For  $R_S \rightarrow 0$  and  $r_{BE} \rightarrow 0$  the expression converges to 1.

3 points

2 points

- b. For the single stage amplifier shown in Figure 1, draw the small-signal equivalent circuit for low frequency operation. State the functions of resistors  $R_1$  and  $R_2$ . Derive an expression for the small signal voltage gain, assuming  $R_1 \gg 1/g_m$ . Show how the expression for the voltage gain can be simplified for large values of  $R_1$  and  $R_2$ .


 


Figure 1

Solution:

The small signal equivalent circuit should look something like

2 points

 

2 points

where  $R_1$  is a feedback resistor connecting input and output and  $R_2$  a bias resistor. Summing all currents at the output node (top right) yields:

$$v_o/(R_L \parallel r_{CE}) + g_m v_{BE} + (v_o - v_{BE})/R_1 = 0$$

Summing all currents at the input node (bottom left) yields:

$$(v_S - v_{BE})/R_S + (v_o - v_{BE})/R_1 - v_{BE}/R_2 - v_{BE}/r_{BE} = 0$$

Both equations can be solved for  $v_{BE}$  and equated:

$$-v_o(1/R_L + 1/r_{CE} + 1/R_1)/(g_m - 1/R_1) = v_{BE} = (v_S/R_S + v_o/R_1)/(1/R_1 + 1/R_2 + 1/R_S + 1/r_{BE})$$

This can be written as (for  $g_m \gg 1/R_1$ ):

$$-v_o/[g_m (R_1 \parallel R_L \parallel r_{CE})] \approx v_S(R_1 \parallel R_2 \parallel R_S \parallel r_{BE})/R_S + v_o(R_1 \parallel R_2 \parallel R_S \parallel r_{BE})/R_1$$

This yields for the voltage gain

$$G = v_o/v_S = -R_1/R_S \times 1/\{1 + R_1/[g_m(R_1 \parallel R_L \parallel r_{CE})(R_1 \parallel R_2 \parallel R_S \parallel r_{BE})]\}$$

For  $R_L \ll R_1, r_{CE}$  and  $R_S \ll R_1, R_2, r_{BE}$  we get

$$G \approx -R_1/R_S \times 1/\{R_1/[g_m R_L R_S]\} = -g_m R_L,$$

as for a standard common emitter amplifier without bias or feedback.

3 points

1 point

- c. Figure 2 shows the circuit of an unbiased single stage amplifier. Identify the type of circuit and state what amplifier class it is, giving reasons for your decisions. Draw small-signal equivalent circuits for both input and output sides when the amplifier in Figure 2 operates at high frequencies. Calculate the cut-off frequency of the amplifier in Figure 2 for a transistor with emitter capacitance and base-collector capacitance of  $C_E = C_{BC} = 20\text{pF}$ , a transconductance of  $g_m = 40\text{mS}$  and a low-frequency current gain of  $\beta_0 = 200$ . Take the Miller effect for the capacitance between input and output into account but neglect  $r_{CE}$ .

 



Figure 2

Solution:

The transistor is connected in common emitter mode (emitter at ground, signal at collector). The lack of a bias means it is operating as class B amplifier (only switched on some time during a voltage input cycle).

The small-signal equivalent circuit for high-frequency transfer should look like

5 points

 

with  $R_S=1\text{k}\Omega$ ,  $R_1=R_2=\infty$  (hence, negligible) and  $R_L=3\text{k}\Omega$ .

voltage gain:  $G = v_o/v_i = -g_m R_L = -40\text{mS} \times 3\text{k}\Omega = -120$

capacitance increase by Miller effect:  $C'_{CB} = (1-G)C_{CB} = 20\text{pF} \times 121 = 2.42\text{nF}$   
 (only for  $C_{CB}$  which bridges the  $g_m v_{be}$  section, not  $C_E$ , as emitter is grounded)

With  $r_{BE}=\beta_0/g_m=5000\Omega$  the cut-off frequency is given by the input side as


$f=\beta_0/[2\pi r_{BE} (C'_{CB}+C_E)] = g_m/\{2\pi [C_{CB}(1+g_m R_L)+C_E]\}=2.61\text{MHz}$

## 2. Early effect and multiple BJTs

- a. Draw a set of common emitter output characteristic curves of  $I_C$  vs.  $V_{CE}$  for four significantly different values of  $v_{BE}$  and include the Early voltage  $V_A$  in your diagram. Describe the physical processes that lead to the Early effect. What would be the output resistance of a BJT without the Early effect?

6 points

Solution:

 

With increasing  $V_{BE}$  the effective base width is reduced. Then more carriers can transit the base per time, because of

- reduced recombination probability and
- increased diffusion gradient, thereby increasing collector current  $I_C$ .

In the output characteristic the result is a finite slope of the set of  $I_C(V_{CE})$  curves that increases with  $V_{BE}$ . Without the Early effect the  $I_C(V_{CE})$  curves would be horizontally flat in the active region, hence the output resistance (i.e. inverse of slope) would be  $\infty$ .

- b. Figure 3 shows an  $N$ -output current mirror. Assume all transistors are matched and have finite small-signal current gain of  $\beta$ . Ignore the effect of finite output resistance. Calculate the ratio of the current at the collector of transistor  $Q_N$ ,  $I_N$ , relative to the input current  $I_{ref}$ . Compare your result to that of a simple current mirror consisting of only two transistors  $Q_{ref}$  and  $Q_1$  where the output is at the collector of  $Q_1$ . How many outputs ( $N$ ) can the current mirror support if the individual output currents current ( $I_N$ ) are to stay within 98% of the reference current ( $I_{ref}$ ) and if  $\beta=200$  is assumed for all transistors?

 


Figure 3

Solution:

At the node just below  $R_{ref}$  apply Kirchoff's Law to the sum of the currents:

$$I_{ref} = I_{C,ref} + I_{b,ref} + I_{b,1} + I_{b,2} + \dots + I_{b,N}$$

5 points

$$= \beta I_b + (N+1)I_b$$

$$= (\beta + N + 1) I_b,$$

because all base currents are identical ( $I_b$ ) and the current gains as well ( $\beta$ ).

At the output we just measure the collector current of transistor  $Q_N$ :

$$I_o = I_{C,N} = \beta I_b$$

The current gain thus is the ratio  $I_o/I_{ref} = \beta/(\beta + N + 1)$

For two transistors the circuit consists of only the reference transistor and  $Q_1$ , hence  $N=1$  in the above equation, which yields  $I_o/I_{ref} = \beta/(\beta + 2)$ . This is identical to the result  $1/(1 + 2/\beta)$  of the simple current mirror discussed in the lecture.

For  $I_o/I_{ref} = \beta/(\beta + N + 1) > 0.98$  we get


$$200/(200 + N + 1) > 0.98 \text{ or } N < 200/0.98 - 201 = 3.08 \dots,$$

i.e. a maximum of  $N=3$  outputs can be supported.

4 points

- c. Sketch the circuit for a class B push-pull amplifier configuration. Draw the voltage characteristic  $V_{out}/V_{in}$  and describe the distortion you would expect. How could the distortion be reduced by biasing to produce a class AB output stage?

Solution:

 

The principle of the class B output stage is an unbiased push-pull complementary pair, as shown on the left with the diodes shorted. Transistor  $T_1$  then follows the dotted line in the right diagram of the voltage characteristic. This leads to a dead band of width  $2V_{BEon}$ , and for input signals between  $-V_{BEon}$  and  $+V_{BEon}$  there will be no output. This causes severe cross-over distortions, particularly for small signals. This is avoided in a class AB stage where  $T_1$  is biased by  $2V_{BEon}$  relative to  $T_2$  such that the dotted curve in the output characteristic shifts left as sketched and continues the straight curve from the output characteristic of  $T_2$  without introducing any distortion of small signals.

5 points


- d. The output characteristic of an emitter coupled pair of BJTs can be written as

$$v_o^{diff} = \alpha I_E R_C \tanh [-v_i^{diff}/(2V_{to})].$$

Define all six parameters in this equation, sketch the curve of  $v_o^{diff}$  as function of  $v_i^{diff}$  and comment on sign, slope and range of the linear approximation.

Solution:

 $V_o^{diff}$  and  $v_i^{diff}$  are differences between output [input] voltages at the collector [base] junctions of the emitter coupled pair,  $\alpha$  is the ratio of collector to emitter current ( $\alpha = \beta/(\beta + 1) \approx 1$ ),  $I_E$  the sum of both emitter currents,  $R_C$  the resistor between each collector and supply rail voltage,  $V_{to}$  the turn-on voltage of the BJTs.



The output characteristic of the emitter coupled pair

- a) inverts the signal,
- b) amplifies small signals by a factor given by the product of  $\alpha I_E R_C$ ,
- c) saturates for larger input values, where there is a trade-off between amplification factor and linear range.

### 3. MOSFETs

3 points

- a. The square law below describes the drain current,  $I_D$ , of a MOSFET as function of gate-source voltage,  $V_{GS}$ :

$$I_D = 0.5 \mu C_{ox} (W/L) (V_{GS} - V_{to})^2 (1 + V_{DS}/V_A)$$

where  $V_{to}$  is a threshold voltage,  $V_{DS}$  the drain-source voltage and  $V_A$  the Early voltage.  $\mu$ ,  $C_{ox}$ ,  $W$  and  $L$  are device parameters. Derive an expression for the mutual conductance  $g_m$  in the active region. State how drain current and over-voltage influence the mutual conductance.

Solution:

mutual conductance:

$$g_m = \partial I_D / \partial V_{GS} = \mu C_{ox} W/L (V_{GS} - V_{to}) (1 + V_{DS}/V_A) = 2I_D / (V_{GS} - V_{to}) = 2I_D / V_{ov}$$

To maximise the mutual conductance and thus the voltage gain in common source configuration, a MOSFET should be operated with a drain current and a small over-voltage, i.e. by a gate-source voltage just above the turn-on voltage.

6 points

- b. Figure 4 shows a MOSFET circuit called centroid layout. Draw the circuit diagram corresponding to the figure, explain how the transistors are interconnected and describe the function of the circuit. What are the advantages and disadvantages of this layout compared to a simple layout using only two transistors?


 


Figure 4

Solution:

 

Transistors M1 and M4 are connected in parallel and do exactly the same, and the same is true for M2 and M3. The circuit is a differential amplifier, as can be seen from the source electrodes connected to a common source and the differential signals being fed into opposite base electrodes. For such differential amplifiers it is important to minimise any mismatch between the two signal paths. Failure to do

this would yield non-zero offsets, thereby increasing the common-mode signal and decreasing the common mode rejection ratio (CMRR).

Replacing single transistors by pairs of transistors at opposite positions on the substrate automatically eliminates linear process gradients, such as variations of gate oxide thickness, that can be decomposed into x- and y-components. The result is a higher CMRR and lower temperature dependence of the performance. The disadvantage is the longer connection lines needed for cross-connection.

- c. Describe the function of each transistor ( $Q_1$ ,  $Q_2$  and  $Q_3$ ) in the circuit shown in Figure 5. Explain the advantage of combining BJTs with a MOSFET in this circuit.

 


Figure 5

4 points

Solution:

This circuit is a second-level BICMOS cascode. BJT  $Q_1$  provides a high transconductance and thereby translates the small input voltage into a large current  $I_C$ , BJT  $Q_2$  ensures that the common emitter stage of  $Q_1$  sees only a resistive load of  $r_{BE2} \ll R_L$ , thereby reducing gain and Miller effect, and MOSFET  $Q_3$  enhances the finite output resistance of the circuit by a factor  $A_{o3}$ .  $R_L$  then translates the current  $I_C$  back into a voltage signal  $V_o = V_{DD} - I_C R_L$ .

7 points

- d. Transistor  $T_1$  in the emitter follower of Figure 6 is biased by a quiescent current  $I_Q$  supplied by transistor  $T_2$ . What class of amplifier output stage is this? For a sinusoidal input voltage  $V_i$ , sketch the waveforms for the full range of output voltage, output current and instantaneous power as a function of time. You may neglect  $V_{CE,sat}$ . Derive an expression for the power conversion efficiency of this output stage amplifier.




 


Figure 6

Solution:

Because of the biasing by a constant current source this is a class A amplifier. For the output signals we get  $V_{CE1} = V_{CC}(1 + \sin \omega t)$  and  $I_{C1} = I_Q(1 - \sin \omega t)$ , which yields for the instantaneous power dissipation:
 
$$P_{C1} = V_{CE1} I_{C1} = V_{CC} I_Q \cos^2 \omega t = \frac{1}{2} V_{CC} I_Q (1 + \cos 2\omega t)$$



Average output power delivered to load:

$$P_L = \langle V_o \rangle \langle I_o \rangle = \frac{1}{2} V_o^{\max} I_o^{\max} \text{ with}$$

$$V_o^{\max} = V_{CC} - V_{CEsat}$$

$$I_o^{\max} = V_o^{\max} / R_L = I_Q, \text{ hence}$$

$$P_L^{\max} = \frac{1}{2} (V_{CC} - V_{CEsat}) I_Q$$

On the other side, the power drawn from the supply is

$$P_{sup} = V_{CC} (I_o + I_Q) \text{ where } \langle I_o \rangle = I_Q, \text{ hence } \langle P_{sup} \rangle = 2 V_{CC} I_Q$$

The ratio is the power conversion efficiency:

$$\eta = P_L^{\max} / \langle P_{sup} \rangle = \frac{1}{4} (1 - V_{CEsat} / V_{CC}) \leq 25\%$$

#### 4. Filters

6 points

- a. State what class of filter is shown in Figure 7. Using qualitative arguments, describe the frequency behaviour of the filter. Draw the leap-frog structure diagram of the filter, deriving equations for the voltages and currents of all components in your leap-frog diagram.


 


Figure 7

Solution:

 The filter is a 3<sup>rd</sup> order LC band-pass filter. It acts as band-pass because  $C_2$  effectively blocks DC signals which  $L_1$  then shortens to ground, while  $C_3$  shortens high-frequency signals to ground. In both cases  $V_o=0$ . The leap-frog structure would look like the following:



With input and output resistors there are 5 components. For each of them we can write down two equations, one from Ohm's Law and one from Kirchhoff's Law. Hence, there are 10 equations to describe the interdependence of 4 voltages  $V_s$  and  $V_{1-3}$  ( $V_i$  and  $\omega$  are given,  $V_o=V_4=V_3$ ) and six currents  $I_s$ ,  $I_{1-4}$  and  $I_L$ . So it is possible to calculate the output voltage  $V_o$  for any given set of  $V_i$  and  $\omega$ .

- (i)  $V_s = I_s R_s$ ;  $V_s = V_i - V_1$
- (ii)  $V_1 = I_1 s L_1$ ;  $I_1 = I_s - I_2$
- (iii)  $V_2 = I_2 / (s C_2)$ ;  $V_2 = V_1 - V_3$
- (iv)  $V_3 = I_3 / (s C_3)$ ;  $I_3 = I_2 - I_4$
- (v)  $V_4 = I_L R_L$ ;  $I_L = I_4$

5 points

- b. Determine the transfer function of the circuit shown in Figure 8. Write down expressions for its zeros and poles. What classification of filter is it? Compare the pole frequency to the time constant of the RC network.

 


Figure 8

Solution:

The transf function is defined as the ratio of output to input voltage, i.e.  $T(s) = V_o(s)/V_i(s)$

With complex impedances  $Z$  and admittances  $Y=1/Z$  we get for current  $I$ :

$$T(s) = Z_o(s) I / [Z_i(s) I] = Y_i(s) / Y_o(s)$$

The admittance for short circuited output is simply:  $Y_i = sC_1$ , as both  $C_2$  and  $R$  appear short circuited.

The admittance for short circuited input is:  $Y_o = sC_1 + sC_2 + 1/R$ , as all components appear in parallel connection.

Thus we get:

$$T(s) = sC_1 / [sC_1 + sC_2 + 1/R] = sRC_1 / [1 + sR(C_1 + C_2)]$$

This function is a first-order network. It acts as band-pass filter with a zero for  $s=0$  and converges to  $\lim_{s \rightarrow \infty} T(s) = C_1 / (C_1 + C_2)$ . It has one pole  $-\omega_0$  at the pole frequency  $\omega_0 = 1/[R(C_1 + C_2)]$ . This is the inverse of the time constant  $\tau = RC_{\text{eff}}$  for two capacitors  $C_1$  and  $C_2$  in parallel connection ( $C_{\text{eff}} = C_1 + C_2$ ).

6 points

- c. For the transfer function below write down the location of the poles and zeros and sketch the magnitude of the Bode plot:

$$T(s) = \frac{10s^2}{(1 + s/10^1)(1 + s/10^4)(1 + s/10^6)}$$

Name the order and the classification of filter. What is the transition frequency of unity gain?

Solution:

zeros:  $s=0$  and  $s=\infty$

poles:  $s=-10^1$ ,  $s=-10^4$  and  $s=-10^6$

The Bode plot can be obtained from the multiplicative superposition of four curves for

(i)  $T(s)=10s^2$ , which is a straight line through (1rad/s, 0db) of slope +40dB/decade.


(ii)  $T(s)=1/(1+s/10^1)$  gives two asymptotes intersecting at  $\omega=10^1$ .

(iii)  $T(s)=1/(1+s/10^4)$  gives two asymptotes intersecting at  $\omega=10^4$ .

 (iii)  $T(s)=1/(1+s/10^6)$  gives two asymptotes intersecting at  $\omega=10^6$ .

This is a 3<sup>rd</sup> order band-pass filter. The transition frequency is

$$f_t = \omega_t / (2\pi) = 15.9 \text{GHz}.$$



3 points

- d.** Explain the principle stages within a typical three-stage operational amplifier. Name all three basic stages, explain their function and briefly discuss possible methods of implementation.

Solution:

A typical 3-stage operational amplifier consists of

- i) a differential input stage for high differential gain and good CMRR
- ii) an intermediate stage with high voltage gain, either as differential pair or emitter (source) follower cascode
- iii) an output stage in push-pull configuration with low output impedance and high output current (high current gain)