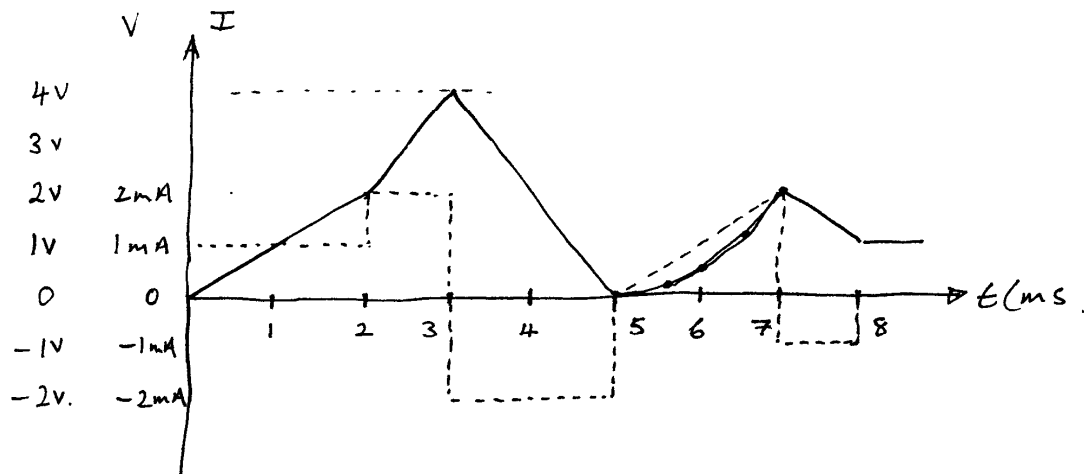


Q1 (i)



In this question, the evolution of charge in the capacitor is the area exposed under the current time graph as t increases. When I is constant, area increases at a constant rate with respect to time. Charge in and voltage across the capacitor are related by $Q = CV$
or $\Delta Q = C \Delta V$.



The only slightly tricky bit is between $t = 5 \text{ ms}$ + $t = 7 \text{ ms}$. Here the area does not change linearly with time; instead it follows a quadratic relationship. The waveform can be sketched by working out the area between 5 ms + 5.5 ms ($= 0.125 \mu\text{C}$), between 5 ms + 6 ms ($0.5 \mu\text{C}$), between 5 ms + 6.5 ms ($= 1.125 \mu\text{C}$) and between 5 ms and 7 ms ($= 2 \mu\text{C}$). Alternatively, if you are good at maths, you can say that between 5 ms + 7 ms $I(t) = t$ (taking 5 ms as the time origin).

$$\text{so } V_C \Big|_{5 \text{ ms} - 7 \text{ ms}} = \frac{1}{C} \int_0^{2 \text{ ms}} t \, dt + V_{\text{initial}}$$

$$= \frac{1}{C} \left[\frac{t^2}{2} \right]_0^{2 \text{ ms}} + V_{\text{initial}}.$$

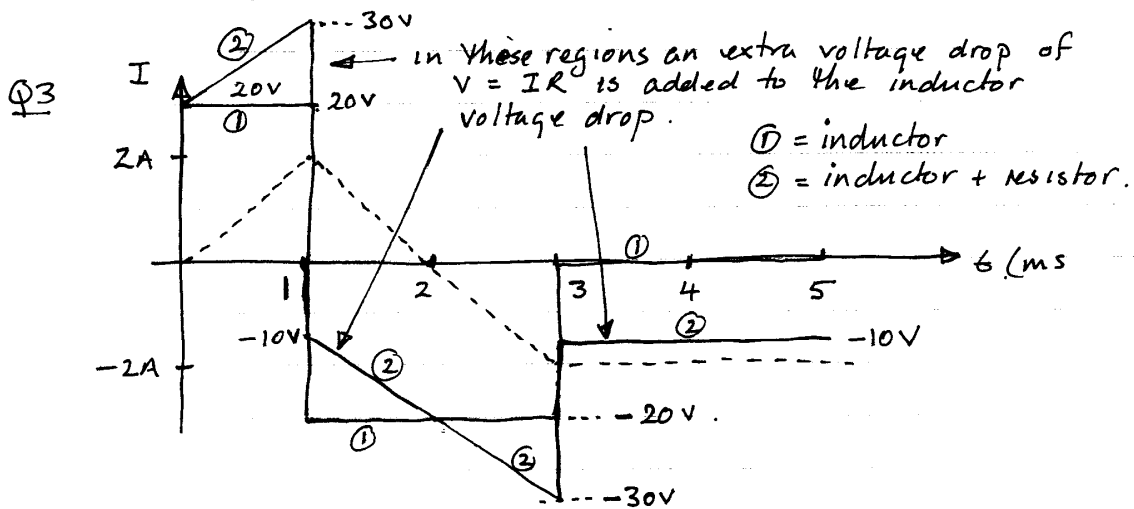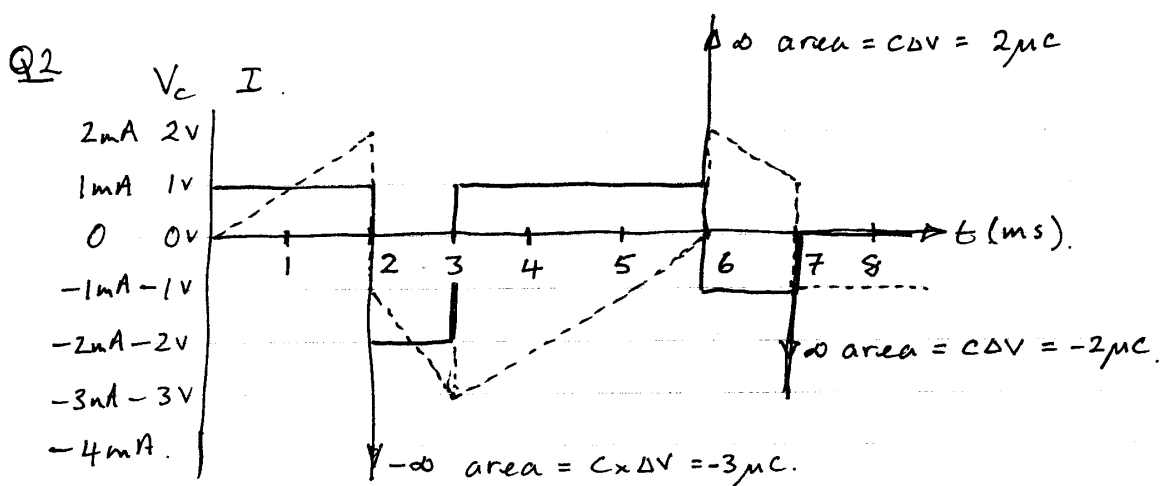(ii) The total +ve area = $6 \mu\text{C}$; total -ve area = $5 \mu\text{C}$.


$$\text{net area @ } 8 \text{ ms} = 6 \mu\text{C} - 5 \mu\text{C} = \underline{\underline{1 \mu\text{C}}}.$$



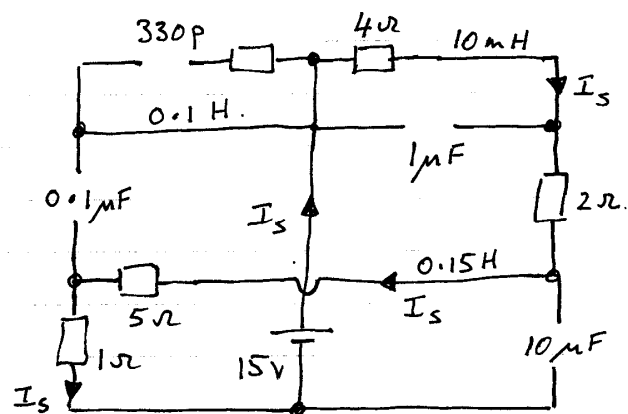Q4 The path of I_s is indicated on the diagram. The total resistance of that path is

$$4 + 2 + 5 + 1 = 12\Omega$$

$$\therefore I_s = \frac{15V}{12\Omega} = 1.25A$$



To find the stored energies, the voltage across each C must be worked out and the current through each L must be worked out.....

Consider the inductors

10mH and 0.15H carry I_s so their stored energies are

$$E_{10\text{mH}} = \frac{1}{2} \cdot 0.01 \times 1.25^2 = \underline{7.8\text{mJ}}.$$

$$E_{0.15\text{H}} = \frac{1}{2} \cdot 0.15 \times 1.25^2 = \underline{117\text{mJ}}.$$

The 0.1H inductor carries a current of zero so ...

$$E_{0.10\text{H}} = \underline{0\text{J}}.$$

Consider the capacitors

The 330pF capacitor has zero volts across it

$$E_{330\text{pF}} = \underline{0\text{J}}$$

The 1 μ F capacitor has a voltage drop across it of $I_s \times 4\Omega$, ie 5V

$$E_{1\mu\text{F}} = \frac{1}{2} \cdot 10^{-6} \cdot 5^2 = \underline{12.5\mu\text{J}}$$

The 0.1 μ F capacitor has 15V on its top terminal and $I_s \times 1\Omega$ on its bottom terminal giving a voltage difference of $15 - 1.25 = 13.75\text{V}$.

$$E_{0.1\mu\text{F}} = \frac{1}{2} \cdot 0.1\mu\text{F} \times 13.75^2 = \underline{9.45\mu\text{J}}.$$


The 10 μ F capacitor has across it the voltage generated by I_s flowing through the $5\Omega + 1\Omega$ resistors

$$E_{10\mu\text{F}} = \frac{1}{2} \cdot 10^{-5} \cdot 7.5^2 = \underline{281\mu\text{J}}.$$

Note that in this circuit the inductors are storing much more energy than the capacitors. If the resistors were all changed to k Ω instead of Ω , the capacitor energy storage would remain the same but the inductor stored energies would be a factor of 10^6 times smaller than they are here — ie nJ instead of mJ. Inductors make very effective energy stores in low voltage high(ish) current applications.

Q5

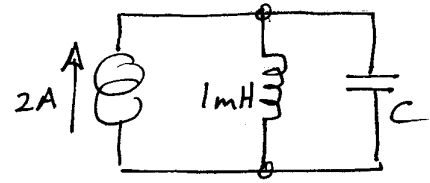(i) Since the 2A is steady and
 $V_L = L \frac{dI}{dt}$, $\frac{dI}{dt} = 0$ and $V_L = 0$



(ii) Energy stored in the inductor
 is $E_{1mH} = \frac{1}{2} \cdot 10^{-3} \cdot 2^2$
 $= 2mJ$

(iii) There is no voltage across the capacitor so
 $E_C = 0 J$.

(iv) $E_C = \frac{1}{2} C V^2 = 2mJ$

$$\text{so for } 1nF \quad V^2 = \frac{2 \times 2mJ}{1nF} = 4 \times 10^6$$

$$\therefore V_{Cmax} = \sqrt{4 \times 10^6} = \underline{2kV}$$

$$\text{for } 10nF \quad V^2 = \frac{2 \times 2mJ}{10nF} = 400 \times 10^3$$

$$V_{Cmax} = \sqrt{400 \times 10^3} = \underline{632 V}$$

$$\text{for } 100nF \quad V^2 = \frac{2 \times 2mJ}{100nF} = 40 \times 10^3$$

$$V_{Cmax} = \sqrt{40 \times 10^3} = \underline{200 V}$$