

Electronic Devices in Circuits Tutorial Sheet

Operational Amplifiers

Q1 An operational amplifier is connected as shown in figure 1. The input offset voltage, v_{os} , is 5mV, the input offset current, i_{os} , is 200nA and the input bias current, which flows into the amplifier inputs, is 400nA.

- (i) What range of output voltages could occur if v_i is grounded? (1.005V to -0.205V)
- (ii) If both v_{os} and i_{os} were zero what would the output voltage be? (0.4V)
- (iii) What value of resistor should be connected between the non-inverting input and ground to make the answer to part (ii) = 0? (9.9k Ω)
- (iv) If the resistor calculated in part (iii) is connected, suggest a modification to the values of all three resistors in the circuit such that the circuit gain remains unchanged but the effects of i_{os} are reduced by a factor of 10. (1k Ω , 100k Ω , 990 Ω)
- (v) If the bipolar input op-amp of figure 1 was replaced by a FET input op-amp, which of the terms, v_{os} , i_b and i_{os} would be the dominant contributor to the output offset voltage?

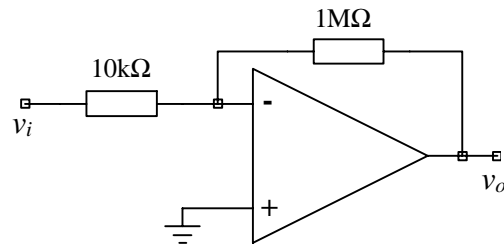


Figure 1

Q2 Derive an expression for the gain-bandwidth product of the circuit of figure 2. (*You should find that this inverting amplifier connection behaves slightly differently from the non-inverting case covered in the lecture notes.*)

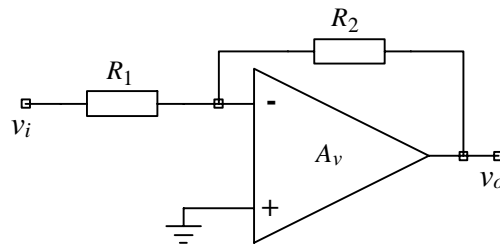


Figure 2

Q3 In medical impedance imaging systems small voltages on the surface of a body are sensed by buffer amplifiers with a very high input impedance. If an op-amp voltage follower circuit is to be used as a sense amplifier which must not introduce a phase error greater than 0.1° at a frequency of 50kHz, what gain-bandwidth product is required of the op-amp? (28.6MHz)

Q4 A particular op-amp for which you have no data is observed to have a step response of the form:

$$k (1 - e^{-t/2.8 \times 10^{-6}})$$

when wired to give a non-inverting gain of 250V/V.

- (i) What is the gain-bandwidth product of the op-amp? (14.2MHz)
- (ii) What 3dB bandwidth would you expect for a non-inverting gain of 10V/V? (1.42MHz)
- (iii) What circuit risetime would you expect for the non-inverting gain of 10V/V? (246ns)

Q5 A non-inverting amplifier circuit with a gain of 10V/V uses an op-amp with a slew rate of 25V/ μ s and a gain-bandwidth product of 15MHz.

- (i) Evaluate $| \text{gain} |$ and phase shift of the amplifier at a frequency of 5MHz. (2.87, -73°)
- (ii) What is the maximum frequency at which a 20V pk-pk sinusoidal output can be supported in undistorted (ie purely sinusoidal) form? (398kHz)
- (iii) At what amplifier circuit gain would the exponential shape of the rising and falling edges of a 15V pk-pk "square wave" output begin to be affected by the amplifier's slew rate capabilities? Would the exponential shape of the edges be affected by a gain of half this value? (56, Yes)
- (iv) Why is the answer to part (iii) independent of the fundamental frequency of the square wave?

Q6 For the circuit of figure 6, show that

$$v_o = \frac{2}{CR} \int v_i dt$$

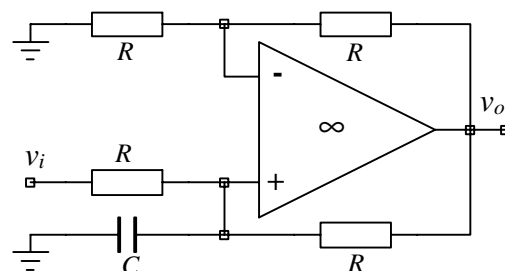


Figure 6

- Q7** Demonstrate that the finite gain defect of the op-amp in figure 7a can be represented by the equivalent circuit of figure 7b where the op-amp is ideal. (This process expresses the effects of finite A_v in terms of normal circuit elements and thus makes them easier to interpret.) **Hint:** approach the problem by showing that both circuits have the same transfer function.

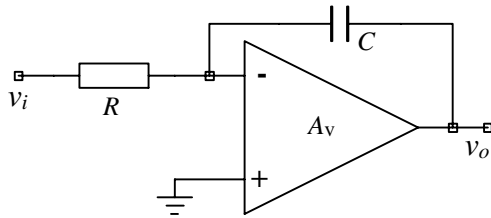


Figure 7a

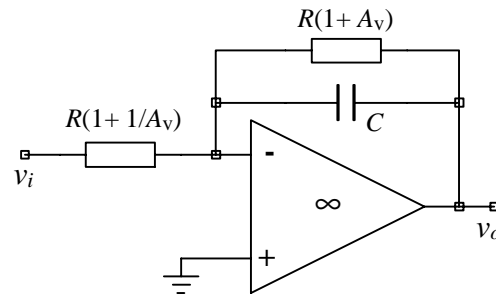


Figure 7b

- Q8** Choose values of R_2 , R_3 , and C in figure 8 to give pole and zero frequencies of 10Hz and 500Hz respectively and a high frequency gain of 10V/V. Sketch the amplitude and phase response of the system. (4.99M Ω , 91.6k Ω , 3.13nF)

If an RC low pass circuit with a time constant of 79 μ s is attached to the op-amp output, sketch the overall frequency response of the circuit. (The overall response is a close approximation to the equalisation characteristic necessary to get a flat response from a magnetic record player cartridge.)

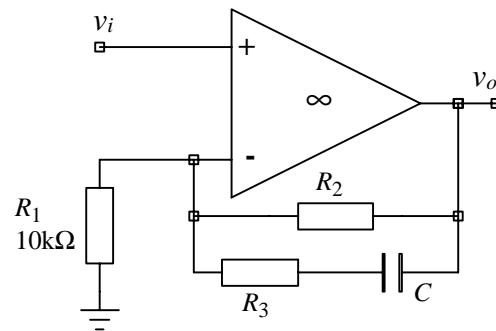


Figure 8