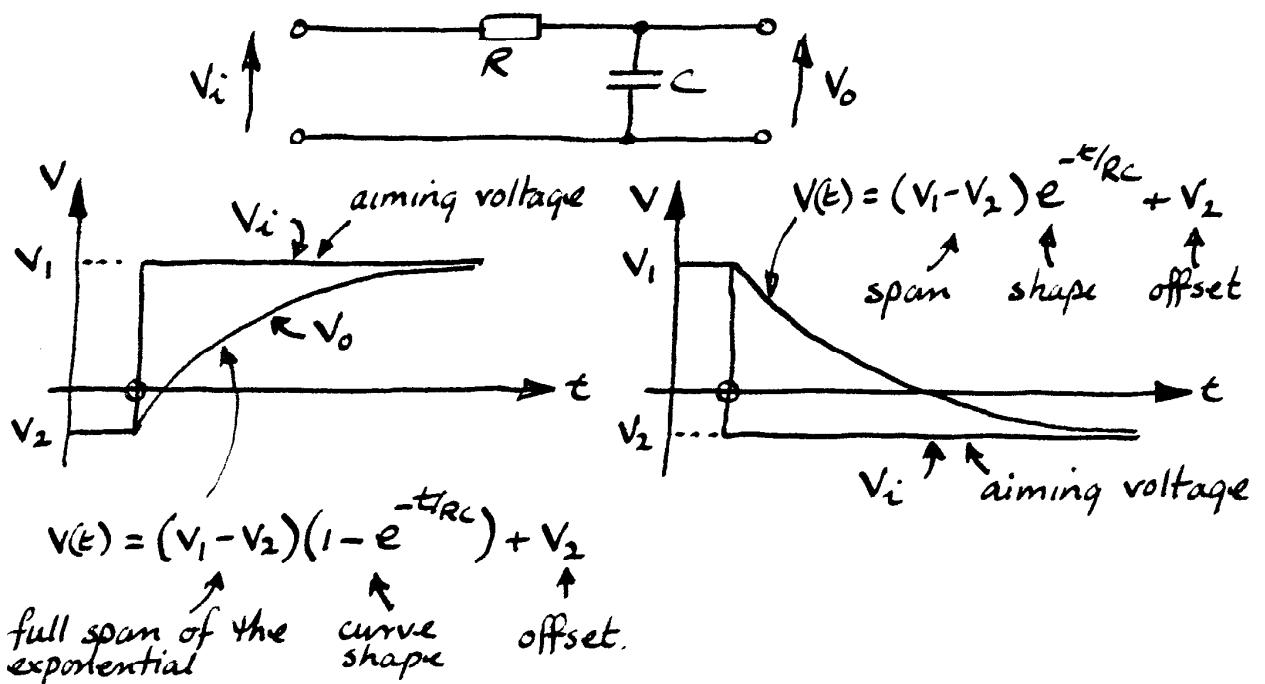


Transient behaviour of first order R-C circuits

- can be derived analytically as done in the Passive Networks course.
- analytical approaches are not much help when it comes to understanding how a circuit works. For this one needs to be able to visualise the behaviour of R-C circuits. You should aim to become as familiar with the behaviour of voltage and current in an R-C circuit driven by transient signals as you are with ohms law.
- all first order R-C circuits will have a transient response involving $e^{-t/RC}$

(1) "low pass" or "simple integrator" circuit




RC is called "time constant", τ . Units = seconds

$$\left[RC = \text{ohms} \times \text{farads} = \frac{\text{volts}}{\text{amps}} \times \frac{\text{coulombs}}{\text{volts}} = \frac{\text{coulombs}}{\left(\frac{\text{coulombs}}{\text{seconds}}\right)} = \text{seconds} \right]$$

$\tau (=RC)$ has some important properties relevant to the geometry of transient responses....


response to a positive going step

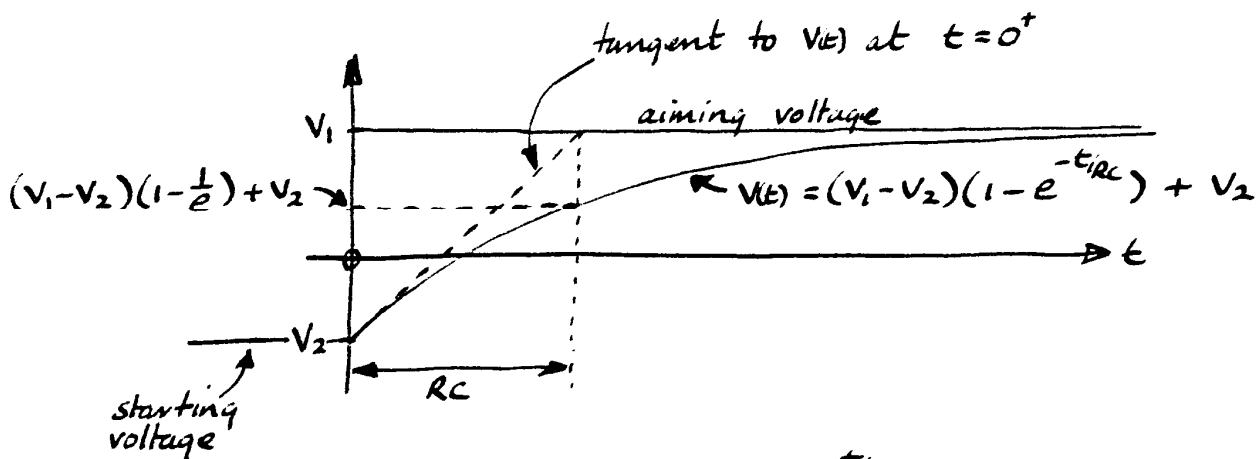

when $t = RC = \tau$, $1 - e^{-t/RC} = 1 - e^{-1} = 1 - \frac{1}{e}$

- after one time constant, the exponential has travelled $(1 - \frac{1}{e}) = 0.63$ (or 63%) of the way from its start voltage, V_2 , to its finish voltage, V_1 .
- a projection of the initial slope of the exponential crosses the aiming voltage at $t = RC = \tau$. (prove this for yourselves).

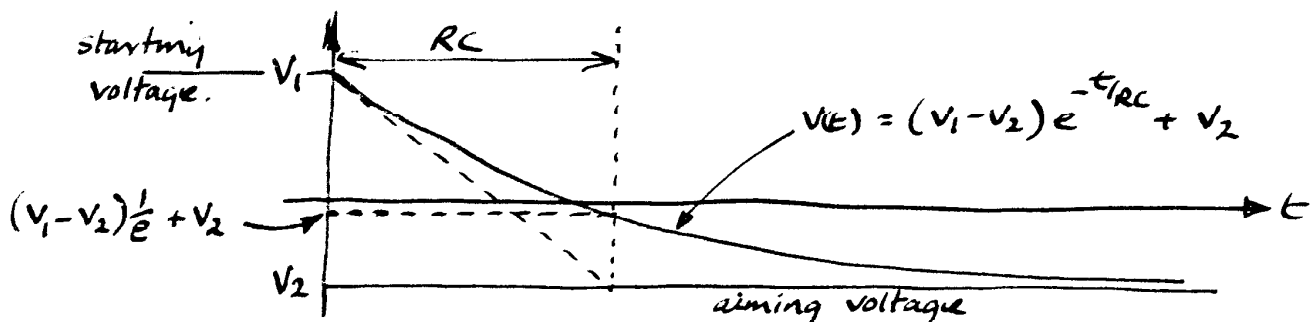
for a negative going step, the geometry is inverted...



- after one time constant, the exponential has travelled 63% of the way from its start voltage to its aiming voltage (it has $\frac{1}{e}$ or 37% of the way still to go)
- as before, a projection of initial slope crosses the aiming voltage at $t = RC = \tau$.
- note that if exponential starts or finishes at 0V, $V_2 = 0$ and the equations are easier.

- knowledge of exponential equation, $V(t)$, describing the behaviour of V_o as function of time enables V_o at given time or time to reach a given V_o to be estimated

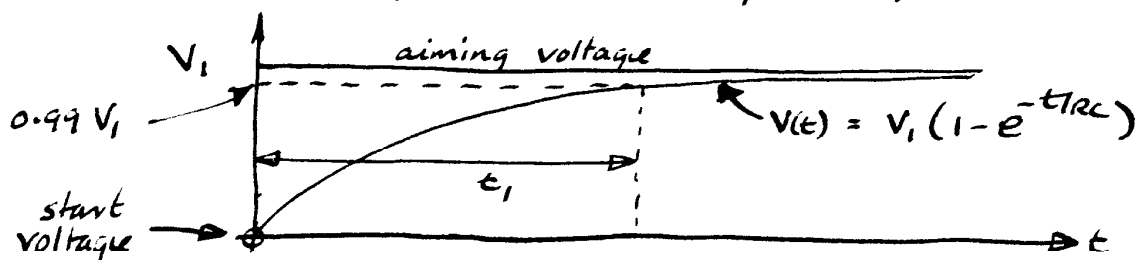eg how long does it take the output voltage of a low-pass R-C circuit to 99% of the way from its start voltage to its aiming voltage?



$$V(t) = V_i(1 - e^{-t/RC})$$

$$0.99 V_i = V_i(1 - e^{-t_1/RC})$$


$$e^{-t_1/RC} = 1 - 0.99 = 0.01$$

$$-t_1/RC = \ln(0.01)$$

$$\frac{t_1}{RC} = \ln\left(\frac{1}{0.01}\right) = \ln(100)$$

$$t_1 = RC \ln(100) = \underline{\underline{4.6 RC}}$$

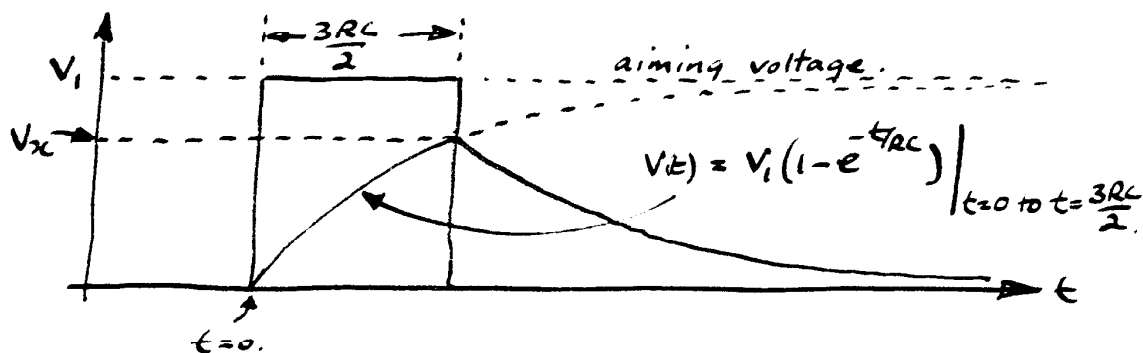eg the input to a low pass RC circuit is a pulse of amplitude V_i and duration $\frac{3RC}{2}$. What is the maximum voltage reached at the output? What is the relationship between V_o and time after the falling edge of the input pulse?





$$V_x = V_i(1 - e^{-\frac{3RC}{2 \cdot RC}}) = V_i(1 - e^{-3/2}) = \underline{\underline{0.777 V_i}}$$

- note that expression for $V(t)$ was based on the voltage the exponential was aiming for, not the voltage at which it was truncated.

for second part, define $t=0$ at falling edge of input pulse...

$$V(t) = (\underbrace{0.777 V_1}_{\text{starting voltage}} - \underbrace{0}_{\text{aiming voltage}}) \underbrace{e^{-t/RC}}_{\text{shape}} + \underbrace{0}_{\text{offset}}$$

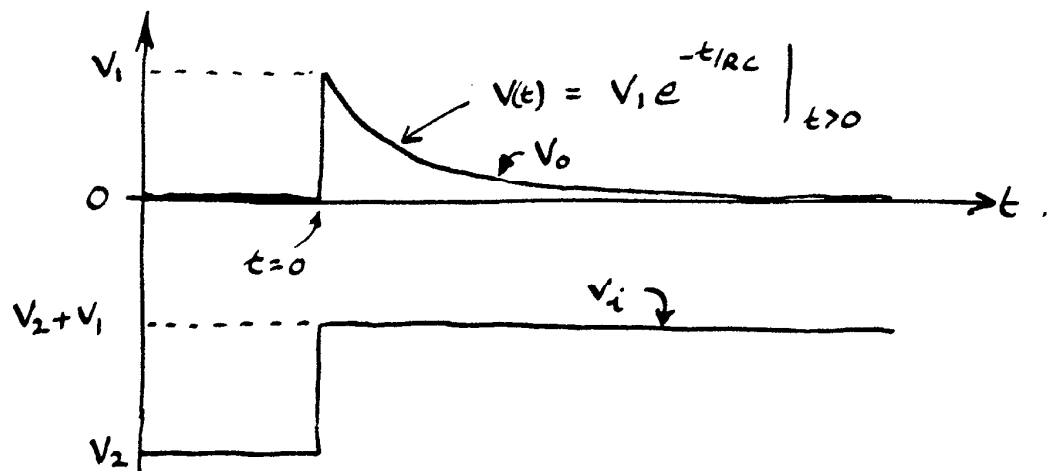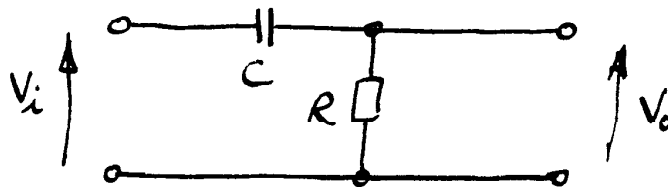
(4) "High-pass" or "simple differentiator" circuit



- notice that V_2 can have any value - it is the height of the step that is important.

- a negative going step will produce an inverted version of the V_o shown above

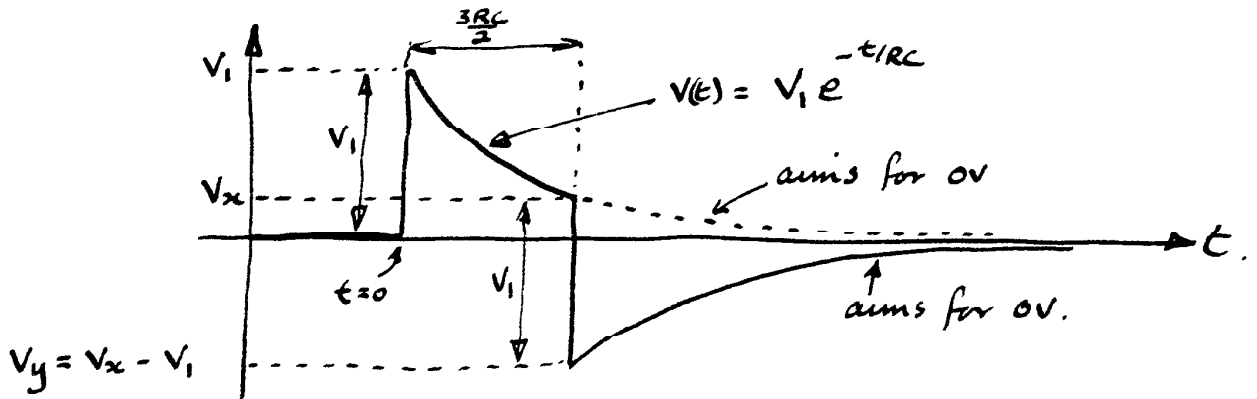eg A high pass RC circuit is driven by an input pulse of amplitude V_i and width $\frac{3RC}{2}$. What is the most negative voltage reached by the output? What is the equation of the exponential following the negative edge of the input pulse?



first find V_x

$$V(t) = V_i e^{-t/RC}$$

$$V(x) = V_i e^{-\frac{3RC}{2}/RC} = V_i e^{-3/2} = 0.223 V_i$$

then find V_y ...

$$\begin{aligned} V_y &= V_x - V_i = 0.223 V_i - V_i \\ &= -V_i (1 - 0.223) \\ &= \underline{\underline{-0.777 V_i}} \end{aligned}$$

to find equation of exponential after falling edge of input pulse, let $t=0$ at falling edge

$$V(t) = [0 - (-0.777 V_i)] [1 - e^{-t/RC}] + (-0.777 V_i)$$


aiming voltage starting voltage shape offset

$$= 0.777 V_i (1 - e^{-t/RC}) - 0.777 V_i$$

$$\left[= -0.777 V_i e^{-t/RC} \text{ which is to be expected since the shape could be regarded as an inverted } e^{-t/RC} \text{ shape} \right]$$

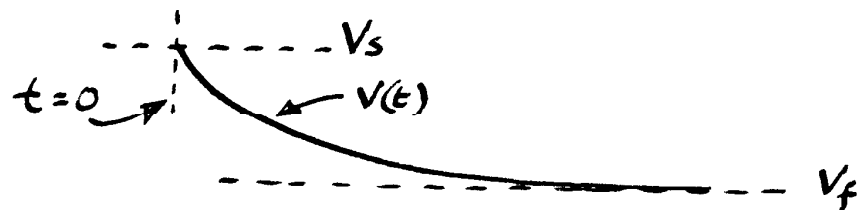(iii) a general approach to both high + low pass


- The main difference between the high + low pass cases is the sign of the exponential term. Rather than defining the two shapes $(1 - e^{-t/\tau})$ and $e^{-t/\tau}$, it is possible to use a general formula based on the $e^{-t/\tau}$ shape which is the fundamental first order response shape.
- Consider an exponential shape starting at V_s and finishing at V_f



$V(t)$ is given by:

$$V(t) = (V_s - V_f) e^{-t/\tau} + V_f.$$

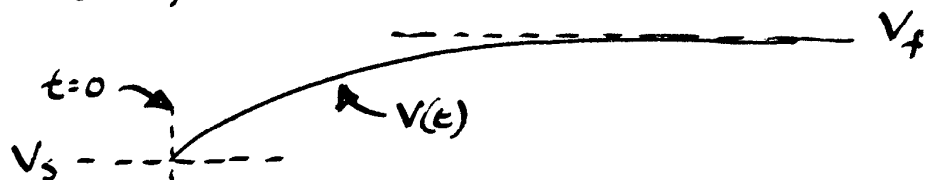This is exactly the same expression as used on pages 1 and 2 for the trailing edge of the low pass response, and on page 4 for the high pass response. If the exponential is redrawn with $V_s < V_f$



The same equation must hold because no condition was placed on the relationship between $V_s + V_f$

$$V(t) = (V_s - V_f) e^{-t/\tau} + V_f$$

this can be written as:

$$\begin{aligned} V(t) &= -(V_f - V_s) e^{-t/\tau} + (V_f - V_s) - (V_f - V_s) + V_f \\ &= (V_f - V_s)(1 - e^{-t/\tau}) + V_s \quad \text{— i.e., the} \end{aligned}$$

same as the equation used on page 1 & 2 to describe the rising exponential of the low pass response.