

Q1 (a)


sum currents at node A

$$I_3 = I_2 + I_1 + 2A$$

$$\frac{5 - V_A}{2\Omega} = \frac{V_A}{1.5\Omega} + \frac{V_A}{3\Omega} + 2$$

$$\frac{5}{2\Omega} - 2 = V_A \left[ \frac{1}{2} + \frac{1}{1.5} + \frac{1}{3} \right] = V_A \cdot 1.5$$

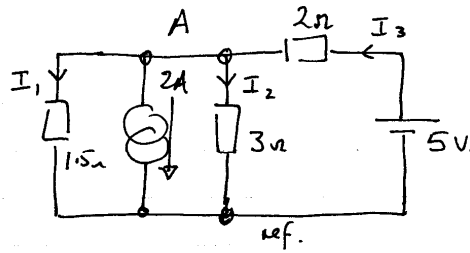
$$2.5 - 2 = V_A \cdot 1.5 \quad \text{or} \quad V_A = \frac{0.5}{1.5} = \underline{\underline{1/3 \text{ V}}}$$



$$V_{(2\Omega)} = 5V - 1/3 V = \frac{14}{3} V$$

$$P_{(2\Omega)} = V^2/R = \frac{14^2}{9} \cdot \frac{1}{2} = \frac{196}{9.2} = \frac{98}{9} = \underline{\underline{10.9W}}$$

(b)

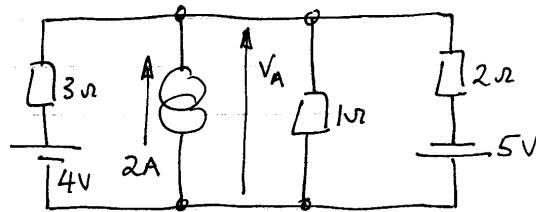

$$V_A|_{4V} = \frac{4(1\Omega // 2\Omega)}{3 + (1\Omega // 2\Omega)} = \frac{4 \cdot 2/3}{3 + 2/3} = \frac{8/3}{11/3} = \frac{8}{11} V$$

$$V_A|_{2A} = 2(3\Omega // 1\Omega // 2\Omega) = 2 \times \frac{1.2}{2.2} = \frac{1.2}{1.1} = \frac{12}{11} V$$

$$V|_{5V} = \frac{-5(3//1)}{2\Omega + (3\Omega // 1\Omega)} = \frac{-5 \cdot 3/4}{2 + 3/4} = \frac{-15/4}{11/4} = -\frac{15}{11} V$$

$$\therefore V_{A \text{ tot}} = \frac{8}{11} + \frac{12}{11} - \frac{15}{11} = \underline{\underline{5/11 V}} \quad (\underline{\underline{0.455V}})$$

Q1 b(i) cont ....

The biggest contributing source is the 5V source

(ii) 4V source.... Since  $V_A < 4V$ , 4V source is driving a current into node A.  $I_{4V} = \frac{(4 - 5/11)V}{3\Omega}$   
 $= \frac{39/11}{3\Omega} = 13/11 \text{ A} =$

$$\therefore P_{(4V)} = 4V \times 13/11 \text{ A} = \underline{4.73 \text{ W}}$$

2A source.... Since  $V_A$  is positive, 2A driving into a positive voltage so....

$$P_{(2A)} = 2 \times V_A = 2 \times 5/11 = \underline{0.909 \text{ W}}$$


5V source.... Since  $V_A$  is positive, current flows from  $V_A$  into the negative side of 5V - a generating direction.  $I_{5V} = \frac{V_A - (-5)}{2} = \frac{5/11 + 5}{2} = \frac{60}{22} = 2.73 \text{ A}$ .

$$P_{(5V)} = 2.73 \text{ A} \times 5 \text{ V} = \underline{13.6 \text{ W}}$$

The sum of these powers should equal the power dissipated in the three resistors - an extra mark to any who check!

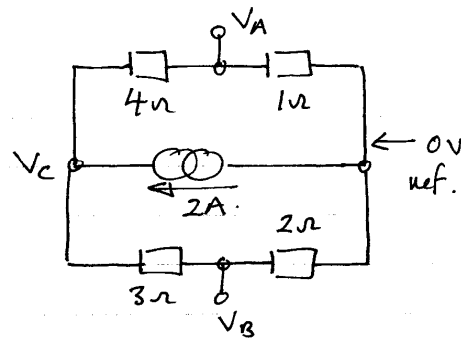Q2 (a)

$$\begin{aligned}
 V_c &= 2A \times (4+1) \parallel (3+2) \\
 &= 2 \times 5 \parallel 5 \\
 &= 2 \times 2.5 = 5V.
 \end{aligned}$$



$$\therefore V_A = \frac{5 \times 1}{1+4} = 1V.$$

$$V_B = \frac{5 \times 2}{3+2} = 2V.$$

$$\therefore V_A - V_B = 1 - 2 = \underline{\underline{-1V.}} = V_{Th}.$$


$$R_{Th} = (1\Omega + 2\Omega) \parallel (4\Omega + 3\Omega)$$

(replace current source by an open circuit and write down resistance between A & B).

$$R_{Th} = 3\Omega \parallel 7\Omega = \frac{21}{10} = \underline{\underline{2.1\Omega}}.$$

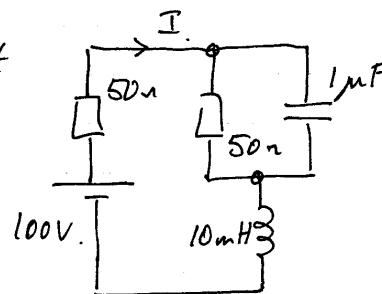(b) (i) C looks like an open ckt  
L " " a short "


$$\therefore I = \frac{100}{50+50} = \underline{\underline{1A}}$$



$$\begin{aligned}
 (ii) E_L &= \frac{1}{2} L I^2 \\
 &= \frac{10^{-2} \times 1}{2} = \underline{\underline{5mJ.}}
 \end{aligned}$$

$$(iii) E_C = \frac{1}{2} C V^2 = \frac{1}{2} 10^{-6} (50V)^2 = \underline{\underline{1.25mJ.}}$$

Q2 (c).

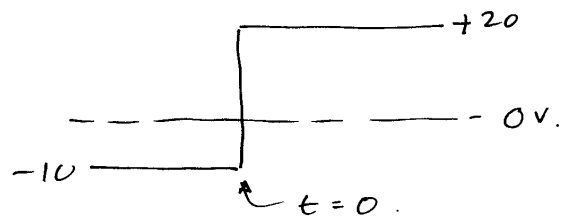(i) at  $t=0^-$   $V_i = -10V$  so ...

$$I = -10/100 = \underline{\underline{-100mA}}$$

$$V_L = 0V \text{ (since } L \text{ looks like a short ckt)}$$

$$V_C = -5V$$

(ii) at  $t=0^+$   $V_i$  becomes  $+20V$ -  $L$  will not allow instantaneous change of  $I$ -  $C$  will not allow instantaneous change of  $V_C$ 

$$\therefore I = -10/100 = \underline{\underline{-100mA}} \text{ (same as } t=0^-)$$

$$V_C = -5V \text{ (same as } t=0^-)$$

$$V_L = 30V \text{ (because if } I \text{ and } V_C \text{ must be the same at } t=0^+ \text{ as they were at } t=0^-, \text{ the voltage difference between } V_i \text{ and the top of } L \text{ must remain the same. Thus if } V_i \text{ rises by } 30V \text{ } V_L \text{ must rise by } 30V \text{ also.)}$$


Q3 (a) (i)

$$Z = \frac{V}{I} = j\omega L + (R \parallel \frac{1}{j\omega C})$$

$$= j\omega L + \frac{R/j\omega C}{R + 1/j\omega C}$$

$$= j\omega L + \frac{R}{1 + j\omega CR} = \frac{j\omega L - \omega^2 LCR + R}{1 + j\omega CR}$$
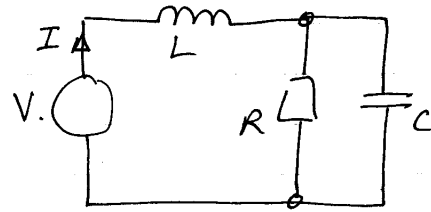
$$= R \left[ \frac{1 - \omega^2 LC + j\omega L/R}{1 + j\omega CR} \right]$$



(ii) For resonance,  $j$  terms must disappear from  $Z$

$$Z = \frac{R(1 - \omega^2 LC + j\omega \frac{L}{R})}{1 + j\omega CR} = \frac{R(1 - \omega^2 LC + j\omega \frac{L}{R})(1 - j\omega CR)}{1 + \omega^2 C^2 R^2}$$

$$= \frac{\text{real} + j\omega(-(1 - \omega^2 LC)CR + \frac{L}{R})}{\text{real}}$$

so to make  $j$  terms disappear....

$$-(1 - \omega^2 LC)CR + \frac{L}{R} = 0$$

$$\text{or } -CR + \omega^2 LC^2 R + \frac{L}{R} = 0$$

$$\omega^2 LC^2 R = CR - \frac{L}{R}$$

$$\omega^2 = \frac{1}{LC} - \frac{1}{C^2 R^2}$$

$$\text{so } \omega = \sqrt{\frac{1}{LC} - \frac{1}{C^2 R^2}}$$

Q3(b)(i)

First find  $Z \dots$ 

$$Z = 3 + j4 + \frac{j10 \cdot -j5}{j10 + (-j5)}$$

$$= 3 + j4 + \frac{50}{j5} = 3 + j4 - j10 = 3 - j6$$

$$= 3(1 - j2) \equiv 6.7 \angle -63.4^\circ$$

$$I = \frac{V}{Z} = \frac{100}{6.7 \angle -63.4^\circ} = \underline{\underline{14.9 \angle 63.4^\circ}}$$

$$\text{or } I = \frac{100}{3(1 - j2)} = \frac{100}{3} \frac{1 + j2}{5} = \underline{\underline{\frac{20}{3}(1 + j2)}}$$

$$V_i = I \frac{j10 \cdot -j5}{j10 + (-j5)} = I \cdot -j10$$

$$= 14.9 \angle 63.4^\circ - 90^\circ = \underline{\underline{14.9 \angle -26.6^\circ}}$$


$$= \frac{20}{3}(1 + j2) \cdot -j10 = \frac{200}{3}(-j + 2)$$

$$= \underline{\underline{\frac{200}{3}(2 - j)}}$$

$$(ii) Z \text{ from above} = \underline{\underline{6.7 \angle -63.4^\circ}}$$

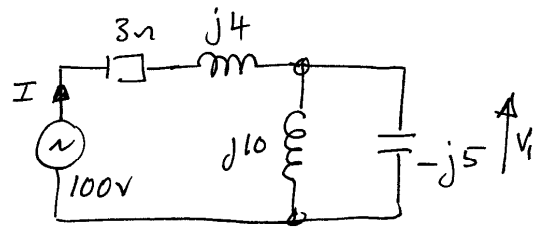
(iii) If  $C$  is  $-j10\Omega$  then  $j10 \parallel -j10 = \infty$  and the parallel combination is resonant.

$$\text{Thus } \underline{\underline{I = 0}} \text{ and } V_i = V_{\text{source}} = \underline{\underline{100V \angle 0^\circ}}$$




Q4 (a) (i) A low pass filter is a circuit that passes low frequencies — i.e. frequencies below a particular frequency and attenuates signals at frequencies above this particular frequency.

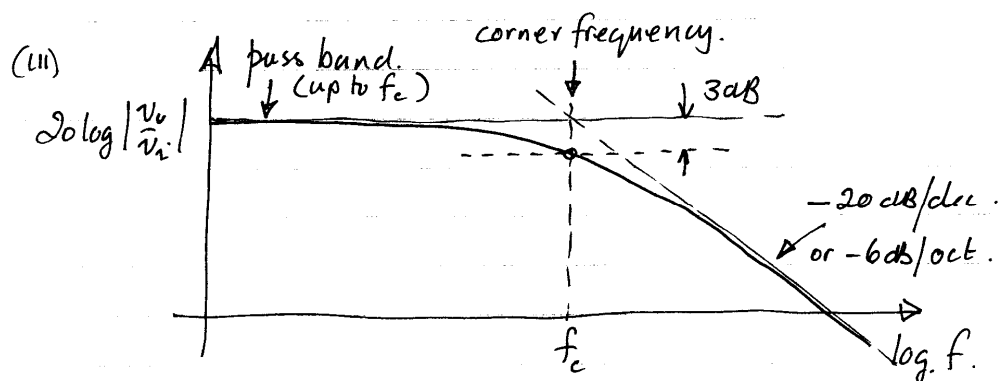(ii) Circuits 4a(ii) and 4a(iii) are low pass filters.



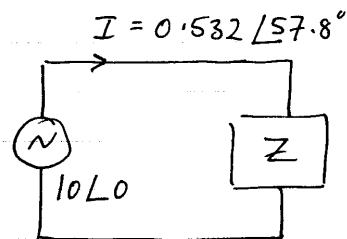(b) If current leads voltage in a series combination of two components by an angle of other than  $90^\circ$ , the two components must be  $R + C$




$$Z = \frac{10}{0.532 / 57.8} = 18.8 \angle -57.8 \approx 10 - j15.9$$

$$10 - j15.9 = R + X_C = R - \frac{j}{\omega C}$$

$$\therefore \underline{R = 10 \Omega} \quad \omega C = \frac{1}{15.9} \quad \text{or} \quad C = \frac{1}{2\pi \cdot 10^3 \cdot 15.9} = \underline{\underline{10 \mu F}}$$

Q4(b) (ii) ...

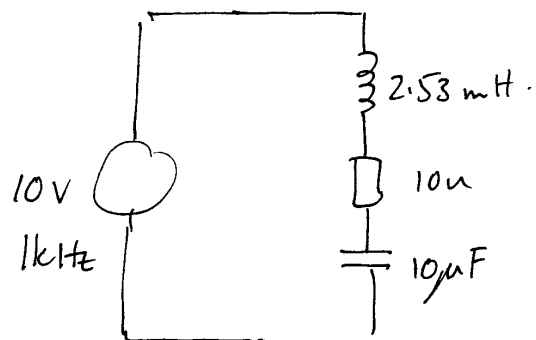

$$Z = j 2\pi \cdot 10^3 L + 10\Omega - \frac{j}{2\pi \cdot 10^3 \cdot C}$$

$$= j15.9 + 10\Omega - j15.9 = 10\Omega$$

$\therefore$  ckt is resonant.

$$I = \frac{10V}{10\Omega} = 1A \quad \therefore P_D = \underline{10W}$$

$$V_L = I X_L = 1A \times 15.9\Omega = \underline{15.9V}$$