


**The University of Sheffield**  
**Department of Electrical and Electronic Engineering**

## EEE117 Homework 7

- Q1.** A pure inductor of value  $4\text{H}$  is connected to a time varying current source in which the current varies as  $i = 5t^2$ .
- (a) Derive an expression for the time variation in voltage
  - (b) Derive an expression for the instantaneous power flowing into the inductor
  - (c) Calculate the total energy stored in the inductor at the end of the interval  $t = 0$  to  $t = 3$  seconds
  - (d) Calculate the average power supplied to the inductor over the period  $t = 0$  to  $t = 3$  seconds
- Q2.** Fill in the blanks in the table for the following loads. Assume phase angle is that of the current with respect the voltage ( $V < 0^\circ$ ) i.e. positive phase angle means the current leads the voltage.

Volt – Amps	Real Power	Reactive Power	Phase Angle	Power Factor
50 kVA				0.8 lagging
	100 W		$+ 45^\circ$	
30 MVA	20 MW			(lagging)
	4 kW	$-3 \text{ kVAR}$		

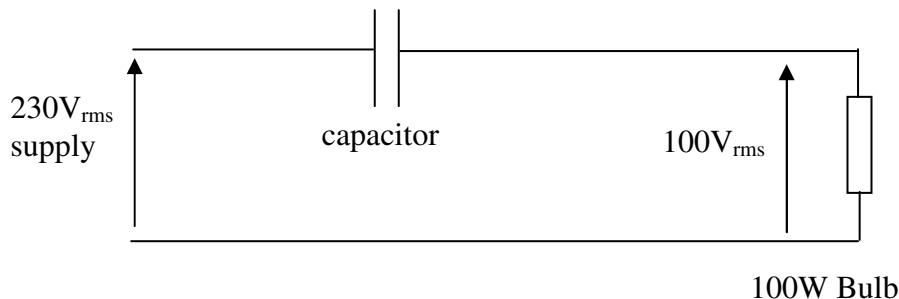- Q3.** A  $100\text{W}$  light bulb, which may be assumed to be a pure resistance, is to be used with a  $230\text{V}_{\text{rms}}$ ,  $50\text{Hz}$  supply. A series capacitor is included in the circuit to reduce the voltage across the bulbs from  $230\text{V}_{\text{rms}}$  to the  $100\text{V}_{\text{rms}}$  required as shown in the figure below.



- (a) Calculate the current required to operate the bulb at its rated voltage and power
- (b) Calculate the voltage across the series capacitor (*hint – it is not  $130\text{V}_{\text{rms}}$* )
- (c) Hence find the value of capacitor required
- (d) Calculate the power-factor of the circuit, and the real and reactive power drawn from the supply.

***Answers should be handwritten. Please remember to include your name or registration number on your answer sheet.***