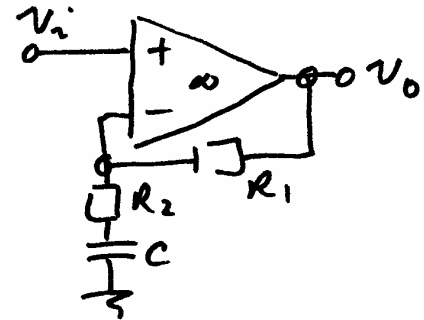


Q1 (i). l.f. gain; $X_c \Rightarrow \infty$

$$\therefore \frac{V_o}{V_i} \Rightarrow 1$$

h.f. gain; $X_c \Rightarrow 0$


$$\therefore \frac{V_o}{V_i} \Rightarrow \frac{R_1 + R_2}{R_2}$$



$$(ii) \quad \frac{V_o}{V_i} = \frac{Z_1 + Z_2}{Z_2} = \frac{R_1 + R_2 + 1/j\omega C}{R_2 + 1/j\omega C}$$

$$= \frac{1 + j\omega C(R_1 + R_2)}{1 + j\omega C R_2} \equiv K \cdot \frac{1 + j\omega/\omega_1}{1 + j\omega/\omega_0}$$
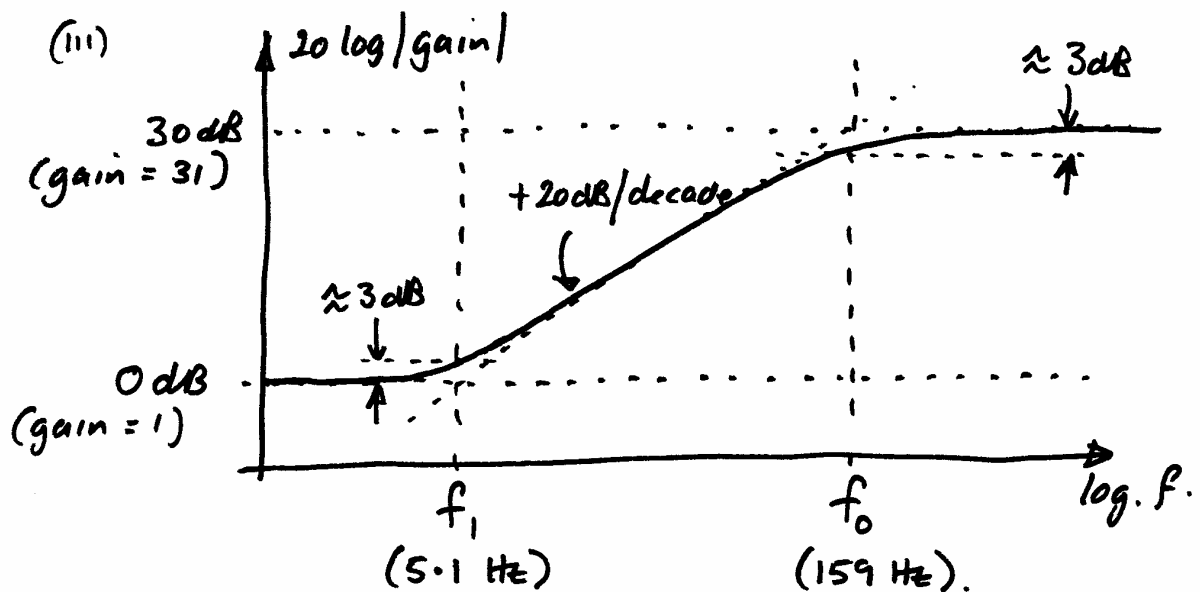
$$\text{where } K=1, \quad f_1 = \frac{1}{2\pi C(R_1 + R_2)}, \quad f_0 = \frac{1}{2\pi C R_2}.$$



(iv) For a -3 dB corner of $\geq 500 \text{ kHz}$,

$$\text{GBP} \geq 500 \text{ kHz} \times 31 = \underline{15.5 \text{ MHz}}$$

(or $97.4 \text{ M rad s}^{-1}$).

- (v) The amplifier must support 10V peak @ 500 kHz

$$\begin{aligned}\text{Max } \frac{dv}{dt} \text{ of } V_p \sin \omega t &= V_p \omega \\ &= 10 \cdot 2\pi \cdot 500 \cdot 10^3\end{aligned}$$

$$\begin{aligned}\text{min slew rate requirement} &= \text{max } \frac{dv}{dt} \text{ specified} \\ \text{ie } SR &\geq 10 \cdot 2\pi \cdot 500 \cdot 10^3 = \underline{\underline{31.4 \text{ V}\mu\text{s}^{-1}}}\end{aligned}$$

- (vi) All of i_b^- will flow through R_1 (C will prevent flow through R_2).

$$i_b^- = i_b \pm i_{os}/2 \text{ so taking worst case...}$$

$$i_b^- = i_b + i_{os}/2 = 100\text{nA} + 50\text{nA} = 150\text{nA}.$$

$$\begin{aligned}\therefore V_{oso} \text{ due to } i_b^- &= i_b^- R_1 = 150 \cdot 10^{-9} \cdot 30 \cdot 10^3 \\ &= 4.5 \text{ mV}.\end{aligned}$$

input offset voltage, $V_{os} = 4 \text{ mV}$. The d.c. gain of the amplifier is unity so V_{oso} due to $V_{os} = 4 \text{ mV}$.

$$\begin{aligned}\text{for the worst case assume effects add so} \\ \text{biggest offset at output} &= 4 \text{ mV} + 4.5 \text{ mV} \\ &= \underline{\underline{8.5 \text{ mV}}}.\end{aligned}$$

- Q2 (i) Active filters are attractive alternatives to LCR filters because they do not use inductors and do not have the same sensitivity to circuit impedances as do LCR circuits. Generally an active filter will be smaller, lighter and more accurate (for a given cost) than the LCR version.


The upper limit to the operating frequency range of active filters is set by the bandwidth of the op-amps (or other amplifying devices) used.

Resistors have parasitic series inductance and parasitic parallel capacitance. These are not usually troublesome until a few 10s of MHz.

Capacitors have series resistance, series inductance and a parallel resistance that is caused by dielectric imperfections.

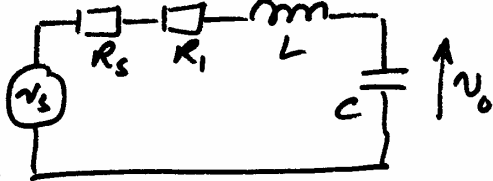(ii)
$$\frac{V_o}{V_s} = \frac{1/j\omega C}{R_s + R_1 + j\omega L + 1/j\omega C}$$

$$= \frac{1}{1 + j\omega C(R_s + R_1) + j^2 \omega^2 LC}$$



(iii)
$$\omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{126.6 \text{ mH} \times 0.2 \mu\text{F}}} = \underline{6.28 \text{ krad s}^{-1}}$$

$$\frac{1}{\omega_n Q} = C(R_s + R_1)$$

$$\text{or } Q = \frac{1}{\omega_n C(R_s + R_1)} = \underline{0.71}$$

- (iv) For the Sallen + Key

$$\omega_n = \frac{1}{R \sqrt{C_1 C_2}}$$

and $\frac{1}{\omega_n q} = 2C_2 R$


or $q = \frac{1}{2C_2 R \omega_n} = \frac{R\sqrt{C_1 C_2}}{2C_2 R} = \frac{1}{2}\sqrt{\frac{C_1}{C_2}}$

\therefore for a q of 0.71,

$\frac{C_1}{C_2} = 4q^2 = \underline{\underline{2.0}}.$


$\omega_n = \frac{1}{R\sqrt{C_1 C_2}} = \frac{1}{R\sqrt{C_2 \cdot 2C_2}} = \frac{1}{\sqrt{2} C_2 R}.$

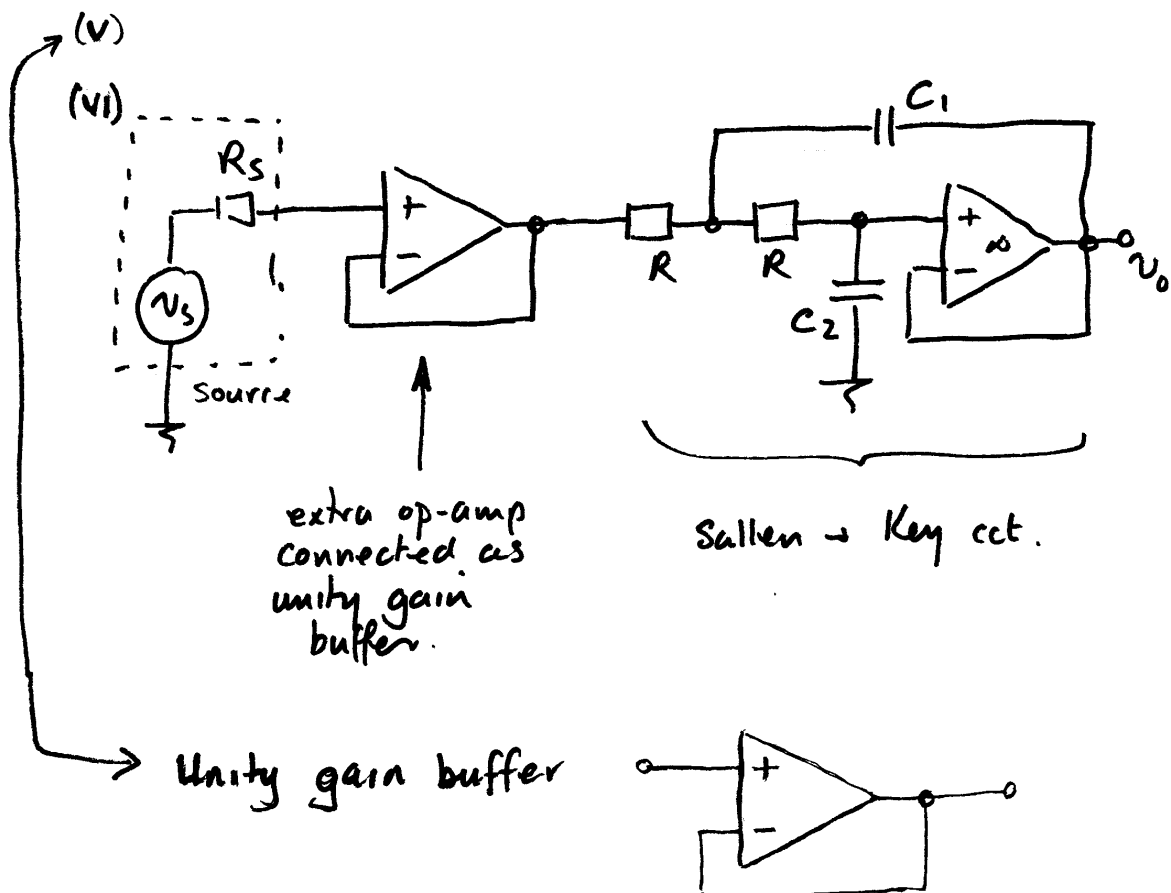$\therefore C_2 R = \frac{1}{\sqrt{2} \omega_n} = \frac{1}{\sqrt{2} \cdot 6.28 \times 10^3} = \underline{\underline{113 \mu s}}$



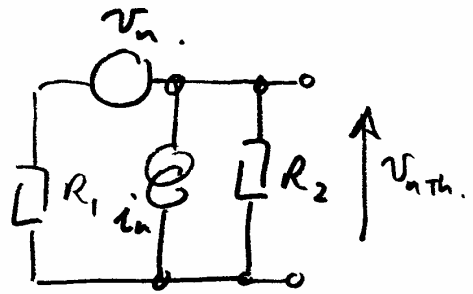Q3 (a) (i)

by inspection, $R_{Th} = R_1 \parallel R_2$
 $= 10k\Omega \parallel 20k\Omega$
 $= \underline{6.67k\Omega}$



$$\overline{v_{on}^2}|_{R_1} = 4kTR_1 \cdot \left(\frac{R_2}{R_1 + R_2}\right)^2 = \frac{331 \times 10^{-18}}{9} = 36.8 \times 10^{-18}$$

$$\overline{v_{on}^2}|_{v_n} = \overline{v_n^2} \left(\frac{R_2}{R_1 + R_2}\right)^2 = \frac{625 \times 10^{-18}}{9} = 69.4 \times 10^{-18}$$

$$\overline{v_{on}^2}|_{i_n} = \overline{i_n^2} (R_1 \parallel R_2)^2 = 1 \times 10^{-24} \times (6.67 \times 10^3)^2 = 44.5 \times 10^{-18}$$

$$\overline{v_{on}^2}|_{R_2} = 4kTR_2 \left(\frac{R_1}{R_1 + R_2}\right)^2 = 166 \times 10^{-18} \cdot \frac{4}{9} = 73.6 \times 10^{-18}$$

$$\overline{v_{onT}^2} = (36.8 + 69.4 + 44.5 + 73.6) \times 10^{-18} = 224 \times 10^{-18}$$

$$\therefore v_{nTh} = \sqrt{224 \times 10^{-18}} = \underline{15nV \text{ Hz}^{-1/2}}$$

(a) (ii) Effective noise temp. of R_{Th} given by


$$4kT_{eff} R_{Th} = 224 \times 10^{-18} \text{ V}^2 \text{ Hz}^{-1}$$

$$\text{or } T_{eff} = \frac{224 \times 10^{-18}}{4 \cdot 1.38 \cdot 10^{-23} \cdot 6.67 \cdot 10^3} = 608 \text{ K.}$$

Total rms across 50pF

$$= \sqrt{\frac{k T_{eff}}{C}} = \sqrt{\frac{1.38 \times 10^{-23} \cdot 608}{50 \times 10^{-12}}} = \underline{13\mu V}$$

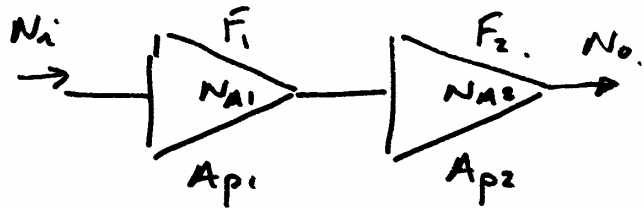(b)(i) The output noise contains three components



No due to N_i
 $= N_{o1} = kT\Delta f \cdot A_{p1} \cdot A_{p2}$. [note that N_i is available noise $kT\Delta f$]

No due to amplifier 1
 $= N_{o2} = N_{A1} \cdot A_{p2} = (F_1 - 1)kT\Delta f \cdot A_{p1} \cdot A_{p2}$.

No due to amplifier 2
 $= N_{o3} = N_{A2} = (F_2 - 1)kT\Delta f \cdot A_{p2}$.

Overall $F = \frac{\text{actual output noise}}{\text{output noise from ideal amp}}$
 $= \frac{kT\Delta f (A_{p1}A_{p2} + (F_1 - 1)A_{p2}A_{p1} + (F_2 - 1)A_{p2})}{kT\Delta f A_{p1} \cdot A_{p2}}$
 $= \underline{\underline{F_1 + \frac{F_2 - 1}{A_{p1}}}}$

(ii) Power gains must be converted to linear ratios ...

6 dB = power gain of 4

10 dB = power gain of 10.



high gain first ... $F = 3 + \frac{2-1}{10} = 3.1$

high gain second .. $F = 2 + \frac{3-1}{4} = 2.5$

So the $F=2$, gain = 6 dB should be the front end and $F_{\text{overall}} = \underline{\underline{2.5}}$.

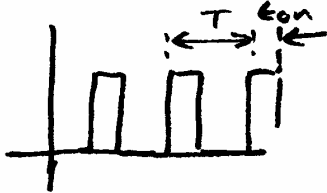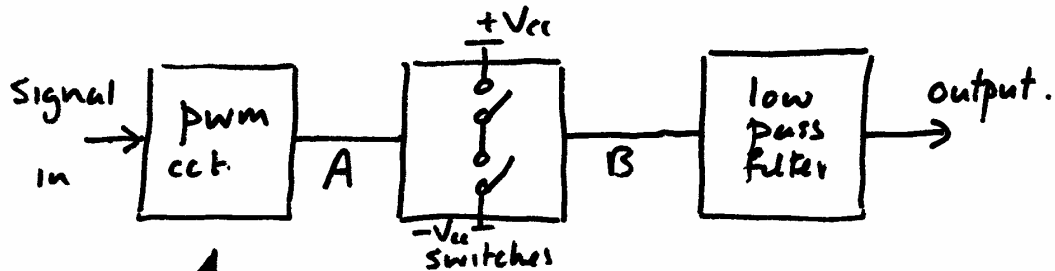Q4 (a) class D is much more efficient than class A or class B.

class A or B are more linear than class D.



Signal converted to pwm - i.e. the duty cycle at point A is proportional to the value of signal at that instant. $\frac{1}{T} \gg \text{max } f_{\text{sig}}$ of interest.

switches switch node B either to $+V_{cc}$ or $-V_{cc}$ depending on whether A is high or low. Level of power at output determined by $\pm V_{cc}$.

B then put through low pass filter to average the pwm at B and hence extract the original signal that is now in amplified form.

(b) (i) $\text{max } \delta/p V = \pm 32V$; $\text{max } \delta/p I = 3A$

$$\therefore R_L \text{ for max power} = \frac{32}{3} = \underline{10\frac{2}{3} \Omega}.$$

$$\text{value of max power} = \frac{V_p I_p}{2} = \frac{96}{2} = \underline{48W}.$$

(ii) for load of 15Ω , $I_p = \frac{32}{15}$ which is less than $3A$ so power output is voltage limited

maximum power into 15Ω is

$$\frac{V_p^2}{2R_L} = \frac{32^2}{2 \cdot 15} = \underline{\underline{34\text{W}}}.$$

(iii). With a 15Ω load, each power supply would need to supply half cycles of current with a peak value of $32/15\text{ A}$.

The supply must be able to cope with the average value of this demand which is

$$I_{\text{ave}} = \frac{I_p}{\pi} = \frac{32}{15 \cdot \pi} = \underline{\underline{0.68\text{A}}}.$$

$$\begin{aligned} \text{(iv)} \quad P_D &= \frac{2V_{cc}^2}{\pi^2 R_L} \\ &= \frac{2 \cdot 35^2}{\pi^2 R_L} \\ &= 16.5\text{W} \end{aligned}$$

$$\begin{aligned} T_j - T_s &= P_D \cdot 2^\circ\text{C/W} \\ &= 33^\circ\text{C}. \end{aligned}$$

so at $T_j = 125$, $T_s = (125 - 33) = 92^\circ\text{C}$. But max $T_s = 90$ so T_s spec is limit.

$$T_s - T_A = (2P_D + 20\text{W}) \cdot \theta_{SA} = 53\theta_{SA}$$

$$90 - 35 = 55 = 53\theta_{SA}$$

$$\underline{\underline{\theta_{SA} \leq 1^\circ\text{C/W.}}} \quad (1.04^\circ\text{C/W})$$

