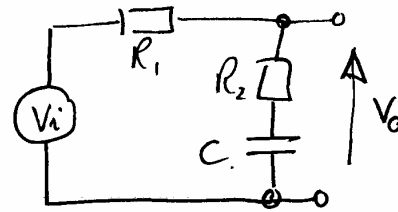


①


Q1(a)(i) h.f. gain = $\frac{R_2}{R_1 + R_2}$
 (C looks like a short cct in comparison to R_2 ...).



l.f. gain = 1
 (C looks like an open cct...)

(ii).
$$\frac{V_o}{V_i} = \frac{R_2 + \frac{1}{j\omega C}}{R_1 + R_2 + \frac{1}{j\omega C}} = \frac{1 + j\omega C R_2}{1 + j\omega C (R_1 + R_2)}$$
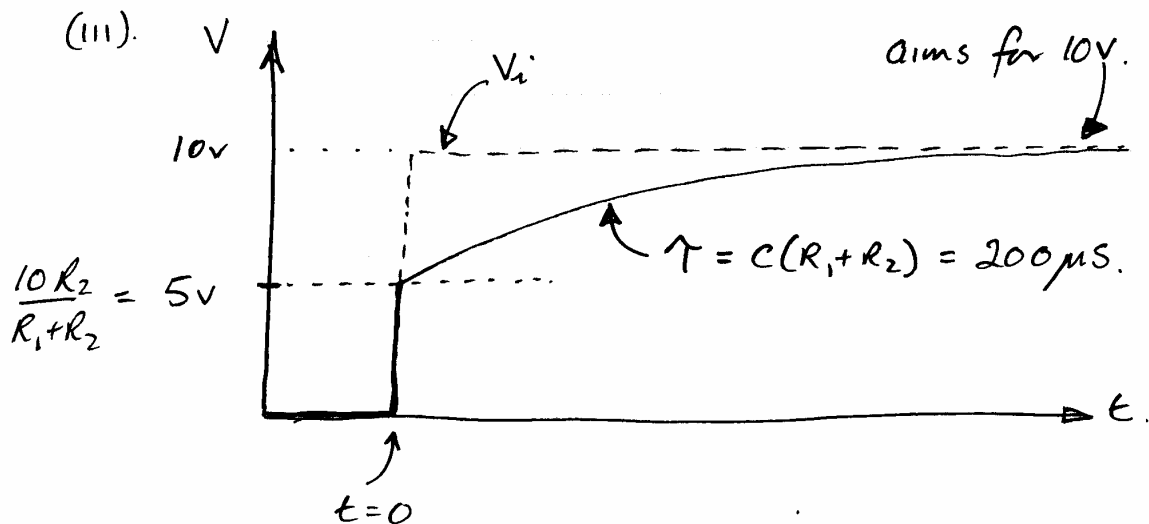
$$\equiv k \cdot \frac{1 + j \frac{f}{f_1}}{1 + j \frac{f}{f_0}} \text{ where } k=1, f_0 = \frac{1}{2\pi C (R_1 + R_2)} + f_1 = \frac{1}{2\pi C R_2}.$$



(b) (i) $-3dB BW = \frac{GBP}{G} = \frac{20 \times 10^6}{50} = \underline{400 kHz} \text{ (or } 2.5 M rad s^{-1})$

associated $\tau = \frac{1}{2\pi \cdot 400 kHz} = \underline{398 ns}.$

(2)

Q1 (b)(ii) The amplifier is a first order system with $k = 50$ and $f_0 = 400 \text{ kHz}$.

$$\therefore \frac{V_o}{V_i} = \frac{50}{1 + j f / 400 \text{ kHz}} \quad \text{So at } 1 \text{ MHz} \dots$$


$$\frac{V_o}{V_i} = \frac{50}{1 + j \frac{1000 \text{ kHz}}{400 \text{ kHz}}} = \frac{50}{1 + j 2.5}$$

$$\therefore \left| \frac{V_o}{V_i} \right| = \frac{50}{(1 + 6.25)^{1/2}} = \underline{18.6}$$

$$\phi\left(\frac{V_o}{V_i}\right) = -\tan^{-1} \frac{\text{Im}}{\text{Re}} = -\tan^{-1} 2.5 = \underline{-68^\circ}$$

(iii) The amplifier slew rate must be equated to max rate of change in the signal

max rate of change.

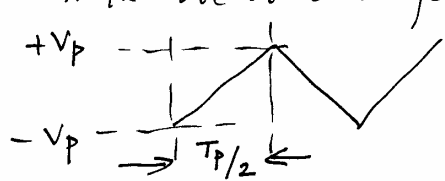

$$= \frac{2V_p}{T_{p/2}} = \frac{4V_p}{T_p}$$


$$= 4V_p f.$$

$$\therefore 70 \times 10^6 = 4 \cdot 10 \cdot f$$


$$\therefore f_{\text{max}} = \underline{1.75 \text{ MHz}}$$

(3)

Q2 (i) Butterworth.

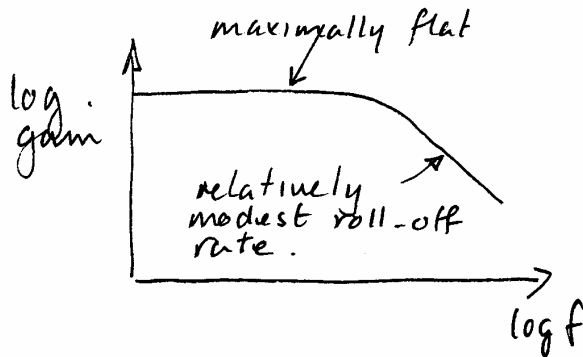


Chebychev...

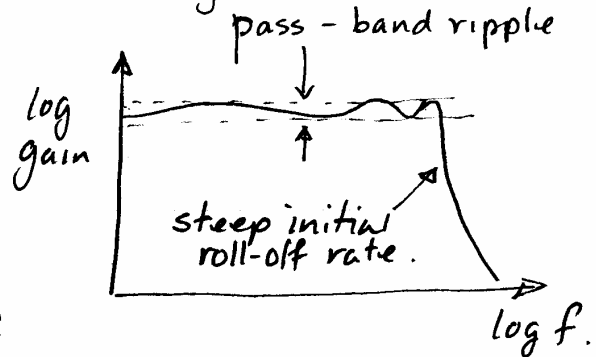

- In pass band, Butterworth is as flat as is possible but Chebychev has gain ripple.
- In cut-off region, Chebychev has much steeper initial roll-off than Butterworth although for $f \gg f_c$ the two roll-off rates converge to $n \times 20 \text{ dB/decade}$ where $n = \text{filter order}$.
- Butterworth is attractive because it is much less sensitive to component tolerance errors than Chebychev.

(ii)

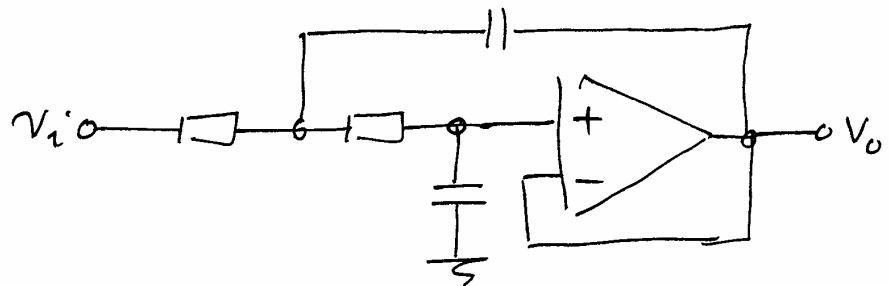

(iii)

$$\frac{V_o}{V_i} = \frac{1}{1 + s 2C_2 R + s^2 C_1 C_2 R^2}$$

$$\therefore \omega_n = \frac{1}{R \sqrt{C_1 C_2}}$$

$$\frac{1}{\omega_n Q} = 2C_2 R \quad \text{or} \quad \frac{1}{Q} = \omega_n 2C_2 R$$

(4)

Q2 (iii) cont...

$$= \frac{2C_2 R}{R\sqrt{C_1 C_2}} = 2\sqrt{\frac{C_2}{C_1}}$$

$$\therefore \underline{q = \frac{1}{2}\sqrt{\frac{C_1}{C_2}}}$$

(iv) - 2nd order factor is $\frac{1}{s^2 + 0.299s + 0.839}$

$$= \frac{1}{0.839 \left(1 + \frac{0.299s}{0.839} + \frac{s^2}{0.839} \right)} \quad \left[\begin{array}{l} \text{the multiplying} \\ \text{term can be} \\ \text{discarded.} \end{array} \right]$$

$$\therefore \frac{\omega_n}{\omega_c} = (0.839)^{1/2} = \underline{0.916}$$

$$\text{and } \frac{1}{\frac{\omega_n}{\omega_c} q} = \frac{0.299}{0.839} \quad \text{or} \quad \frac{1}{q} = \frac{0.299 \times 0.916}{0.839} = 0.326$$

$$\therefore \underline{q = 3.06}$$

$$\text{so for cut off of } 20 \text{ kHz, } f_n = 0.916 \times 20 \text{ kHz} = \underline{18.3 \text{ kHz}}$$

$$\text{— first order factor } \frac{1}{s + 0.299} = \frac{1}{0.299(1 + s/0.299)}$$


$$\therefore f_0 = 0.299 \times 20 \text{ kHz} = 5.98 \text{ kHz}$$

$$\text{and } \tau = \frac{1}{2\pi f_0} = \underline{26.6 \mu\text{s}}$$



$$(v) \quad 3.06 = \frac{1}{2}\sqrt{\frac{C_1}{C_2}} \quad \text{or} \quad \frac{C_1}{C_2} = 4 \times 3.06^2 = \underline{37.5}$$

(5)

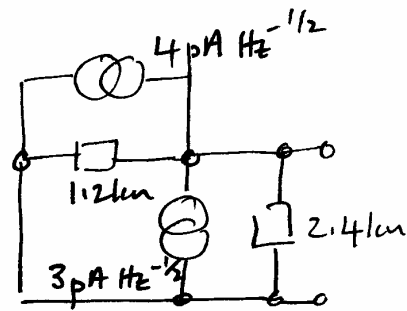Q3 (a) (i) By inspection...
 $R_{Th} = \underline{\underline{0.8\text{ k}\Omega}}$



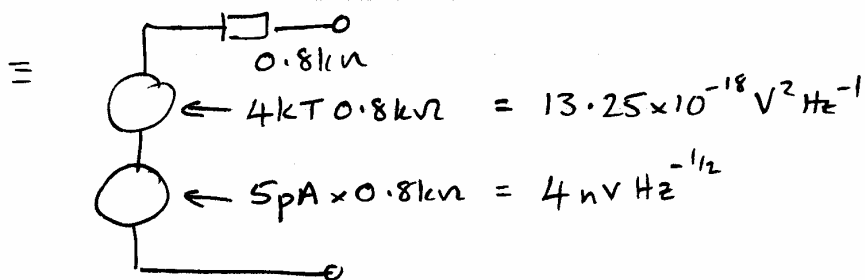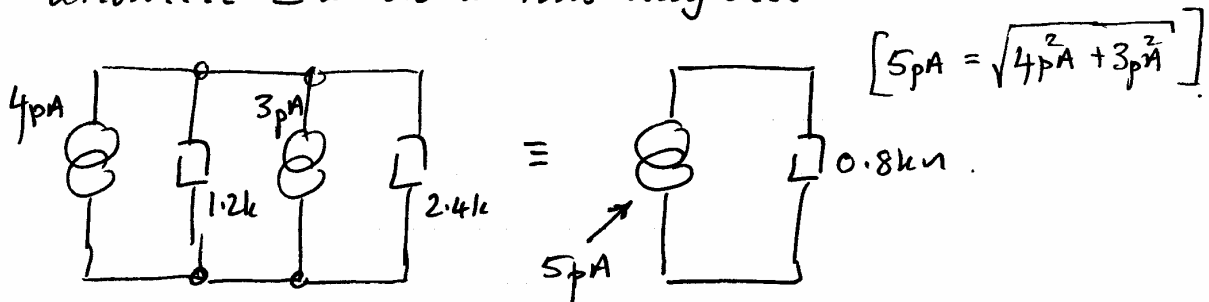There are several ways of approaching the next bit...
 Both the current sources and the resistors could be combined to produce a single parallel combination.... I'll do it this way....



$$\therefore \overline{V_{nTh}^2} /_{tot} = 13.25 \times 10^{-18} + 16 \times 10^{-18} = 29.25 \times 10^{-18}$$

$$\therefore V_{nTh} = \underline{\underline{5.4 \text{ nV Hz}^{-1/2}}}$$

(ii) If all the noise came from R_{Th} ...

$$4kT_e R_{Th} = 29.25 \times 10^{-18}$$

$$\text{or } T_e = \frac{29.25 \times 10^{-18}}{4 \cdot k \cdot 0.8 \text{ k}\Omega} = \underline{\underline{662 \text{ K}}}$$

(b) By definition $F = \frac{S_i/N_i}{S_o/N_o} = \frac{S_i}{S_o} \cdot \frac{N_o}{N_i}$

⑥

Q3(b) cont...


$$\text{but } \frac{S_i}{S_o} = \frac{1}{A_p}$$

$$\text{and } N_o = A_p N_i + N_A$$

\uparrow amplified input noise \uparrow amplifier "added" noise.

$$\therefore F = \frac{N_o}{A_p N_i} = \frac{A_p N_i + N_A}{A_p N_i} = \underline{\underline{1 + \frac{N_A}{A_p N_i}}}$$

(c)

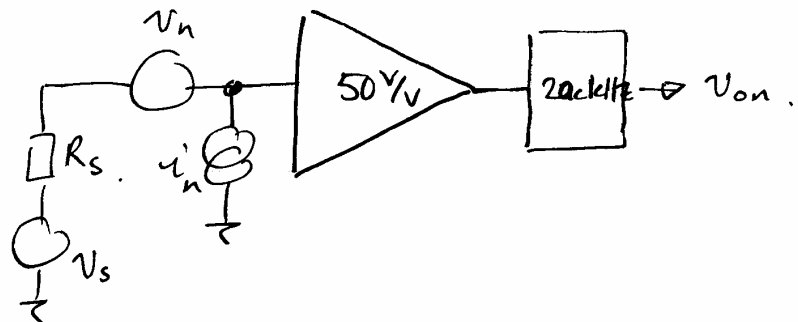

$$\begin{aligned}
 \overline{V_{on}^2} &= 50^2 \left[V_n^2 + i_n^2 R_s^2 + 4kTR_s \right] \times 20 \text{ kHz} \\
 &= 2500 \left[144 \times 10^{-18} + 400 \times 10^{-18} + 165 \times 10^{-18} \right] \times 20 \text{ kHz} \\
 &= 2500 \left[710 \times 10^{-18} \right] \times 20 \text{ kHz} = \underline{\underline{35.5 \times 10^{-9} \text{ V}^2}}
 \end{aligned}$$

$$\overline{V_{o \text{ sig}}^2} = (30 \mu\text{V})^2 (50)^2 = \underline{\underline{2.25 \times 10^{-6} \text{ V}^2}}$$

$$\therefore S/N = \frac{2.25 \times 10^{-6}}{35.5 \times 10^{-9}} = \underline{\underline{63.4}} \left[= 18 \text{ dB} \right]$$

(7)

Q4 (a)

(i) T_1 , R_1 and R_2 form a floating voltage source with a value of approximately 1.4V. It is included in order to bias out the missing 1.4V due to the transistor base-emitter voltage drops that would otherwise give rise to serious crossover distortion.

(ii) Because transistor characteristics are not perfect and because they drift slightly with temperature, designers aim to ensure a smooth transition from conduction in one to conduction in the other by designing in a small conduction overlap.

(iii) • $R_3 + R_4$ together with the voltage across T_1 allow the output quiescent current to be defined
 • They also give the circuit a defence against the destructive process of "thermal runaway".

(b)

$$(i) \quad P_{\text{supplied}} = P_{\text{Diss}} + P_{\text{LOAD.}}$$

\uparrow \uparrow \uparrow
 $2V_{CC} I_{\text{SAVE}}$ $?$ $\frac{V_p^2}{2R_L}$

$$\text{or} \quad P_{\text{Diss}} = 2V_{CC} \frac{V_p}{\pi R_L} - \frac{V_p^2}{2R_L} \quad \text{————— (1)}$$

to find max P_{Diss} , equate $\frac{dP_{\text{Diss}}}{dV_p}$ to zero...

$$\frac{dP_{\text{Diss}}}{dV_p} = \frac{2V_{CC}}{\pi R_L} - \frac{2V_p}{2R_L} = 0$$

$$\text{or} \quad V_p = \frac{2V_{CC}}{\pi} \quad \text{————— (2)}$$

substituting condition (2) back into (1) gives

$$P_{\text{Diss}} = \frac{2V_{CC} \left(\frac{2V_{CC}}{\pi} \right)}{\pi R_L} - \frac{\left(\frac{2V_{CC}}{\pi} \right)^2}{2R_L}$$

(8)


Q4 (b) (i) cont...

$$\text{so } P_{\text{Diss}} = \frac{4V_{cc}^2}{\pi^2 R_L} - \frac{4V_{cc}^2}{2\pi^2 R_L} = \frac{2V_{cc}^2}{\pi^2 R_L}$$

but this is the total power dissipated, i.e. the dissipation in both devices. The dissipation in one device will be half of this..., i.e.,

$$P_{\text{Diss}} / \text{device} = \frac{V_{cc}^2}{\pi^2 R_L}$$
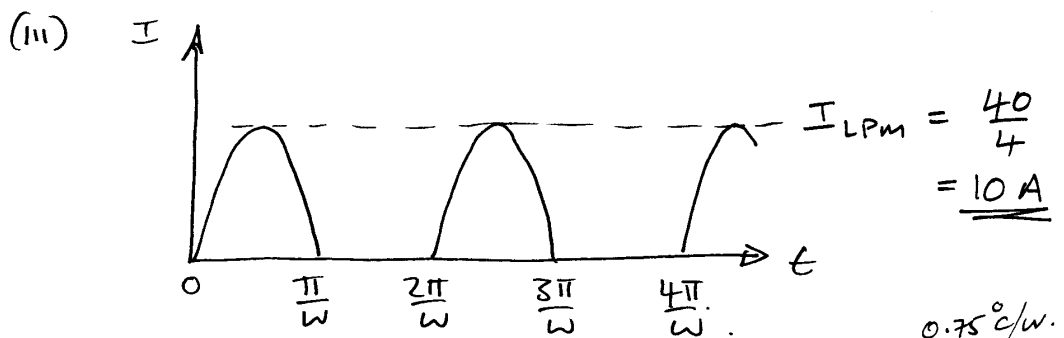
$$(ii) \max P_L = \frac{V_{cc}^2}{2R_L} = \frac{1600}{8} = \underline{\underline{200 \text{ W}}}$$



$$(iv) P_{\text{Diss}} = 40.5 \text{ W/device}$$

Assume T_j is the limiting factor...

$$T_s = T_j - (0.75 + 1) \times 40.5 \\ = 150 - 70.1 = 79.9$$

which is lower than max T_s allowed $\rightarrow T_j$ is limiting factor

$$\therefore T_s - T_A = 2P_{\text{Diss}} \theta_{SA} = 81 \theta_{SA}$$

$$\text{or } \theta_{SA} = \frac{T_s - T_A}{81} = \frac{79.9 - 35}{81} = \underline{\underline{0.55^\circ \text{C/W}}}$$

