

The University of Sheffield
Department of Electrical and Electronic Engineering

EEE117 Homework 5

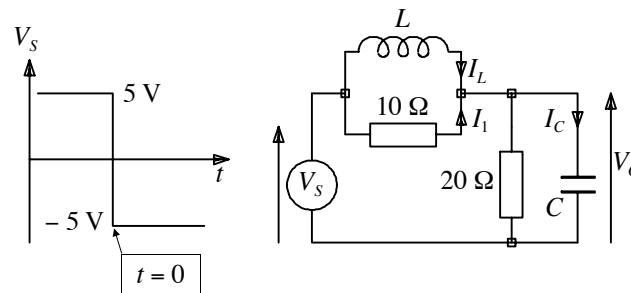


Figure 1

- 1** The circuit of figure 1 is subjected to a transient, V_s , as shown in figure 1. Assume that V_s is unchanged over all time before $t = 0^-$ and remains at its $t = 0^+$ value for all time after $t = 0^+$.
 - (i) Work out I_1 , I_L , I_C and V_C at $t = 0^-$.
 - (ii) Draw an equivalent circuit of figure 1 at $t = 0^+$. Remember to replace L by a current source and C by a voltage source. Label the magnitudes and directions of these sources.
 - (iii) Work out I_1 , I_L , I_C and V_C at $t = 0^+$.
 - (iv) Work out I_1 , I_L , I_C and V_C as $t \Rightarrow \infty$.

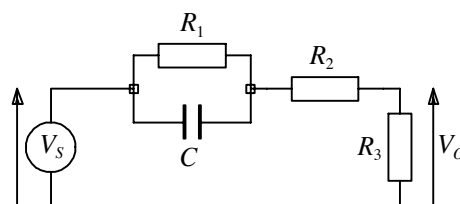


Figure 2

- 2** For the circuit of figure 2
 - (i) What is the circuit time constant? (*Remember to replace sources by their internal impedances and then look at the circuit from the capacitor's point of view to identify the resistance seen by the capacitor.*)
 - (ii) What are the $t = 0^+$ and $t \Rightarrow \infty$ values of V_o expressed in terms of the V_s values and the circuit components?