

EEE204

"Electronic Devices in Circuits"

Richard Tozer E135b. r.c.tozer@shef.ac.uk

What is the module about?

First look at R-C circuits

- transfer functions
- Bode plots
- standard forms

Operational Amplifiers

- review of ideal behaviour
- offsets
- frequency dependence
 - gain-bandwidth product
 - slew rate
- control of frequency response by using frequency dependent feedback
- filters → an introduction to low pass filters.

- Noise

- what is it?
- how is it modelled
- what effect does it have on circuits
- can its effects be minimised by design.

Power Amplifiers


- concentrating on output stages
- amplifier classes
- getting rid of dissipated heat.

Booklist.

Connor "Noise" (Library reference)
 Smith R.J. "Circuits Devices & Systems" 5th ed.
 Sedra + Smith R.C. "Microelectronic Circuits" 5th ed.
 Horowitz + Hill "The art of electronics"
 DeMottman "Microelectronics"

Robert Spencer "Introductory Circuits"

First order circuits

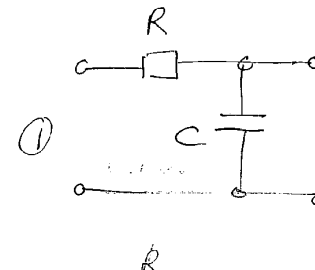


$$(Z_C = \frac{1}{j\omega C})$$

If gain $\rightarrow 1$ as $f \rightarrow 0$

hf gain $\rightarrow 0$ as $f \rightarrow \infty$


$$\tau = RC$$

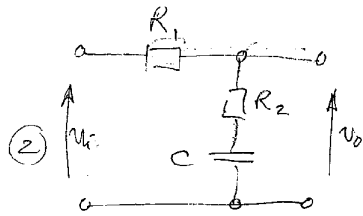

If gain $\rightarrow 1$ as $f \rightarrow 0$

h.f. gain $\rightarrow \frac{R_2}{R_1 + R_2}$ as $f \rightarrow \infty$


$$\tau = (R_2 + R_1)C$$

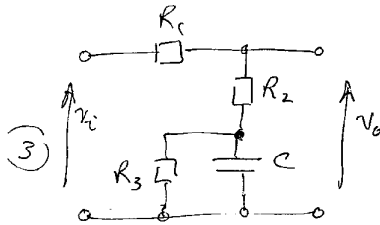

If gain $\rightarrow \frac{R_2 + R_3}{R_1 + R_2 + R_3}$ as $f \rightarrow 0$

h.f. gain $\rightarrow \frac{R_2}{R_1 + R_2}$ as $f \rightarrow \infty$


$$\tau = [(R_1 + R_2) \parallel R_3]C$$

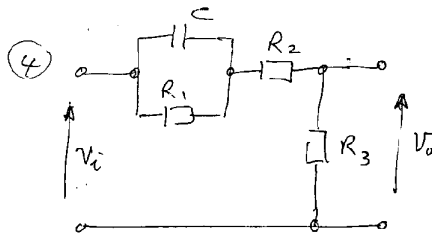

If gain $\rightarrow \frac{R_3}{R_1 + R_2 + R_3}$ as $f \rightarrow 0$

h.f. gain $\rightarrow \frac{R_3}{R_2 + R_3}$ as $f \rightarrow \infty$

$$\tau = [R_1 \parallel (R_2 + R_3)]C$$

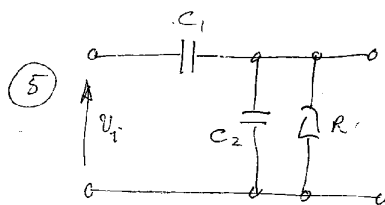

If gain $\rightarrow 0$ as $f \rightarrow 0$

h.f. gain $\rightarrow \frac{X_{C2}}{X_{C1} + X_{C2}}$

$$= \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}} = \frac{C_1 C_2}{C_1 + C_2} \cdot \frac{1}{C_2}$$


$$= \frac{C_1}{C_1 + C_2}$$

$$\tau = (C_1 + C_2)R$$

Working out transfer functions

Transfer function is $\frac{V_o}{V_i}$ as a function of ω
— will usually be complex.

lets look at circuit no 5.

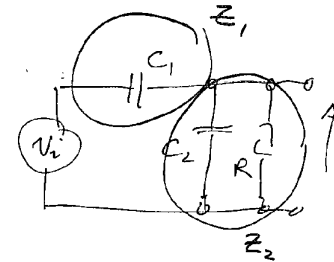

$$\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2}$$

$$Z_1 = \frac{1}{j\omega C_1}$$

$$Z_2 = \frac{1}{j\omega C_2} \parallel R = \frac{R / j\omega C_2}{R + 1/j\omega C_2} = \frac{R}{1 + j\omega C_2 R}$$

$$\therefore \frac{V_o}{V_i} = \frac{\frac{R}{1 + j\omega C_2 R} \times (1 + j\omega C_1 R)}{\frac{1}{j\omega C_1} + \frac{R}{1 + j\omega C_2 R}} = \frac{R}{\frac{(1 + j\omega C_2 R)}{j\omega C_1} + R} \times j\omega C_1$$

$$= \frac{j\omega C_1 R}{1 + j\omega C_2 R + j\omega C_1 R} = \frac{j\omega C_1 R}{1 + j\omega (C_1 + C_2) R}$$

$$= \frac{C_1}{C_1 + C_2} \cdot \frac{j\omega (C_1 + C_2) R}{1 + j\omega (C_1 + C_2) R} \quad \leftarrow \text{this is a standard form.}$$

$$k \cdot \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}$$

$$\therefore k = \frac{C_1}{C_1 + C_2} \quad \omega_0 = \frac{1}{(C_1 + C_2)R}$$

$$\text{if } \omega \Rightarrow \infty \quad \left| \frac{V_o}{V_i} \right| = \left| \frac{C_1}{C_1 + C_2} \cdot \frac{j\omega (C_1 + C_2) R}{1 + j\omega (C_1 + C_2) R} \right|$$

$$= \frac{C_1}{C_1 + C_2} \left[\frac{w^2 (C_1 + C_2)^2 R^2}{1 + w^2 (C_1 + C_2)^2 R^2} \right]^{1/2}$$

for $w \Rightarrow \infty$ $w^2 (C_1 + C_2)^2 R^2 \gg 1$

$$\left| \frac{V_o}{V_i} \right| \Rightarrow \frac{C_1}{C_1 + C_2}$$

Consider number ②

$$\frac{V_o}{V_i} = \frac{Z_2}{Z_2 + Z_1}$$

$$Z_1 = R_1$$

$$Z_2 = R_2 + \frac{1}{j\omega C}$$

$$\frac{V_o}{V_i} = \frac{R_2 + \frac{1}{j\omega C}}{R_1 + R_2 + \frac{1}{j\omega C}} \times \frac{j\omega C}{j\omega C} = \frac{R_2 j\omega C + 1}{(R_1 + R_2) j\omega C + 1}$$

$$= k \cdot \frac{1 + j\omega/\omega_1}{1 + j\omega/\omega_0}$$

$$\omega_1 = \frac{1}{CR_2}$$

$$\omega_0 = \frac{1}{C(R_1 + R_2)}$$

standard form: $k = 1$


called lead-lag circuit
pole-zero circuit

$$\left| \frac{1 + j\omega R_2 C}{1 + j\omega (R_1 + R_2) C} \right| = \left[\frac{1 + j^2 R_2^2 C^2}{1 + w^2 (R_1 + R_2)^2 C^2} \right]^{1/2}$$

if $w \Rightarrow \infty$ gain $\Rightarrow \left[\frac{w^2 R_2^2 C^2}{w^2 (R_1 + R_2)^2 C^2} \right]^{1/2}$
(since both w^2 terms $\gg 1$)

if $w \Rightarrow 0$ gain $\Rightarrow \left[\frac{1}{1} \right]^{1/2}$ since both w^2 terms $\ll 1$
= 1
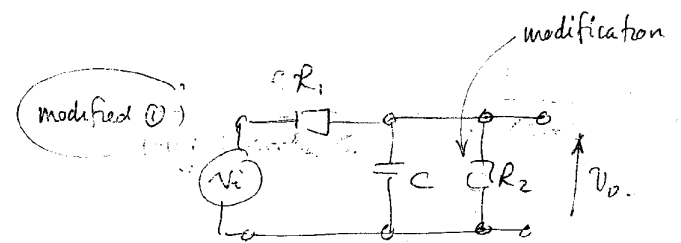
$$\left[\frac{1 + j\omega R_2 C}{1 + j\omega (R_1 + R_2) C} = \frac{1}{1 + j\omega (R_1 + R_2) C} + \frac{j\omega R_2 C}{1 + j\omega (R_1 + R_2) C} \right]$$



$$\frac{V_o}{V_i} = \frac{R_2 / j\omega C}{R_2 + \frac{1}{j\omega C}} = \frac{R_2}{1 + j\omega C R_2}$$

$$= \frac{R_2}{R_1 + \frac{R_2}{1 + j\omega C R_2}} = \frac{R_2}{(1 + j\omega C R_2) R_1 + R_2}$$

$$\left[\text{standard form } k \cdot \frac{1}{1 + j\omega/\omega_0} \right]$$

$$= \frac{R_2}{(R_1 + R_2) + j\omega C R_1 R_2}$$

$$= \frac{K_2}{(R_1 + R_2) \left(1 + j\omega \frac{R_2 R_1}{R_1 + R_2} \right)}$$

$$= K \frac{1}{1 + j\omega/\omega_0}$$

notice that $j\omega$ has been kept together.

Shapes of magnitude responses

Consider $\frac{1}{1 + j\omega/\omega_0}$

$$\left| \frac{1}{1 + j\omega/\omega_0} \right| = \left[\frac{1}{1 + (\omega/\omega_0)^2} \right]^{1/2}$$

what if $\omega \ll \omega_0$

$$\rightarrow \left| \frac{V_o}{V_i} \right| \Rightarrow \left[\frac{1}{1} \right]^{1/2}$$

— unity gain is an asymptote as $\omega \rightarrow 0$.

gain usually expressed in dB

$$\text{gain in dB} = 20 \log \left| \frac{V_o}{V_i} \right| = 20 \log 1$$

in this case,

$$= 0 \text{ dB}$$

what if $\omega = \omega_0$

$$\left| \frac{V_o}{V_i} \right| = \left[\frac{1}{1 + 1} \right]^{1/2} = \frac{1}{\sqrt{2}}$$


$$\text{in dB} \dots 20 \log \frac{1}{\sqrt{2}} = -3 \text{ dB}$$

what if $\omega \gg \omega_0$

$$\left| \frac{V_o}{V_i} \right| \Rightarrow \left[\frac{1}{(\omega/\omega_0)^2} \right]^{1/2} \Rightarrow \frac{\omega_0}{\omega}$$

— if ω increases by a factor of 10 (a decade), $\left| \frac{V_o}{V_i} \right|$ decreases by a factor of 10. A reduction of a factor 10 in gain is -20 dB .

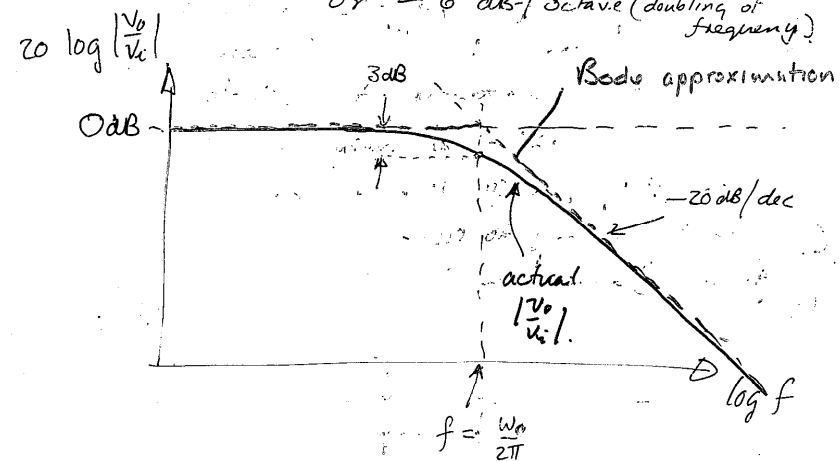
— slope of roll off asymptote is -20 dB/decade (of frequency)
or -6 dB/octave (doubling of frequency)



what about other forms?

$$\frac{V_o}{V_i} = \frac{1 + j\omega/\omega_1}{1 + j\omega/\omega_0}$$


$$\begin{aligned}
 20 \log \left| \frac{V_o}{V_i} \right| &= 20 \log \left| \frac{1+j\omega/\omega_1}{1+j\omega/\omega_0} \right| \\
 &= 20 \log |1+j\omega/\omega_1| + 20 \log \left| \frac{1}{1+j\omega/\omega_0} \right| \\
 &= -20 \log \left| \frac{1}{1+j\omega/\omega_1} \right| + 20 \log \left| \frac{1}{1+j\omega/\omega_0} \right|
 \end{aligned}$$

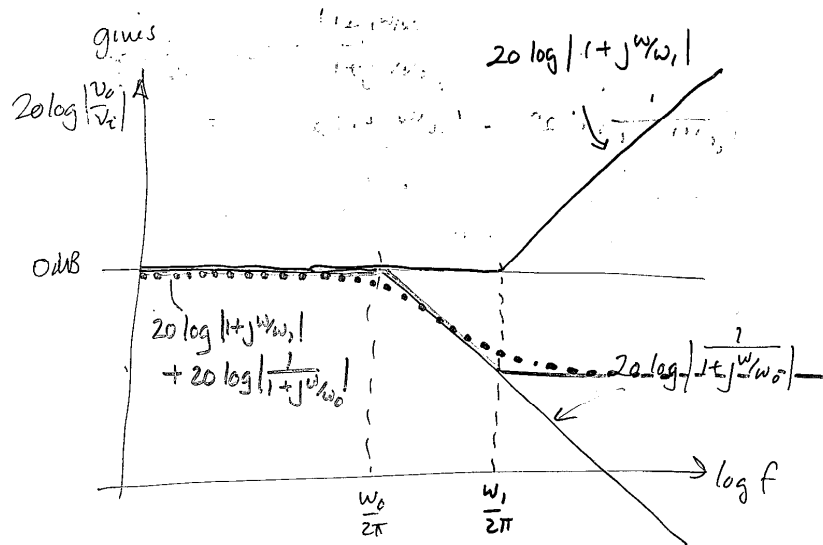

Phase responses -----

$$\frac{V_o}{V_i} = \frac{1}{1+j\omega/\omega_0} \quad \phi \text{ of } V_o \text{ w.r.t. } V_i = -\tan^{-1} \omega/\omega_0$$

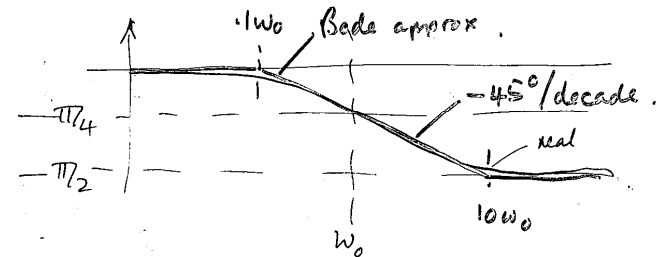
$$\frac{V_o}{V_i} = \frac{1+j\omega/\omega_1}{1+j\omega/\omega_0} \quad \phi = \tan^{-1} \omega/\omega_1 - \tan^{-1} \omega/\omega_0$$



Step response

— can be done by inspection for a first order system if 3 pieces of information are available

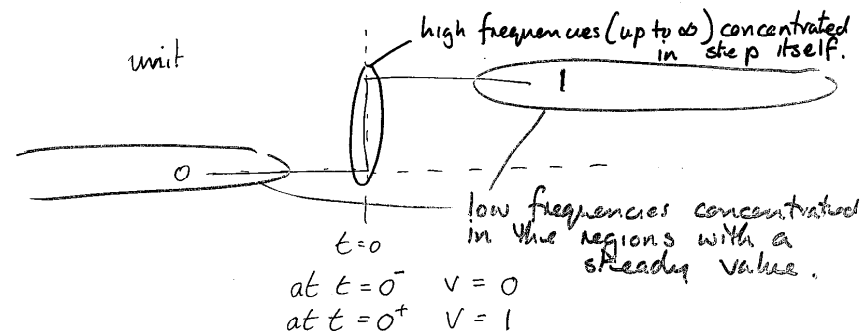- high frequency gain (gain as $\omega \rightarrow \infty$)
- low frequency gain (gain as $\omega \rightarrow 0$)
- time constant.



high frequency gain operates on the step.

low frequency gain operates on the initial voltage (ie from $t=-\infty$ to $t=0^-$) and on final (or aiming) voltage — ie $t \rightarrow \infty$

the voltage reached at $t \Rightarrow \infty$.


An example...

$$k \frac{1+j\omega/\omega_1}{1+j\omega/\omega_0}$$

low frequ. gain = k .

high frequ. gain = $k \frac{\omega_0}{\omega_1}$

$$\tau = 1/\omega_0$$

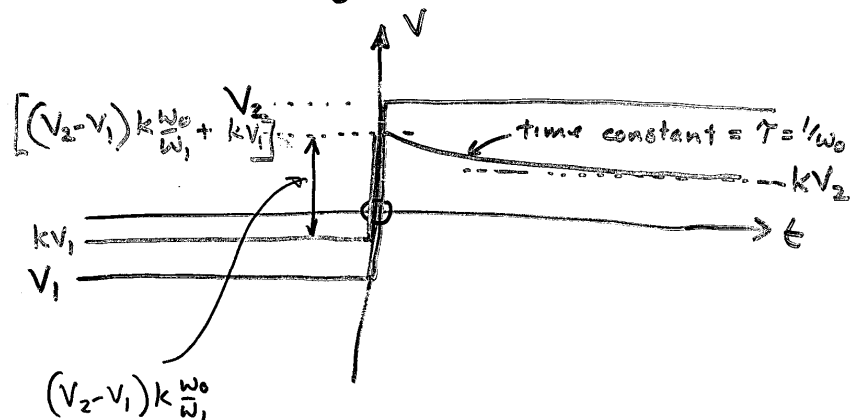


span of the exponential

$$\begin{aligned} &= V_{\text{start}} - V_{\text{finish}} \\ &= \left[\left[(V_2 - V_1) k \frac{\omega_0}{\omega_1} + kV_1 \right] - kV_2 \right] \\ &\quad \underbrace{\hspace{10em}}_{V_{\text{span}}} \end{aligned}$$


$$V(t) = V_{\text{span}} e^{-t/\tau} + kV_2$$

TRY THIS.

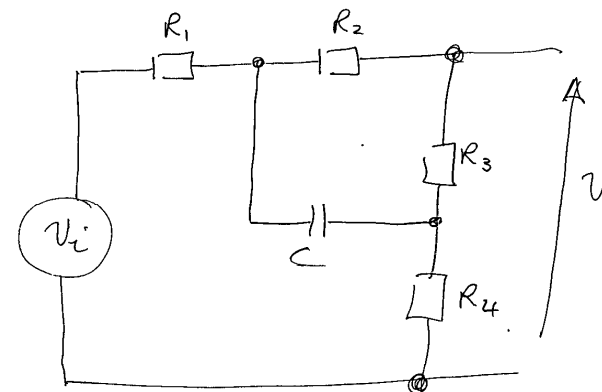

high frequency gain $\frac{R_4}{R_1 + R_4} \checkmark$
 low frequency gain $\frac{R_3 + R_4}{R_1 + R_2 + R_3 + R_4}$
 time constant $\rightarrow C(R_1 + R_4) \parallel (R_2 + R_3)$

$$\frac{V_o}{V_i} =$$

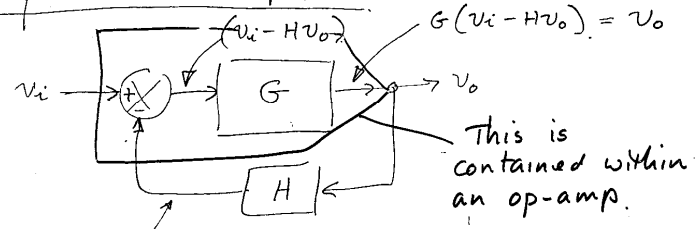Operational Amplifiers HV_o

$$G(V_i - HV_o) = V_o$$

$$G V_i = V_o + GHV_o$$


$$\text{or } \frac{V_o}{V_i} = \frac{G}{1 + GH}$$

classical feedback system equation.

If G is very very large — in particular
if G so big that $GH \gg 1$

$$\frac{V_o}{V_i} \approx \frac{G}{GH} \quad (\text{since } 1 + GH \approx GH)$$

$$\text{or } \frac{V_o}{V_i} \approx \frac{1}{H}$$

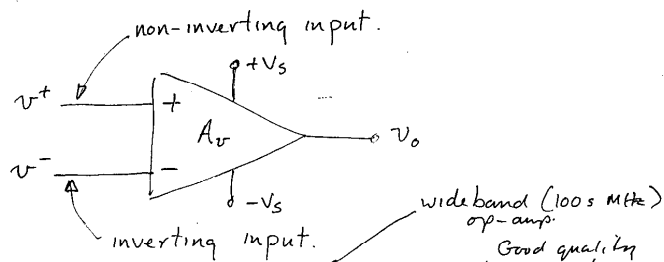op-amps proper

A_v is typically $10^4 V/V$ and $10^5 V/V$

A_v operates on the difference $(v^+ - v^-)$

input impedance is designed to be
very high
typically $10^5 \rightarrow 10^{15} \Omega$

bipolar
input
wideband.


cmos input
(FET input)
device.

output impedance is designed to be low

typically 3Ω to 100Ω

wideband
amps.

low power
general purpose

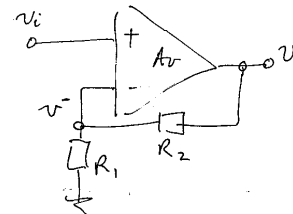Basic op-amp connections

non-inverting
amplifier


if $A_v \Rightarrow \infty$
 \Rightarrow usual design assumption.

$$v^- = \frac{V_o R_1}{R_1 + R_2}$$

if gain is large
 $v^+ - v^-$ must be ≈ 0

$$v_i \approx v^-$$
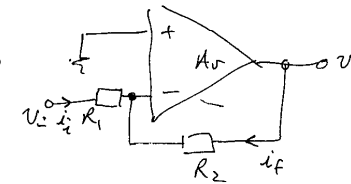
$$\text{and } v_i \approx \frac{V_o R_1}{R_1 + R_2}$$



inverting amplifier.

if $A_v \Rightarrow \infty$

$$v^+ \approx v^-$$

$$\text{But } v^+ = 0$$

$$\text{so } v^- \approx 0$$

$$i_i + i_f = 0 \quad \left(\begin{array}{l} \text{the op-amp} \\ \text{input resistance} \\ \text{is so high} \\ \text{that we can} \\ \text{ignore any} \\ \text{current that} \\ \text{flows into it.} \end{array} \right)$$

$$\frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} = 0$$

or $\frac{V_o}{V_i} \approx \frac{R_1 + R_2}{R_1}$ but $v^- \approx 0$

$$\frac{V_i}{R_1} + \frac{V_o}{R_2} = 0 \quad \text{or} \quad \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

Input and output impedance

Output impedance

Output impedance of an op-amp is modified by the feedback used to control the gain

It can be shown that


$$r_{o\text{eff}} = \frac{r_o}{(1 + A_v \frac{R_1}{R_1 + R_2})} \equiv \frac{r_o}{1 + G_H}$$

output resistance of feedback amplifier circuit

↑ this is true for inverting and non-inverting amplifiers.

Input resistance

— inverting

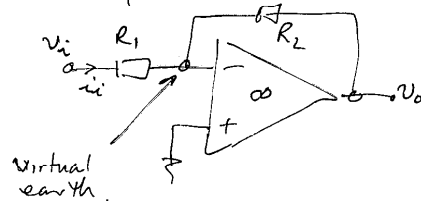

$$\frac{V_o}{i_i} = r_{i\text{eff}} = R_1$$

$$\frac{V_o}{i_i} = r_{i\text{eff}} = R_1$$

— non-inverting


— intrinsically high input resistance because input applied directly to + input of op-amp.

But the feedback does make a difference

$$r_{i\text{eff}} = r_i \left(1 + \frac{A_v R_1}{R_1 + R_2}\right)$$

effective input resistance of circuit $\frac{V_o}{i_i}$

intrinsic op-amp input resistance

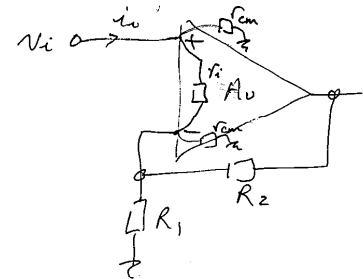

Offset effects

$$V_o = A_v (v^+ - v^-) \quad \leftarrow \text{the op-amp equation}$$


∴ if $v^+ = v^-$ $V_o = 0$ but it doesn't.

— the output that occurs when $v^+ = v^-$ is an error called an offset error.

Question — what is the effect of offset errors

on-circuit performance
 — what can be done — by design —
 to minimize those effects.

an offset model.

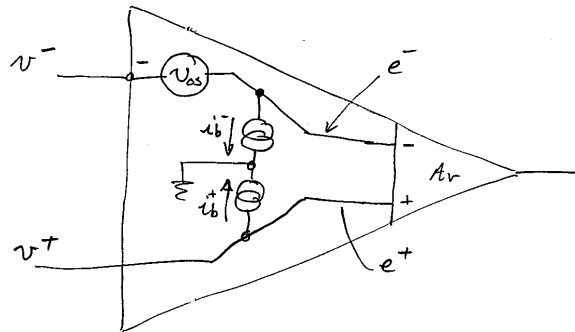

V_{os} = "equivalent input offset voltage generator"



V_{os} is equal to and opposite to the voltage that must be applied between v^+ and v^- in order to get a v_o of 0V.

i_b^+ and i_b^- are the input bias currents required by the op-amp.

Circuits must allow i_b^+ and i_b^- to flow.

i_{os} is "equivalent input offset current generator"

$$i_{os} = |i_b^+ - i_b^-|$$

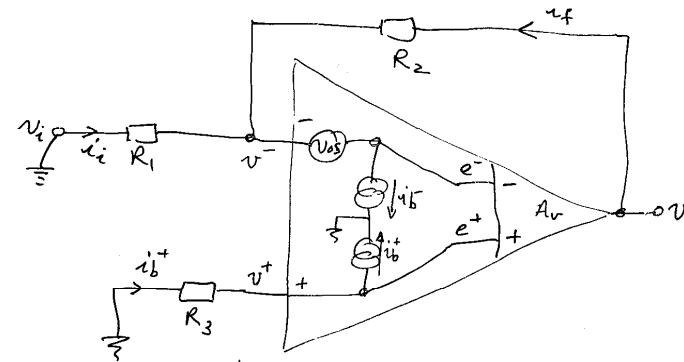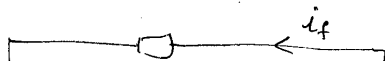

sum currents at v^- node

$$i_i + i_f = i_b^-$$

$$0 = \frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} = i_b^-$$

can be rearranged to give v^- explicitly

$$v^- = -\frac{R_1 R_2}{R_1 + R_2} \left[i_b^- - \frac{v_o}{R_2} \right] \quad (1)$$

$$v^- = v^- + V_{os} \quad (2)$$

$$v^+ = v^+ = -i_b^+ R_3 \quad (3)$$

Using the op-amp equation ...

$$v_o = A_v (v^+ - v^-)$$


$$v_o = A_v \left(-i_b^+ R_3 + i_b^- \frac{R_1 R_2}{R_1 + R_2} - \frac{v_o R_1}{R_1 + R_2} + V_{os} \right)$$

Can be neglected if $\frac{1}{A_v} \ll \frac{R_1}{R_1 + R_2}$

$$v_o \left[\frac{1}{A_v} + \frac{R_1}{R_1 + R_2} \right] = -i_b^+ R_3 + i_b^- \frac{R_1 R_2}{R_1 + R_2} + V_{os} \approx v_o \frac{R_1}{R_1 + R_2}$$


Manufacturers specify i_b = average input bias current = $\frac{i_b^+ + i_b^-}{2}$ and i_{os} .

$$i_b^+ = i_b + i_{os}/2$$

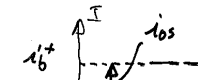

if $i_b^+ = i_b + i_{os}/2$
 $i_b^- = i_b - i_{os}/2$
 or if $i_b^+ = i_b - i_{os}/2$
 $i_b^- = i_b + i_{os}/2$
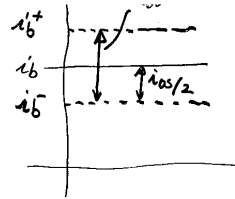
$$\boxed{\begin{aligned} i_b^+ &= i_b \pm i_{os}/2 \\ i_b^- &= i_b \mp i_{os}/2 \end{aligned}}$$



$$V_o \frac{R_1}{R_1 + R_2} = -(i_b \mp i_{os}/2) R_3 + (i_b \pm i_{os}/2) \frac{R_1 R_2}{R_1 + R_2} \mp V_{os}$$

$$V_o \frac{R_1}{R_1 + R_2} = i_b \left(-R_3 + \frac{R_1 R_2}{R_1 + R_2} \right) \pm \frac{i_{os}}{2} \left(\frac{R_1 R_2}{R_1 + R_2} + R_3 \right) \mp V_{os}$$

$$V_o = \underbrace{i_b \left(\frac{R_1 R_2}{R_1 + R_2} - R_3 \right) \frac{R_1 + R_2}{R_1}}_{\text{can be eliminated by making } \frac{R_1 R_2}{R_1 + R_2} = R_3} \pm \underbrace{\frac{i_{os}}{2} \left(\frac{R_1 R_2}{R_1 + R_2} + R_3 \right) \frac{R_1 + R_2}{R_1}}_{\text{can be affected by choosing low values of resistance}} \mp V_{os} \underbrace{\frac{R_1 + R_2}{R_1}}_{\text{stuck with this}}$$

putting $R_3 = \frac{R_1 R_2}{R_1 + R_2}$ into the result....


$$\begin{aligned} V_o &= 0 \pm \frac{i_{os}}{2} \left(\frac{R_1 R_2}{R_1 + R_2} + \frac{R_1 R_2}{R_1 + R_2} \right) \frac{R_1 + R_2}{R_1} \mp V_{os} \frac{R_1 + R_2}{R_1} \\ &\quad \pm \frac{i_{os}}{2} \left(\frac{2 R_1 R_2}{R_1 + R_2} \right) \frac{R_1 + R_2}{R_1} \\ &\quad \pm i_{os} R_2 \mp V_{os} \frac{R_1 + R_2}{R_1} \end{aligned}$$

Many op-amps offer an offset null capability


Many op-amps offer an offset null capability

offset nulls allow users to slightly alter the balance of currents through the op-amp input stages.

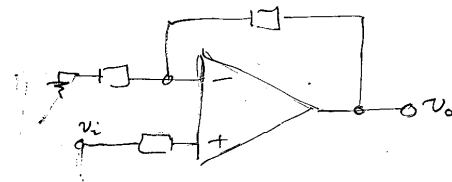application tends to be different for different op-amps LOOK AT DATA SHEET.




OFFSETS ARE DC EFFECTS

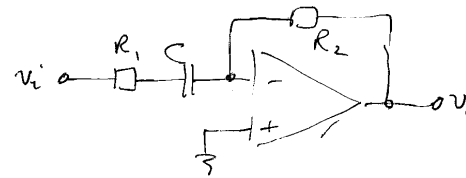

frequency Dependent feedback

The integrator

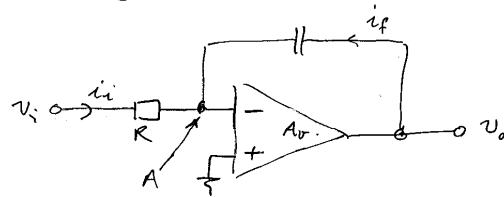

time domain
Sum currents at A.

frequency domain



$$i_i + i_f = 0$$

$$\frac{v_i - v^-}{R} + \frac{v_o - v^-}{1/sC} = 0 = \frac{v_i - v^-}{R} + (v_o - v^-)sC$$


$$\text{if } A_v \gg 1, v^- \approx v^+ = 0$$

$$\frac{v_i}{R} + v_o sC = 0 \quad \text{or} \quad \frac{v_o}{v_i} = -\frac{1}{sCR}$$

($s = j\omega$)

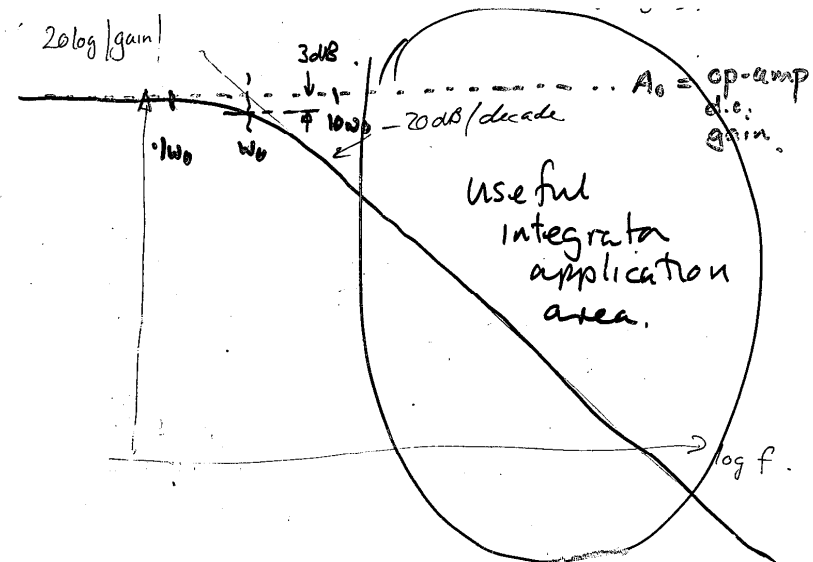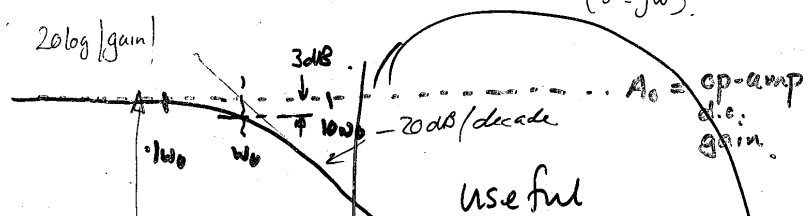


Differentiator cct

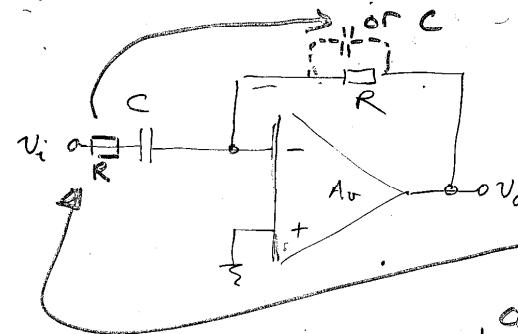


$$v_o = -CR \frac{dv_i}{dt}$$

$$\text{or } v_o = -sCR v_i$$

can be limited by.

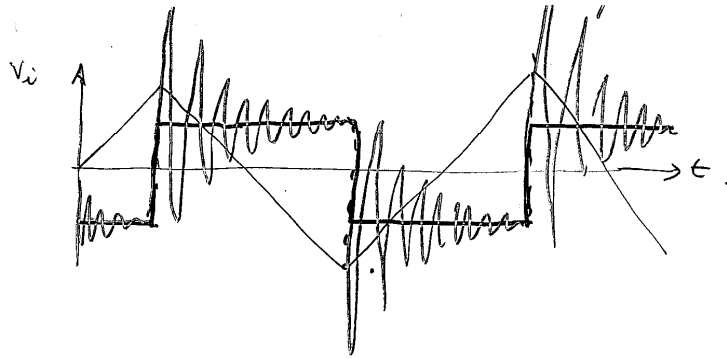

Pole-zero circuits

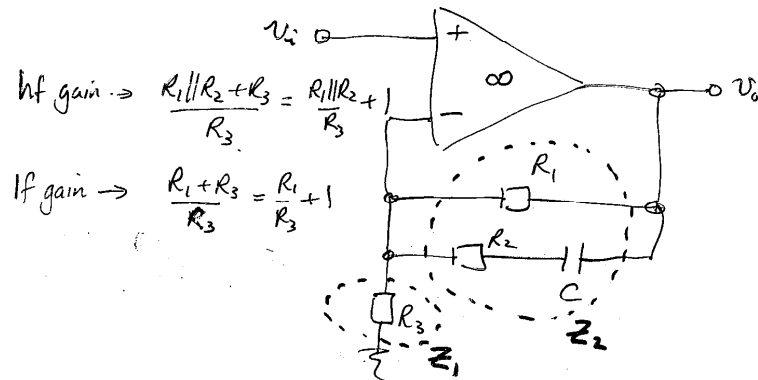

Want to find $\frac{v_o}{v_i}$ as function of $s (= j\omega)$.

$$\frac{v_o}{v_i} = \frac{Z_1 + Z_2}{Z_1}$$

$$Z_2 = R_1 \parallel (R_2 + 1/sC)$$

$$= \frac{R_1(R_2 + 1/sC)}{R_1 + R_2 + 1/sC} = \frac{R_1(1 + R_2 sC)}{1 + (R_1 + R_2) sC}$$

$$Z_1 = R_3$$


$$\frac{v_o}{v_i} = \frac{R_3 + \frac{R_1(1 + R_2 sC)}{1 + (R_1 + R_2) sC}}{R_3}$$


$$= \frac{R_3(1 + (R_1 + R_2) sC) + R_1(1 + R_2 sC)}{R_3(1 + (R_1 + R_2) sC)}$$

$$= \frac{R_3 + (R_1 + R_2) sC + R_1 + R_1 R_2 sC}{R_3(1 + (R_1 + R_2) sC)}$$


$$= \frac{(R_1 + R_3) + sC(R_1 R_3 + R_2 R_3 + R_1 R_2)}{R_3(1 + sC(R_1 + R_2))}$$
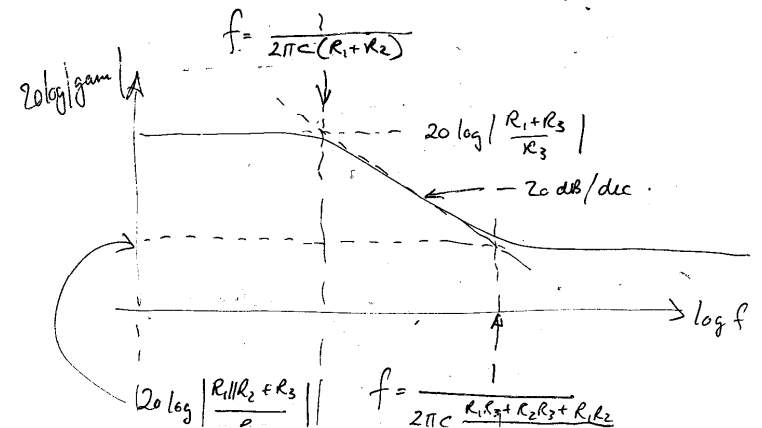
$$= \frac{R_1 + R_3}{R_3} \cdot \frac{1 + sC \frac{(R_1 R_3 + R_2 R_3 + R_1 R_2)}{R_1 + R_3}}{1 + sC(R_1 + R_2)}$$





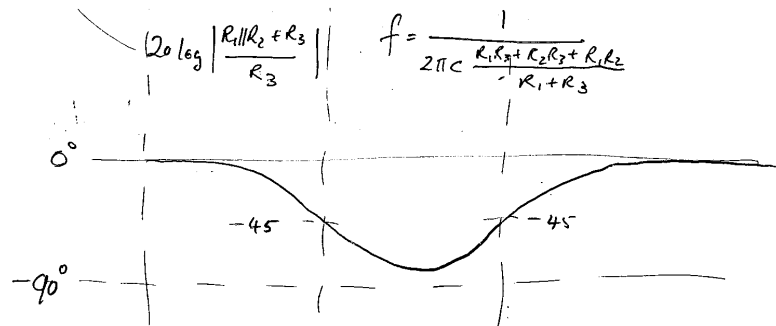

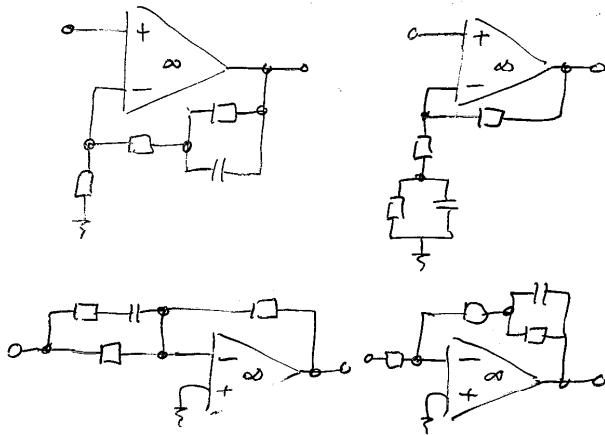
Can occur in a range of different shapes...




Intrinsic frequency response of op-amp.

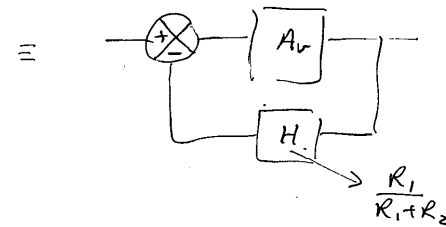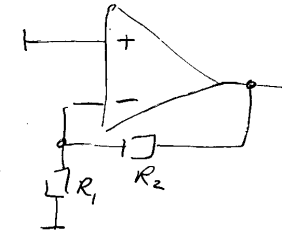

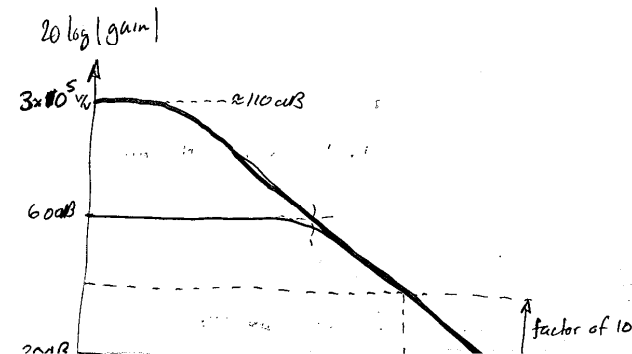- op-amp is designed to be first order by the manufacturer so that sales will be big.
- a few uncompensated amplifiers with 2nd and occasionally 3rd order responses are available for specialist use.



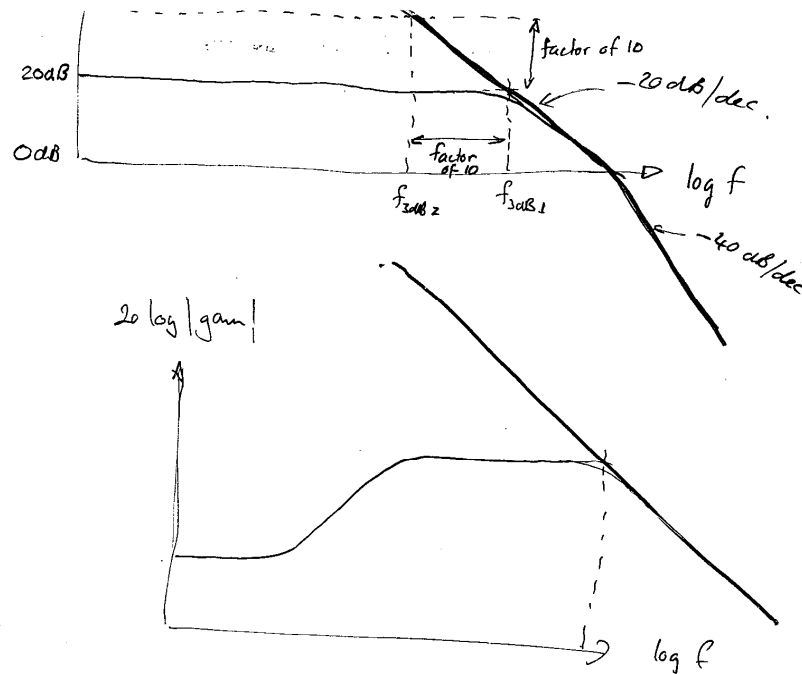


Cascades.

Sometimes it is necessary to use more than one amplifier to achieve a desired gain over a specified BW.

eg suppose a gain of 100 required with a BW of 500kHz.

— Single amp GBP needed is 50MHz.

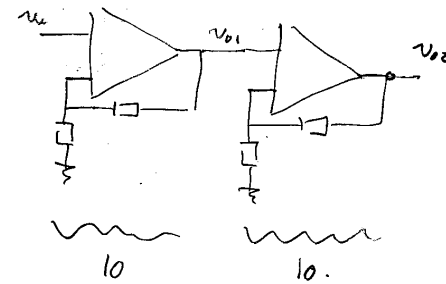The gain of 100 could be obtained by using two gains of 10 in series



$$\begin{aligned} \frac{v_{o1}}{v_i} &= \frac{10}{1 + j\omega/\omega_0} \\ &= \frac{10}{1 + jf/f_0} \\ &= 10 \times \frac{1}{1 + jf/f_0} \end{aligned} \quad \begin{aligned} \frac{v_{o2}}{v_{o1}} &= \frac{10}{1 + j\omega/\omega_0} \\ &= \frac{10}{1 + jf/f_0} \end{aligned}$$

at what f does $\left| \frac{1}{1 + jf/f_0} \right| = 10^{-1.5/20}$?

$$\left[\frac{1}{1 + (f/f_0)^2} \right]^{1/2} = 10^{-1.5/20}$$

$$\text{or } \frac{1}{1 + (f/f_0)^2} = 10^{-3/20} \approx \frac{1}{\sqrt{2}}$$


$$\sqrt{2} = 1 + (f/f_0)^2$$

$$\sqrt{(\sqrt{2} - 1)} = f/f_0 \approx 0.64$$

$$f = 0.64 f_0$$

Second Order Circuits

Example of 2nd order cct

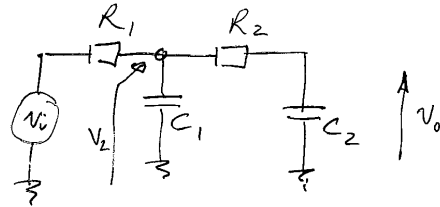

$$\frac{V_z}{V_i} = \frac{\frac{1}{sC_1} \left(R_2 + \frac{1}{sC_2} \right)}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}}$$

$$R_1 + \frac{\frac{1}{sC_1} \left(R_2 + \frac{1}{sC_2} \right)}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}}$$

$$\frac{\frac{1}{sC_1} \left(R_2 + \frac{1}{sC_2} \right)}{\frac{1}{sC_1} + R_2 + \frac{1}{sC_2}} = \frac{R_2 + \frac{1}{sC_2}}{1 + \frac{1}{sC_1}R_2 + \frac{C_1}{C_2}}$$

$$\frac{1 + sC_2R_2}{sC_2 + s^2C_1C_2R_2 + s \frac{C_1}{C_2}} = \frac{1 + sC_2R_2}{s(C_1 + C_2) + s^2C_1C_2R_2}$$

$$\frac{V_z}{V_i} = \frac{1 + sC_2R_2}{s(C_1 + C_2) + s^2C_1C_2R_2}$$

$$R_1 + \frac{1 + sC_2R_2}{s(C_1 + C_2) + s^2C_1C_2R_2}$$

$$= \frac{1 + sC_2R_2}{R_1(s(C_1 + C_2)) + s^2C_1C_2R_1R_2 + 1 + sC_2R_2}$$

$$= \frac{1 + sC_2R_2}{1 + s(R_1(C_1 + C_2) + C_2R_2) + s^2C_1C_2R_1R_2}$$

$$\frac{V_o}{V_z} = \frac{\frac{1}{sC_2}}{R_2 + \frac{1}{sC_2}} = \frac{1}{1 + sC_2R_2}$$

$$\frac{V_o}{V_i} = \frac{V_o}{V_z} \times \frac{V_z}{V_i} = \frac{1 + sC_2R_2}{1 + s(R_1(C_1 + C_2) + C_2R_2) + s^2C_1C_2R_1R_2} \cdot \frac{1}{1 + sC_2R_2}$$

$$= \frac{1}{1 + s(R_1C_1 + R_1C_2 + R_2C_2) + s^2C_1C_2R_1R_2}$$

Low pass standard form is

$$\frac{V_o}{V_i} = K \cdot \frac{1}{1 + \frac{s}{\omega_n Q} + \frac{s^2}{\omega_n^2}}$$

so for this transfer function

$$\omega_n = \sqrt{\frac{1}{C_1C_2R_1R_2}}$$

$$\frac{1}{\omega_n Q} = R_1C_1 + R_1C_2 + R_2C_2$$


$$\frac{1}{Q} = \omega_n (R_1C_1 + R_1C_2 + R_2C_2)$$

$$\begin{aligned}\frac{1}{Q} &= \omega_n (R_1 C_1 + R_1 C_2 + R_2 C_2) \\ &= \frac{R_1 C_1 + R_1 C_2 + R_2 C_2}{\sqrt{C_1 C_2 R_1 R_2}} \\ &= \sqrt{\frac{R_1 C_1}{R_2 C_2}} + \sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2 C_2}{R_1 C_1}}\end{aligned}$$

$$\frac{V_o}{V_i} = \frac{1}{1 + \frac{s^2}{\omega_0^2} + \frac{s^2}{\omega_0^2}}$$

$$\frac{1}{1 + \frac{s^2}{\omega_0^2}} \Rightarrow \frac{1}{1 + \frac{(j\omega)^2}{\omega_0^2}} = \frac{1}{1 - \frac{\omega^2}{\omega_0^2}}$$

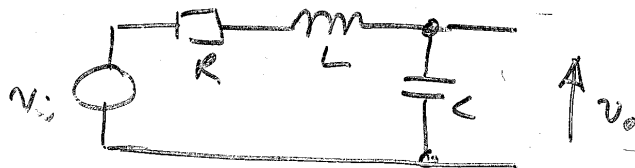high pass... k . $\frac{s^2/\omega_0^2}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$



$$\underline{V_o} = \underline{1/sC}$$

$$\begin{aligned}\frac{V_o}{V_i} &= \frac{1/sC}{R + sL + 1/sC} \\ &= \frac{1}{1 + sCR + s^2 LC}\end{aligned}$$



Compare with


$$\frac{1}{1 + \frac{s}{\omega_0 Q} + \frac{s^2}{\omega_0^2}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{1}{\omega_0 Q} = CR \quad \frac{1}{Q} = \frac{CR}{\sqrt{LC}} = R\sqrt{\frac{C}{L}}$$
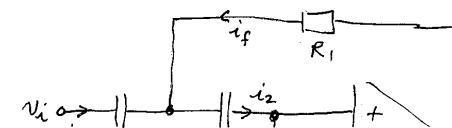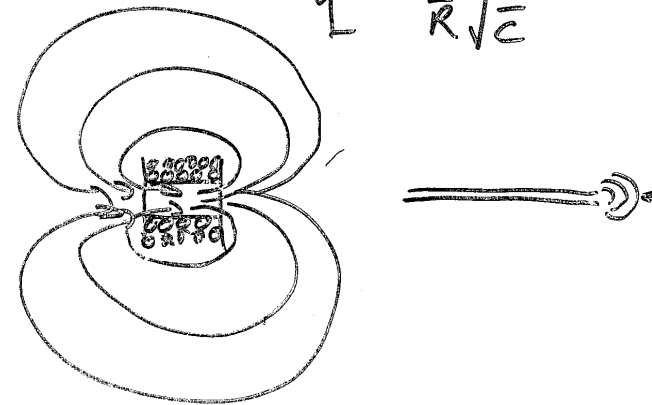
$$\therefore Q = \frac{1}{R}\sqrt{\frac{L}{C}}$$



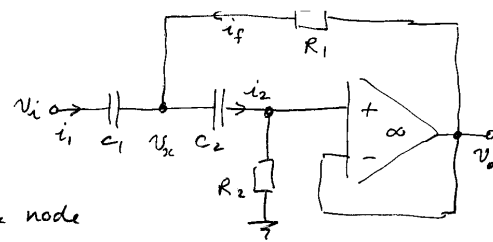

Sum currents at v_x node

$$i_1 + i_f = i_2$$

$$\frac{v_i - v_x}{1/sC_1} + \frac{v_o - v_x}{R_1} = \frac{v_x}{R_2 + 1/sC_2}$$

$$v_i sC_1 - v_x sC_1 + \frac{v_o - v_x}{R_1} = \frac{v_x \cdot sC_2}{R_2 sC_2 + 1}$$

$$v_i sC_1 + \frac{v_o}{R_1} = v_x \left[\frac{sC_2}{1 + sC_2 R_2} + \frac{1}{R_1} + sC_1 \right]$$

$$\begin{aligned} v_i sC_1 R_1 + v_o &= v_x \left[\frac{sC_2 R_1}{1 + sC_2 R_2} + 1 + sC_1 R_1 \right] \\ &= v_x \left[\frac{sC_2 R_1 + (1 + sC_2 R_2)(1 + sC_1 R_1)}{1 + sC_2 R_2} \right] \\ &= v_x \left[\frac{sC_2 R_1 + 1 + s(C_2 R_1 + C_1 R_1) + s^2 C_1 C_2 R_1 R_2}{1 + sC_2 R_2} \right] \end{aligned}$$

$$v_x = \frac{(v_i sC_1 R_1 + v_o)(1 + sC_2 R_2)}{1 + s(C_2 R_1 + C_1 R_1) + s^2 C_1 C_2 R_1 R_2}$$

The v^+ node relates v_x to v^+ by potential division and $v^+ = v_o$ since amplifier gain is unity

$$v^+ = \frac{v_x \cdot R_2}{R_2 + 1/sC_2} = v_o$$

$$v = \frac{v_x \cdot R_2}{R_2 + 1/sC_2} = v_o$$

$$\text{or } \frac{v_x sC_2 R_2}{1 + sC_2 R_2} = v_o$$

$$\text{or } v_x = \frac{v_o(1 + sC_2 R_2)}{sC_2 R_2}$$

eliminating v_x

$$\frac{v_o(1 + sC_2 R_2)}{sC_2 R_2} = \frac{(v_i sC_1 R_1 + v_o)(1 + sC_2 R_2)}{1 + s(C_2 R_1 + C_1 R_1) + s^2 C_1 C_2 R_1 R_2}$$

$$v_o \left[1 + s(C_2 R_1 + C_1 R_1) + s^2 C_1 C_2 R_1 R_2 - sC_2 R_2 \right] = v_i s^2 C_1 C_2 R_1 R_2$$

$$\frac{v_o}{v_i} = \frac{s^2 C_1 C_2 R_1 R_2}{1 + s(C_2 R_1 + C_1 R_1) + s^2 C_1 C_2 R_1 R_2}$$

standard HP form

$$\frac{s^2/w_0^2}{1 + s/w_0 Q + s^2/w_0^2}$$

$$w_0 = \sqrt{\frac{1}{C_1 C_2 R_1 R_2}}$$

$$\frac{1}{w_0 Q} = R_1(C_1 + C_2)$$

$$\text{so } \frac{1}{Q} = w_0 R_1(C_1 + C_2) = \frac{R_1(C_1 + C_2)}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$= \sqrt{\frac{R_1}{R_2}} \left[\sqrt{\frac{C_1}{C_2}} + \sqrt{\frac{C_2}{C_1}} \right]$$

is there a relationship b.t. v.i.

is there a relationship between the "C"s that will maximise q

$$\text{let } \sqrt{\frac{C_1}{C_2}} = x$$

$$\frac{1}{q} = \sqrt{\frac{R_1}{R_2}} \left[x + \frac{1}{x} \right]$$

maximising q is same as minimising $\frac{1}{q}$
so what x minimises $\frac{1}{q}$?

$$\frac{d(\frac{1}{q})}{dx} = \sqrt{\frac{R_1}{R_2}} \left[1 - \frac{1}{x^2} \right] = 0 \text{ for minimum}$$

$$\text{ie } \frac{1}{x^2} = 1 \text{ or } x = 1$$

$$\text{ie } \sqrt{\frac{C_1}{C_2}} = 1 \text{ or } C_1 = C_2$$

using this condition....

$$\frac{1}{q} = \sqrt{\frac{R_1}{R_2}} [1 + 1] = 2 \sqrt{\frac{R_1}{R_2}}$$

$$\text{or } q = \frac{1}{2} \sqrt{\frac{R_2}{R_1}}$$

and w_0 becomes $\frac{1}{\sqrt{R_1 R_2 C.C.}} = \frac{1}{C \sqrt{R_1 R_2}}$
 \uparrow
 "C"s are now equal