

$$\begin{aligned}
 Z &= \frac{\frac{1}{j\omega C}(R + j\omega L)}{\frac{1}{j\omega C} + R + j\omega L} \\
 &= \frac{R + j\omega L}{1 + j\omega CR + (j\omega)^2 LC} \\
 &= \frac{R + j\omega L}{(1 - \omega^2 LC) + j\omega CR} \\
 &= \frac{(R + j\omega L)(1 - \omega^2 LC - j\omega CR)}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2}
 \end{aligned}$$

taking just the j-term products from the top line (ie only the j x real terms)

$$\frac{j\omega L(1 - \omega^2 LC) - j\omega CR^2}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2} = 0$$

for resonance

$$1e \quad L - \omega^2 LC - CR^2 = 0$$

$$L - CR^2 = \omega^2 L^2 C$$

$$\frac{L - CR^2}{L^2 C} = \omega^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\therefore \omega = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Series to parallel transformations allow an impedance

$$Z = a + jb$$



to be expressed as an

admittance

$$Y = c + jd$$



$$eg \quad \frac{1}{Z} = \frac{1}{a + jb} = Y = \frac{a - jb}{a^2 + b^2}$$

$$\therefore c \equiv \frac{a}{a^2 + b^2}$$

$$d \equiv \frac{-jb}{a^2 + b^2}$$

Transient behaviour of circuits

— what is the response of the circuit to a sudden step change in its input conditions?


for C $I = C \frac{dV}{dt}$ or $V = \frac{1}{C} \int I dt$.

for L $V = L \frac{dI}{dt}$ or $I = \frac{1}{L} \int V dt$

Initial Conditions

- what is the state of the circuit before the step?
- what will be the conditions just after the step.

consider the cct

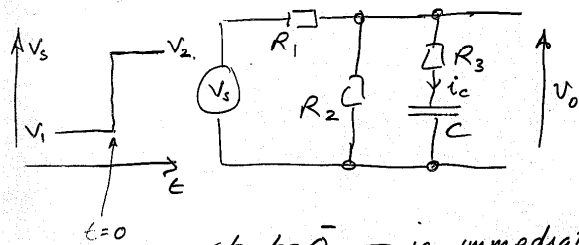

at $t=0^-$ — ie immediately before the step.

$i_c = 0$ (because no d.c. current flows through a capacitor).


$$V_0 = V_s \frac{R_2}{R_1 + R_2} = V_1 \frac{R_2}{R_1 + R_2}$$

$$\left[V_c = V_0 = \frac{V_1 R_2}{R_1 + R_2} \right]$$

at $t=0$ — ie immediately after the step.

$$\left[V_c = \frac{V_1 R_2}{R_1 + R_2} \rightarrow \text{between } t=0^- \text{ and } t=0^+ \text{ } C \text{ behaves like a voltage source.} \right]$$

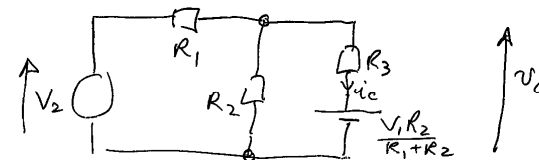We can re-draw the circuit at $t=0^+$ with C replaced by a voltage source of value $\frac{V_1 R_2}{R_1 + R_2}$




the $t=0^+$ equivalent cct.

$$V_0 = V_2 \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} + \frac{V_1 R_2}{R_1 + R_2} \cdot \frac{R_1 \parallel R_2}{R_3 + R_1 \parallel R_2}$$

$$i_c = \frac{V_0 - \frac{V_1 R_2}{R_1 + R_2}}{R_3}$$

Consider another cct

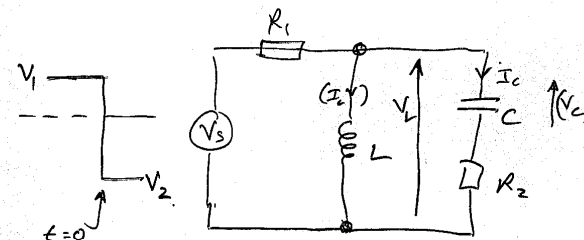


conditions at $t=0^-$

$$V_L = 0$$

$$I_c = 0$$

$$\left[V_c = 0, I_L = \frac{V_1}{R_1} \right]$$

at $t = 0^+$

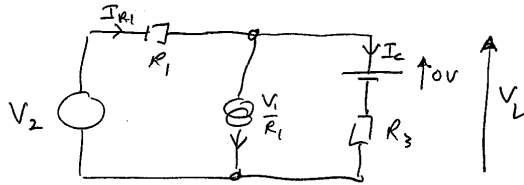


$$V_L = V_2 \frac{R_3}{R_1 + R_3} + \left(-\frac{V_1}{R_1} \cdot R_1 \parallel R_3 \right)$$

$$I_{R1} = \frac{V_2 - V_L}{R_1}$$

$$I_c = I_{R1} - \frac{V_1}{R_1}$$

An example transient analysis

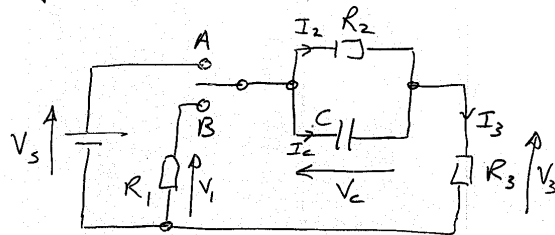

assume switch has been in position A for a long time

— aim is to form a differential equation with V_c as the subject

... ..

— first sum voltages at $t = 0^+$

$$V_1 = V_c + V_3$$

$$-I_3 R_1 = V_c + I_3 R_3$$

$$\text{or } 0 = V_c + I_3 (R_1 + R_3)$$

Summing currents at the R_3, R_2 node.

$$I_3 = I_c + I_2 = C \frac{dV_c}{dt} + \frac{V_c}{R_2}$$

$$0 = V_c + \left(C \frac{dV_c}{dt} + \frac{V_c}{R_2} \right) (R_3 + R_1)$$

$$-V_c \left[1 + \frac{R_3 + R_1}{R_2} \right] = C \frac{dV_c}{dt} (R_1 + R_3)$$

$$- \left[1 + \frac{R_3 + R_1}{R_2} \right] \frac{dV_c}{V_c} = \frac{dV_c}{dt} C (R_1 + R_3)$$

let this = k

Integrate both sides

$$-k t + \text{const} = \ln V_c$$

$$e^{(-kt + \text{const})} = V_c = e^{-kt} e^{\text{const}} = A e^{-kt}$$

where $A = \text{const. (another one)}$

The conditions at $t = 0^+$ will give the value

at A
when $t=0^+$ $V_c = V_s \frac{R_2}{R_3+R_2}$

$$\therefore V_c(t) = V_s \frac{R_2}{R_3+R_2} e^{-kt}$$

$$k = \frac{R_2+R_3+R_1}{CR_2(R_1+R_3)} = \frac{1}{\tau}$$

$$V_c(t) = V_s \frac{R_2}{R_3+R_2} e^{-t/\tau}$$

$$\tau = \frac{1}{k} = \frac{CR_2(R_1+R_3)}{R_2+R_3+R_1}$$


If at the outset one had gone for an equation with I_c as the subject.

$$-I_c = \frac{dI_c}{dt} \cdot \frac{C(R_1+R_3)R_2}{R_1+R_2+R_3}$$

— This is the same equation as the one just derived except that V_c is replaced by I_c . This because all voltages & currents in the circuit arising as a response to the step will have the same exponential form.

Exponential Geometry:

$$\int \frac{dx}{a+bx} =$$

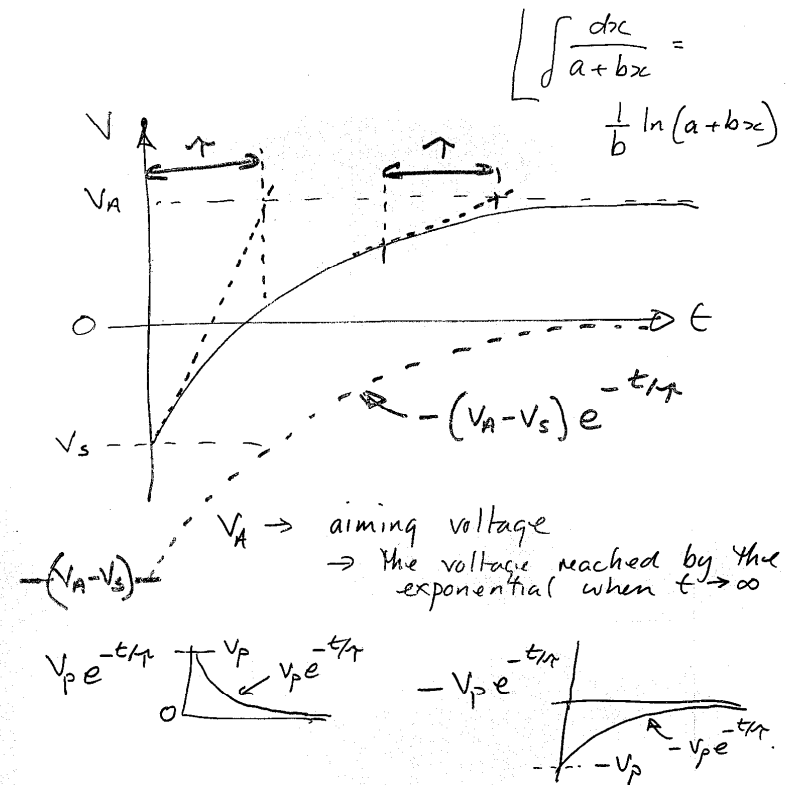

need to add V_A to the basic shape


$$-(V_A - V_s)e^{-t/\tau}$$

to give $V(t) = V_A - (V_A - V_s)e^{-t/\tau}$

For any simple exponential

$$V(t) = (V_{\text{start}} - V_{\text{aiming}})e^{-t/\tau} + V_{\text{aiming}}$$


To find τ

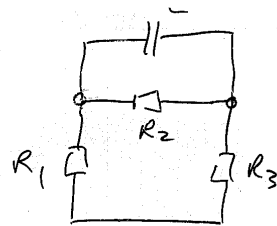

look at cct from point of view of C


$$\tau = C R_2 \parallel (R_1 + R_3)$$

look at another circuit

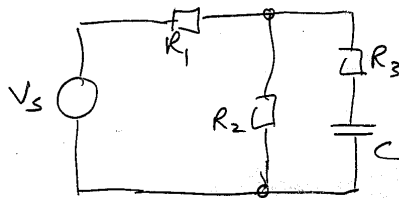


$$\tau = C (R_3 + (R_1 \parallel R_2))$$

look at another cct

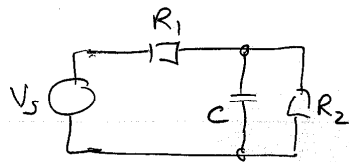

$$\tau = C (R_1 \parallel R_2)$$

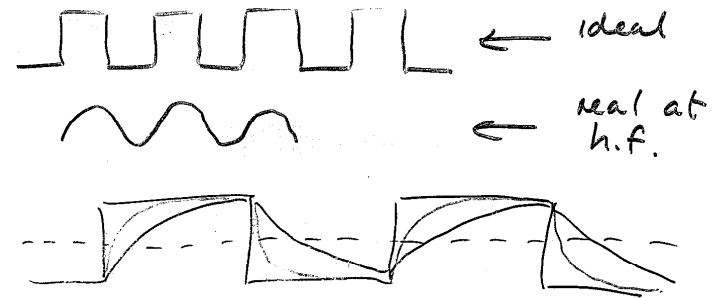

Feedback on Homework 4.

$$V \angle \phi \Rightarrow a + jb.$$

$$a = V \cos \phi$$

$$b = V \sin \phi$$


$$3 \cos(\omega t + 45^\circ) \quad \cos(\omega t + 0^\circ)$$

↑ ↑
magnitude phase.

$$3 \angle (\omega t + 45^\circ) \rightarrow \text{X} \quad \text{should be } 3 \angle 45^\circ$$

$$4 \sin \omega t = 4 \cos(\omega t - 90^\circ)$$

$$4 \angle -90^\circ.$$

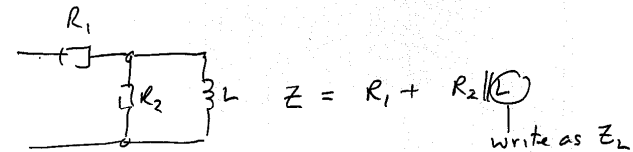

$$R_1 + \frac{R_2 L}{R_2 + L}$$

$$= R_1 + \frac{R_2 j\omega L}{R_2 + j\omega L}$$

Decibels

— originally a power ratio

$$P \text{ in dB} = 10 \log \frac{P_1}{P_2}$$

often power (acoustically) is specified in terms of dB

eg 90 dB

- only makes sense if a reference level is defined
- usually human hearing threshold $\approx 10^{-12} \text{ W}$.




In terms of voltage

$$\text{dB} = 20 \log \frac{V_2}{V_1}$$

$$\text{dBV} = 20 \log \frac{V}{1 \text{ V}_{\text{rms}}}$$

In terms of electrical

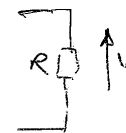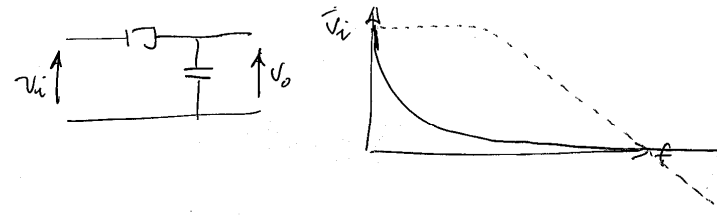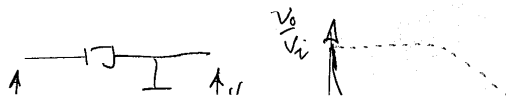
$$\text{dB}_m = 10 \log \frac{P}{1 \text{ mW into } 50 \Omega}$$



Voltage in dB $20 \log \frac{V}{V_{\text{ref}}}$

Power in dB $10 \log \left(\frac{V}{V_{\text{ref}}} \right)^2$

Standard forms of 1st order xcts.

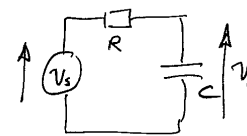


$$\frac{V_o}{V_s} = \frac{1/j\omega C}{R + 1/j\omega C}$$

$$= \frac{1}{1 + j\omega RC}$$

define constant ω_0
where $\omega_0 = \frac{1}{RC}$

$$= \frac{1}{1 + j\omega/\omega_0}$$

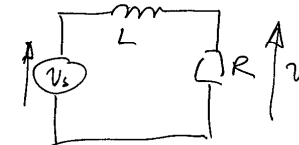

$$\frac{V_o}{V_s} = \frac{R}{R + j\omega L}$$

$$= \frac{1}{1 + j\omega L/R}$$

define a constant ω_1
where $\omega_1 = \frac{1}{L/R}$

$$= \frac{1}{1 + j\omega/\omega_1}$$

This function has a well defined response
— look at 3 frequencies

$$\begin{aligned} f &\ll f_0 \quad (\omega \ll \omega_0) \\ f &\gg f_0 \quad (\omega \gg \omega_0) \\ f &= f_0 \quad (\omega = \omega_0) \end{aligned}$$

$$\frac{V_o}{V_s} = \frac{1}{1 + j\omega/\omega_0}$$

$$\left| \frac{V_o}{V_s} \right| = \left[\frac{1}{1 + (\omega/\omega_0)^2} \right]^{1/2}$$

$$\left| \frac{V_o}{V_s} \right|_{f \ll f_0} = \left[\frac{1}{1} \right]^{1/2} \left[\text{because } \left(\frac{\omega}{\omega_0} \right)^2 \ll 1 \right] = 1 \Rightarrow 0 \text{ dB}$$


$$\left| \frac{V_o}{V_s} \right|_{f=f_0} = \left[\frac{1}{1+1} \right]^{1/2} = \frac{1}{\sqrt{2}} \Rightarrow -3 \text{ dB}$$

$$\left| \frac{V_o}{V_s} \right|_{f \gg f_0} = \left[\frac{1}{(\omega/\omega_0)^2} \right]^{1/2} \left[\text{because } \left(\frac{\omega}{\omega_0} \right)^2 \gg 1 \right] = \frac{\omega_0}{\omega}$$

\Rightarrow slope of -20 dB/decade on a logarithmic plot.

or -6 dB/octave

(an octave = factor of 2 change in f .)

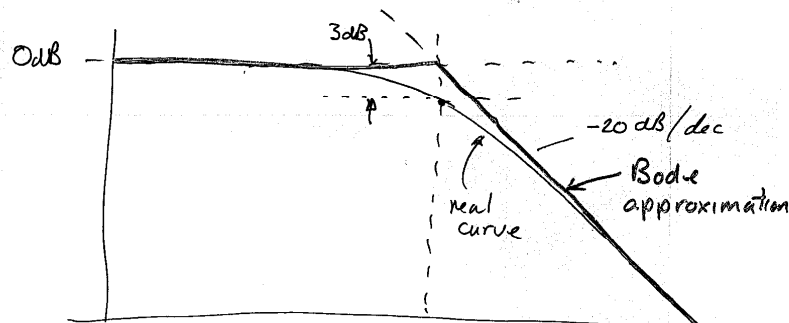

What about phase.


$$\frac{V_o}{V_s} = \frac{1}{1 + j\omega/\omega_0}$$

$$\angle \left(\frac{V_o}{V_s} \right) = -\tan^{-1} \frac{\omega/\omega_0}{1}$$


when $\omega \ll \omega_0$ $\phi \Rightarrow -\tan^{-1}(\text{a small fraction})$
 $\Rightarrow 0$ from below.

when $\omega = \omega_0$ $\phi = -\tan^{-1} 1 = -45^\circ$

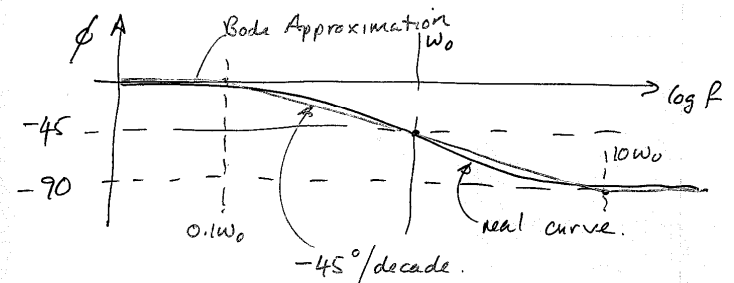when $\omega \gg \omega_0$ $\phi = -\tan^{-1}(\text{a large number})$
 $\Rightarrow -90$ from above.



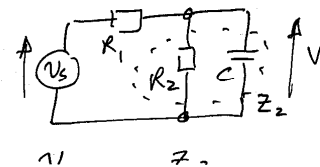
The most common complication is the introduction of a gain term.



$$\begin{aligned}\frac{V_o}{V_s} &= \frac{Z_2}{R_1 + Z_2} \quad Z_2 = R_2 \parallel Z_C = \frac{R_2 / j\omega C}{R_2 + 1/j\omega C} \\ &= \frac{\frac{R_2}{1+j\omega CR_2}}{R_1 + \frac{R_2}{1+j\omega CR_2}} = \frac{R_2}{R_1(1+j\omega CR_2) + R_2} = \frac{R_2}{(R_1+R_2) + j\omega CR_1 R_2} \\ &= \frac{R_2}{(R_1+R_2)(1 + j\omega C \frac{R_1 R_2}{R_1+R_2})} \\ &= k \cdot \frac{1}{1+j\omega\omega_0} \quad \text{where } k = \frac{R_2}{R_1+R_2} \quad \omega_0 = \frac{1}{C \frac{R_1 R_2}{R_1+R_2}}\end{aligned}$$

$$\begin{aligned}20 \log \left| k \cdot \frac{1}{1+j\omega\omega_0} \right| \\ = 20 \log k + 20 \log \left| \frac{1}{1+j\omega\omega_0} \right|\end{aligned}$$

High pass circuits

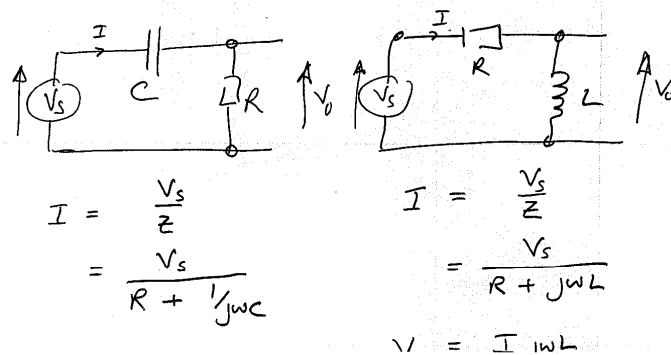

$$\begin{aligned}V_o &= IR \\ &= \frac{V_s R}{R + 1/j\omega C}\end{aligned}$$

$$\frac{V_o}{V_s} = \frac{j\omega CR}{1 + j\omega CR}$$

$$\text{let } CR = \frac{1}{\omega_0}$$

$$\frac{V_o}{V_s} = \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}$$

$$\begin{aligned}V_o &= \frac{1}{j\omega L} \\ &= \frac{V_s j\omega L}{R + j\omega L}\end{aligned}$$

$$\frac{V_o}{V_s} = \frac{j\omega L/R}{1 + j\omega L/R}$$


$$\text{let } \frac{L}{R} = \frac{1}{\omega_0}$$

$$\frac{V_o}{V_s} = \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}$$

$$\begin{aligned}20 \log \left| \frac{V_o}{V_s} \right| &= 20 \log \left| \frac{j\omega/\omega_0}{1 + j\omega/\omega_0} \right| \\ &= 20 \log |j\omega/\omega_0| + 20 \log \left| \frac{1}{1 + j\omega/\omega_0} \right|\end{aligned}$$


$$\begin{aligned}|j\omega/\omega_0| &= \frac{\omega}{\omega_0} \\ \text{ie } |j\omega/\omega_0| &\propto \omega\end{aligned}$$

Response is

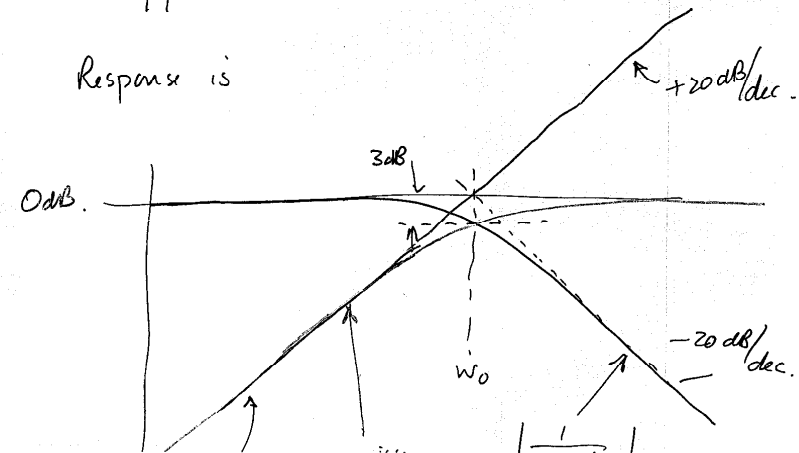

$$\sqrt{\frac{1}{1 + j\omega/\omega_0}} \quad \left| \frac{j\omega/\omega_0}{1 + j\omega/\omega_0} \right| \quad \left| \frac{1}{1 + j\omega/\omega_0} \right|$$

Linear sum of high pass + low pass

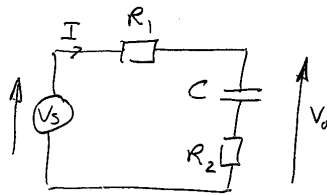

$$\frac{V_s}{Z} = I$$

$$I = \frac{V_s}{R_1 + \frac{1}{j\omega C} + R_2}$$

$$V_o = I(R_2 + \frac{1}{j\omega C})$$

$$= \frac{V_s (R_2 + \frac{1}{j\omega C})}{R_1 + R_2 + \frac{1}{j\omega C}}$$

$$\frac{V_o}{V_s} = \frac{1 + j\omega C R_2}{1 + j\omega C (R_1 + R_2)}$$

$$\text{let } \frac{1}{C R_2} = \omega_0 \quad \text{let } \frac{1}{C (R_1 + R_2)} = \omega_1$$


$$\frac{V_o}{V_s} = \frac{1 + j\omega/\omega_0}{1 + j\omega/\omega_1}$$

ASIDE


ω_1

$$\begin{aligned} \frac{1 + j\omega/\omega_0}{1 + j\omega/\omega_1} &= \frac{1}{1 + j\omega/\omega_1} + \frac{j\omega/\omega_0}{1 + j\omega/\omega_1} \\ &= \frac{1}{1 + j\omega/\omega_1} + \frac{\frac{1}{\omega_0} \cdot \omega_1 \cdot j\omega/\omega_1}{1 + j\omega/\omega_1} \\ &= \frac{1}{1 + j\omega/\omega_1} + \frac{\omega_1}{\omega_0} \cdot \frac{j\omega/\omega_1}{1 + j\omega/\omega_1} \end{aligned}$$

$$\begin{aligned} 20 \log \left| \frac{V_o}{V_s} \right| &= 20 \log \left| \frac{1 + j\omega/\omega_0}{1 + j\omega/\omega_1} \right| \\ &= 20 \log \left| 1 + j\omega/\omega_0 \right| + 20 \log \left| \frac{1}{1 + j\omega/\omega_1} \right| \end{aligned}$$

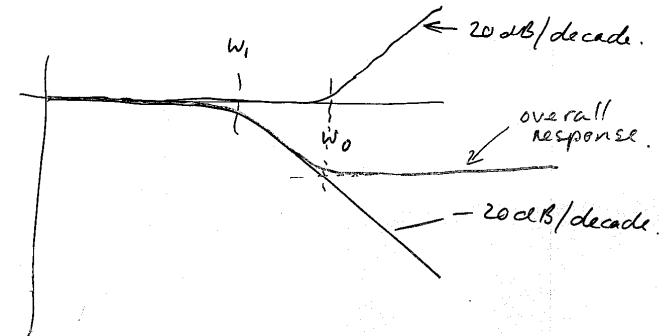


scope probe

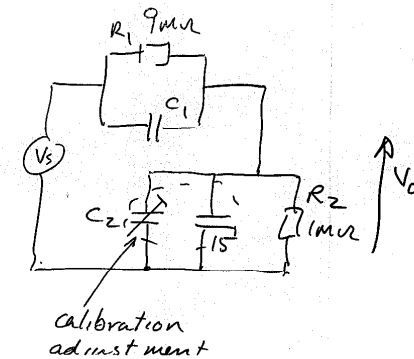


$$\begin{aligned}
 \frac{V_o}{V_i} &= \frac{\frac{R_2/j\omega C_2}{R_2 + j\omega C_2}}{\frac{R_1/j\omega C_1}{R_1 + j\omega C_1} + \frac{R_2/j\omega C_2}{R_2 + j\omega C_2}} = \frac{\frac{R_2}{1+j\omega C_2 R_2}}{\frac{R_1}{1+j\omega C_1 R_1} + \frac{R_2}{1+j\omega C_2 R_2}} \\
 &= \frac{\left(\frac{R_2}{1+j\omega C_2 R_2}\right)}{\left(\frac{R_1(1+j\omega C_2 R_2) + R_2(1+j\omega C_1 R_1)}{(1+j\omega C_1 R_1)(1+j\omega C_2 R_2)}\right)} \\
 &= \frac{R_2(1+j\omega C_1 R_1)}{R_1 + R_2 + j\omega(C_1 + C_2)R_1 R_2} \\
 &= \frac{R_2}{R_1 + R_2} \cdot \frac{1+j\omega C_1 R_1}{1+j\omega(C_1 + C_2)\frac{R_1 R_2}{R_1 + R_2}}
 \end{aligned}$$

To make the frequency dependent terms disappear, need to make time constants in the numerator and denominator the same
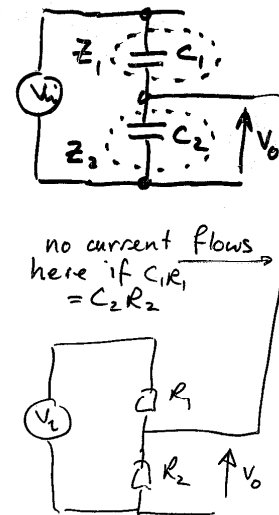
$$\begin{aligned}
 \text{ie } C_1 R_1 &= (C_1 + C_2) \frac{R_1 R_2}{R_1 + R_2} \\
 \text{or } C_1 R_1 (R_1 + R_2) &= (C_1 + C_2) R_1 R_2 \\
 \text{or } C_1 R_1^2 + C_1 R_1 R_2 &= C_1 R_1 R_2 + C_2 R_1 R_2 \\
 C_1 R_1^2 &= C_2 R_1 R_2 \\
 \text{or } C_1 R_1 &= C_2 R_2
 \end{aligned}$$



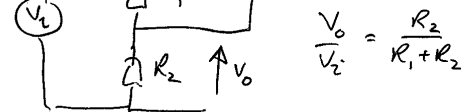
$$\begin{aligned}
 \frac{V_o}{V_i} &= \frac{Z_2}{Z_1 + Z_2} \\
 &= \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_1} + \frac{1}{j\omega C_2}} = \frac{\frac{1}{C_2}}{\frac{1}{C_1} + \frac{1}{C_2}} \\
 &= \frac{\frac{1}{C_2}}{\frac{C_1 + C_2}{C_1 C_2}} = \frac{C_1 C_2}{C_1 + C_2} = \frac{C_1}{C_1 + C_2}
 \end{aligned}$$




$$\frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2}$$

Time constant by inspection

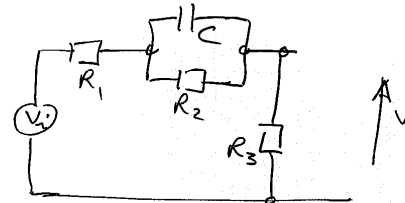


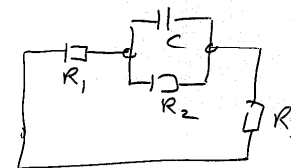(i) replace source by its internal impedance




from C's point of view there are two possible discharge paths

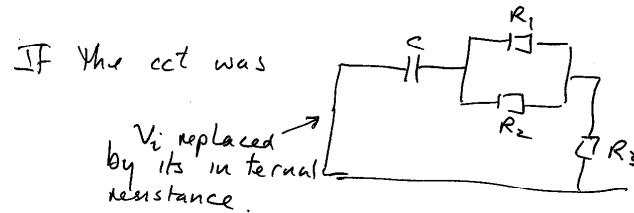one through R_2
 — one through the R_1, R_3 combination
 The two paths are in parallel
 Net resistance seen by C is $R_2 \parallel (R_1 + R_3)$
 so $\tau = C R_2 \parallel (R_1 + R_3)$



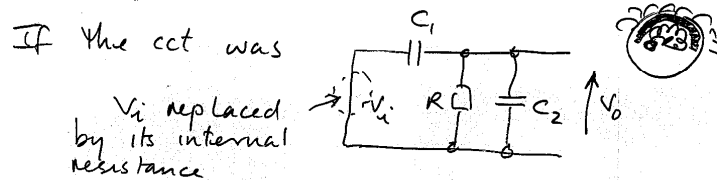Here there is only one path
 out of C through $R_1 \parallel R_2$ and through
 R_3
 $\tau = C (R_3 + (R_1 \parallel R_2))$



$$\tau = R(C_1 + C_2)$$


$$\frac{V_o}{V_i} = \frac{\frac{R}{1 + j\omega C_2 R}}{\frac{1}{j\omega C_1} + \frac{R}{1 + j\omega C_2 R}} = \frac{\frac{R}{1 + j\omega C_2 R}}{\frac{1 + j\omega C_2 R + j\omega C_1 R}{1 + j\omega C_2 R}} = \frac{R}{1 + j\omega C_1 R + j\omega C_2 R} = \frac{R}{1 + j\omega R(C_1 + C_2)}$$

$$= \frac{C_1 R}{1 + j\omega R(C_1 + C_2)}$$


$$= \frac{C_1 R}{R(C_1 + C_2)} \frac{j\omega R(C_1 + C_2)}{1 + j\omega R(C_1 + C_2)}$$

$$= k \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}$$

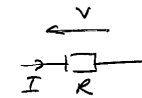
Some practical issues with inductors resistors
 and capacitors.



$$V = IR$$

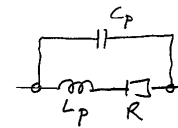

← a more realistic model of
 a resistor

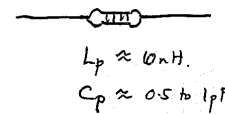

$$L_p \approx 10 \text{ nH}$$

$$C_p \approx 0.5 \text{ to } 1 \text{ pF}$$

$$Z \text{ of } 10 \text{ nH @ } 100 \text{ MHz} \approx 2\pi f L$$


$$6.10^8 \cdot 10^{-8}$$

$$\approx 6 \Omega$$

$$Z \text{ of } 1 \text{ pF at } 1 \text{ MHz}$$



$$Z_c = \frac{1}{2\pi f C} \approx \frac{1}{6 \times 10^{-12} \times 10^6} \approx 0.16 \times 10^6$$

$$\approx 160 \text{ k}\Omega$$

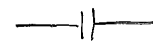


ideal model



— dominant loss mechanisms

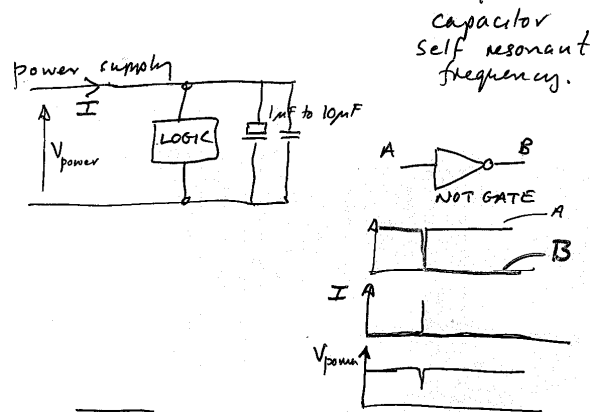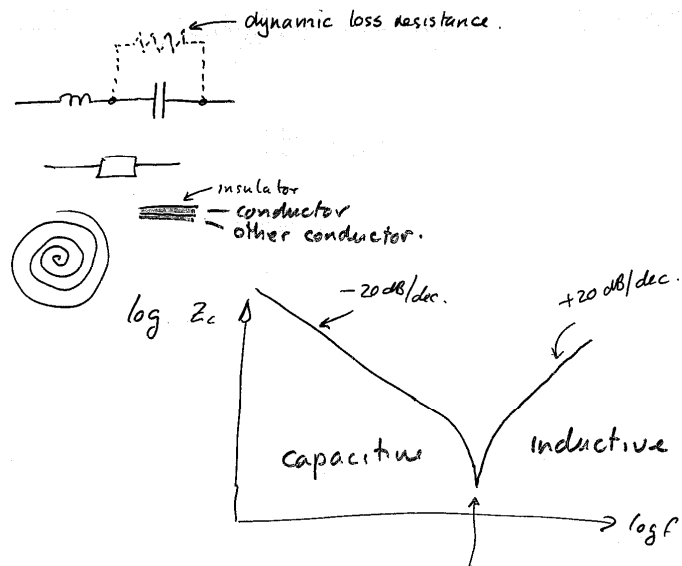


structure of
h.f. caps.

 

inductor

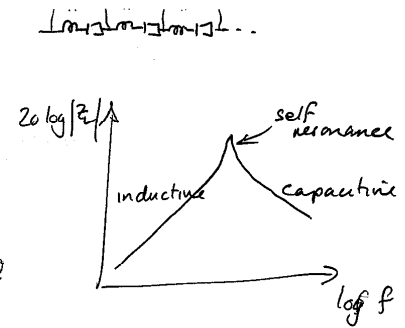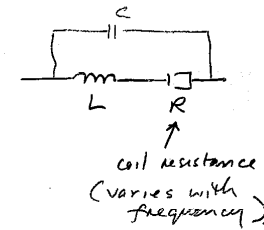

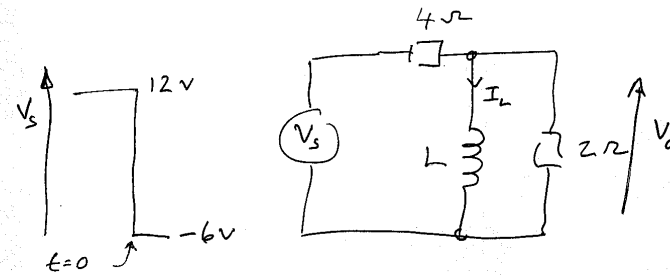inductor $Q = \frac{\omega L}{R}$
specified by manufacturers
at a particular frequency





Find $I_L + V_o$ at $t=0^-$ $t=0^+$ and as $t \rightarrow \infty$
at $t=0^-$ $V_o = V_L = 0V$ since $\frac{dI_L}{dt}$ must be zero at dc.

$$I_L = \frac{V_s - V_o}{4\Omega} = \frac{V_s - 0}{4\Omega}$$

$$= \frac{12}{4} = 3A$$

since $V_o = 0V$ so $I_{2\Omega} = 0$

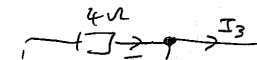at $t=0^+$ 

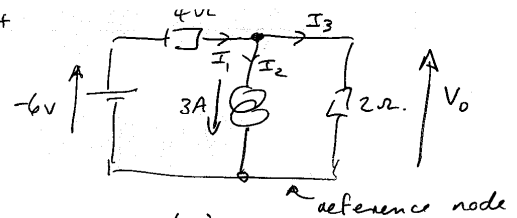at $t = 0^+$ 

Could use superposition

$$V_o \Big|_{-6V} = -6 \times \frac{2}{2+4} = -2V$$

$$V_o \Big|_{3A} = -3A \times \frac{2 \times 4}{2+4} = -\frac{8 \times 3}{6} V = -4V$$

$$V_o \Big|_{t=0^+} = (-2 + -4)V = -6V$$

A nodal approach $I_1 = I_2 + I_3$

$$\frac{-6 - V_o}{4} = 3 + \frac{V_o}{2}$$

$$\frac{-6}{4} - 3 = \frac{V_o}{2} + \frac{V_o}{4}$$

$$-6 - 12 = 2V_o + V_o$$


$$-18 = 3V_o$$

$$V_o = -6V$$

As $t \Rightarrow \infty$



— all the changes that happened at the transient will have ~~settled~~ settled down

— all quantities will be constant — i.e. dc.

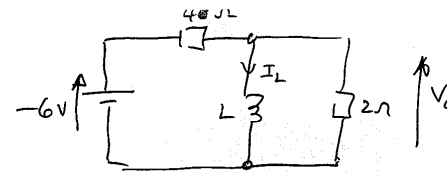4Ω

since this is a dc problem $V_L = 0$
(because $\frac{dI_L}{dt} = 0$)


$$I_L = \frac{-6V - 0}{4\Omega} = -1.5A$$

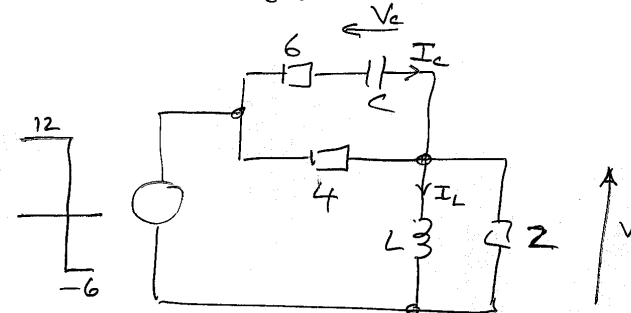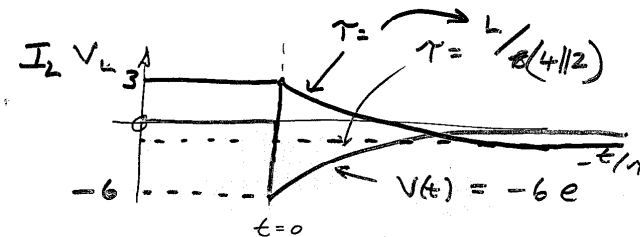at $t = 0^-$

$I_C = 0$ C doesn't conduct at dc
 $V_o = 0$ L looks like oz at d.c.

$$I_L = \frac{12 - V_o}{4} = \frac{12}{4} = 3A$$

$$V_o = V$$

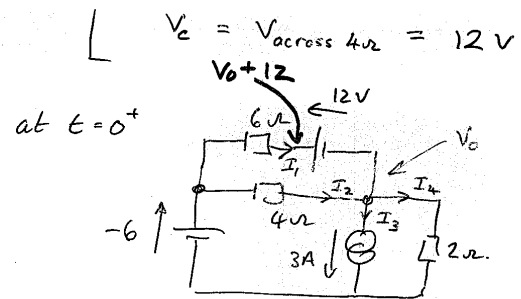

$$I_1 + I_2 = I_3 + I_4$$

$$3 + (-4.09)$$

$$= -1.64 + 0.55$$

$$\frac{-6 - (V_0 + 12)}{6} + \frac{-6 - V_0}{4} = 3 + \frac{V_0}{2}$$

$$-1 - \frac{V_0}{6} - 2 + (-1.5) - \frac{V_0}{4} = 3 + \frac{V_0}{2}$$

$$-4.5 - 3 = \frac{V_0}{2} + \frac{V_0}{4} + \frac{V_0}{6}$$

$$\frac{-6 - (-8.18)}{4}$$

$$-27 - 18 = 3V_0 + 1.5V_0 + V_0$$

$$-45 = 5.5V_0$$

$$\frac{2.18}{4} \quad 0.55$$

$$V_0 = \frac{-45}{5.5} = -8.18\text{ V}$$

$$I_c = I_1 = \frac{-6 - (-8.18 + 12)}{6}$$

$$= -1 - \frac{3.82}{6}$$

$$= -1.64\text{ A}$$