

Examination Feedback for EEE307 / 6023 – Power Electronics
Spring Semester 2012-13

Feedback for EEE307 / 6023 Session: 2012-2013

Feedback: Please write simple statements about how well students addressed the exam paper in general and each individual question in particular including common problems/mistakes and areas of concern in the boxes provided below. Increase row height if necessary.

General Comments:

Good exam. Generally answered well with a good average.

Question 1:

Solicited good answers, except for the people who described a hard switched buck converter instead of describing resonant switching as asked.

Question 2:

Well answered question, similar to one used before

Question 3:

Mostly good answers, people not knowing the difference between inductive and resistive loads for the derivation.

Question 4:

Good answers, most people forgot to work out the power rating of the snubber resistor