

EER 225

Exam Ques:

Q₁: From 2014 APRIL Q3


THIS Q₁ IS ABOUT ANATOMY OF AN OPAMP:-
TO SHOW THAT THE hFE OF THE DARLINGTON PAIR

IS GIVEN BY :

$$h_{FE0} = h_{FE1} + h_{FE2} + h_{FE1} \cdot h_{FE2}$$

WHERE h_{FE1} IS THE CURRENT GAIN OF T₁ &
 h_{FE2} " "

(3)

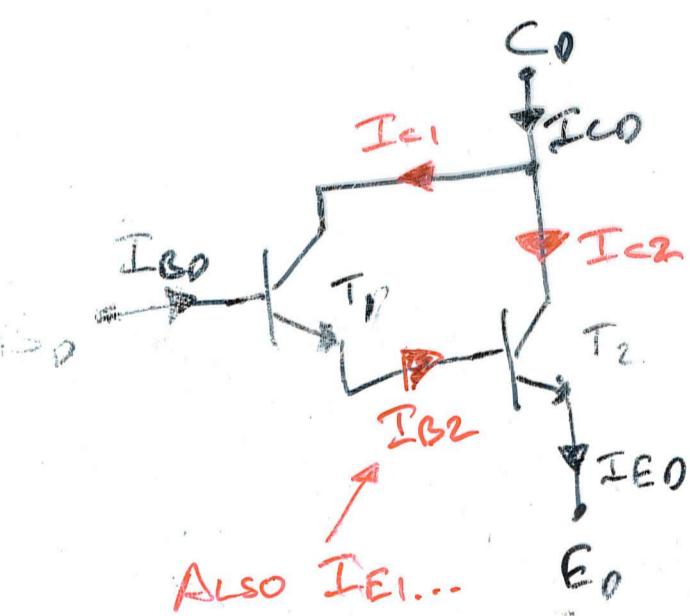

SOLUTION:

* NEED TO FIND I_{c0} IN TERMS OF

I_{B0} S. THAT I_{c0}/I_{B0} CAN BE COMPUTED...

* ADD CURRENTS I_{c1} , I_{c2} & I_{B2} TO THE DIAGRAM.

$$I_{c1} = h_{FE1} \cdot I_{B0}$$

$$I_{B2} + I_{E1} = I_{c1} + I_{B0} = h_{FE1} \cdot I_{B0} + I_{B0}$$

$$I_{c2} = h_{FE2} \cdot I_{B2}$$

$$I_{cA} = I_{c1} + I_{c2}$$

* COLLECT TERMS AND FIND I_{c0}/I_{B0} ...

$$I_{c0} = h_{FE1} \cdot I_{B0} + I_{c2} \cdot (h_{FE1} \cdot I_{B0} + I_{B0})$$

SIMPLIFY...


$$\frac{I_{CO}}{I_{BO}} = \frac{h_{FE1} \cdot I_{BO} + h_{FE2} \cdot (h_{FE1} \cdot I_{BO} + I_{SO})}{I_{BO}}$$

$$\frac{I_{CO}}{I_{SO}} = h_{FE1} + h_{FE2} \cdot h_{FE1} + h_{FE2}$$

Q.E.D.

ii) THE DARLINGTON IS USED TO MAKE A COMMON Emitter AMPLIFIER... E_1 IS CONNECTED TO GROUND, B_1 TO A SIGNAL SOURCE, C_0 IS CONNECTED TO A LOAD RESISTOR R_L , THE OTHER END OF WHICH IS CONNECTED TO A POWER SUPPLY.


WHAT DOES THIS LOOK LIKE?

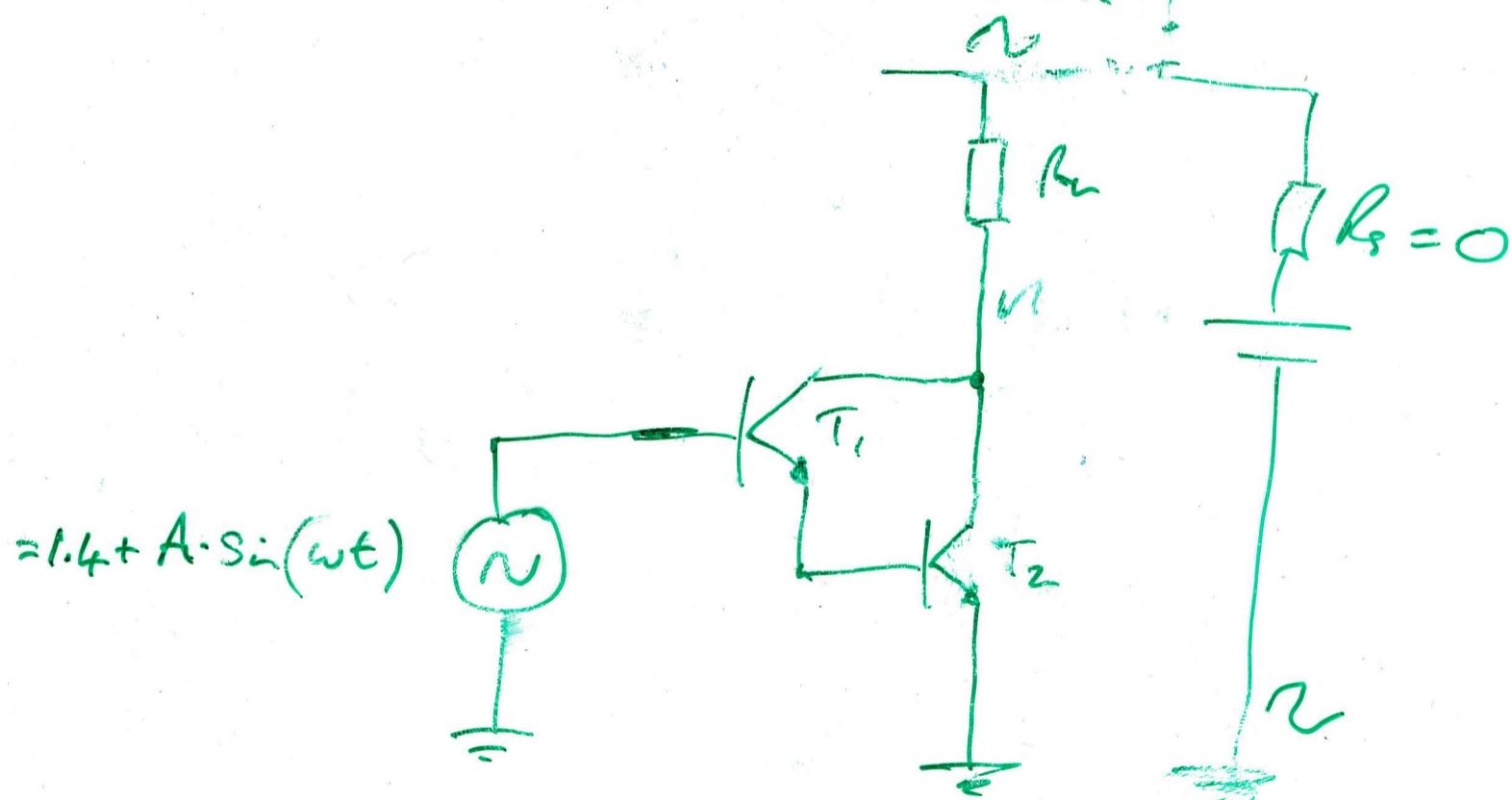

... DRAW A SMALL SIGNAL EQUIVALENT CIRCUIT ASSUMING β_{ce} OF T_1 & T_2 HAS NEGLIGIBLE EFFECT ON PERFORMANCE.

SMALL SIGNAL MODEL ...

(4)

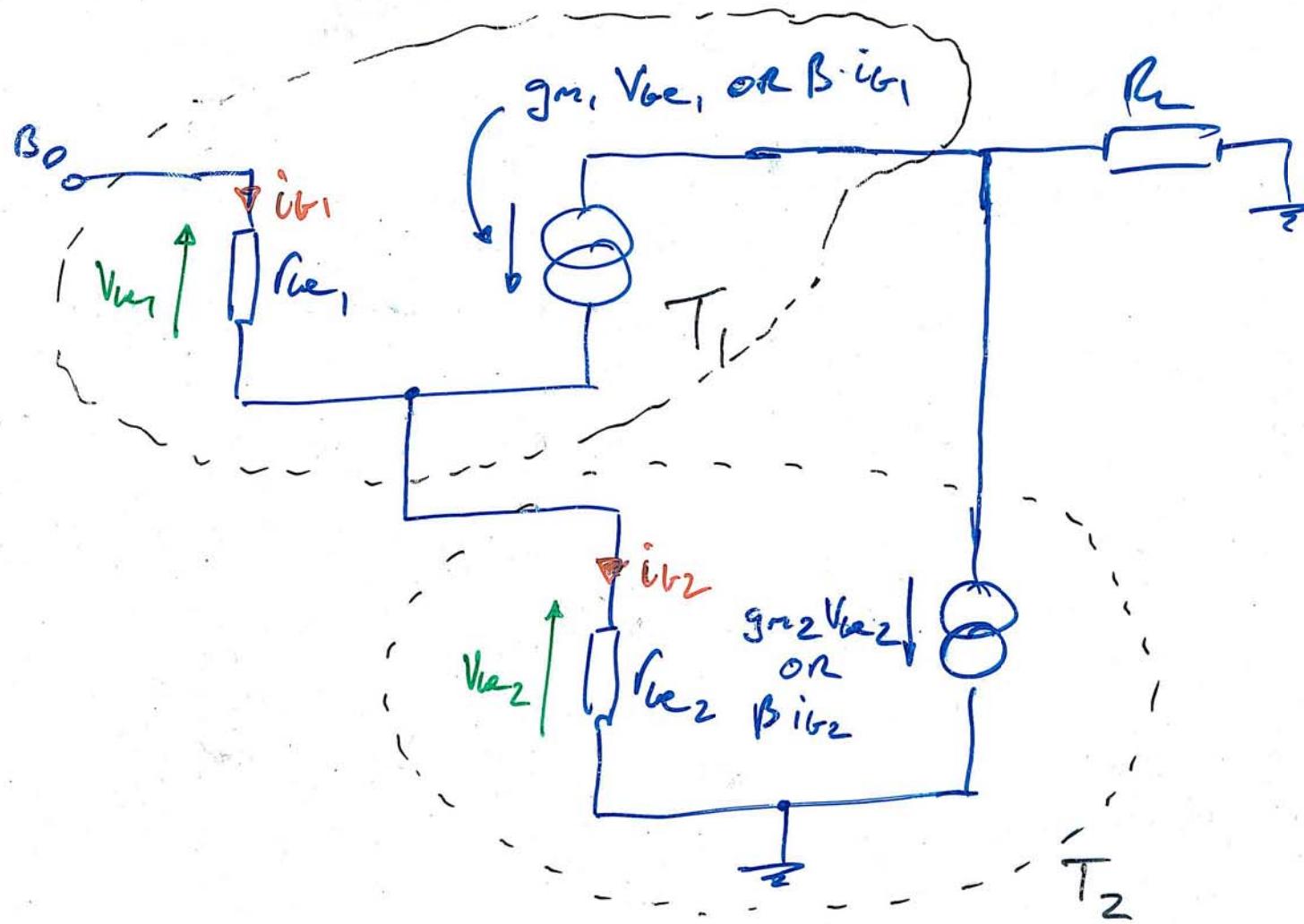

- iii) BOTH T_1 & T_2 HAVE $h_{FE} = 100$ & $\beta = 200$
 THE BIAS CIRCUIT DEFINES $I_{C2} = 1\text{mA}$.
 WHAT IS THE INPUT RESISTANCE ?

(5)

$$g_m = \frac{cI_c}{kT}; V_{be} = \beta g_m \quad \frac{kT}{e} = 0.026\text{V}$$

SOLUTION:

- COLLECTOR CURRENT OF T_1 IS MUCH LESS THAN T_2 . ASSUME THAT $I_{R1} \approx I_{C1} \dots$

OR IF YOU WANT TO INCLUDE IT

$$I_{R1} = I_{C1} + I_{B1} = I_{C1} \left(1 + \frac{1}{h_{FE1}} \right)$$

- CALCULATE g_m , & g_{m2} AND FROM THESE COMPUTE r_{be1} & r_{be2} .

$$g_{m1} = \frac{cI_{C1}}{kT} = \frac{1.6 \times 10^{-19} \cdot 10 \times 10^{-6}}{1.38 \times 10^{-23} \cdot 301.45}$$


$$= 385 \times 10^{-6} \text{ A/V}$$

$$g_{m2} = \frac{e I_{E2}}{K T} = \frac{1.6 \times 10^{-19} \cdot 1 \times 10^{-3}}{1.38 \times 10^{-23} \cdot 301.45} \\ = \underline{\underline{38.5 \text{ mA/V}}}$$

$$r_{in1} = \frac{B_1}{g_{m1}} = \frac{200}{38.5 \mu\text{A/V}} = \underline{\underline{520 \text{ k}\Omega}}$$

$$r_{in2} = \frac{B_2}{g_{m2}} = \frac{200}{38.5 \text{ mA/V}} = \underline{\underline{5.2 \text{ k}\Omega}}$$

Now How About THE Input RESISTANCE ?

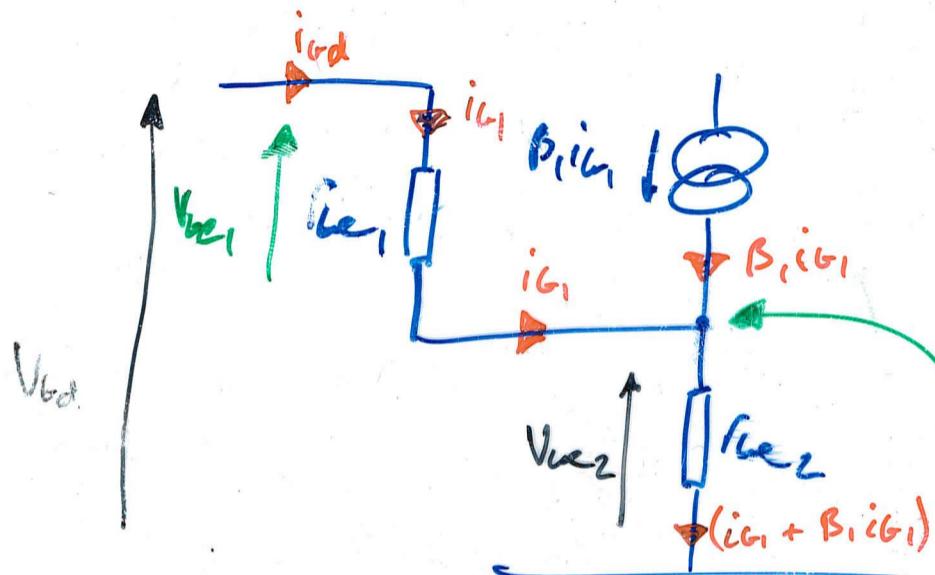

$$r_i = \frac{V_{bd}}{i_{bd}} = \frac{V_{bd}}{i_{b1}}$$

$$V_{bd} = V_{be1} + V_{be2} \\ i_{b1} \cdot r_{in1} + i_{b1} (1 + B_1) r_{in2}$$

Got THIS BY
SUMMING I
AT THE Emitter
OF T₁

Now ONLY NEED TO DO some MATHS...

$$i_{bd} = i_{b1} \cdot r_{in1} + i_{b1} (1 + B_1) r_{in2}$$

$$V_{bd} = i_{b1} (r_{in1} + (1 + B_1) r_{in2})$$

$$\frac{V_{bd}}{i_{b1}} = (r_{in1} + (1 + B_1) r_{in2})$$

$$= 520 \text{ k}\Omega + (1 + 200) \cdot 5.2 \text{ k}\Omega$$


$$= \underline{\underline{1.565 \text{ M}\Omega}}$$

THERE ARE USUALLY DC CONDITIONS
PARTS AND SMALL SIGNAL CALCULATION
PARTS TO THIS SORT OF QUESTION.

A NON-INVERTING OPAMP AMPLIFIER IS MADE USING AN OPAMP WITH GBP = 40×10^6 Hz. THE CLOSED LOOP GAIN IS 50.

i) IS A -3dB POINT OF 2MHz POSSIBLE? (1)

GAIN = 50 AT LOW FREQUENCIES...

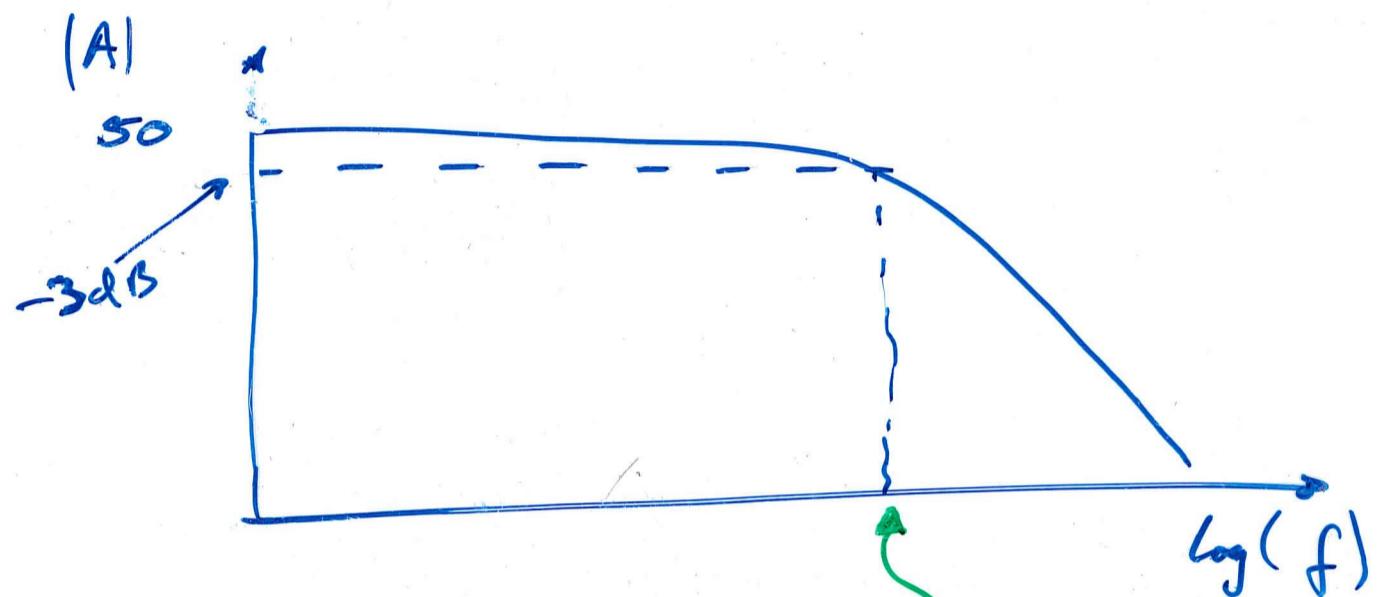


$$\text{MAX } -3\text{dB BANDWIDTH} = \frac{\text{GBP}}{\text{GAIN}} = \frac{40 \times 10^6}{50}$$

$$= 800 \text{ kHz}$$

~~800 kHz~~) SO NO 2MHz IS NOT POSSIBLE.

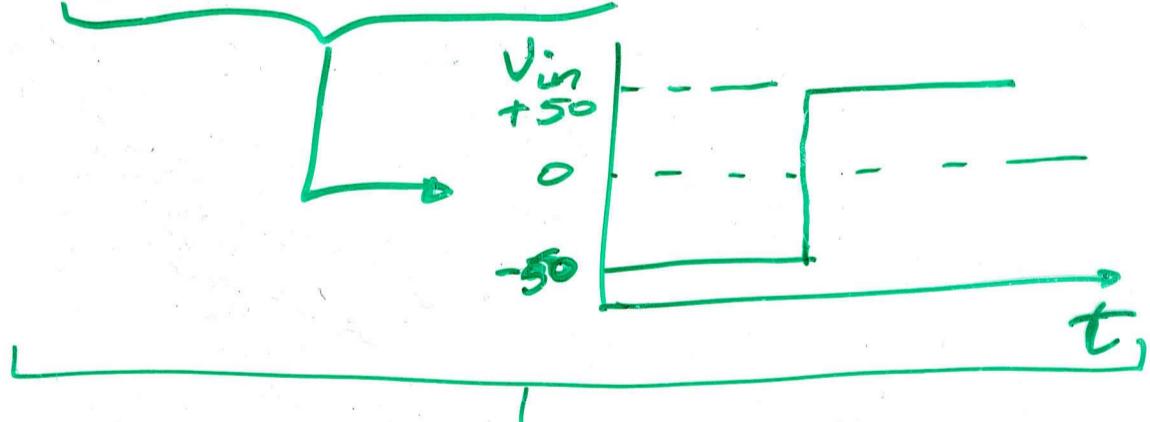ii) WHAT IS THE RISE TIME IN RESPONSE TO A STEP INPUT OF $-50\text{mV} \rightarrow +50\text{mV}$.




THIS IS PADDING AND IS NOT NEEDED TO ANSWER THE QUESTION...

$$\bullet T = \frac{1}{\omega_{-3\text{dB}}} = \frac{1}{2\pi f_{-3\text{dB}}} \quad \left. \right\} \text{For A 1ST ORDER SYSTEM...}$$

$$\bullet t_R = 2.2T$$

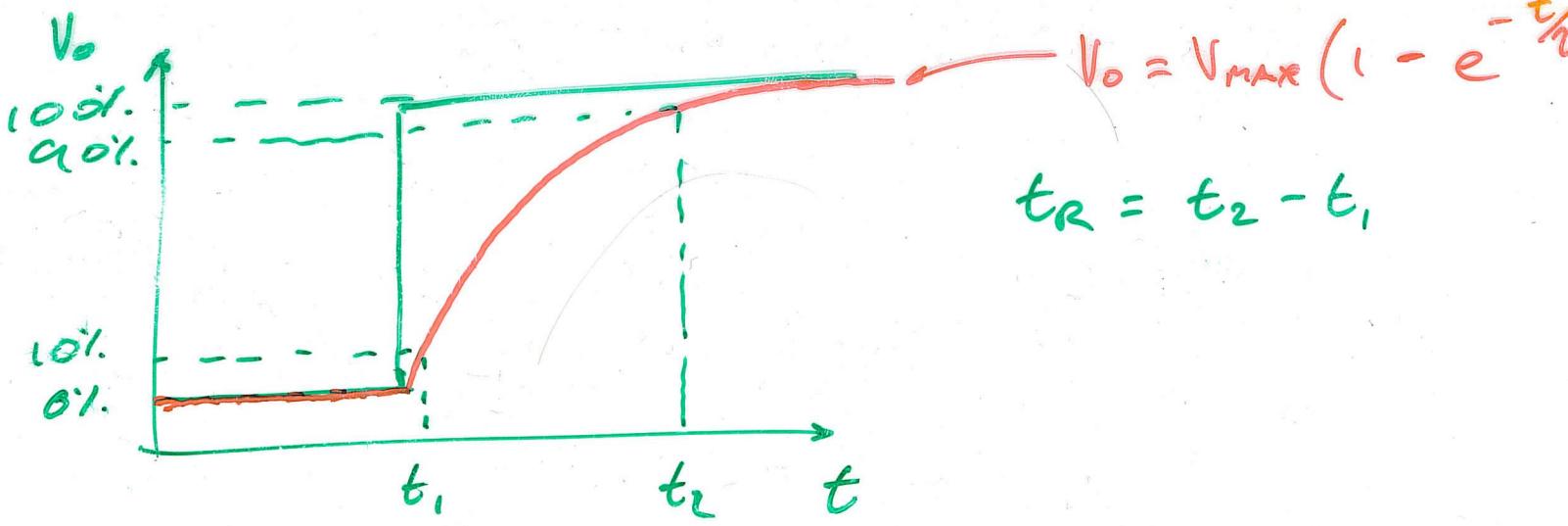RISE TIME FROM 10% TO 90% OF TOTAL OUTPUT.



Some EASY (ISH) MATHS: From PART i


$$\omega_{3dB} = 2\pi \cdot 800 \times 10^3 = 5.026 \times 10^6 \text{ rads}^{-1}$$

$$T = \frac{1}{5.02 \pi \text{ rads}^{-1}} = \underline{\underline{198.94 \text{ ns}}}$$

$$t_R = 2.2T = \underline{\underline{437.67 \text{ ns}}}$$

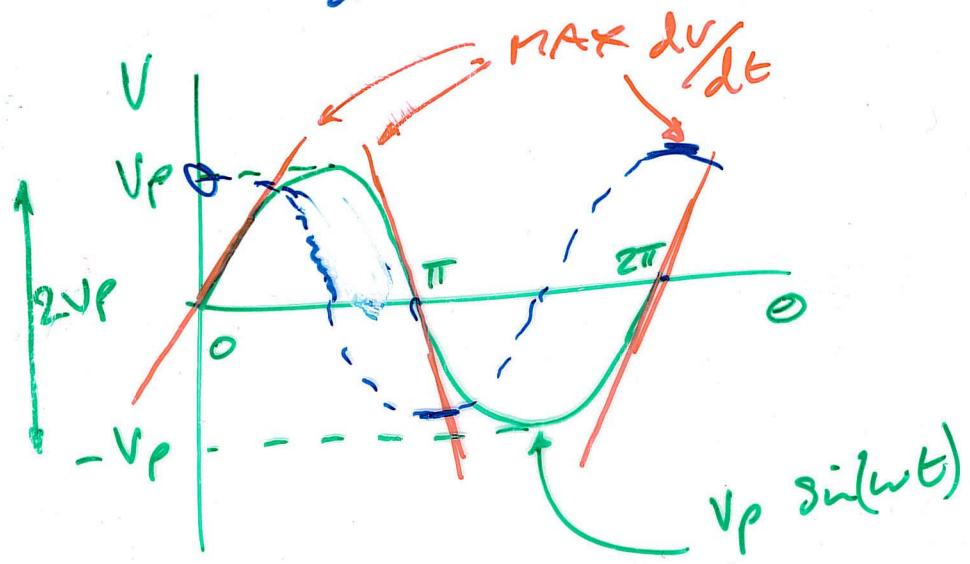iii) IF THE AMP. SLOW RATE IS $50 \text{ V}/\mu\text{s}$ WHAT IS THE MAX PEAK-PEAK VOLTAGE THAT CAN BE SUPPORTED AT 2 MHz ?

- NEED TO REMEMBER (OR DRAKE) THAT MAX $\frac{dV}{dt}$ OF A SINE IS $V_p \cdot \omega$



$$V_p \sin(\omega t) \rightarrow \frac{d(V_p \sin(\omega t))}{dt}$$

$$= V_p \omega \cos(\omega t) \Big|_{\text{max}}$$

$$\cos(0) = 1 \dots$$

$\therefore V_p \cdot \omega$ IS MAX $\frac{dV}{dt}$ OF $V_p \sin(\omega t)$.

$$V_p \cdot \omega = 50 \times 10^6$$


$$2 \text{ MHz} \cdot 2\pi$$

$$V_p = \frac{50 \times 10^6}{2 \pi} = \underline{\underline{3.9788 \text{ V}}}$$

$50 \text{ V}/\mu\text{s}$ IS $\frac{V}{s} \dots$

THERE IS ALMOST ALWAYS SOME QUESTION THAT USES THE FIRST ORDER APPROXIMATIONS.

EEE 225 2014 PAPER Q4.

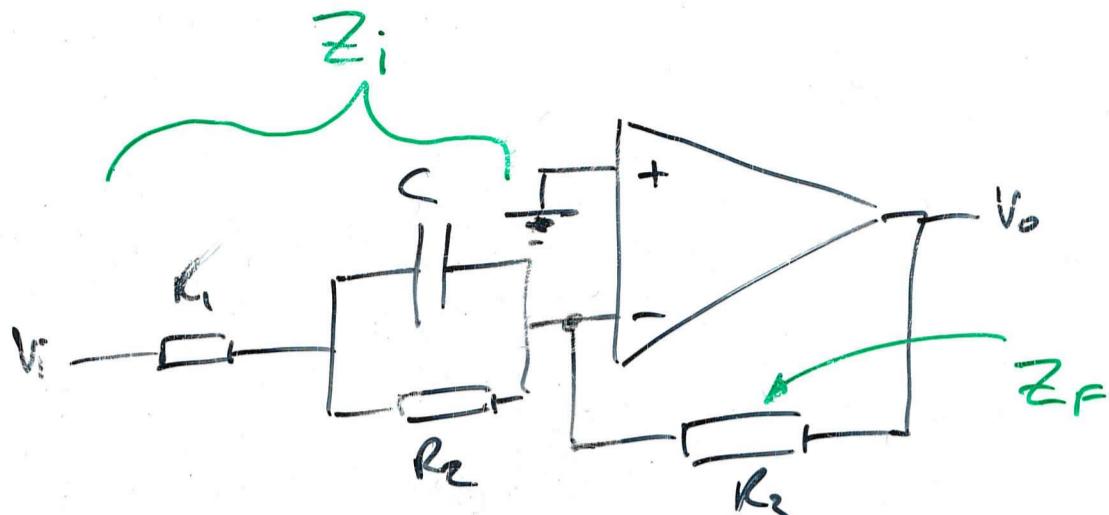

a i) WRITE DOWN THE H.F. & L.F. GAINS IN TERMS OF R_1, R_2, C & R_3 .

- AT LF $X_C \rightarrow \infty$ OR $\omega \rightarrow 0$. SO $Z_i = R_1 + \left(\frac{1}{sC} // R_2 \right)$

- GAIN = $\frac{-Z_f}{Z_i} = \frac{-R_3}{R_1 + R_2}$ $\rightarrow \infty \because R_2$

- AT H.F $X_C \rightarrow 0$ OR $\omega \rightarrow \infty$ SO $Z_i = R_1 + 0$

- GAIN $\frac{-Z_f}{Z_i} = \frac{-R_3}{R_1}$ $\frac{1}{sC} = 0$ SO R_2 IS S/C.

ii) IF $f_o = 50\text{Hz}$, $f_i = 1000\text{Hz}$ & $K = 10$ FIND R_3/R_1 , R_2/R_1 AND $C \cdot R_2$ (THE TIME CONSTANT). SUGGEST COMPONENT VALUES.

$$\frac{V_o}{V_i} = -K \cdot \frac{1 + j\frac{f}{f_o}}{1 + j\frac{f}{f_o}}, K = \frac{R_3}{R_1 + R_2} \Rightarrow f_o = \frac{1}{2\pi C R_2}$$

$$f_i = \frac{R_1 + R_2}{2\pi C_1 R_1 R_2}$$

- MANIPULATE THE GIVEN EQUATIONS TO YIELD THE RATIOS REQUIRED.

- TACKLE R_2/R_1 FIRST. DIVIDE f_i/f_o :

$$\frac{f_1}{f_0} = \frac{\frac{R_1 + R_2}{2\pi C_1 R_1 R_2}}{1} = \frac{R_1 + R_2}{R_1} = \frac{R_1}{R_1} + \frac{R_2}{R_1}$$

$$\frac{f_1}{f_0} = 1 + \frac{R_2}{R_1} = \frac{1000}{50} = 1 + \frac{R_2}{R_1}$$

$$\therefore 20 - 1 = \frac{R_2}{R_1} \text{ & } 19 \cdot R_1 = R_2 \quad \frac{1000}{50} = \frac{100}{5} = 20 \dots$$

Let $R_2 = \underline{\underline{100 \text{ k}\Omega}}$ so $R_1 = \underline{\underline{5.26 \text{ k}\Omega}}$

Now Do R_3/R_1 : THIS IS A CHOICE!

$$K = \frac{R_3}{R_1 + R_2} \div R_1 \quad \frac{\frac{R_3}{R_1}}{\frac{R_1}{R_1} + \frac{R_2}{R_1}} = \frac{\frac{R_3}{R_1}}{1 + \frac{R_2}{R_1}}$$


$$\therefore K = \frac{\frac{R_3}{R_1}}{20} \quad \& \quad K = 10 \quad \text{So:} \quad 19$$

$$20 \cdot 10 = \frac{R_3}{R_1} = \underline{\underline{200}} \quad R_1 = 5.26 \text{ k} \quad \text{So:}$$

$$R_3 = \underline{\underline{1.052 \text{ M}\Omega}} \quad (200 \cdot R_1)$$

ONE CAN'T CHOOSE VALUES LESS THAN ABOUT 1 K Ω OR MORE THAN 1 M Ω . $< 1 \text{ k}\Omega$ AND THE OPAMP WON'T BE ABLE TO SUPPLY THIS NECESSARY CURRENT. $> 1 \text{ M}\Omega$ AND INSUFFICIENT BEASING CURRENT WILL BE AVAILABLE TO THE INVERTING AND/OR NON-INVERTING INPUTS.

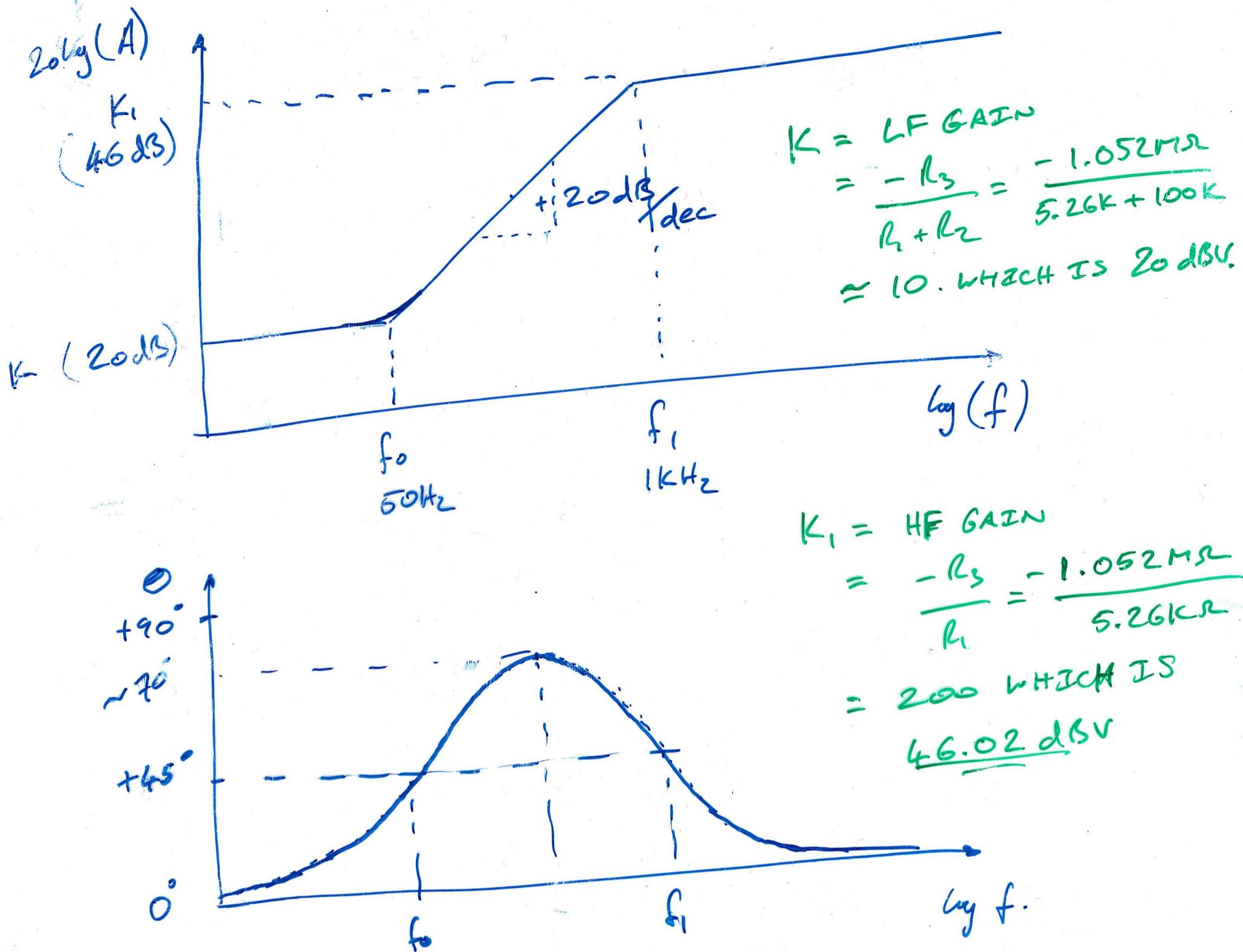iii) SKETCH A BODE PLOT OF THE POLE-ZERO CIRCUIT..



- A ZERO GIVES $+20\text{dB}/\text{dec}$ IN MAGNITUDE AND $+90^\circ$ PHASE (LEADING)
- A POLE GIVES $-20\text{dB}/\text{dec}$ IN MAGNITUDE AND -90° PHASE (LAGGING).

IT WOULD BE USEFUL TO ENSURE YOU'RE CONFIDENT AT SKETCHING THE MAGNITUDE AND PHASE PLOTS FOR POLE-ZERO CIRCUITS.
IT USUALLY COMES UP ON EXAMS.

4(bi) DEFINING SIGNAL TO NOISE RATIO. WHY IS IT USELESS AS A MEASURE OF SYSTEM PERFORMANCE?


- SNR IS THE RATIO OF THE MEAN SQUARED SIGNAL AND THE MEAN SQUARED NOISE.
- SNR TELLS THE RELATIVE CORRUPTION OF THE SIGNAL AT THE POINT IN THE CIRCUIT FOR WHICH IT IS CALCULATED BUT SINCE THE ACTUAL VALUE OF SIGNAL AND/OR NOISE ARE NOT KNOWN IT CAN'T BE RELATED TO A SYSTEM'S SPECIFICATIONS WITHOUT EXTRA INFO.

ii) An AMPLIFIER WITH $i_{in} = \infty \Omega$ & NOISE EQUIVALENT BANDWIDTH OF 10kHz & GAIN = 100 HAS A INPUT NOISE VOLTAGE GENERATOR OF $8\text{nV}/\sqrt{\text{Hz}}$ & INPUT NOISE CURRENT GENERATOR OF $3\text{pA}/\sqrt{\text{Hz}}$. THE AMPLIFIER IS PREIVED BY A THÉVENIN SOURCE WHO'S $R_s = 1.8\text{k}\Omega$.

- CALCULATE THE RMS NOISE AT THE OUTPUT WHEN NO SIGNAL IS PRESENT.

SOLUTION

- USE STD. AMPLIFIER NOISE MODEL.

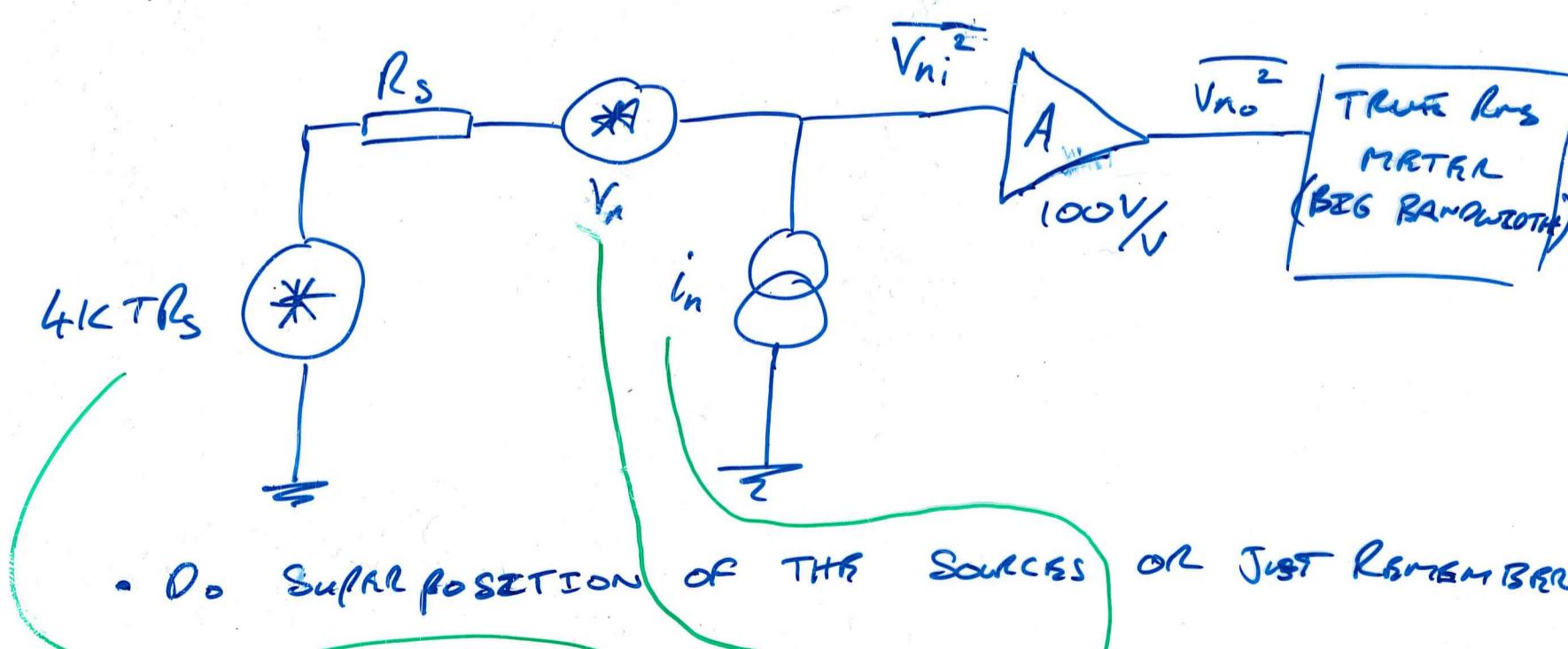

• Do SUPERPOSITION OF THE SOURCES OR JUST REMEMBER...

$$\overline{V_n^2} = 4KTR_s + \overline{V_n^2} + \overline{i^2 R_s^2} \quad \text{V}^2/\text{Hz}$$

$\overline{V_n^2}$ IS THE MEAN SQUARED NOISE AT THE INPUT

$\overline{i^2 R_s^2}$ IS THE MEAN SQUARED NOISE AT THE OUTPUT.

THE METER READS THE Root OF THE MEAN SQUARED NOISE (RMS)

$$V_m = \sqrt{V_{no}^2 \cdot B_N}$$

(10kHz IN THF)
QUESTION

So $\overline{V_{ni}^2} = 4kT \cdot 1.8 \times 10^3 + (8 \times 10^{-9})^2 + (3 \times 10^{-12})^2 \cdot (1.8 \times 10^3)^2$

$$= 2.99 \times 10^{-17} + 64 \times 10^{-18} + 9 \times 10^{-24} \cdot 3.24 \times 10^6$$

$$= 1.2306 \times 10^{-16} \text{ V}_H^2 \text{ @ THF Input}$$

$$\overline{V_{no}^2} = A^2 \cdot \overline{V_{ni}^2} = 100^2 \cdot 1.2306 \times 10^{-16}$$

\uparrow
IN THF Q⁻

$$= 1.2306 \times 10^{-12} \text{ V}_H^2 \text{ @ THF Output}$$

$$V_m = \sqrt{\overline{V_{no}^2} \cdot B_N} = \sqrt{(1.2306 \times 10^{-12} \cdot 10 \times 10^3)^{1/2}}$$


$$= \underline{110.93 \mu\text{V RMS}}$$

iii) WHAT AMPLITUDE OF INPUT SIGNAL WILL GIVE AN SNR OF UNITY AT THE OUTPUT?

ONE WAY TO APPROACH THIS IS BY THINKING ABOUT THE POWER THE NOISE DISSEMINATES.

$$P = \frac{V^2}{R}$$

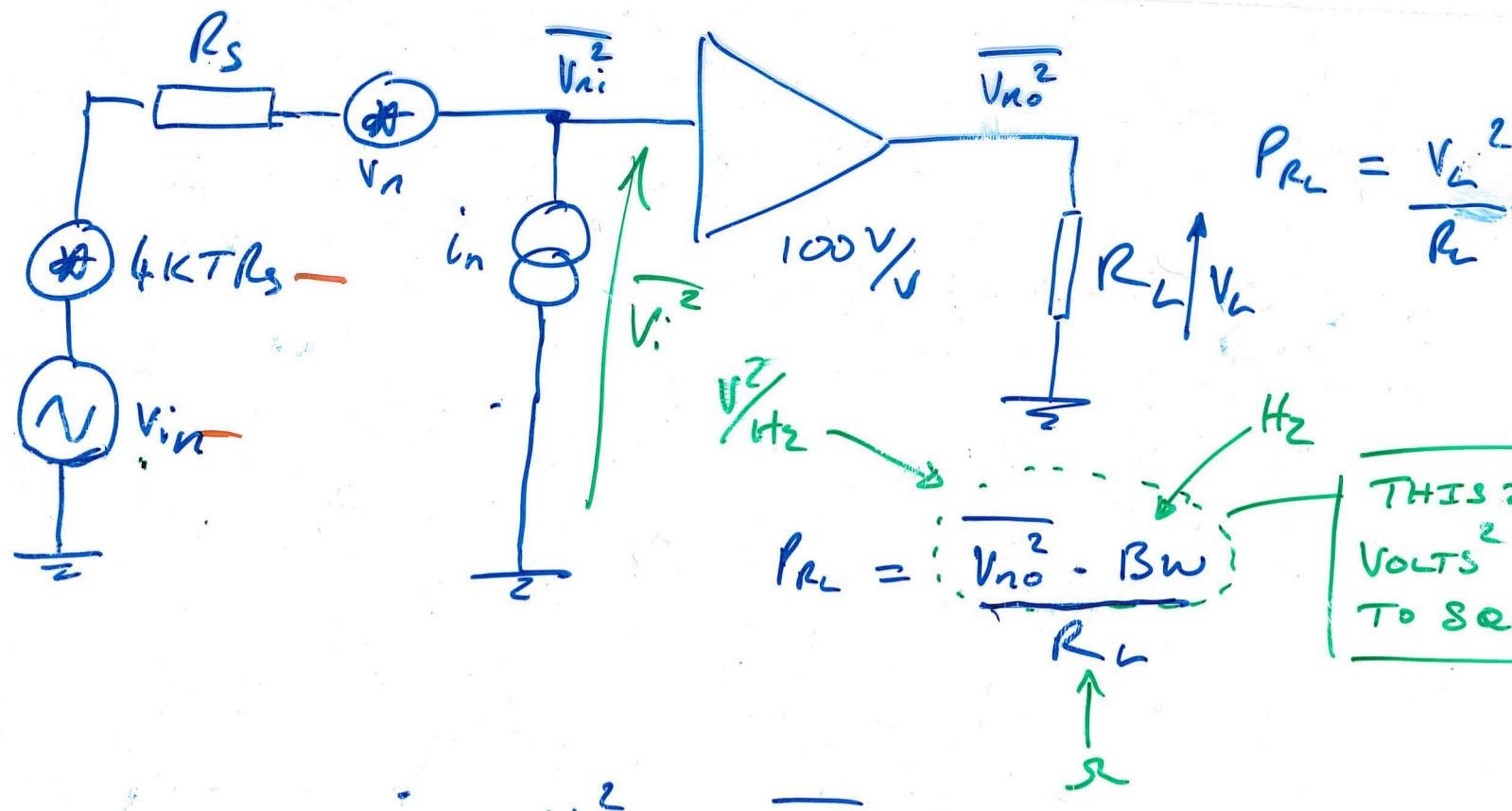- To GET AN SNR OF UNITY SIGNAL POWER AT THE OUTPUT AND NOISE POWER AT THE OUTPUT MUST BE EQUAL.
- DEFINING A LOAD RESISTANCE R_L



$$\therefore \frac{V_L^2}{R_L} = \frac{\overline{V_{no}^2} \cdot B_W}{R_L}$$

THE R_L CANCELS ...

$$V_L^2 = \overline{V_{no}^2} \cdot B_W$$

$$(110.93 \times 10^{-6})^2 \text{ V}^2$$

$$V = 110.93 \times 10^{-6} \text{ V}$$

÷ By GAIN → $1.1093 \mu\text{V}$ rms

$$V_p = \sqrt{2} \cdot V_{\text{rms}} \text{ (For SINE)}$$

$$= \underline{\underline{1.568 \mu\text{V}}}$$

NOISE ALWAYS SHOWS UP ON THE PAPER.
THE "TRICK" OF THINKING ABOUT POWER
IS ALWAYS HELPFUL BECAUSE IF YOU'RE
WORKING IN V^2 PER UNIT BANDWIDTH
YOU'RE ALREADY WORKING WITH POWER!!

Exam Format

- SECTION A
 - ANSWER FIVE OF NINE
 - EACH WORTH 8 MARKS
 - 3 ON DIGITAL, 3 ON ANALOGUE
3 ON SEMICONDUCTORS.
 - WORTH 40% OF THE TOTAL.
($5 \times 8 = 40$ MARKS).
- SECTION B
 - ANSWER ALL QUESTIONS
 - EACH WORTH 20 MARKS. ($3 \times 20 = 60$ MARKS)
 - 1 ON DIGITAL, 1 ON ANALOGUE
1 ON SEMICONDUCTORS.

THE TOTAL TIME AVAILABLE IS 3 Hours.

- PLAN TO SPEND:- JUST OVER 1 HOUR ON PART A
 - " " 1h 30 " PART B
 - 20 MINUTES CHECKING EVERYTHING
(i.e. ABOUT 1.6 MINUTES/MARK.)

FORMULA GIVEN ON THIS SCRIPT:

$$g_m = \frac{eI_c}{KT}, \quad r_{ce} = \frac{\beta}{g_m}, \quad h_{FE} = \frac{I_c}{I_B}$$

$$\frac{KT}{e} = 0.026 \text{ V}$$

PHYSICAL CONSTANTS GIVEN ON THIS SCRPT.

$$e = 1.6 \times 10^{-19} C$$

$$m_0 = 9.11 \times 10^{-31} \text{ kg}$$

$$c = 2.998 \text{ ms}^{-1}$$

$$h = 6.626 \times 10^{-34} \text{ Js}$$

$$k = 1.381 \times 10^{-23} \text{ JK}^{-1}$$

$$0^\circ\text{C} = 273.15 \text{ K.}$$

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ Fm}^{-1}$$

$$\mu_0 = 4\pi \times 10^{-7} \text{ Hm}^{-1}$$

