

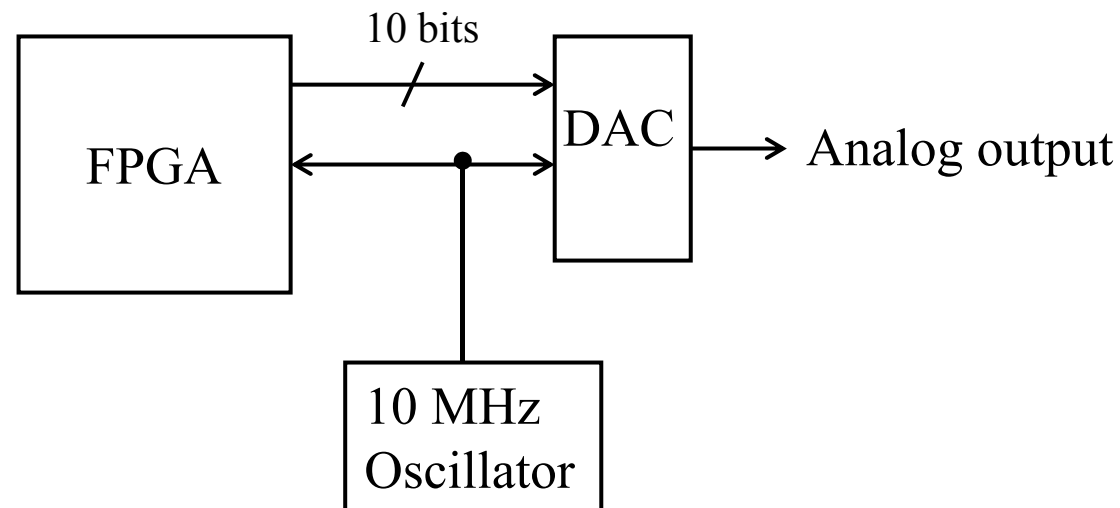
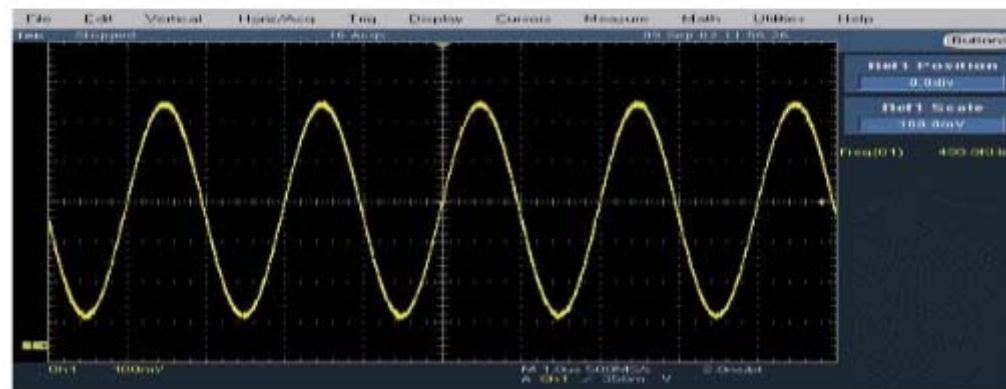


Direct Digital Synthesis (DDS)

- Direct Digital Synthesis (DDS)

 - Method to produce an analog waveform
- Generate time varying signal in digital form
- Convert to analog form using Digital-to-Analog Converter (DAC)
- Fast switching between output frequencies
- Fine frequency resolution
- Operation over a broad spectrum of frequencies



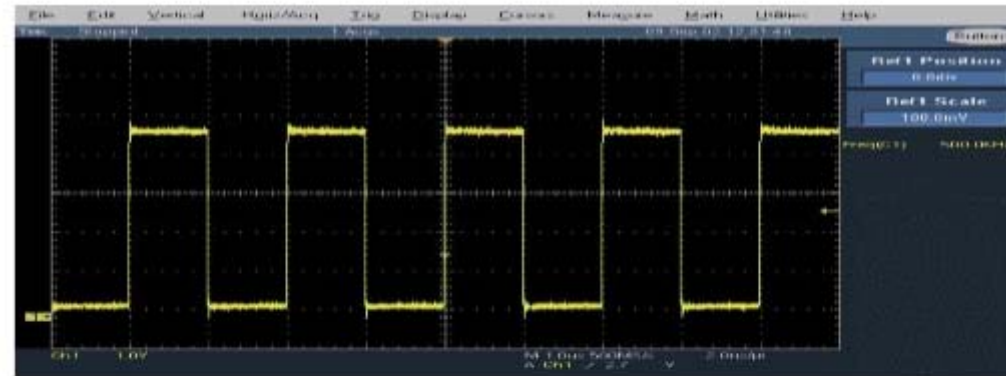

```

module DDS_Square (DAC_clk, DAC_data);
  input DAC_clk;
  output [9:0] DAC_data;
  reg [15:0] cnt;
  always @(posedge DAC_clk) cnt <= cnt + 16'h1;
  wire cnt_tap = cnt[5];
  assign DAC_data = {10{cnt_tap}};
endmodule

```

Create a 16 bit register
for a binary counter

Take one bit out
of the counter

Duplicate it 10 times to
create the 10-bits DAC
value


Using the 6th bit to generate the output:

Let the counter clock = 10 MHz

Then 6th bit toggles at $10\text{MHz} / 2^6 = 156.25\text{ KHz}$

DAC output is a 156.25 KHz square wave

Amplitude is maximum value

 

```

module DDS_SawTooth (DAC_clk, DAC_data);
  input DAC_clk;
  output [9:0] DAC_data;
  reg [15:0] cnt;
  always @(posedge DAC_clk) cnt <= cnt + 16'h1;
  assign DAC_data = cnt[9:0];
endmodule

```



```


module DDS_Triangle (DAC_clk, DAC_data);
  input DAC_clk;
  output [9:0] DAC_data;
  reg [15:0] cnt;
  always @(posedge DAC_clk) cnt <= cnt + 16'h1;
  assign DAC_data = cnt[10] ? ~cnt[9:0] : cnt[9:0];
endmodule

```



Arbitrary signals

 Use a LUT (lookup table) to hold the shape of the analog signal that we want to generate. The most common shape to generate is a sine wave.



On an FPGA, the LUT would typically be implemented as blockram and would be instantiated as shown:

```
wire [9:0] LUT_output;

blockram512x10bits
  DDS_LUT(
    .rdclock(clk),
    .rdaddress(cnt[8:0]),
    .q(LUT_output)
  );
```

The size of the LUT can be reduced by exploiting the symmetry of a sine wave.

$$\sin(\theta) = \sin(\pi - \theta)$$

```
wire [9:0] LUT_output;
```

```
blockram512x10bits
```

```
  DDS_LUT(
```


```
    .rdclock(clk),
```

```
    .rdaddress (cnt[9] ? ~cnt[8:0] : cnt[8:0]),
```

```
    .q(LUT_output)
```

```
  );
```

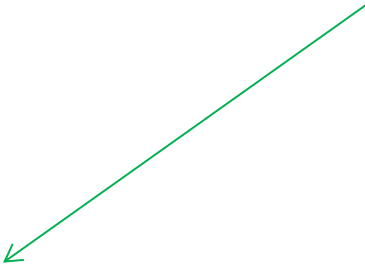The direction of reading the LUT has been reversed after a half-period.



Thus LUT appears to be 1024 x 10 bits instead of 512 x 10 bits.

A second symmetry can be exploited to make it appear 2048 x 10 bits.

```
wire [7:0] LUT_output;
```

```
blockram16x8bits
```

```
DDS_LUT(  
  .rdclock(clk),  
  .rdaddress (cnt[3] ? ~cnt[2:0] : cnt[2:0]),  
  .q(LUT_output)  
);
```

0000	0
0001	0.22
0010	0.44
0011	0.63
0100	0.79
0101	0.91
0110	0.98
0111	0.99
1000	0.99
1001	0.98
1010	0.91
1011	0.79
1100	0.63
1101	0.44
1110	0.22
1111	0

