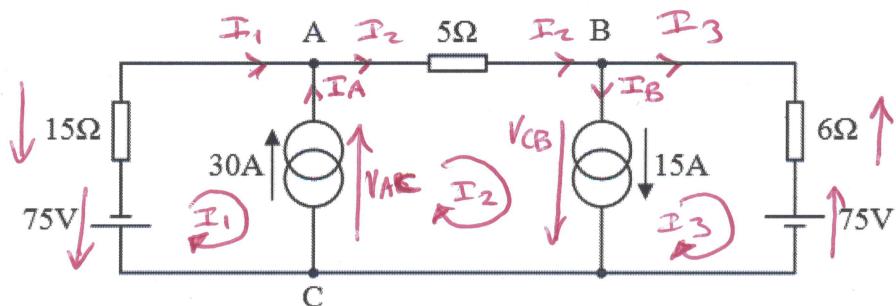


KEEPING CURRENT SOURCE POTENTIALS IN PHASE WITH CURRENT DIRECTION:

Q1(a) i



KIRCHHOFF CURRENT: $I_2 = I_1 + I_A \quad (1), \quad I_3 = I_2 - I_B \quad (2)$

KIRCHHOFF VOLTAGE:

$$I_1: 15I_1 + 75 + V_{AC} = 0 \Rightarrow V_{AC} = -75 - 15I_1 \quad (3)$$

$$I_2: V_{AC} + V_{CB} - 5I_2 = 0 \quad (4)$$

$$I_3: V_{CB} + 75 + 6I_3 = 0 \Rightarrow V_{CB} = -75 - 6I_3 \quad (5)$$

$$\text{SUB } (3) \text{ IN } (4): -75 - 15I_1 + V_{CB} - 5I_2 = 0 \quad (6)$$

$$\text{SUB } (5) \text{ IN } (6): -75 - 15I_1 - 75 - 6I_3 - 5I_2 = 0$$

$$\Rightarrow 15I_1 + 6I_3 + 5I_2 = -150 \quad (7)$$

$$\text{SUB } (1) \& (7) \text{ IN } (7) \quad 15I_1 + 6I_2 - 6I_3 + 5I_1 + 5I_A = -150$$

$$\text{OR } 15I_1 + 6I_1 + 6I_A - 6I_3 + 5I_1 + 5I_A = -150$$

$$\Rightarrow 26I_1 = -150 - 180 + 90 = 150 = -390$$

$$\therefore \underline{I_1 = -15A} \quad \text{So } \underline{I_2 = 15A} \quad \& \underline{I_3 = 0A}$$


From (3): $V_{AC} = -75 - 15 \times -15 = 150V$

$$\therefore \text{POWER DELIVERED BY } 30A \text{ SOURCE} = 150 \times 30 \\ = \underline{\underline{4.5kW}}$$


ii

SINCE $I_3 = 0A$, Batt 2 ONLY PROVIDES A VOLTAGE AND NEITHER SOURCES OR SINKS CURRENT

Q1(b) i

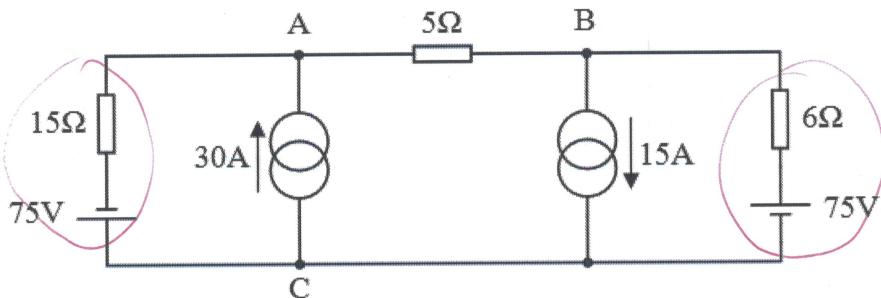


TRANSFORM TO NORTON EQUIVALENT:

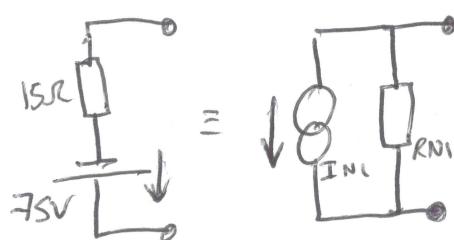

$$RN1 = R_{th} = 15\Omega$$

$$IN1 = \frac{V_{th}}{RN1} = 5A$$


NOTE DIRECTION!

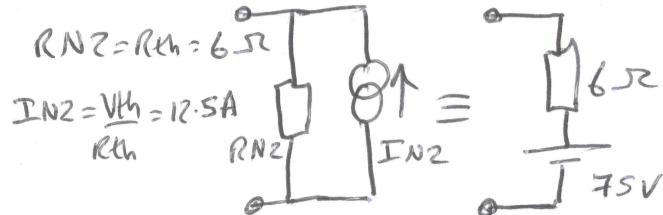


$$RN2 = R_{th} = 6\Omega$$

$$IN2 = \frac{V_{th}}{RN2} = 12.5A$$

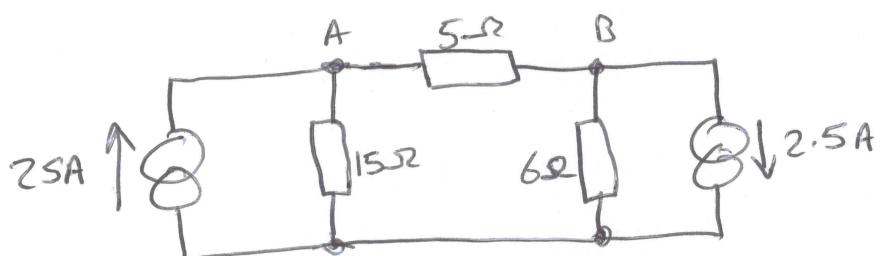
CONSIDERING CONTRIBUTIONS FROM ALL CURRENT SOURCES:



TRANSFORM TO THEVENIN EQUIVALENT:

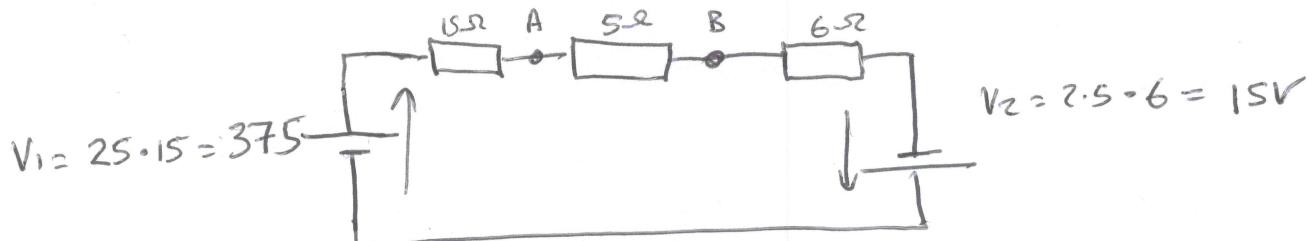


TOTAL IMPEDANCE:

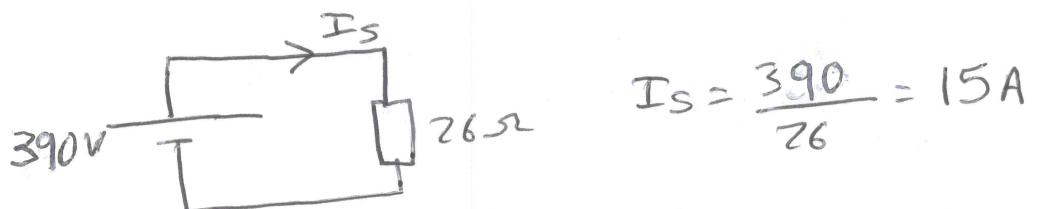

$$IS = \frac{390}{26} = 15A$$

THEVENIN EQUIVALENT CIRCUIT:

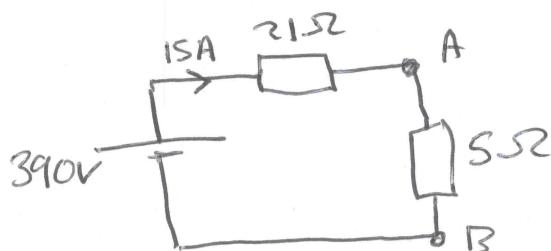


ii


So power dissipated in 5Ω : $P = I^2 R$

$$P = 15^2 \cdot 5 = 1125W \text{ or } 1.1kW$$

Q1 (c)



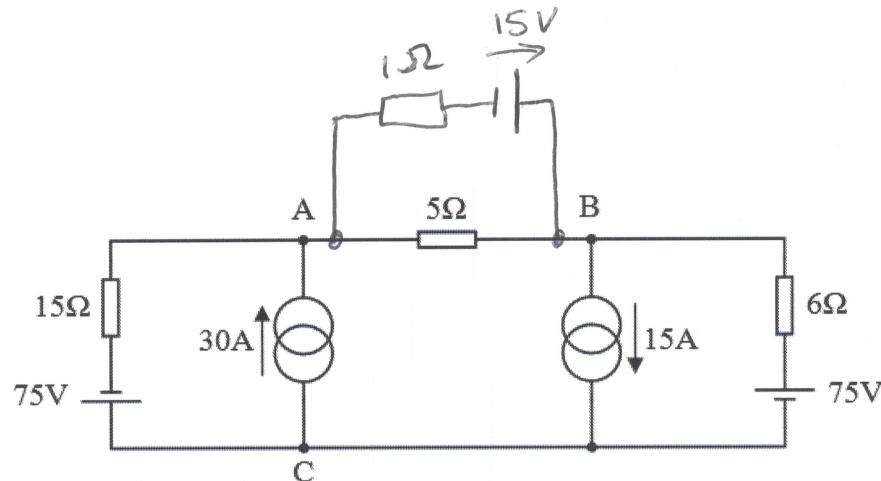


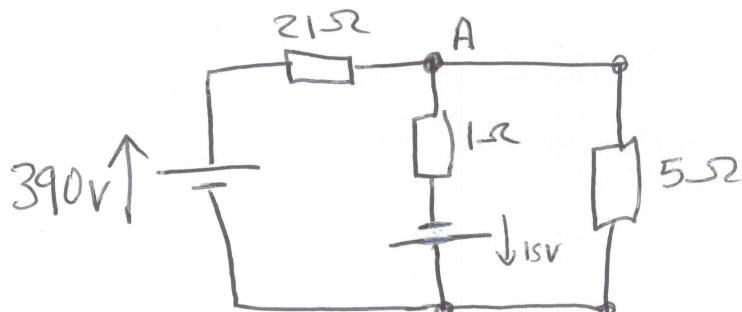CONSIDERING ANSWER TO Q1(b), CIRCUIT BECOMES :



NORTON EQUIVALENT CCT OF NEW BATTERY :
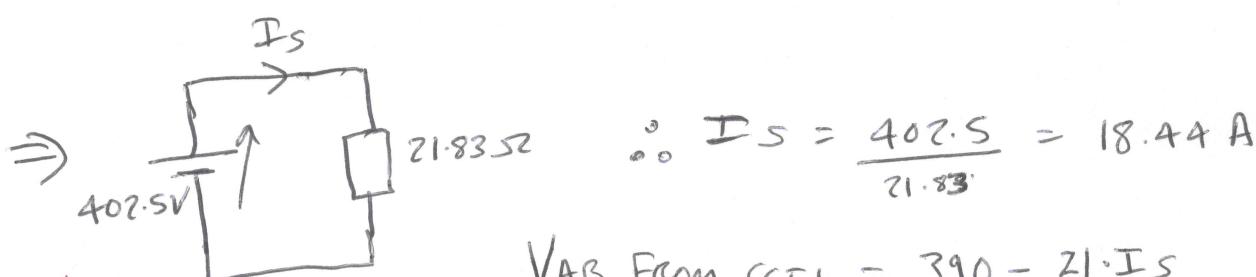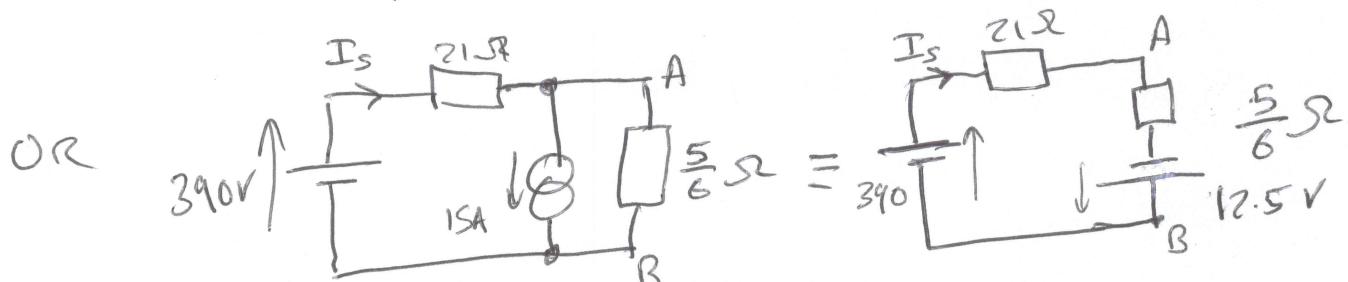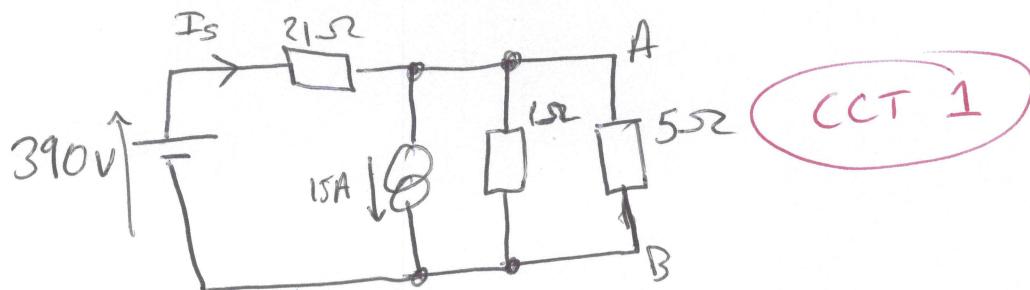
$$I_N = \frac{V_{th}}{R_{th}} = \frac{15}{1} = 15A, R_N = R_{th} = 1\Omega$$



$$\therefore I_S = \frac{402.5}{21.83} = 18.44A$$


$$V_{AB} \text{ from CCT 1} = 390 - 21 \cdot I_S$$

$$\therefore V_{AB} = 2.76V \quad \text{SO NEW POWER DISSIPATED} = 1.52W$$

Q2(a) i

A in STEADY-STATE:

INDUCTOR = SHORT CIRCUIT

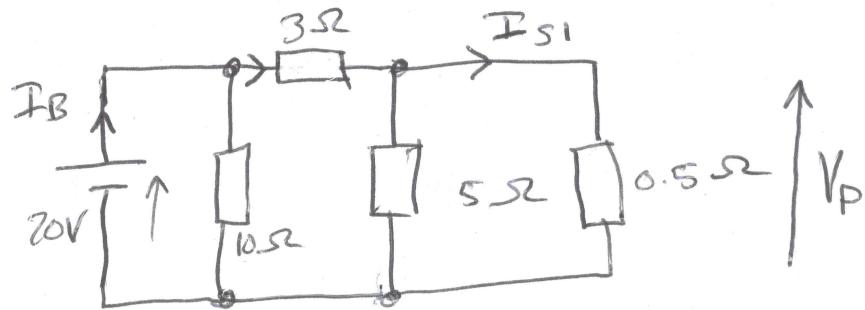

$$R_{\text{TOT}} = 10 \parallel (3 + 5 \parallel 0.5) = 2.568 \Omega$$

$$\therefore I_B = \frac{20}{2.568} = 7.788 \text{ A}$$

$$\text{So current in } 3\Omega \text{ resistor} = I_B - \frac{20}{10} = 5.788 \text{ A}$$


$$\therefore V_P = 20 - (3 \times 5.788) = 2.636 \text{ V}$$

$$\therefore I_{S1} = \frac{V_P}{0.5} = 5.271 \text{ A}$$

IMMEDIATELY AFTER SWITCH:

CAPACITOR OPPOSES CHANGE IN VOLTAGE \rightarrow zeroVOLTS = SHORT-CIRCUIT

So

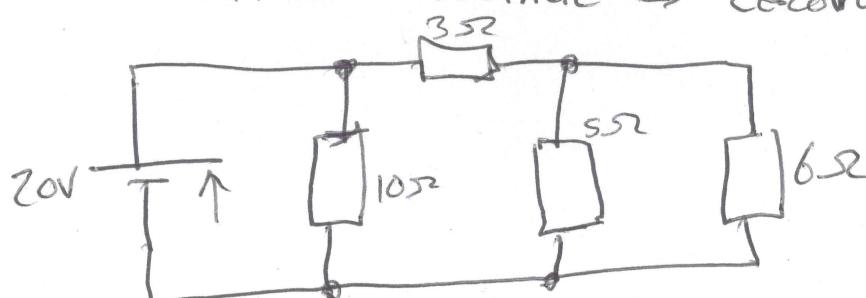

$$R_{\text{TOT}} = 10 \parallel (3 + 5 \parallel 6) = 3.642 \Omega$$

$$\therefore I_B = \frac{20}{3.642} = 5.492 \text{ A}$$

$$\text{So current in } 3\Omega \text{ resistor} = I_B - \frac{20}{10} = 3.492 \text{ A}$$

$$\therefore V_P = 20 - (3 \times 3.492) = 9.524 \text{ V}$$


$$\therefore I_{S1} = \frac{V_P}{6} = 1.587 \text{ A}$$

Q2(a)i cont'd

B IN STEADY-STATE:

CAPACITOR = OPEN CIRCUIT

$$\text{so } \underline{I_{S1} = 0A}$$

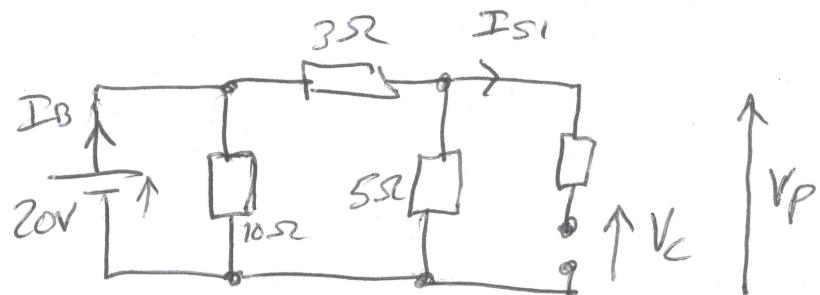

(Q2(a)ii)

POSITION A: C DISCHARGED SO $E_C = 0J$

$$I_{\text{in } L} = I_{S1} = 5.271A$$

$$\therefore E_L = \frac{1}{2} LI^2 = \underline{0.139J}$$

POSITION B: L DISCHARGED IF STEADY-STATE SO $E_L = 0$
AS $I = 0$

VOLTAGE ACROSS C = $V_C = V_P$ if open-circuited

$$R_{\text{TOT}} = 10 \parallel (3+5) = 4.444\Omega$$

$$\therefore I_B = \frac{20}{4.444} = 4.5A$$

$$\text{CURRENT IN } 3\Omega \text{ RESISTOR} = I_B - \frac{20}{10\Omega} = 2.5A$$

$$\text{So } V_P = V_C = 20 - (2.5 \times 3) = 12.5V$$

$$E_C = \frac{1}{2} CV^2 = \underline{7.8mJ}$$

(Q2(a)iii)

THE INDUCTOR IS CHARGED AT COMMUTATION,
HOWEVER IN POSITION B THERE IS NO DISCHARGE
CIRCUIT PATH AND SO ~~EXPERIENCES~~ HUGE $\frac{dI}{dt}$.

THIS INDUCES HUGE VOLTAGE SPARKS INTO THE CIRCUIT
AND MAY DAMAGE DEVICES / CAUSE EMI PROBLEMS

Q2(a)ir)

$$\text{POSITION A: } R_{\text{TOT}} = 10 \parallel (3 + 5 \parallel 0.3) = 2.568 \Omega$$


$$P = \frac{V^2}{R} = \frac{20^2}{2.568} = 155.76 \text{ W}$$

$$\text{POSITION B: } R_{\text{TOT}} = 10 \parallel (3 + 5) = 4.444 \Omega$$

$$P = \frac{V^2}{R} = \frac{20^2}{4.444} = 90 \text{ W}$$


Q2(a)iV

CCT:

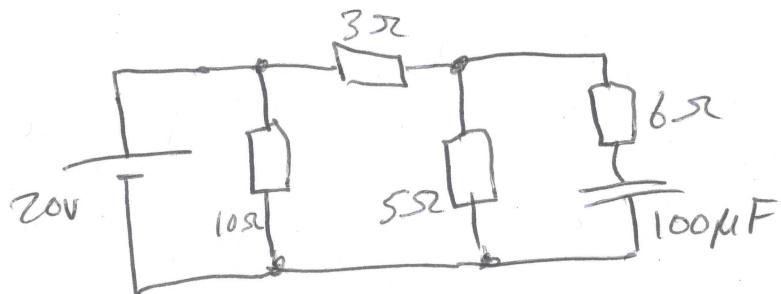

BY INSPECTION: VOLTAGE SOURCE GOES TO SHORT-CCT

SO CAPACITOR "SEES"

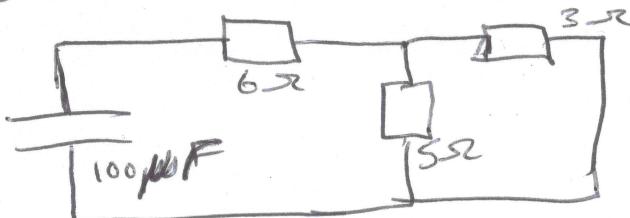

$$\text{So } \tau = C(6 + 3 \parallel 5)$$

$$= 0.788 \text{ ms}$$

REMEMBERING THAT A CAPACITOR 10% \rightarrow 90% CHARGE


$$\text{TIME} = 2.2\tau = 1.73 \text{ ms}$$

So 2ms would NOT be sufficient to assume a steady-state value.

PREFER TO USE 5x RISE TIME OR $\approx 10 \times \tau$

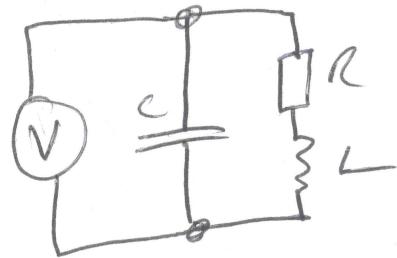Q3(a)i

$$Z = \frac{1}{j\omega C} \parallel (R + j\omega L)$$



$$Z = \frac{(R + j\omega L) \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}}$$

$$Z = \frac{R + j\omega L}{j\omega CR + (j\omega)^2 LC + 1} = \frac{R + j\omega L}{1 - \omega^2 LC + j\omega CR}$$

Q3(a)ii

SYSTEM BECOMES RESONANT WHEN j TERMS FORCED TO ZERO:

COMPLEX CONJUGATE?

$$\frac{(R + j\omega L)(1 - \omega^2 LC - j\omega CR)}{(1 - \omega^2 LC)^2 + \omega^2 C^2 R^2}$$

NUMERATOR THEREFORE
IN TERMS OF τ : $j\omega L(1 - \omega^2 LC) - R j\omega CR = 0$

$$\text{OR } j\omega L = j\omega CR^2 + j\omega^3 L^2 C \\ L = C(R^2 + \omega^2 L^2)$$

$$\text{So } C = \frac{L}{R^2 + \omega^2 L^2}$$

Q3(a)iii


$$I_{\text{LAMP}} = \frac{V}{Z_{\text{LAMP}}} = \frac{230}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\Rightarrow |I_L| = \frac{230}{\sqrt{4 \times 10^4 + 16\pi^2 50^2}}$$

$$= \frac{230}{659.4} = 0.349 \text{ A}$$

$$\therefore P_{\text{LAMP}} = I^2 R = 0.349^2 \times 100 = \underline{\underline{12.2 \text{ W}}}$$


Q3(b)i

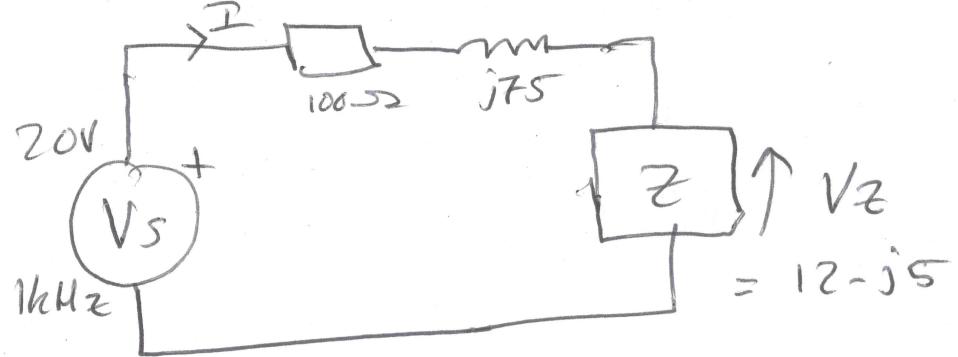

$$I = \frac{V_s - V_z}{100 + j75} = \frac{20 - (12 + j5)}{100 + j75} = \frac{8 + j5}{100 + j75}$$

CONVERT TO POLAR:
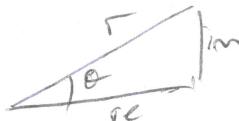
$$\frac{9.43 \angle 32.0^\circ}{125 \angle 36.9^\circ} = \underline{0.0754 \angle -4.9^\circ}$$



$$= \underline{0.075 - j 0.006}$$

$$\sin \theta = \frac{\text{opp}}{\text{hyp}}$$

$$\tan \theta = \frac{\text{adj}}{\text{hyp}}$$

$$Z = \frac{V_z}{I} = \frac{12 - j5}{0.0754 \angle -4.9^\circ} = \frac{13 \angle -72.6^\circ}{0.0754 \angle -4.9^\circ}$$

$$= \underline{172 \angle -17.7^\circ}$$

$$= \underline{164 - 52.3j}$$

Q3(b)ii

SINCE THERE IS A -VE j COMPONENT, MUST BE

$$R \& C \rightarrow R = \underline{164 \Omega}$$

$$X_C = \frac{1}{2\pi f C} = 52.3 \Rightarrow C = \frac{1}{2\pi \cdot 1\text{kHz} \cdot 52.3} = \underline{3\mu\text{F}}$$

QUESTION 4

KM 1

- a) [Note: It is not incorrect to draw the exact equivalent circuit - this will be awarded full marks. If the approximate equivalent circuit is used then the basis for moving the magnetizing branch needs to be included.]

Since the magnetizing reactance and the core loss resistance are much greater than the primary resistance and reactance, the magnetizing branch can be moved to the terminals to give the approximate equivalent circuit which is easier to solve.

Secondary impedances are referred to the primary winding:


$$Z_2' = \left(\frac{N_1}{N_2} \right)^2 Z_2$$

$$\therefore R_2' = (12)^2 \cdot 0.06 = 8.64 \Omega$$

$$X_2' = (12)^2 \cdot j0.09 = j12.96 \Omega$$

$$Z_L = (12)^2 (4 + j3) = 576 + j432 \Omega$$

Approximate equivalent circuit:

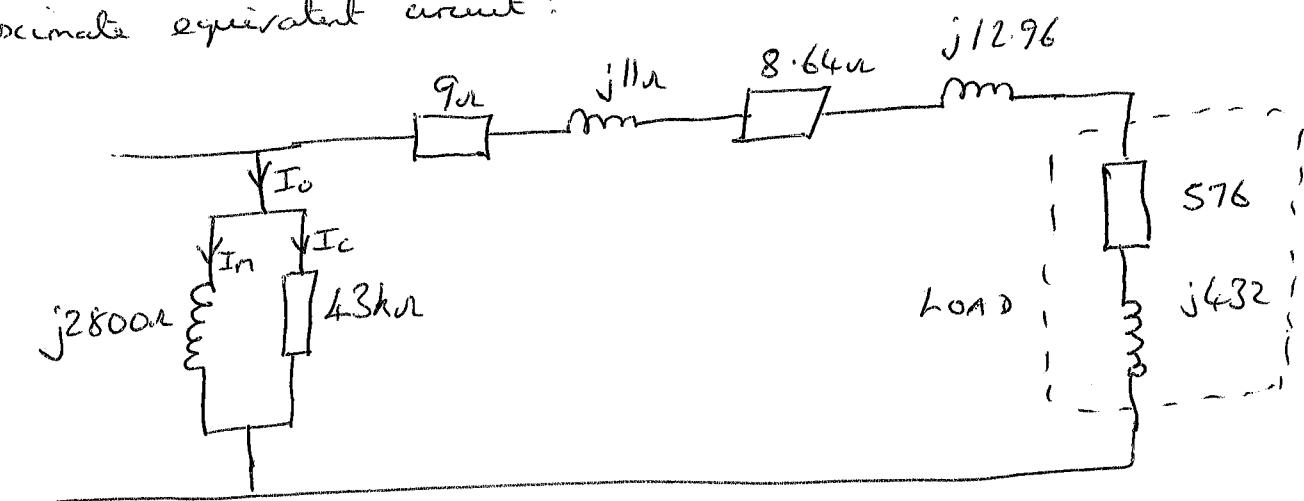

$$(b) \text{ No load current } = I_o = I_m + I_c$$

$$\therefore I_o = \frac{3300}{j2800} + \frac{3300}{43000} = 0.07674 - j1.1786 \\ \equiv \underline{1.18L-8627^\circ}$$

QUESTION 4 (CONTINUED)

KM2

(c) Core losses = Power dissipated in 43k Ω resistor:

$$\text{Either } P_{FE} = I_c^2 R_c = 0.07674^2 \times 43000 = 253.2 \text{ W}$$

$$\text{or } P_{FE} = V^2/R_c = 3300^2/43000 = \underline{\underline{253.2 \text{ W}}}$$

(d) With the load now connected:

$$(i) I_2' = \frac{V}{Z_{L\text{TOT}}} = \frac{3300}{(9+8.64+576)+j(11+12.96+432)} \\ = \frac{3300}{(593.64+j455.96)} = 4.41 L-37.52^\circ$$

To find the actual load current this needs referring back to the secondary:

$$\frac{I_2'}{I_2} = \frac{N_2}{N_1} \Rightarrow I_2 = \frac{N_1}{N_2} \times I_2' = 12 \times 4.41 L-37.52^\circ \\ = \underline{\underline{52.92 L-37.52^\circ \text{ A}}}$$

(ii) The input current to the transformer is:

$$I_1 = I_0 + I_2' = 1.18 L-86.27^\circ + 4.41 L-37.52^\circ \\ = \underline{\underline{5.263 L-47.22^\circ \text{ A}}}$$

(iii) Actual output voltage:-

$$V_2 = V_2' \cdot \frac{N_2}{N_1} = I_2' \cdot Z_2' \cdot \frac{N_2}{N_1} = 4.41 L-37.52 \times (576+j432) \times \frac{1}{12} \\ = \underline{\underline{264.5 L-0.65^\circ \text{ V}_{rms}}}$$

$$\text{No load voltage: } V_2 = 3300 \times \frac{1}{12} = 275 \text{ V}_{rms}$$

$$\therefore \text{Regulation} = \frac{\text{No-load V} - \text{On-load V}}{\text{No-load V}} = \frac{275 - 264.5}{275} \times 100 = \underline{\underline{3.82\%}}$$

QUESTION 4 (CONTINUED)

[Km 3]

$$(iv) \text{ Copper losses} = I_2' (R_1 + R_2') = 4.4I^2 (9 + 8.64)$$

$$= \underline{\underline{343 \text{ W}}}$$

(v) Real component of output power:

$$P_{\text{out}} = 4.4I^2 \times 576 = \underline{\underline{11202 \text{ W}}}$$

$$\text{Total losses} = P_{\text{Fe}} + P_{\text{Cu}} = 343 + 253.2 = 596.2 \text{ W}$$

$$\text{Hence efficiency} = \frac{P_{\text{out}}}{P_{\text{out}} + P_{\text{loss}}} = \frac{11202}{11202 + 596.2} \times 100 = \underline{\underline{94.9\%}}$$

(e) The use of a solid iron core would significantly increase the core (iron) loss within the device as usually laminations are used to limit circulating eddy currents within the core during operation. Therefore whilst the device may be deeper to produce it would be much less efficient in operation.

QUESTION 5

KM 4

(a) (i) Phase impedance $Z = 8.1 + j6.7 \Omega$

$$\text{Phase voltage} = \frac{6600}{\sqrt{3}} = 3810.5 \text{ V}_{\text{rms}}$$

$$\therefore \text{Phase current} = \frac{V_{L0^\circ}}{Z} = \frac{3810.5 L^\circ}{(8.1 + j6.7)} = \underline{\underline{362.5 L - 39.6^\circ A}}$$

Since the system is star-connected phase current = line current, hence

$$\text{line current} = \underline{\underline{362.5 L - 39.6^\circ A}_{\text{rms}}}$$


$$\text{(ii) Real power} = \sqrt{3} V_L I_L \cos \phi = \cancel{\sqrt{3} \times 6600 \times 362.5 \cos 39.6^\circ} \\ = \underline{\underline{3.193 \text{ MW}}}$$

$$\text{Reactive power} = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} \times 6600 \times 362.5 \sin 39.6^\circ \\ = \underline{\underline{2.641 \text{ MVAR}}}$$

$$\text{Apparent power} = \sqrt{3} V_L I_L = \sqrt{3} \times 6600 \times 362.5 \\ = \underline{\underline{4.144 \text{ MVA}}}$$

(b) (i) Adding the capacitor bank will not affect the real power.

After the capacitors are added:

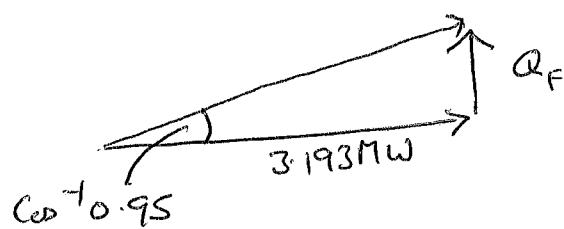

$$\phi = \cos^{-1} 0.95 = 18.19^\circ \Rightarrow \tan \phi = 0.3287$$

$$\text{Hence } Q_f = 3.193 \times \tan \phi = 3.193 \times 0.3287 = 1.05 \text{ MVAR}$$

QUESTION 5 (CONTINUED)

KM 5

Therefore the capacitor bank must provide:

$$2.641 - 1.05 = 1.591 \text{ MVAR or } 0.5303 \text{ MVAR/phase.}$$

Capacitor voltage = $6600 \text{ V}_{\text{rms}}$ since they are delta connected.

$$\text{Now } Q_{c-\text{phase}} = \frac{V_{\text{phase-rms}}^2}{X_C} \Rightarrow X_C = \frac{6600^2}{0.5303 \times 10^6} = 82.14 \Omega$$

$$\text{Hence } C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 82.14} = \underline{\underline{38.75 \mu\text{F/phase}}}$$

$$(b)(ii) I_{\text{ph-cap}} = \frac{6600}{82.14} = 80.35 \text{ A}_{\text{rms}}$$

$$I_{\text{line-cap}} = \sqrt{3} \times 80.35 = 139.17 \text{ A}_{\text{rms}}$$

$$\text{Original plant current} = 362.5 L - 39.6^\circ = 279.31 - j231.1 \text{ A}_{\text{rms}}$$

$$\therefore \text{New current with caps} = 279.31 - j231.1 + j139.17 \\ = 279.31 - j91.93 = \underline{\underline{294.05 L - 18.2^\circ \text{ A}_{\text{rms}}}}$$

$$(\text{Alternatively } P = \sqrt{3} V_L I_L \cos \phi \\ \therefore I_L = I_{\text{ph}} = \frac{P}{\sqrt{3} V_L \cos \phi} = \frac{3.193 \times 10^6}{\sqrt{3} \times 6600 \times 0.95} = \underline{\underline{294 \text{ A}_{\text{rms}}}}$$

$$\text{and phase angle} = \cos^{-1} 0.95 = -18.2^\circ \quad (-\text{since p.f. lagging})$$


$$(iii) \text{ Maximum voltage rating of capacitors} = \text{peak voltage} \\ = \sqrt{2} \times 6600 = \underline{\underline{9334 \text{ V}}}$$

QUESTION 5 (CONTINUED)

KM 6

- (iv) Either: Reduce cable/line losses
Reduce voltage drops along lines.

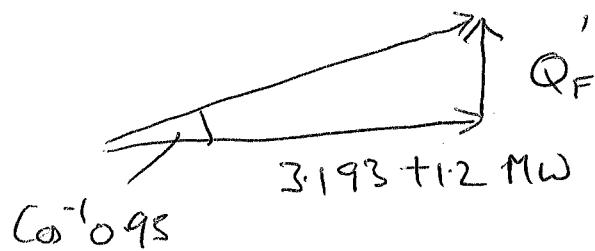(c) (i) With the synchronous machine the new power demand will be:



$$Q_F' = 4.393 \tan(\cos^{-1} 0.95) = 1.444 \text{ MVAR.}$$

Hence the synchronous machine provides $2.641 - 1.444 = \underline{\underline{1.197 \text{ MVAR}}}$

(ii) The synchronous machine MVA:

$$S = \sqrt{P^2 + Q^2} = \sqrt{1.2^2 + 1.197^2} = \underline{\underline{1.695 \text{ MVA}}}$$

and it operates at a power factor of:

$$\cos \phi = \text{p.f.} = \frac{1.2}{1.695} = \underline{\underline{0.708 \text{ leading}}}$$

$$(iii) I_L = I_{ph} = \frac{S_{sn}}{\sqrt{3} V_L} = \frac{1.695 \times 10^6}{\sqrt{3} \times 6600} = 148.27 L + 44.93^\circ \text{ A}_{\text{rms}}$$

$$\text{Hence } Z_{ph} = \frac{6600 L 0^\circ}{148.27 L 44.93^\circ} = 25.7 L - 44.93^\circ = \underline{\underline{18.19 - j18.15 \Omega}}$$

QUESTION 6

Km 7

(a) (i) The total flux in the airgap is:

$$\phi = B \cdot A = 0.8 \times 100 \times 10^{-6} = 8 \times 10^{-5} \text{ Wb}$$

Hence the total reluctance is:

$$S_T = \frac{NI}{\phi} = \frac{200 \times 4}{8 \times 10^{-5}} = 1 \times 10^7 \text{ H}^{-1}$$

Now the reluctance can also be calculated as:

$$S_T = S_{IRON} + S_{AIR}$$

$$= \frac{\pi \cdot 0.12 - g}{2000 \mu_0 \times 100 \times 10^{-6}} + \frac{g}{\mu_0 \times 100 \times 10^{-6}}$$

$$\therefore \frac{\pi \cdot 0.12 - g}{2000} + g = 1 \times 10^7 \times \mu_0 \times 100 \times 10^{-6} \times 2000$$

$$\therefore 1999g + 0.377 = 1.257 \times 10^{-3} \times 2000$$

$$\therefore \underline{\underline{g = 1.07 \text{ mm}}}$$

(ii) The inductance is given by:

$$L = \frac{N^2}{S} = \frac{200^2}{1 \times 10^7} = \underline{\underline{4 \text{ mH}}}$$

(b) The peak current of the AC supply must be 4 since

from part (a) 4A DC produced a flux density of 0.8T in the airgap. Hence the rms current = $\frac{4}{\sqrt{2}}$ A.

The impedance of the device is:

$$Z = R + j2\pi f L = 5 + j \cdot 2\pi f \cdot 0.004$$

$$\text{or } |Z| = \sqrt{5^2 + (0.025f)^2}$$

QUESTION 4 (CONTINUED)


KM 8

$$\therefore \frac{V_{rms}}{Z} = \frac{100}{\sqrt{5^2 + (0.025f)^2}} = \frac{4}{\sqrt{2}}$$

$$\therefore 25 + (0.025f)^2 = \left(\frac{100\sqrt{2}}{4}\right)^2$$

$$\therefore f = \underline{\underline{1.4 \text{ kHz}}}$$

(C)(i)

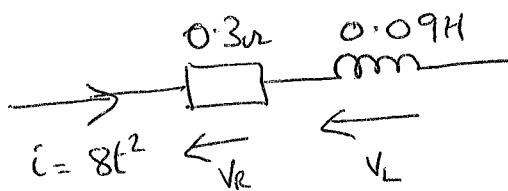

$$\text{At } t = 1.5s \quad i = 8t^2 = 18A$$

$$V_R = 0.3 \times 18 = 5.4V$$

$$V_L = L \frac{di}{dt} = 0.09 \cdot 16t = 2.16V$$

$$\text{Hence total voltage is } 5.4 + 2.16 = \underline{\underline{7.56V}}$$

(ii) Since both V_R and V_L will be at their highest values at $t=4.5s$

then:

$$V_R = 0.3 \cdot 8t^2 = 2.4t^2 = 2.4 \times 4.5^2 = 48.6V$$

$$V_L = 0.09 \times 16t = 0.09 \times 16 \times 4.5 = 6.48V$$

$$\therefore \text{Maximum voltage required} = 48.6 + 6.48 = \underline{\underline{55.08V}}$$

(iii) Power dissipation in the resistor = $I^2 R$

$$P = (8t^2)^2 \times 0.3 = 19.2t^4$$

at $t = 2s$

$$P = \underline{\underline{307W}}$$

QUESTION 4 (CONTINUED)

KM 9

(iv) Since when $t=0$ there is no energy stored in the inductor, then the total energy stored in the inductor at $t=4.5s$ can be found from:

$$E = \frac{1}{2} L i^2$$

$$\therefore E = \frac{1}{2} L (8t^2) = 2.88 \times 4.5^4 = 1181 \text{ J}$$

Energy dissipated in the resistor over the 4.5s period?

$$E_R = \int_0^{4.5} V_R \cdot i dt = \int_0^{4.5} i^2 R dt = \int_0^{4.5} 0.3 \times 64t^4 dt$$

$$\therefore E_R = 0.3 \left[\frac{64t^5}{5} \right]_0^{4.5} = 7086 \text{ J}$$

$$\begin{aligned} \therefore \text{Total energy supplied from source} &= 7086 + 1181 \\ &= \underline{\underline{8267 \text{ J}}} \end{aligned}$$

$$\therefore \text{Average power drawn} = \frac{8267}{4.5} = \underline{\underline{1837 \text{ W}}}$$