
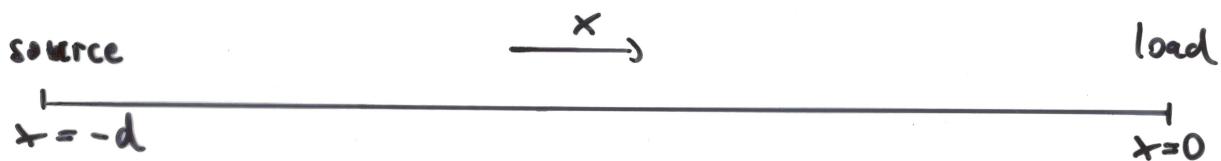


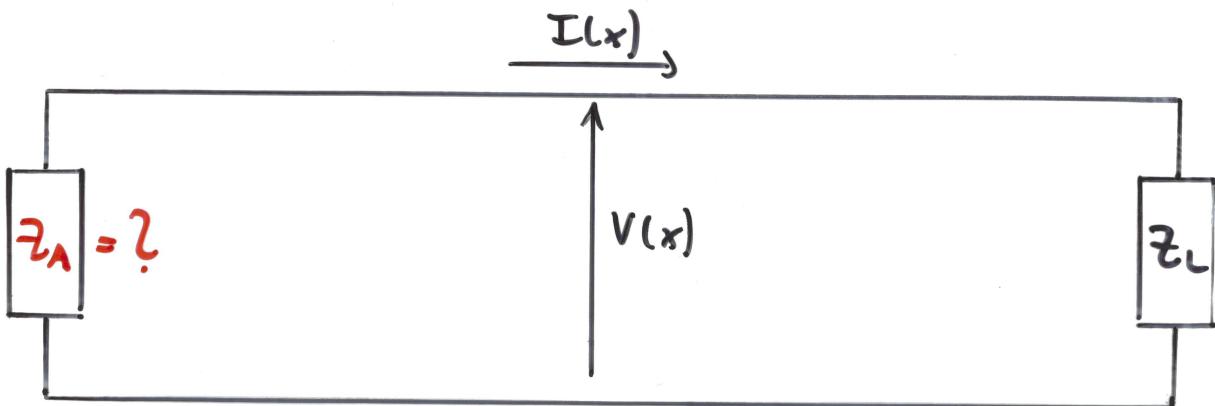current reflection and apparent impedance at source



$$V_0^+ = Z_0 I_0^+ \quad \& \quad V_0^- = -Z_0 I_0^-$$

$$\Rightarrow \Gamma = \frac{V_0^-}{V_0^+} = -\frac{I_0^-}{I_0^+} \quad (\text{reversed sign of current SWR !})$$

$$\text{if } V(x,t) = V_0^+ e^{j\omega t} (e^{-j\tilde{k}x} + \Gamma e^{+j\tilde{k}x})$$

$$\text{then } I(x,t) = \frac{V_0^+}{Z_0} e^{j\omega t} (e^{-j\tilde{k}x} - \Gamma e^{+j\tilde{k}x})$$

\Rightarrow apparent impedance at source:

$$\boxed{Z_A = \frac{V(-d)}{I(-d)}} = \frac{\cancel{V_0^+} e^{j\omega t} (e^{+j\tilde{k}d} + \Gamma e^{-j\tilde{k}d})}{\cancel{V_0^+} e^{j\omega t} (e^{+j\tilde{k}d} - \Gamma e^{-j\tilde{k}d})}$$

$$= Z_0 \frac{e^{+j\tilde{k}d} + \Gamma e^{-j\tilde{k}d}}{e^{+j\tilde{k}d} - \Gamma e^{-j\tilde{k}d}} \quad \text{with } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$= Z_0 \frac{(Z_L + Z_0) e^{+j\tilde{k}d} + (Z_L - Z_0) e^{-j\tilde{k}d}}{(Z_L + Z_0) e^{+j\tilde{k}d} - (Z_L - Z_0) e^{-j\tilde{k}d}}$$

$$= Z_0 \frac{\cancel{Z_L} \cos \tilde{k}d + j \cancel{Z_L} \sin \tilde{k}d + \cancel{Z_0} \cos \tilde{k}d + j \cancel{Z_0} \sin \tilde{k}d + \cancel{Z_L} \cos \tilde{k}d - j \cancel{Z_L} \sin \tilde{k}d}{\cancel{Z_L} \cos \tilde{k}d + j \cancel{Z_L} \sin \tilde{k}d + \cancel{Z_0} \cos \tilde{k}d + j \cancel{Z_0} \sin \tilde{k}d - \cancel{Z_L} \cos \tilde{k}d + j \cancel{Z_L} \sin \tilde{k}d + \cancel{Z_0} \cos \tilde{k}d - j \cancel{Z_0} \sin \tilde{k}d}$$

$$= Z_0 \frac{2 \cancel{Z_L} \cos \tilde{k}d + 2j \cancel{Z_0} \sin \tilde{k}d}{2 \cancel{Z_0} \cos \tilde{k}d + 2j \cancel{Z_L} \sin \tilde{k}d}$$

$$= Z_0 \frac{Z_L + j Z_0 \tan \tilde{k}d}{Z_0 + j Z_L \tan \tilde{k}d}$$

divide numerator
and denominator
by $2 \cos \tilde{k}d$

transforms Z_L into Z_A

consider some special cases at load end :

i) $d=0 \Rightarrow \tan \tilde{\kappa}d = \tan 0^\circ = 0 \Rightarrow Z_A = Z_L$
(consistency)

ii) $d=\lambda/4 \Rightarrow \tan \tilde{\kappa}d = \tan\left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{4}\right) = \tan \pi/2 = \infty$
 $\Rightarrow Z_A = \frac{Z_0^2}{Z_L}$

iii) $d=\lambda/2 \Rightarrow \tan \tilde{\kappa}d = \tan\left(\frac{\pi}{\lambda} \cdot \frac{\lambda}{2}\right) = \tan \pi = 0$
 $\Rightarrow Z_A = Z_L$

iv) short-cut with $Z_L=0$

$$\Rightarrow Z_A = j Z_0 \tan \tilde{\kappa}d = j \omega L_A \text{ purely inductive}$$

v) open line with $Z_L=\infty$

$$\Rightarrow Z_A = \frac{Z_0}{j \tan \tilde{\kappa}d} = \frac{1}{j \omega C_A} \text{ purely capacitive}$$

application examples:

a) choice of Z_0 to match load and source

given: $Z_L = 100 \Omega$, $Z_A = 25 \Omega$, use line of length $d=\lambda/4$

calculate Z_0

At $d=\lambda/4$ see (ii) above: $Z_A = \frac{Z_0^2}{Z_L}$

$$\Rightarrow Z_0 = \sqrt{Z_A \cdot Z_L} = \sqrt{25 \cdot 100} \Omega = 50 \Omega \text{ (geometrical mean !)}$$

b) choice of line length to get purely inductive or purely capacitive load

given: $Z_0 = 50 \Omega$, $f = 2 \text{ GHz}$, $v = \gamma_3 \cdot c$, $L_A = 10 \text{nH}$

calculate d

Short-circuit line and use iv) above; i.e.

$$j Z_0 \tan \tilde{\kappa}d = Z_A = j \omega L_A$$

with $\tilde{\kappa} = \frac{2\pi}{\lambda}$ and $v = \lambda \cdot f \Rightarrow \tilde{\kappa} = \frac{2\pi f}{v}$ and $\omega = 2\pi f$


$$\Rightarrow \tan \tilde{\kappa}d = \frac{2\pi f L_A}{Z_0} = 2.5133 = \tan 68.3^\circ$$

$$\Rightarrow \tilde{\kappa}d = 68.3^\circ = 1.192$$

$$\Rightarrow d = \frac{1.192}{\tilde{\kappa}} = \frac{1.192}{2\pi} \cdot \lambda = \frac{1.192}{2\pi f} v = 0.019 \text{ m} = 1.9 \text{ cm}$$

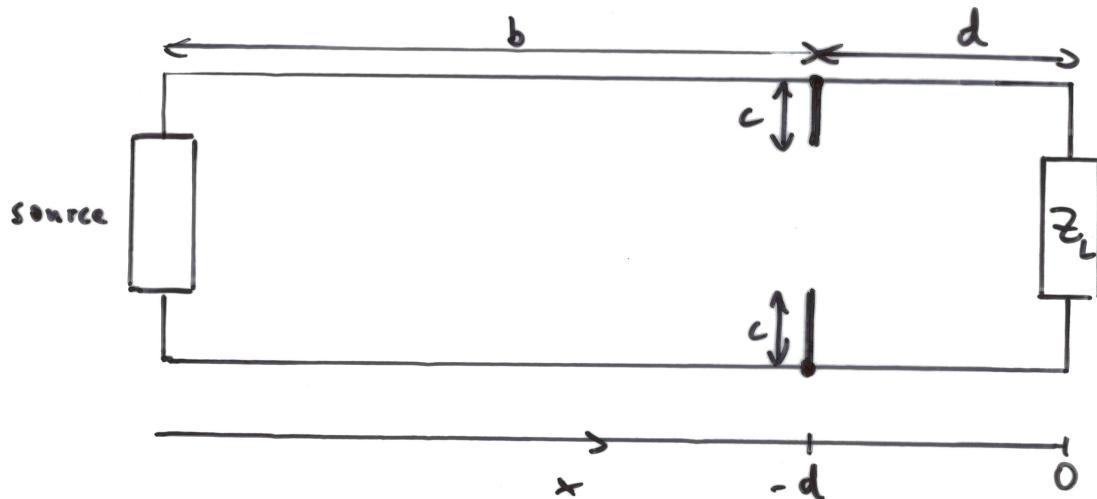c) use of tuning stubs to reduce Z_A

By adding another transmission line, Z_0 can be increased to match Z_L . If Z_0 needs to be reduced, short terminated "stubs" are added in parallel to tune the transmission line impedance.



total apparent admittance at $x = -d$

$$\frac{1}{Z} = \frac{1}{Z_{\text{line}}} + \frac{1}{Z_{\text{stub}}}$$

For the stub, the line appears open with $Z_L = \infty$, hence

$$Z_{\text{stub}} = \frac{Z_0}{j \tan \theta_{\text{sc}}}$$

$$\rightarrow \frac{1}{Z} = \frac{1}{Z_A(-d)} + \frac{j \tan \theta_{\text{sc}}}{Z_0}$$

gives modified Z_A at position $x = -d - b$ of source.