


Q1 (a)

$$(i) \text{ h.f. gain} = 1 \quad (\text{since } X_{C_1} \ll R_1 + R_2)$$

$$\text{l.f. gain} = \frac{R_2}{R_1 + R_2} \quad (\text{since } X_{C_1} \gg R_1 + R_2).$$

$$\begin{aligned} (ii) \quad \frac{V_o}{V_i} &= \frac{R_2}{R_2 + R_1 \parallel X_{C_1}} = \frac{R_2}{R_2 + \frac{R_1 / j\omega C_1}{R_1 + 1/j\omega C_1}} \\ &= \frac{R_2}{R_2 + \frac{R_1}{1 + j\omega C_1 R_1}} \\ &= \frac{R_2 (1 + j\omega C_1 R_1)}{R_2 (1 + j\omega C_1 R_1) + R_1} = \frac{R_2 (1 + j\omega C_1 R_1)}{R_2 + R_1 + j\omega C_1 R_1 R_2} \\ &= \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j\omega C_1 R_1}{1 + j\omega C_1 \frac{R_1 R_2}{R_1 + R_2}} \equiv k \cdot \frac{1 + j f/f_1}{1 + j f/f_0} \end{aligned}$$
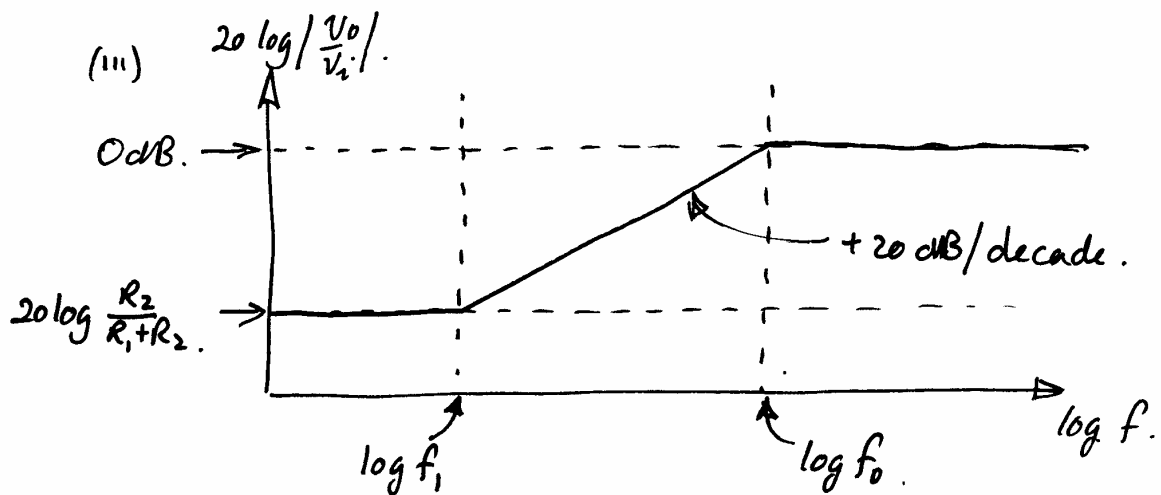
$$k = \frac{R_2}{R_1 + R_2}, \quad f_1 = \frac{1}{2\pi C_1 R_1}, \quad f_0 = \frac{R_1 + R_2}{2\pi C_1 R_1 R_2}.$$




(iv) addition of C_2 in parallel with R_2 must give $C_1 R_1 = C_2 R_2$ or alternatively, $\frac{R_2}{R_1 + R_2} = \frac{C_1}{C_1 + C_2}$.

$$\text{so } C_2 = \frac{C_1 R_1}{R_2} = \frac{10^{-9} \times 10^4}{10^3} = \underline{\underline{10 \text{ nF}}}.$$

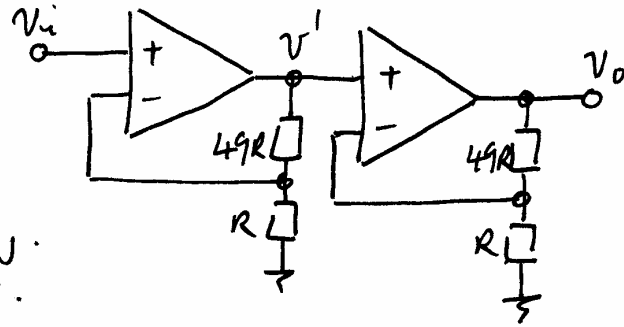Q1(b)

(i). total gain
 $= \text{gain}(1) \times \text{gain}(2)$
 $= 50 \times 50 = \underline{\underline{2500 \text{ V/V}}}$



(ii) GBP of each amplifier is 20MHz.

\therefore for gain of 50, $\text{BW} = \frac{20 \times 10^6}{50} = \underline{\underline{400 \text{ kHz}}}$
 for each op-amp.

-3dB frequency of cascade is -1.5dB frequency of each op-amp. Considering only the frequency dependence.....

each op-amp $\frac{V_o}{V_i} = k \frac{1}{1 + j f / 400 \text{ kHz}}$

ignore this because
 it doesn't affect frequency domain

$\frac{V_o}{V_i} = -1.5 \text{ dB}$ when

$$\left| \frac{1}{1 + j f / 400 \text{ kHz}} \right| = 10^{-1.5/20}$$

or $\frac{1}{1 + f^2 / (400 \text{ kHz})^2} = 10^{-3/20} = 0.708$

or $1.413 = 1 + \frac{f^2}{16 \times 10^{10}}$

or $0.413 = \frac{f^2}{(400 \text{ kHz})^2} = (0.642)^2$

$\therefore f = 400 \text{ kHz} \times 0.642 = \underline{\underline{257 \text{ kHz}}}$

= -1.5dB f of each amp
 = -3dB f of cascade.

Q1 (b)

(iii)

max rate of change of sinusoid is

$$\frac{d(V_p \sin \omega t)}{dt} = V_p \omega \cos \omega t.$$

$$\max \cos \omega t = 1 \text{ so } \max \frac{dv}{dt} = V_p \omega.$$

max signal frequency when its max $\frac{dv}{dt}$
= slew rate.

$$\text{ie } 70 \times 10^6 = V_p \omega = 10 \cdot 2 \cdot \pi \cdot f$$

$$\text{or } f_{\max} = \underline{\underline{1.1 \text{ MHz}}}$$

Q2 (i) sum currents at v' node

$$\frac{v_o - v'}{1/s_{c_1}} + \frac{v_i - v'}{R} = \frac{v' - v_x}{R}$$

Since gain is 2, $v_x = v_o/2$.

$$\text{so } v_o s_{c_1} R - v' s_{c_1} R + v_i - v' = v' - v_o/2$$

$$\text{or } v' = \frac{2v_i + v_o(1 + 2s_{c_1}R)}{2(2 + s_{c_1}R)}$$

$$\text{also } v_x = v' \frac{1/s_{c_2}}{R + 1/s_{c_2}} \text{ or } v' = \frac{v_o(1 + s_{c_2}R)}{2}$$

$$\therefore \frac{v_o(1 + s_{c_2}R)}{2} = \frac{2v_i + v_o(1 + 2s_{c_1}R)}{2(2 + s_{c_1}R)}$$

$$v_o [(1 + s_{c_2}R)(2 + s_{c_1}R) - (1 + 2s_{c_1}R)] = 2v_i$$

$$v_o [1 + 2s_{c_2}R - s_{c_1}R + s^2 c_1 c_2 R^2] = 2v_i$$

$$\text{or } \frac{v_o}{v_i} = \frac{2}{1 + s(2c_2R - c_1R) + s^2 c_1 c_2 R^2}$$

(ii) second order, analogue, low pass,
active, conditionally stable.

Q2 (iii) $k = 2.$

$$\omega_0^2 = \frac{1}{C_1 C_2 R^2} \quad \text{or} \quad \omega_0 = \frac{1}{R \sqrt{C_1 C_2}}$$

$$\frac{1}{\omega_0 q} = R(2C_2 - C_1).$$

$$\text{or } \frac{1}{q} = \omega_0 R(2C_2 - C_1) = \frac{\cancel{R}(2C_2 - C_1)}{\cancel{R} \sqrt{C_1 C_2}}$$

(They can leave it as $1/q$ or invert it).

(iv) For stability, damping term must be positive

$$(2C_2 - C_1)R > 0.$$

$$\text{or } 2C_2 - C_1 > 0$$

$$2C_2 > C_1$$

$$\text{or } \frac{C_2}{C_1} > \frac{1}{2} \text{ for stability.}$$

Q3(a). (i) R_{th} , by inspection = $1.2 \text{ k}\Omega$.

$$\overline{v_o^2} \Big|_{10 \text{ nV}} = \left[10 \text{ nV} \cdot \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 3 \text{ k}\Omega} \right]^2 = 10^{-16} \times \frac{4}{25} = 16 \times 10^{-18} \text{ V}^2 \text{ Hz}^{-1}$$

$$\overline{v_o^2} \Big|_{3 \text{ pA}} = \left[3 \times 10^{-12} (2 \text{ k}\Omega \parallel 3 \text{ k}\Omega) \right]^2 = 9 \times 10^{-24} \times 1.44 \times 10^6 = 12.96 \times 10^{-18} \text{ V}^2 \text{ Hz}^{-1}$$

$$\overline{v_o^2} \Big|_{2 \text{ k}\Omega} = 4kT 2 \text{ k}\Omega \left(\frac{3 \text{ k}\Omega}{5 \text{ k}\Omega} \right)^2 = 33.1 \times 10^{-18} \times \frac{9}{25} = 11.9 \times 10^{-18} \text{ V}^2 \text{ Hz}^{-1}$$

$$\overline{v_o^2} \Big|_{3 \text{ k}\Omega} = 4kT 3 \text{ k}\Omega \left(\frac{2 \text{ k}\Omega}{5 \text{ k}\Omega} \right)^2 = 49.7 \times 10^{-18} \times \frac{4}{25} = 7.9 \times 10^{-18} \text{ V}^2 \text{ Hz}^{-1}$$

$$\overline{v_{onT}^2} = [16.0 + 12.96 + 11.9 + 7.9] \times 10^{-18} = 48.76 \times 10^{-18} \text{ V}^2 \text{ Hz}^{-1}$$

$$\therefore v_{nTh} = \sqrt{48.76 \times 10^{-18}} = \underline{\underline{7.0 \times 10^{-9} \text{ V Hz}^{-1/2}}}.$$

(ii) First find the noise temperature of R_{th}

$$4kT_{eff} R_{th} = 48.76 \times 10^{-18}$$

$$\text{or } T_{eff} = \frac{48.76 \times 10^{-18}}{4 \times 1.38 \times 10^{-23} \times 1.2 \times 10^3} = 736 \text{ K}.$$

Then use $\overline{v_{nT}^2} = \frac{kT}{C} \text{ V}^2$ from the useful info. page ...

$$\overline{v_{nT}^2} = \frac{1.38 \times 10^{-23} \times 736}{10 \text{ pF}} = 1.016 \times 10^{-9} \text{ V}^2$$

$$\therefore v_{nT} = \underline{\underline{31.9 \mu\text{V}}}.$$

Q3 (b)

- (1) Signal to Noise ratio is the ratio of signal power to noise power at a node in the circuit/system. It measures only signal quality.


Noise factor is defined as

$$\frac{\text{Signal to noise ratio at input}}{\text{Signal to noise ratio at output.}}$$

Since $S_i + S_o$ are related by system power gain (A_p) the signal is eliminated from the expression. NF is thus a measure of system performance and gives no information about signal quality.

(C). System is ...

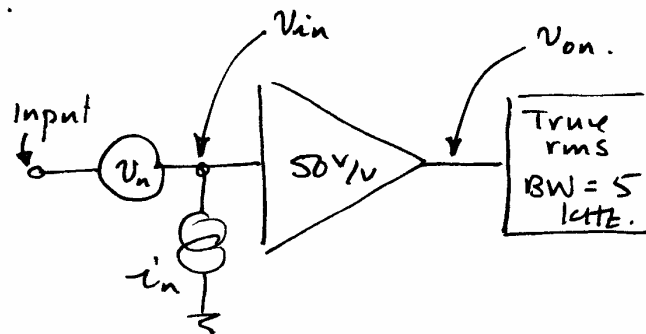When input is grounded, i_n does not contribute to output..... so



$$\begin{aligned}\overline{v_{on}^2} &= 50^2 \cdot \overline{v_{in}^2} \\ &= 50^2 \cdot \overline{v_n^2}.\end{aligned}$$

True rms will read $\sqrt{\overline{v_{on}^2} \times \text{BW}}$

$$\text{So } v_n = \frac{45 \mu\text{V}}{\sqrt{5 \text{ kHz}} \cdot 50} = 12.7 \text{ nV} \cdot \text{Hz}^{-1/2}.$$


When input grounded via a noisy $8.2 \text{ k}\Omega$ resistor...

$$\begin{aligned}\overline{v_{on}^2} &= \left(\frac{84 \times 10^{-6}}{5 \text{ kHz}} \right)^2 = 50^2 \left[\overline{v_n^2} + \overline{i_n^2} (8.2 \text{ k}\Omega)^2 + 4kT \cdot 8.2 \text{ k}\Omega \right] \\ &= 50^2 \left[162 \times 10^{-18} + (8.2 \times 10^3)^2 \overline{i_n^2} + 136 \times 10^{-18} \right]\end{aligned}$$

$$\text{or } \overline{i_n^2} (8.2 \times 10^3)^2 = 5.65 \times 10^{-16} - 1.62 \times 10^{-16} - 1.36 \times 10^{-16}$$

$$\text{or } i_n = \sqrt{3.96 \times 10^{-24}} = \underline{\underline{2 \text{ pA} \cdot \text{Hz}^{-1/2}}}.$$


Q4(a)
(1)

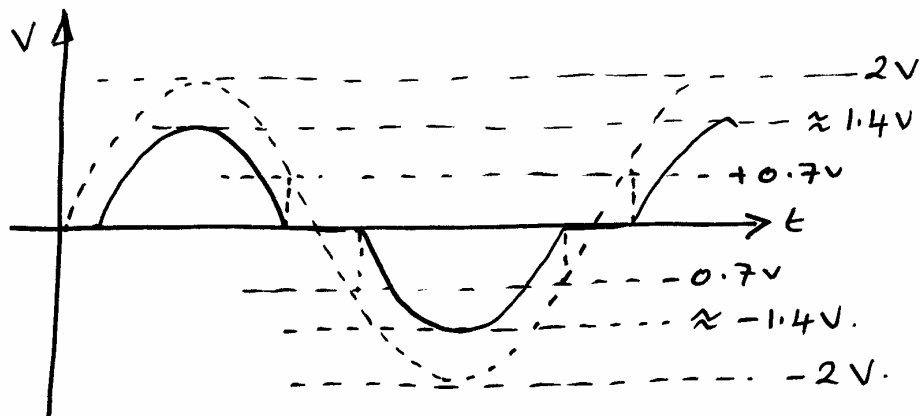


The flat region in the output waveform is "crossover distortion". It arises because of the finite turn on voltages of $T_1 + T_2$. There is no positive output until V_i reaches $0.7V$ and no negative output until V_i falls below $-0.7V$.

(ii)

batteries could be added as shown.

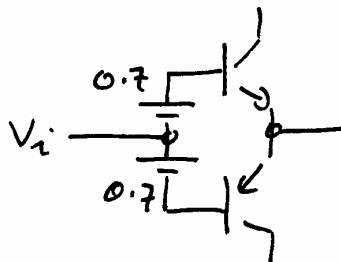

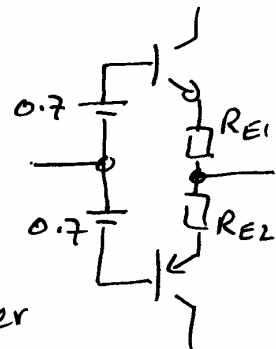(iii) Thermal runaway arises because of the negative temperature coefficient of V_{BE} for a given I_c or the positive temp coefficient of I_c for a given V_{BE} .



With const. V_{BE} (as in part (ii)), power dissipation in transistors will heat them up causing an increase in I_c which heats them up further and so on. There is no mechanism in the set of part (ii) to limit this process. By adding $RE1 + RE2$, I_c develops a voltage between the transistor emitters and this voltage reduces V_{BE} if the voltage between the bases is constant. Thus as I_c tries to increase the circuit action is to reduce V_{BE} + hence limit the possible rise in I_c .

Q4 (b)

(i) First identify whether current or voltage would limit output power....

$\frac{15V}{4\Omega} = 3.75A$... but I_c can only provide 3A so the limit is current

$$P_{Lmax} = \frac{I_p^2 R_L}{2} \left[\equiv I_{rms}^2 R_L \right]$$

$$= \frac{3^2 \times 4}{2} = \underline{\underline{18W}}$$


(ii) Each I_c will dissipate.

$$\frac{2 \cdot 18^2}{\pi^2 \cdot 4} = \underline{\underline{16.4W}}$$

$$\Delta T = (2.5^\circ C/W \times 16.4)^\circ C$$

$$= \underline{\underline{41^\circ}}$$

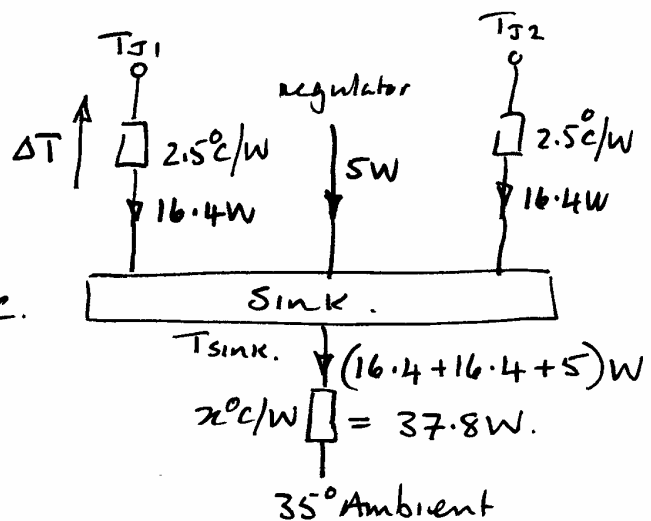When T_{J1} (and T_{J2}) are $120^\circ C$, T_{sink}
 $= 120 - 41 = 79^\circ C$.



$$\therefore x = \frac{T_{sink} - T_{amb}}{\text{Total Power}} = \frac{79 - 35}{37.8}$$

$$= \underline{\underline{1.16^\circ C/W}}$$