

# EEE118: Electronic Devices and Circuits

## Lecture XIII

James E. Green

Department of Electronic Engineering  
University of Sheffield  
j.e.green@sheffield.ac.uk

1 / 20

EEE118: Lecture 13

Review

## Review

- Discussed the properties of the third class of 'switch': Electronic.
- Considered how the switching action of a transistor is represented on the output characteristics.
- Introduced the idea of a 'load line'.
- Considered power dissipation in the "on" state
- Provided design equations for MOS and BJT switches using a large signal model. Note that in general design work it is often unnecessary to actually draw out this model.
- Performed switching circuit example calculation (exam/tutorial sheet style)

2 / 20

EEE118: Lecture 13

Review

## Outline

- 1 Review
- 2 Alternating Current Circuits for Switching Transistors
  - Half Wave
  - Full Wave
  - Full Wave Bridge
- 3 H-Bridge
- 4 Switching Inductive Loads
  - Single Transistor Switch with Inductive Load
  - H Bridge with Inductive Load
- 5 Review
- 6 Bear

3 / 20


EEE118: Lecture 13

Alternating Current Circuits for Switching Transistors

Half Wave
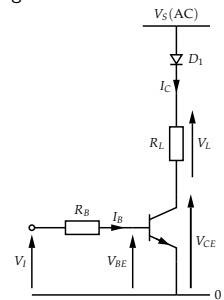
## AC Transistor Switching Circuits

The NPN BJT and N-Ch MOSFET should only be operated with conventional current flowing from collector to emitter and drain to source. What about switching voltages that have both positive and negative values?



- One option is to include a diode in series with the load.
- When  $V_S$  falls below 0 V the diode is reverse biased.
- Only provides half wave rectification.
- On state diode power loss is  $0.7 \cdot I_C$


4 / 20

EEE118: Lecture 13

Alternating Current Circuits for Switching Transistors

Full Wave

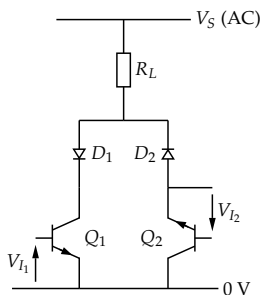To produce a full wave rectifying AC transistor switching circuit, two NPN transistors can be used together each dealing with one half of the AC cycle.



- $Q_1$  and  $D_1$  are responsible for the current in  $R_L$  while  $V_S > 0$  V
- $Q_2$  and  $D_2$  are responsible for the current in  $R_L$  while  $V_S < 0$  V
- The control input for  $Q_2$  is a little inconvenient but it can easily be overcome in practice.


5 / 20

EEE118: Lecture 13

Alternating Current Circuits for Switching Transistors

Full Wave Bridge

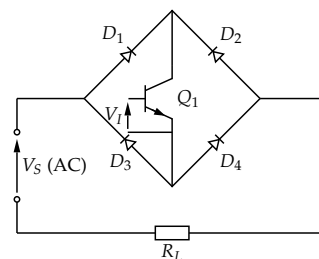
To produce an AC transistor switching circuit with only one switch,



The control voltage is still referenced to a tricky location, but it is not too troublesome.

6 / 20


For one half cycle,

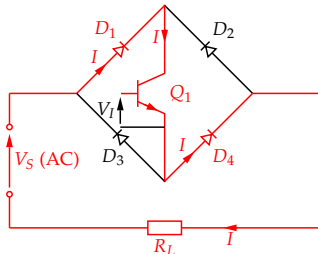

Note that the transistor current is DC, but the load current is AC.

7 / 20

For one the other half cycle,

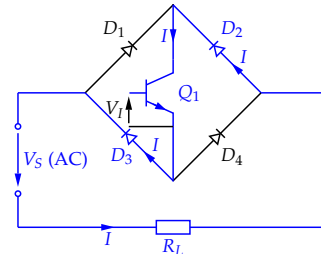


Whatever happens to  $V_S$ ,  $I_C$  is always flowing into the collector.

8 / 20

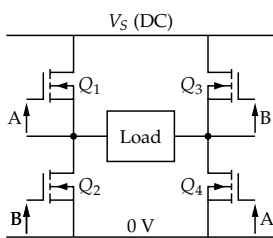
## H Bridge

Often used for motor control from a DC supply.



- Four switches in an "H" shape. The load is the cross bar.
- For Toyota Prius  $V_S \approx 220 \text{ V}$ ,  $I \approx 110 \text{ A}$
- By controlling the switches current can flow in either direction.
- DC motors can run in both directions.
- Average power can also be controlled.

9 / 20

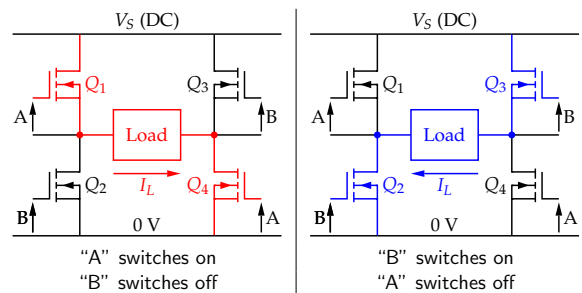


If both "A" and "B" are on together a large 'shoot through' current results, usually destroying the switches. Both "A" and "B" can be time varying which modulates the load current, dissipating a predetermined average power in the load.

10 / 20
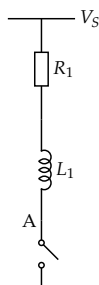
## Switching Inductive Loads


Inductors always try to keep current flowing.  $V = L \frac{dI}{dt}$ . If a switch is opened its current falls to zero very rapidly and  $\frac{dI}{dt} \rightarrow \infty$ . Consequently  $V_{L1} \rightarrow \infty$  too.

- When the switch is "on", a current  $\frac{V_S}{R_1}$  flows.
- When the switch turns "off",  $L_1$  attempts to maintain the prior "on" current by increasing the voltage across its terminals.
- The charge attempting to leave the inductor as its magnetic field collapses appears at node A, but has no where to go thereafter



11 / 20

- Node A has some small stray parasitic capacitance due to its physical dimensions.
- The charge arriving on node A charges this stray capacitance according to  $Q = C V$ .
- Since  $C$  is small,  $V$  must become very large to accommodate even a modest charge,  $Q$ .
- The very high voltage spikes which occur may damage any semiconductor switches in the circuit.
- The solution is to provide another path for the charge leaving the inductor to escape from node A.

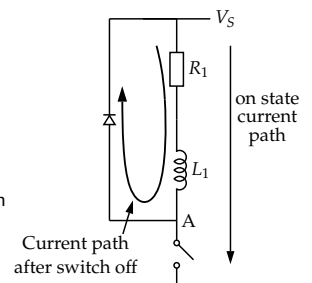


12 / 20

- The diode is reverse biased under normal circumstances. If  $V_A > (V_S + 0.7)$  the diode will conduct any charge on A back into the power supply.
- Just after the switch off event, the diode current is equal to the on state inductor current
- After switch off this current falls exponentially with a time constant of  $\frac{L}{R_T}$  where  $R_T$  is the total resistance of the return or "free wheeling" pathway.
- In some applications the "inductive kick" is desirable for example, "boost" and "flyback" converters (types of Switched Mode Power Converter). Also in CRT power supplies and in internal combustion engine ignition systems. Often though, it is highly undesirable and methods to control it are used.

The energy stored in the inductor drives the "back EMF" process. The situation is similar for electrical machines (motors & generators).


13 / 20

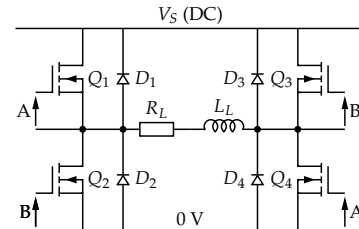

- Operation is as before,  $Q_1$  and  $Q_4$  operate together as do  $Q_2$  and  $Q_3$ .
- Now the energy stored in the inductor must be considered.
- As soon as the switches turn off the inductor current must continue.
- There are six interesting states in total, but only four are considered here.

14 / 20

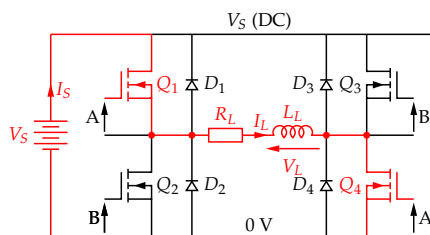
### H Bridge with Inductive Load - A switches "on"



- "A" switches have been on for a long time.
- $I_L$  is constant and flows out of the battery.
- The machine is drawing electrical power from the supply and converting it to mechanical power.

15 / 20

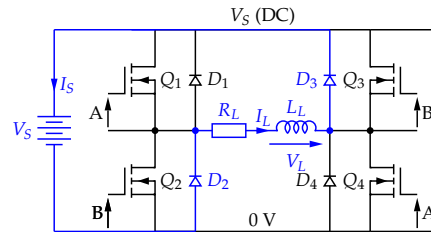
### H Bridge with Inductive Load - A switches "off"



- "A" switches, having been on for a long time, switch off.
- $I_L$  has not yet changed due to the inductive load, note the direction of  $V_L$ ,  $I_L$  and  $I_S$ . From a circuit perspective  $L_L$  is now a generator.
- The machine is returning electrical power stored in its inductance to the battery.

16 / 20

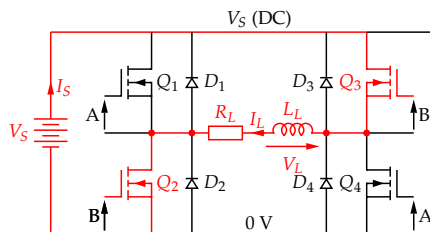
### H Bridge with Inductive Load - B switches "on"



- "B" switches have been on for a long time.
- $I_L$  is constant and flows out of the battery.
- The machine is drawing electrical power from the supply and converting it to mechanical power (rotating in opposite direction).

17 / 20
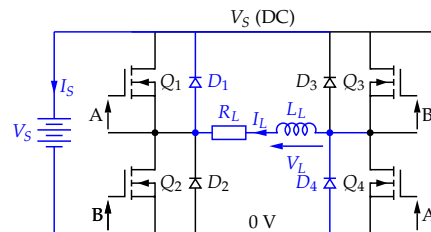
### H Bridge with Inductive Load - B switches "off"



- "B" switches, having been on for a long time, switch off.
- $I_L$  has not yet changed due to the inductive load, note the direction of  $V_L$ ,  $I_L$  and  $I_S$ . From a circuit perspective  $L_L$  is now a generator.
- The machine is returning electrical power stored in its inductance to the battery.

18 / 20

## Review

- Considered several transistor switching circuits for AC including,
  - Half wave single transistor switch
  - Full wave two transistor switch
  - Bridge full wave single transistor switch
- Introduced the H-bridge as a circuit commonly used to drive electrical machines from a DC supply.
- Considered the effects of inductance in the load of a transistor switch in terms of rate of change of current and provided a diode as an alternate current pathway.
- Applied the parallel diode approach to the H bridge and considered four states of operation.

