
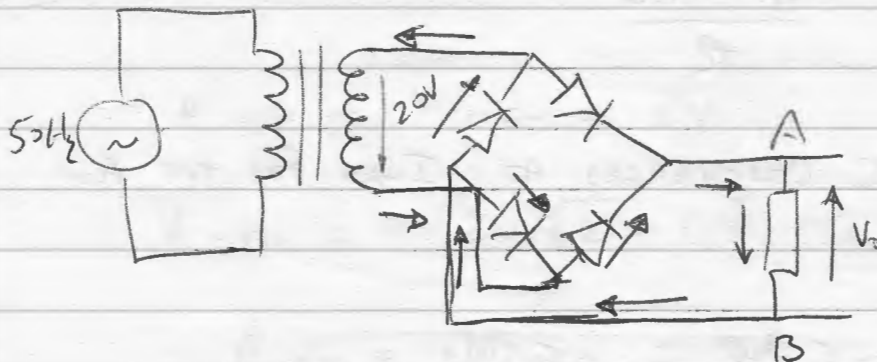


a. a i

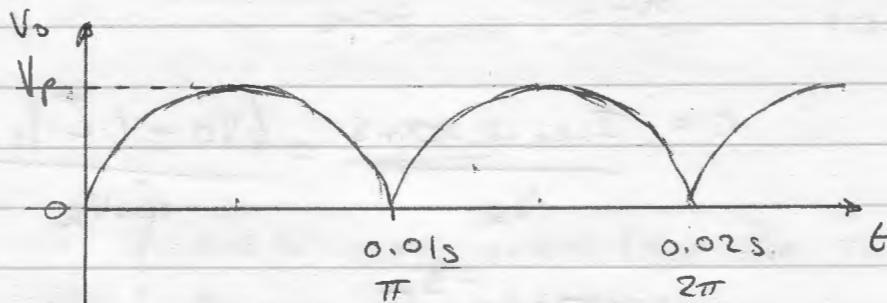

ii



1 SHAPE
1 TIME
1 PEAK AMP.
LABEL
1 CALC.

$$V_p = 20 \cdot \sqrt{2} - (0.7 + 2)$$

$$= \underline{\underline{26.88 \text{ V}}}$$

iii

$$V_{AV} = \frac{1}{T/2} \int_0^{T/2} V_p \sin(\omega t) dt$$

2


$$= \frac{1}{\frac{1}{2}(2\pi/\omega)} \int_0^{\pi/\omega} V_p \sin(\omega t) dt$$

2

$$= \frac{V_p}{\pi} \left[-\frac{V_p}{\omega} \cos(\omega t) \right]_0^{\pi/\omega}$$

1

$$= \frac{V_p}{\pi} [(+1) + (+1)]$$

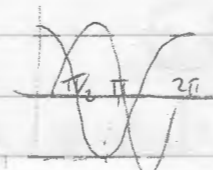

$$= \frac{2V_p}{\pi}$$

1

Q1 a iv

$$I_{max} = \frac{V_p - 1.4}{R}$$

2

Assume C DISCHARGES AT I_{max} FOR THE FULL 10ms.

$$I_{max} = \frac{C \frac{dV}{dt}}{10ms} = \frac{C \cdot V_R}{10ms}$$


2

$$\therefore C = \frac{I_{max} \times 10ms}{V_R} = \frac{(V_p - 1.4) \times 10ms}{R \cdot V_R}$$


$$= 6.7 \times 10^{-3} F$$

1

1

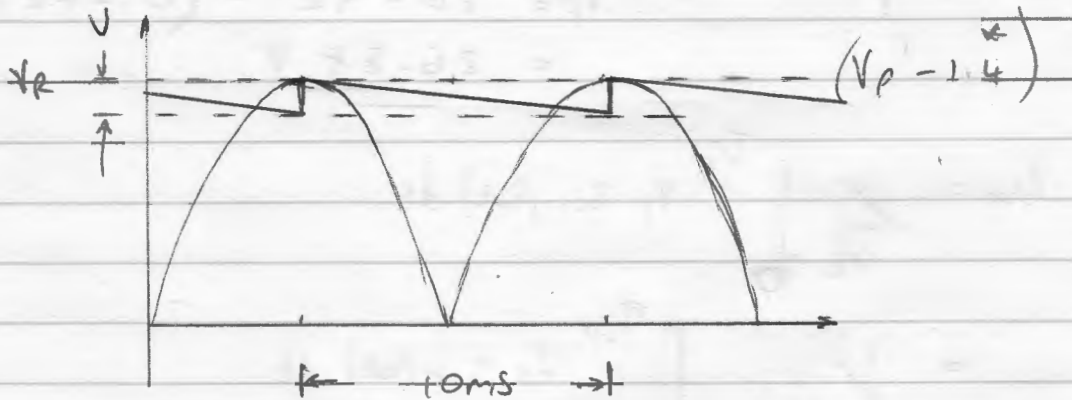

Q1 b i

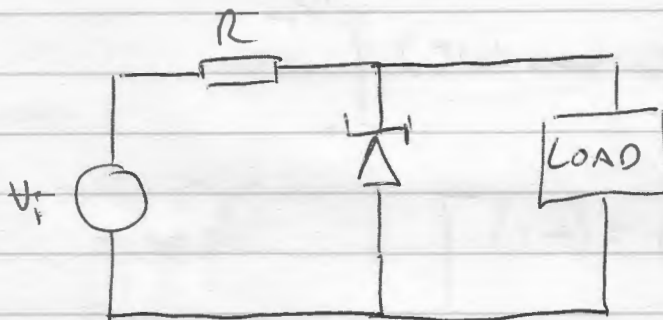

$$I_L(min) = 5mA$$

$$I_L(max) = 10mA$$

$$I_Z(min) = 2mA$$

Q16i (CONT'D)

$$V_{i, \text{MAX}} - V_{i, \text{MIN}} = 2V.$$


$$V_{i, \text{MIN}} = 20\sqrt{2} - 1.4^* - 2 = 24.9V$$

$$R_{\text{MAX}} = \frac{V_{i, \text{MIN}} - 9V}{I_{L, \text{MAX}} + I_{Z, \text{MIN}}} = \frac{24.9 - 9}{10\text{mA} + 2\text{mA}} = 1.3\text{k}\Omega$$

(1.4k IF 1.4V DROP DUE TO PROTECTOR DIODES IS NEGLECTED)

*2 SECOND MARK IS FOR IMPLICIT JUSTIFICATION OF $I_{L, \text{MAX}}$ AS OPPOSED TO $I_{L, \text{MIN}}$.

Q16ii

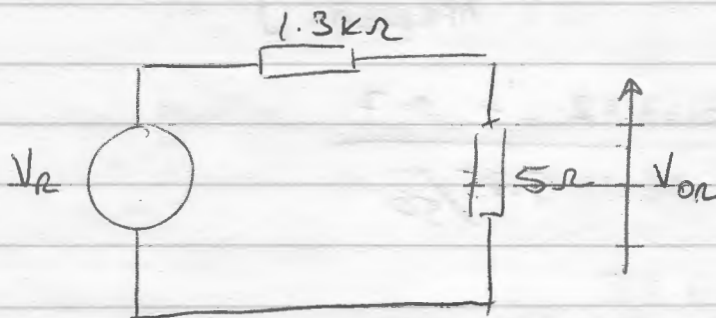

$$V_{O2} = V_R \cdot \frac{5}{5 + 1.3k} = 2 \cdot \frac{5}{1305}$$


$$= 7.6\text{mV}_{\text{approx}}$$

EEE118 Exam solutions 2016

Question 2:


(a)

i) Open circuit

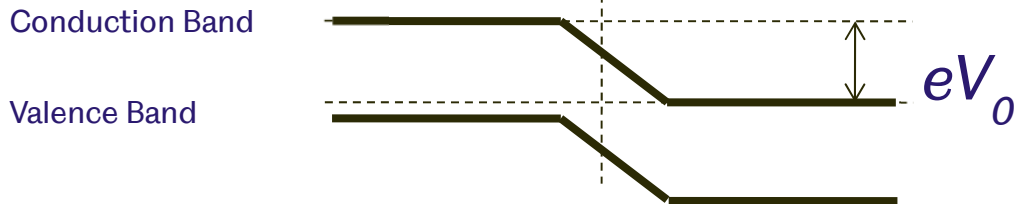


1 mark
each

ii) Forward Bias

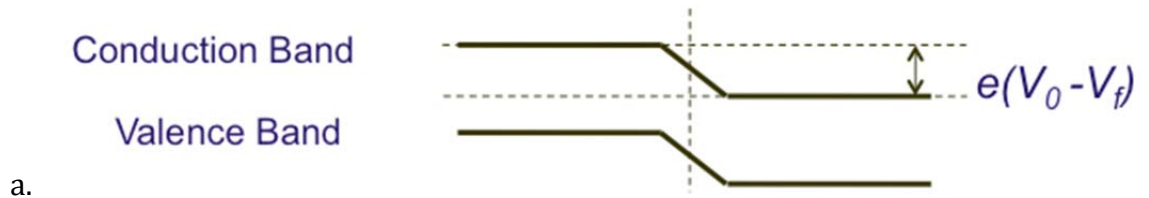

iii) Reverse Bias

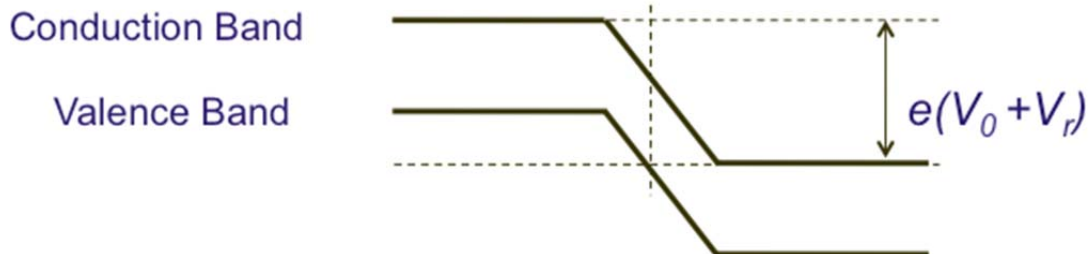

Explanation:

Open circuit, zero applied bias diode has inbuilt voltage V_0 and drift and diffusion currents are balanced hence no net current flows

In forward bias the junction voltage is reduced by V_f . This leads to a reduction in the potential barrier for electrons and holes and diffusion current increases strongly (exponentially).

In reverse bias, the junction voltage is increased by V_r . This increases the barrier potential for electrons and holes and reduces the diffusion current. The drift current remains approximately the same, and hence a small reverse bias current flows due to drift.

2 mark
each

$$\begin{aligned}
 \text{(b)} \quad I &= I_0 \left[e^{\frac{eV}{kT}} - 1 \right] \\
 0.02 &= I_0 \left[e^{\frac{e}{kT}(0.2)} - 1 \right], \quad \frac{kT}{e} = 0.026 \text{ eV} \\
 \text{(i)} \quad \Rightarrow 0.02 &= I_0 \left[e^{\frac{0.2}{0.026}} - 1 \right] \\
 &= I_0 \times 2190 \\
 \Rightarrow I_0 &= 9.1 \times 10^{-6} \text{ A} \\
 J_0 &= 9 \text{ A m}^{-2} \\
 A &= \frac{I_0}{J_0} = \frac{9.1 \times 10^{-6}}{9} \approx 1 \times 10^{-6} \text{ m}^2 = 1 \text{ mm}^2 \\
 \boxed{A = 1 \text{ mm}^2}
 \end{aligned}$$


3 marks

$$\begin{aligned}
 \text{(ii)} \quad C &= \frac{\epsilon A}{W} \Rightarrow \frac{1}{C^2} = \frac{W^2}{\epsilon^2 A^2} \\
 W^2 &= \frac{2e(V_0 - V)}{e} \frac{1}{N_d} \quad \text{for case where } N_a \gg N_d \\
 \therefore \frac{1}{C^2} &= \frac{2}{\epsilon e A^2 N_d} (V_0 - V) \\
 \Rightarrow \text{slope} &= \frac{2}{\epsilon e A^2 N_d} \\
 1.177 \times 10^{19} &= \frac{2}{12(8.85 \times 10^{-14})(1.6 \times 10^{-19})^2 (10^{-4})^2} (N_d) \\
 N_d &= \frac{1.177 \times 10^{19}}{1.177 \times 10^{19}} = 1 \times 10^{22} \text{ m}^{-3} \\
 \boxed{N_d = 1 \times 10^{22} \text{ m}^{-3}}
 \end{aligned}$$

7 marks


$$(c) \quad W = \left[\frac{2 \epsilon V_0}{q} \left(\frac{N_a + N_d}{N_a N_d} \right) \right]^{1/2}, \quad N_a = N_d = N$$
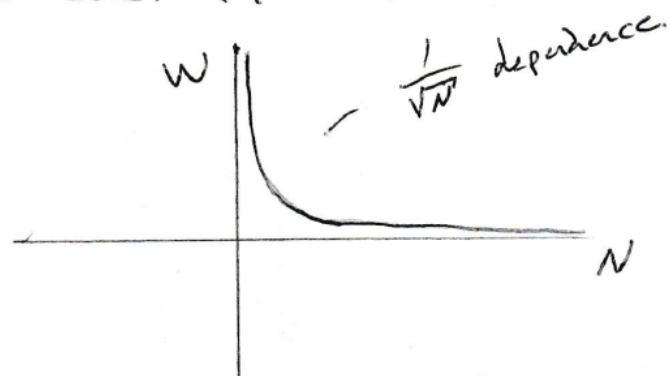
$$W = \text{const} \times \left(\frac{1}{N} \right)^{1/2}$$



3 marks

(d)

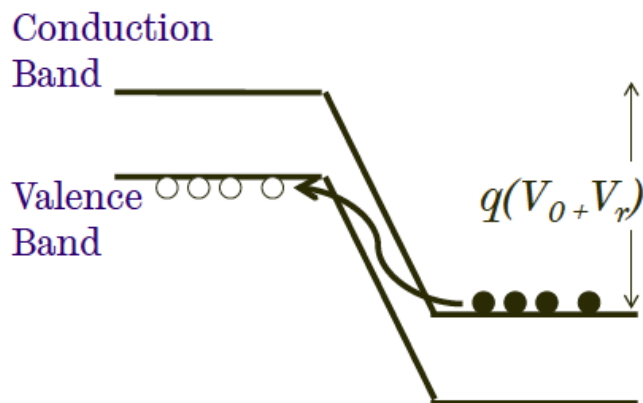


3 marks

At high reverse bias, the electrons in the can tunnel from the n-region across the barrier and into empty energy states in the valence band of the p-region.
At high p-type doping levels there are more available states in the valence band and it is therefore more likely an electron can tunnel into these states.

3a i

$$I_{C(on)} = \frac{V_{supply} - V_{CE(sat)}}{R_L}$$

$$= 5.85 A$$

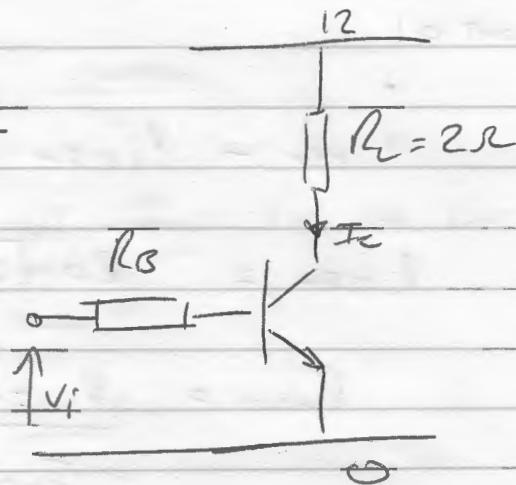

ii

$$P = I^2 R$$

$$= 5.85^2 \cdot 2$$

$$= 68.445 \text{ WATTS}$$

iii

LARGEST R_B IS ACTUALLY A SMALL NUMBER AND IS OBTAINED USING THE LOWEST POSSIBLE h_{FE} .

$$R_{B(max)} = \frac{V_i - V_{BE(sat)}}{\frac{I_C}{h_{FE(min)}}} \left. \vphantom{\frac{I_C}{h_{FE(min)}}} \right\} I_{B...}$$

$$= \frac{12 - 0.7}{5.85/50}$$

$$= 96.58 \Omega$$

iv

$$P = I \cdot V$$

$$= 5.85 \cdot V_{CE(sat)}$$

$$= 5.85 \cdot 0.3$$

$$= 1.755 \text{ WATTS}$$

Q3a v

POWER LOSS MUST BE THE SAME...

$$P = I^2 R \quad R = \frac{P}{I^2} = \frac{1.755}{5.85^2}$$

$$R = \underline{\underline{0.0513 \Omega}}$$

6i Assume I_B IS NEGLECTABLE...

$$V_B = 20 \times \frac{R_2}{R_1 + R_2} = 20 \times \frac{30}{150} = \underline{\underline{4V}}$$

$$I_E \approx I_C = \frac{V_B - 0.7}{R_E} = \frac{4 - 0.7}{2.3k\Omega} = \underline{\underline{1mA}}$$


$$V_C = V_{CC} - I_C R_C = 20 - 8.2 = \underline{\underline{11.8V}}$$

$$g_m = \frac{e I_C}{kT} = \frac{1.6 \times 10^{-19} \cdot 1 \times 10^{-3}}{1.38 \times 10^{-23} \cdot 300}$$

$$= \underline{\underline{38.64 \text{ mA/V}}}$$

$$r_{he} = \frac{\beta}{g_m} = \frac{400}{38.64 \text{ mA/V}} = \underline{\underline{10.35k\Omega}}$$

Q36 ii

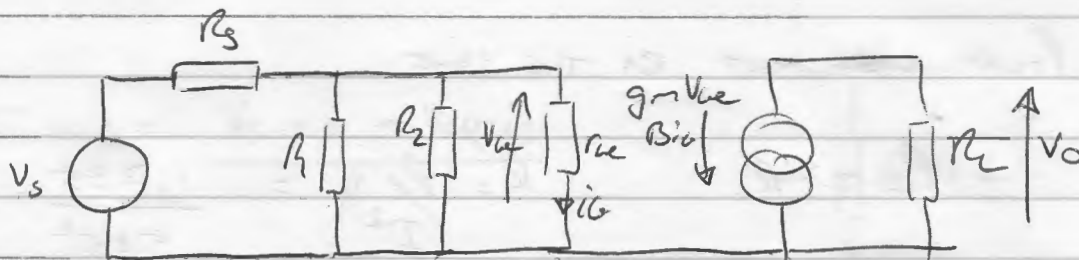

iii

C₁ COUPLES SIGNALS INTO THE AMPLIFIER AND PREVENTS DC CURRENT FLOWING FROM SOURCE TO AMPLIFIER ON THE OTHER WAY. REMOVED BY OPENING THE BIASING CONDITIONS.

C₂ DECOUPLES R_E FROM THE SIGNAL'S POINT OF VIEW. THIS ALLOWS SIGNALS TO EXPERIENCE THE FULL GAIN AVAILABLE BUT ALLOWS THE DESIGNER TO MAINTAIN CONTROL OF THE DC CONDITIONS EVEN AS h_{FE} & TEMPERATURE VARY.

iv

$$\frac{V_o}{V_{be}} = -g_m R_L = -315.7$$


$$\frac{V_{be}}{V_s} = \frac{r_{\pi} \parallel R_1 \parallel R_2}{R_s + R_1 \parallel R_2 \parallel r_{\pi}} = \frac{7.26 \text{ k}\Omega}{2.2 \text{ k}\Omega + 7.26 \text{ k}\Omega} = 0.767$$

$$\frac{V_o}{V_s} = \frac{V_o}{V_{be}} \cdot \frac{V_{be}}{V_s} = -315.7 \cdot 0.767 = \underline{\underline{-242}}$$

Question 4:

- (a) Emitter-base junction in forward bias, base-collector junction in reverse bias.

2 marks

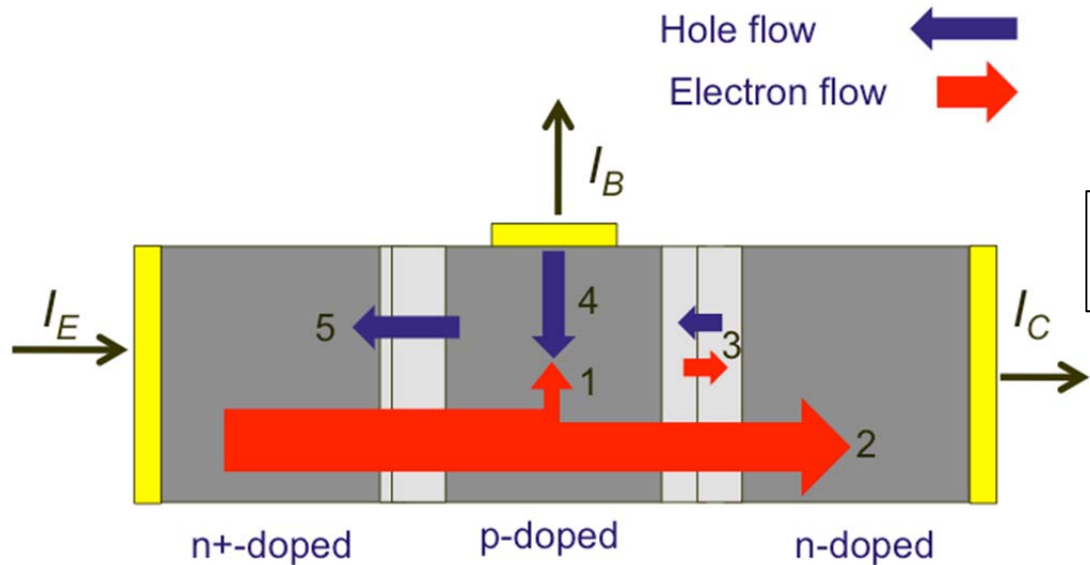

4 marks

- i) Hole current from emitter to base reduces gain, as this current does not appear in the collector
Electrons can recombine with majority holes in the base, and are lost to collector current
- ii) Ensure the emitter doping is much greater than base doping
Base width should be smaller than the minority carrier diffusion length

2 marks

2 marks

(b)

$$V_c = 4.5V$$

$$I_c = \left(\frac{4.5}{150}\right) = 0.3A$$

$$\beta = \text{gain} = \frac{I_c}{I_b} = \frac{0.3}{0.003} = 100$$

7 marks

Must calculate $B = \frac{\alpha}{\gamma}$

$$\beta = 100 = \frac{\alpha}{1-\alpha} \Rightarrow \alpha = 0.99$$

$$B = \frac{\alpha}{\gamma} = \frac{0.99}{0.997} = 0.99298$$

(c) $B = 1 - \frac{1}{2} \left(\frac{L_b}{L_c} \right)^2$ is relation to base lengths.

Call B_1 original, and B_2 new

$$B_1 = 1 - \frac{1}{2} \left(\frac{L_b}{L_c} \right)^2, \therefore \frac{1}{2} \left(\frac{L_b}{L_c} \right)^2 = 1 - B_1$$

$$B_2 = 1 - \frac{1}{2} \left(\frac{2L_b}{L_c} \right)^2, \therefore 4 \left(\frac{1}{2} \left(\frac{L_b}{L_c} \right)^2 \right) = 1 - B_2$$

$$\Rightarrow \frac{1 - B_2}{1 - B_1} = 4$$

$$4 - 4B_1 = 1 - B_2$$

$$\Rightarrow \underline{B_2 = 4B_1 - 3}$$

$$\therefore B_2 = 4(0.99298) - 3 = 0.97192$$

$$\alpha_2 = B_2 \gamma = 0.969$$

$$\boxed{\beta_2 = \frac{\alpha_2}{1 - \alpha_2} = 31.26}$$

8 marks

Question 5:

(a) Conduction band is the lowest *unoccupied* band of energy levels for electrons in a semiconductor. Or, the conduction band is where free electrons in a semiconductor reside.

6 marks

Valence band is the highest *occupied* band of energy levels for electrons in a semiconductor. Or the valence band is where free holes in a semiconductor reside.

The band gap of a semiconductor is the energy gap between the top of the valence band and the bottom of the conduction band

(b) A hole is a positive charge equivalent to a missing electron in the valence band of a semiconductor. It occurs in the valence band.

2 marks

(c) An intrinsic semiconductor is one in which free electrons and holes are generated by thermal excitation across the band gap, and where the number of electrons is equal to the number of holes.

4 marks

An extrinsic semiconductor is one where majority electrons or holes are present due to donor or acceptor impurity atoms in the semiconductor

$$(d) \quad n_i = C T^{3/2} e^{-\frac{E_g}{2kT}} \quad E_g \text{ in electron volts.}$$

$$1 \times 10^{16} = C (293)^{3/2} e^{-\frac{1.12}{2k(293)}}$$

$$\Rightarrow C = 8.38 \times 10^{21}$$

$$n_i^{350K} = (8.38 \times 10^{21})(350)^{3/2} e^{-\frac{1.12}{2k(350)}}$$

$$\boxed{n_i = 4.81 \times 10^{17} \text{ m}^{-3}}$$

6 marks

Conductivity increases because there are more free carriers in the conduction and valence bands.

7 marks

$$(c) \quad n_1 = C T_1^{3/2} e^{-\frac{E_g}{2kT_1}}$$

$$n_2 = C T_2^{3/2} e^{-\frac{E_g}{2kT_2}}$$

Ignoring the $T^{3/2}$ term $\Rightarrow \frac{n_2}{n_1} = e^{-\frac{E_g}{kT}(\frac{1}{T_2} - \frac{1}{T_1})}$

$$\ln\left(\frac{n_2}{n_1}\right) = \ln(1000) = 6.91 = -\frac{E_g}{kT}\left(\frac{1}{T_2} - \frac{1}{T_1}\right)$$

$$= 6492\left(\frac{1}{T_2} - \frac{1}{293}\right)$$


$$\Rightarrow \boxed{T_2 = 426 \text{ K}}$$

Using full equation at this temperature

$$\underline{n_i = C T^{3/2} e^{-\frac{E_g}{2kT}} = 1.77 \times 10^{19} \text{ m}^{-3}}$$

\therefore error is 77%


Q6a:

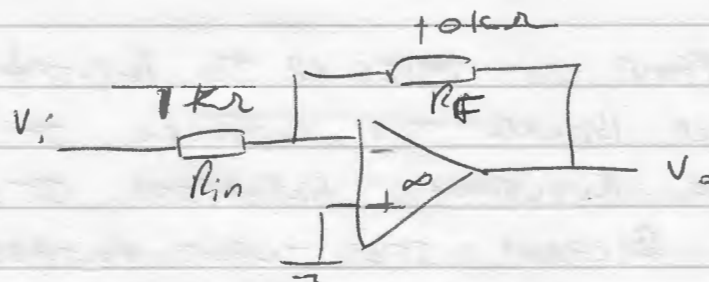

4

$$\frac{V_o}{V_i} = \frac{-R_F}{R_{in}} = \frac{-10k\Omega}{1k\Omega} = -10 \frac{V}{V}$$

ii

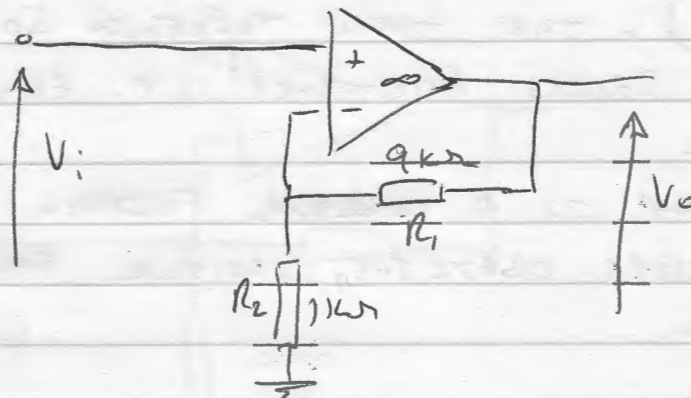

4

$$\frac{V_o}{V_i} = \frac{R_1 + R_2}{R_2} = \frac{9k + 1k}{1k} = 10 \frac{V}{V}$$

Gi

$$V_o = A_v (V^+ - V^-)$$

1

V_o - Output Voltage

1

V^+ - Non-Inverting Input

1

V^- - Inverting Input

A_v - Open Loop Gain


1

Q66ii

THE OPAMP IS DESIGNED TO AMPLIFY THE DIFFERENCE BETWEEN TWO VOLTAGES. IT IS THEREFORE A VOLTAGE AMPLIFIER. IT SHOULD RECEIVE ITS INPUT VOLTAGES WITHOUT LOADING THE SOURCE(S) DRIVING IT. THEREFORE IT SHOULD HAVE VERY HIGH INPUT RESISTANCE (IDEALLY INFINITE).

THE OPAMP, LIKE AN VOLTAGE AMPLIFIER, SHOULD APPEAR AS A THEVENIN SOURCE TO ITS LOAD (OUTPUT). THE IDEAL THEVENIN SOURCE HAS NO SERIES RESISTANCE I.E. ZERO OUTPUT RESISTANCE.

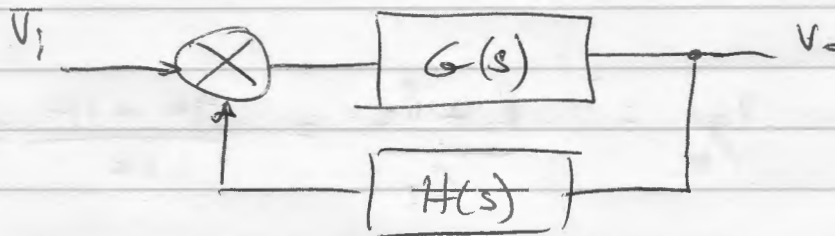THE OPAMP IS A CLASSICAL FEEDBACK SYSTEM. IT THEREFORE OBEYS THE CLASSICAL FEEDBACK EQUATION.



$$\frac{V_o}{V_i} = \frac{G(s)}{1 + G(s)H(s)}$$


IF $G(s)$ IS VERY LARGE THE EQUATION APPROXIMATES AS,

$$\frac{V_o}{V_i} = \frac{1}{H(s)}$$

WE CAN CONTROL $H(s)$ BY MAKING THE FOLLOWING PREVISIONS.

206 ii (Cont'd)

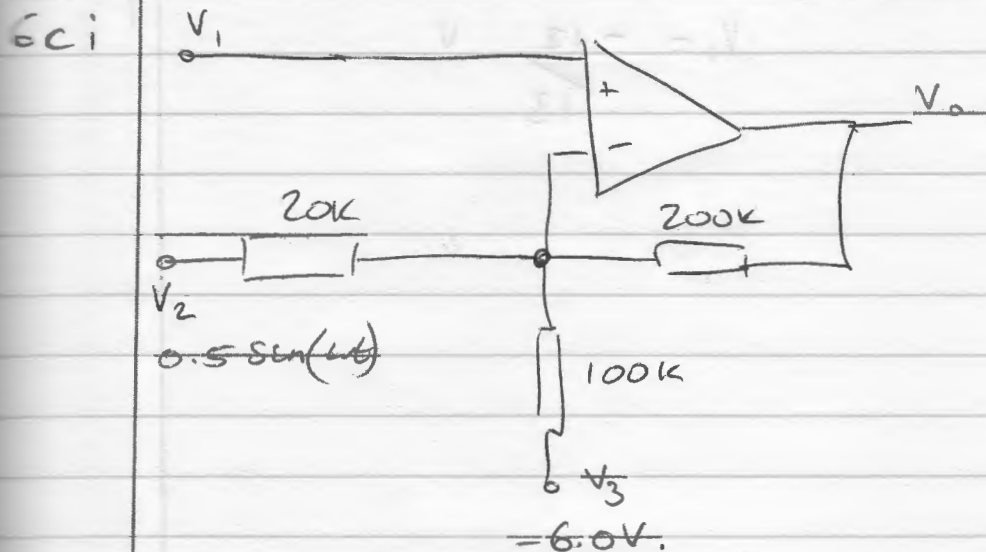IF $H(s)$ IS IN CONTROL OF THE CIRCUIT PARAMETERS
THE EXACT VALUE OF $G(s)$ IS NOT IMPORTANT AND
ANY AMPLIFIER CAN BE EXCHANGED FOR ANOTHER SIMILAR
BUT NOT IDENTICAL ONE WITH NO LOSS IN
DESIGN PERFORMANCE.



AC ONLY SO DC CAN BE IGNORED

$$\frac{V_0}{V_2} = \frac{-200k}{20k} \therefore V_0 = 0.5 \cdot \frac{-200}{20} \sin(4t)$$

$$= -5 \sin(4t)$$

ii DC ONLY SO AC IS IGNORED

$$\frac{V_0}{V_3} = \frac{-200}{100} = -2 \quad \frac{V_0}{V_3} = +12V$$

GRK 118 2015-2016

10/10

$$V_o|_{V_1} = \frac{200k + \frac{100k \cdot 20k}{100k + 20k}}{\frac{100k \cdot 20k}{100k + 20k}}$$

$$= \frac{200k + 16.66k}{-16.66k} = 13 \frac{V}{V}$$

To ZERO $V_o = 0$ $V_o|_{V_1} + V_o|_{V_3}$ MUST
 BE TO ZERO \therefore

$$V_1 = -12 \frac{V}{13}$$