

Q1 (If any mistakes are made following on marks will be awarded for correct methods)

$$L=100\text{cm}$$

$$D=0.3\text{cm}$$

$$\text{i. } M = 2 * L \left(\ln \left(\frac{2L}{D} \right) - 1 + \frac{D}{L} \right) \quad (2 \text{ marks})$$

$$M = 1100nH$$

$$C = \frac{0.0885\pi L}{\cosh^{-1} \left(\frac{D}{d} \right)} \quad (2 \text{ marks})$$

$$C = 15.8pF$$

ii. The voltage and current are both square waves, using the equation given the envelope of the frequency spectrum is

$$V(n) = \frac{2V}{n\pi} \quad (3 \text{ marks})$$

$$I(n) = \frac{2V}{n\pi}$$

$$V(n) = \frac{2 * 2.5}{\pi} = 1.6V \quad (1 \text{ mark})$$

$$I(n) = \frac{2 * 5}{\pi} = 3.18A$$

$$\text{iii. } V_m = \omega MI(1) = 2 * \pi * 50 * 10^3 * 1100 * 10^{-9} * 3.18 \quad 3 \text{ marks}$$

$$V_m = 1.1V$$

$$V_C = \omega CV(1) * \frac{R_1 R_2}{R_1 + R_2} = 2 * \pi * 50 * 10^3 * 15.8 * 10^{-12} * 1.6 * \frac{10 * 100 * 10^3}{10 + 100 * 10^3} \quad 3 \text{ marks}$$

$$V_C = 79\mu V$$

Almost all of the voltage is dropped across the data logger

iv. The dominant source is inductive 1 mark

b.

The frequency of interest (50kHz) is 5 time higher than the cut-off frequency hence the induced voltage will be a maximum of:-

$$V_N = M \frac{R_S}{L_S} I(1) \quad 2 \text{ marks}$$

$$\text{Also, } f_0 = \frac{R_S}{2\pi L_S}, \text{ hence}$$

$$\begin{aligned} V_N &= 2\pi f_0 M I(1) \\ V_N &= 2\pi * 10 * 10^3 * 1100 * 10^{-9} * 3.18 \\ V_N &= 0.2V \end{aligned} \quad 3 \text{ marks}$$

Q2

i)

The power density is given by

$$P = \frac{P_t D \cos(\theta)}{4\pi R^2} \quad 1 \text{ mark}$$

The distance, R can be found from Pythagoras

$$R = \sqrt{10^2 + 17} = 19.7m$$

The angle can be found from trig

$$\theta = \tan^{-1}\left(\frac{17}{10}\right) = 59 \text{ deg}$$

Hence the power density is

$$P = \frac{30 * 10 \cos(59)}{4\pi * 19.7^2} = 31.4W / m^2 \quad 2 \text{ marks}$$

ii)

The E-field can be found from

$$E = \sqrt{PZ_0} = 3.44V / m \quad 1 \text{ mark}$$

iii)

The wavelength is

$$\lambda = \frac{c}{f} = 3m \quad 1 \text{ mark}$$

iv)

We need to choose the correct equation from the information given at the end of the paper, which is

$$\frac{V_2}{E} = \frac{Z_2 D(Z_0[1 - \cos(\beta l)] + jZ_1 \sin(\beta l))}{(Z_0 Z_1 + Z_0 Z_2) \cos(\beta l) - j(Z_0^2 + Z_1 Z_2) \sin(\beta l)}$$

1 marks

$$D=0.02\text{m}$$

$$d=0.0001\text{m}$$

$$Z_1=10\Omega$$

$$Z_2=100\text{k}\Omega$$

$$L=0.1\text{m}$$

The required calculations needed for the equation above are

$$\beta l = \frac{2\pi}{\lambda} l = 0.209\text{rad}$$

1 mark

The characteristic impedance of the cables is

$$Z_0 = 120 \ln\left(\frac{2 \cdot 20}{1}\right) = 443\Omega$$

1 mark

Hence, the coupling factor is

$$\frac{V_2}{E} = \frac{100\text{k} * 0.02(443[1 - \cos(0.209)] + jZ_1 \sin(0.209))}{(443 * 10 + 443 * 100\text{k}) \cos(0.209) - j(443^2 + 10 * 100\text{k}) \sin(0.209)}$$

$$\frac{V_2}{E} = \frac{9.746 + j2.08}{22.15\text{k} - j124.5}$$

3 marks

$$\left| \frac{V_2}{E} \right| = 4.49 * 10^{-4}$$

Hence the induced voltage is $4.49 * 10^{-4} * 3.44 = 1.5\text{mV}$

1 mark

B

First step is to choose the correct Reflection loss equation.

The far field can region can be approximated by $\frac{\lambda}{2\pi} = \frac{3}{2\pi} = 0.5m$, hence the shield is in the far field

So the reflection loss equation is

$$R = 168 - 10 \cdot \log_{10} \left(\left(\frac{\mu_r}{\sigma_r} \right) \cdot f \right)$$

1 mark

The reflection loss from the aluminium shield is

$$R = 168 - 10 \cdot \log_{10} \left(\left(\frac{1}{0.6} \right) \cdot 100 \cdot 10^6 \right) = 85.8dB$$

2 marks

Hence we need at least 14.2dB from absorption to meet the SE requirement

$$A = 8.69 \frac{d}{\delta}$$

$$\delta = \frac{1}{\sqrt{\pi \mu \sigma f}} = 8.5 \mu m$$

2 marks

$$d > 8.69 \cdot 8.5 \mu = 73.8 \mu m$$

Solutions

Q3(a)

The Smith chart can be used to solve transmission line problems by using the following steps

- Normalise load impedance and find reflection coefficient at load
- Rotate reflection coefficient
- Record normalised input impedance
- De-normalise input impedance

(2 marks)

Q3(b)

$$\lambda = \frac{c}{f} = 10\text{cm}$$

Therefore

$$\beta\ell = \frac{2\pi}{\lambda} \times 3 = 0.1884 \quad \textbf{(1 mark)}$$

$$Z_{\text{in}} = Z_o \frac{Z_L + jZ_o \tan(\beta\ell)}{Z_o + jZ_L \tan(\beta\ell)} = (27 + j8.9)\Omega \quad \textbf{(1 mark)}$$

$$\Gamma_{\text{in}} = \frac{Z_{\text{in}} - Z_o}{Z_{\text{in}} + Z_o} = -0.28 + j0.148 \quad \textbf{(1 mark)}$$

$$\text{VSWR} = \frac{1 + |\Gamma_{\text{in}}|}{1 - |\Gamma_{\text{in}}|} = 1.93 \quad \textbf{(1 mark)}$$

Q3(c)

$$Z_o = \sqrt{Z_{\text{in}} Z_L} = \sqrt{75 \times 40} = 55\Omega \quad \textbf{(1 mark)}$$

The input impedance is given by

$$Z_{\text{in}} = Z_o \frac{Z_L + jZ_o \tan(\beta\ell)}{Z_o + jZ_L \tan(\beta\ell)}$$

The frequency dependence comes from the $(\beta\ell)$ term, which can be written in terms of f/f_o as

$$\beta\ell = \left(\frac{2\pi}{\lambda} \right) \left(\frac{\lambda_o}{4} \right) = \left(\frac{2\pi f}{v_p} \right) \left(\frac{v_p}{4f_o} \right) = \frac{\pi f}{2f_o} \quad \textbf{(1 mark)}$$

i.e.


$$Z_{\text{in}} = Z_o \frac{Z_L + jZ_o \tan\left(\frac{\pi f}{2f_o}\right)}{Z_o + jZ_L \tan\left(\frac{\pi f}{2f_o}\right)}$$

The input reflection coefficient and VSWR can be calculated as

$$|\Gamma_{in}| = \left| \frac{Z_{in} - Z_o}{Z_{in} + Z_o} \right| \quad \text{VSWR} = \frac{1 + |\Gamma_{in}|}{1 - |\Gamma_{in}|} \quad (1 \text{ mark})$$

f/f_o	Z_{in}	VSWR
0	$40 + j0.$	1.875
0.5	$52 + j16.7$	1.56
1	$75 + j0.$	1
1.5	$52 - j16.7$	1.56
2	$40 + j0.$	1.875

(2 marks)

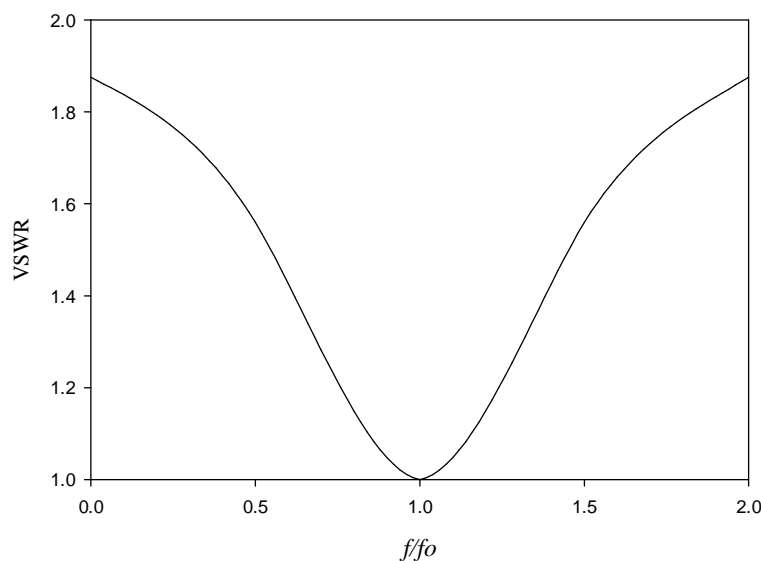



(1 mark)

Q3(d)

At higher frequencies, resistors and capacitors have inductance due to the leads, and energy stored in the magnetic field. In addition, there is a parasitic capacitance both internally and due to the proximity with the surrounding structures. (1 mark)

The equivalent circuit of a resistor include a series inductance in the order of 5 to 10 nH as well as a parallel capacitance up to few pico Farads. Therefore, the equivalent impedance is given by
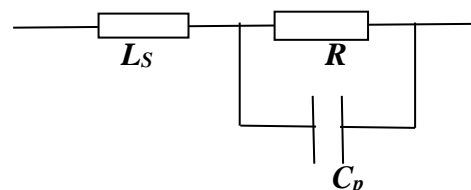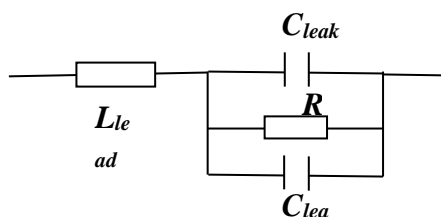
$$Z_{resistor}(f) = \frac{X_L(X_C + jR)}{(R - jX_C)}$$



(2 marks)


At low frequencies $Z_{resistor}(f) \approx R$ since the inductance and capacitance can be represented as short and open circuits, respectively. However, as the frequency increases, the capacitive reactance reduces and at a frequency of

f_1 it becomes equal to R , i.e. $f_1 = \frac{1}{2\pi RC_p}$. (1 mark)

Further frequency increment, results in a higher current through the capacitor compared to that in the resistor. For higher frequencies, the impedance reduces until the resonance is achieved at a frequency of

$f_0 = \frac{1}{2\pi\sqrt{L_S C_p}}$. (1 mark)

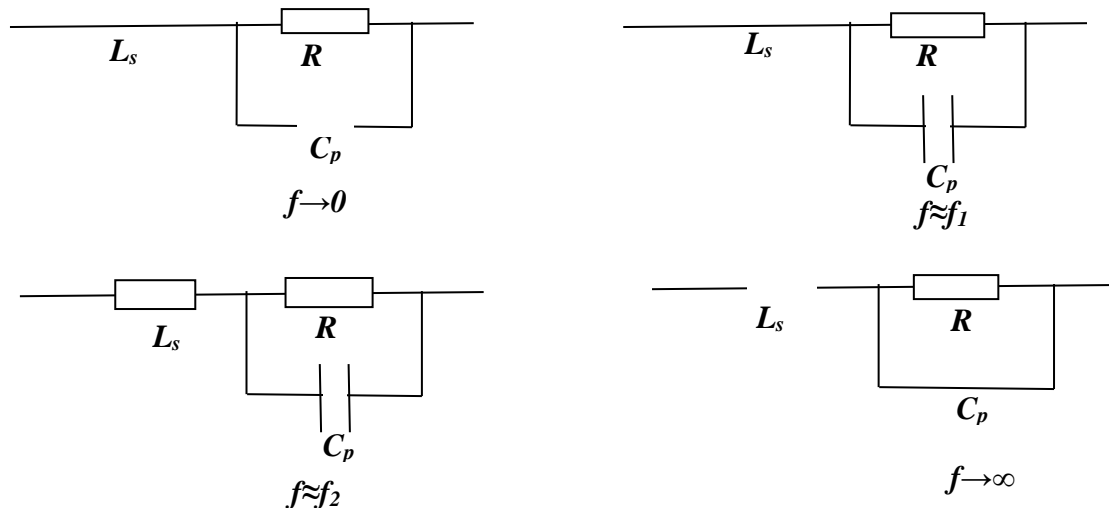After this frequency the lead inductance dominates until it approaches infinite while the capacitive reactance approaches zero, thus the resistor impedance can be modelled as an open circuit. (1 mark)



(2 marks)

Q4(a)

There are two basic components of any SFD:

Nodes; each port in the network has two nodes a_n and b_n . The node a_n represents a wave entering port n , while node b_n represents a wave reflected from port n . (1 mark)

Branches; each branch represents a direct path between a-node and b-node. For each branch there is an associated S parameter or reflection coefficient. (1 mark)

Q4(b)

Consider the following input signal


$$v_i = V_0 (\cos \omega_1 t + \cos \omega_2 t)$$

Substituting in

$$v_o = a_0 + a_1 v_i + a_2 v_i^2 + a_3 v_i^3 + \dots$$

gives six third-order inter-modulation products, four of them will be outside the pass band of the amplifier, but two products will be located near the original input signals. **(2 marks)**

This is shown in the following diagram;

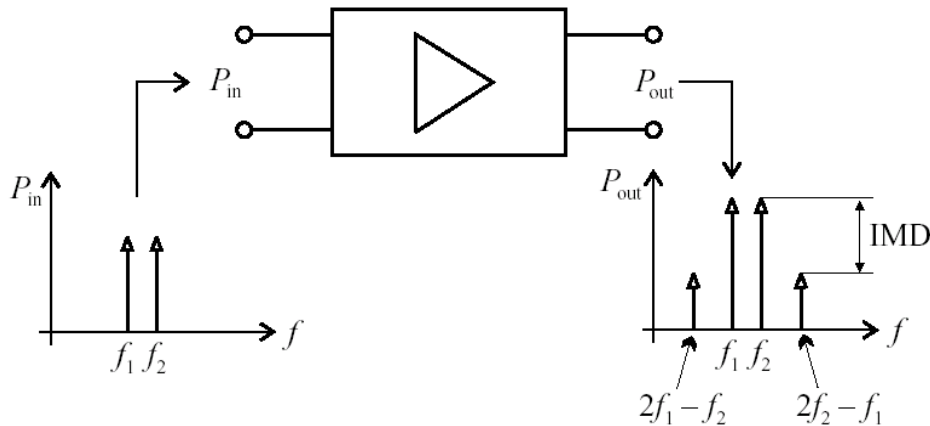

(1 mark)

For an amplifier these products should be as small as possible. The difference between the desired and undesired power levels (in dBm) is the IMD (in dB)

$$IMD(dB) = P_{out}(f_2)(dBm) - P_{out}(2f_2 - f_1)(dBm)$$

(1 mark)

Q4(c)

The scattering parameter S_{11} is calculated when port is terminated with $Z_L = Z_{o2} = 50\Omega$ as

$$S_{11} = \Gamma_{in} = \frac{Z_{in1} - Z_{o1}}{Z_{in1} + Z_{o1}}$$

$$Z_{in1} = 15 + \left[\frac{75.6(15 + 50)}{75.6 + 15 + 50} \right] = 50\Omega$$

i.e. $S_{11} = 0$

(1.5 mark)

and

$$S_{21} = \frac{2Z_o Z_3}{Z_1(Z_1 + 2Z_3) + 2Z_o(Z_1 + Z_3) + Z_o^2}$$

$$= \frac{75.6 \times 100}{15(15 + 151.2) + 100(15 + 75.6) + (2500)} = 0.53$$

(1 mark)

In the same way it can be shown that $S_{22} = 0$ and $S_{12} = 0.53$

(0.5 mark)

The input and output powers are

$$P_{in} = \frac{|V_{i1}|^2}{2Z_{o1}} \quad P_{out} = \frac{|V_{r2}|^2}{2Z_{o2}} \quad (1 \text{ mark})$$

then

$$\frac{P_{out}}{P_{in}} = \frac{|V_{r2}|^2}{|V_{i1}|^2} = \frac{|S_{21}V_{i1}|^2}{|V_{i1}|^2} = |S_{21}|^2 = 0.28 = -5.5\text{dB} \quad (1 \text{ mark})$$

This means that the above circuit is a passive circuit, which provides 5.5dB attenuation. (1 mark)

Q4(d)

$$N = \frac{NF - NF_{min}}{4R_N/Z_o} |1 + \Gamma_{opt}|^2 = \frac{1.58 - 1.445}{80/50} |1 + 0.62 \angle 100^\circ|^2 = 0.0986$$

$$C_{NF} = \frac{\Gamma_{opt}}{(N + 1)} = 0.56 \angle 100^\circ$$

$$r_{NF} = \frac{\sqrt{N(N + 1 - |\Gamma_{opt}|^2)}}{(N + 1)} = 0.24 \quad (1.5 \text{ mark})$$

Next we calculate data for several input section constant gain circles

G_s	g_s	C_s	r_s
1.0dB	0.805	$0.52 \angle 60^\circ$	0.3
1.5dB	0.904	$0.56 \angle 60^\circ$	0.205
1.7dB	0.946	$0.58 \angle 60^\circ$	0.15

(2 marks)

The noise figure and constant gain circles are plotted on the Smith chart and the $G_s = 1.7\text{dB}$ circle just intersects the noise figure circle, and any higher gain will results in a worse noise figure. (4 marks,

one for each circle)

From the Smith chart the optimum solution is then $\Gamma_s = 0.53 \angle 75^\circ$ and $NF = 2\text{dB}$. (0.5 mark)

