

Q1

$$v_1 = 212 \sin(\omega t + 45) \Rightarrow 212 \angle 45$$

$$v_2 = 141 \sin(\omega t - 90) \Rightarrow 141 \angle -90$$

$$v_3 = 127 \cos(\omega t + \pi/6) = 127 \sin(\omega t + \pi/6 + \pi/2) \Rightarrow 127 \angle 120$$

$$v_4 = 85 \cos(\omega t - 45) = 85 \sin(\omega t - 45 + 90) \Rightarrow 85 \angle 45$$

$$v_5 = 141 \sin(\omega t + 180) \Rightarrow 141 \angle 180$$


$$v_6 = 100 \cos(\omega t - \pi/3) = 100 \sin(\omega t - \pi/3 + \pi/2) \Rightarrow 100 \angle 30$$

notice that in each case the ωt is understood but not explicitly stated. π radians = 180°

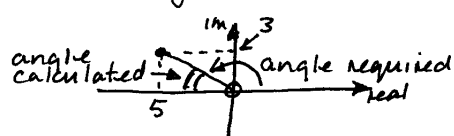Q2 $(2-j2)$ $r = \sqrt{2^2 + 2^2} = \sqrt{8} = 2.83$ $\phi = \tan^{-1} \frac{-2}{2} = -45^\circ$
 $\therefore 2.83 \angle -45$


$(3+j8)$ $r = \sqrt{3^2 + 8^2} = \sqrt{73} = 8.54$ $\phi = \tan^{-1} \frac{8}{3} = 69.4^\circ$
 $\therefore 8.54 \angle 69.4$

$(-5+j3)$ $r = \sqrt{5^2 + 3^2} = \sqrt{34} = 5.83$ $\phi = \tan^{-1} \frac{3}{-5} = -31^\circ$



This phase shift is in the -ve real area so angle w.r.t. positive real = $180^\circ + (-31^\circ) = 149^\circ$
 $\therefore 5.83 \angle 149$

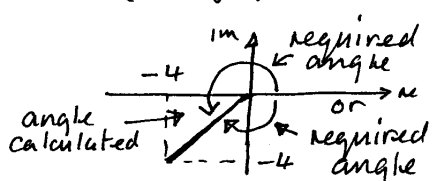$(-4-j4)$ $r = 4\sqrt{1+1} = 5.66$ $\phi = \tan^{-1} \frac{-4}{-4} = 45^\circ$




This phase shift is in the -ve real area so angle w.r.t. positive real = $180 + 45 = 225^\circ$ or $-180 + 45 = -135^\circ$
 $\therefore 5.66 \angle 225$ or $5.66 \angle -135$

$(2-j2)(3+j8) = 22+j10$ $r = \sqrt{584} = 24.2$ $\phi = 24.4^\circ$
 $\therefore 24.2 \angle 24.4$

[check using first two.. $(2.83 \angle -45) \times (8.54 \angle 69.4)$
 $= 2.83 \times 8.54 \angle (-45 + 69.4) = 24.2 \angle 24.4$]
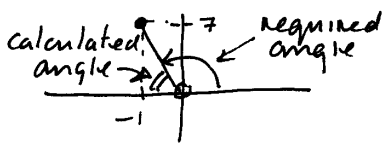
$$(-5+j3) - (-4-j4) = -1+j7 \quad r=7.1 \quad \phi = \tan^{-1} \frac{7}{-1} = -81.9$$



This angle is in the negative real area so angle required = $180 + (-81.9)$
 $= 98.1$

$$\therefore \mathbf{7.1 \angle 98.1}$$

Q3

$$6 \angle 45 = 6 \cos 45 + j 6 \sin 45 = 4.2 + j 4.2$$

$$50 \angle -170 = 50 \cos(-170) + j 50 \sin(-170) = -49.2 - j 8.7$$


$$4 \angle 105 = 4 \cos 105 + j 4 \sin 105 = -1 + j 3.9$$

$$3 \angle -90 = 3 \cos(-90) + j 3 \sin(-90) = 0 - j 3$$

$$(5 \angle -30)(6 \angle 120) = 30 \angle 90 = 0 + j 30$$


$$3 \angle 15 + 3 \angle 135 + 3 \angle -105 = 2.90 + j 0.78 - 2.12 + 2.12j - 0.78 - 2.9j = 0 + j 0$$

Q4 (i)

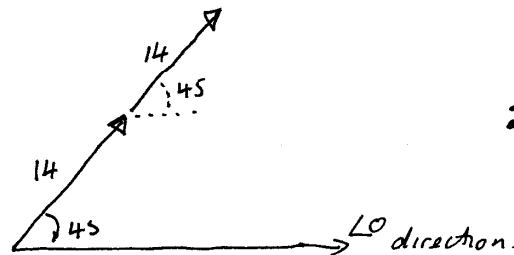


$$\mathbf{28 \angle 45}$$

(ii)

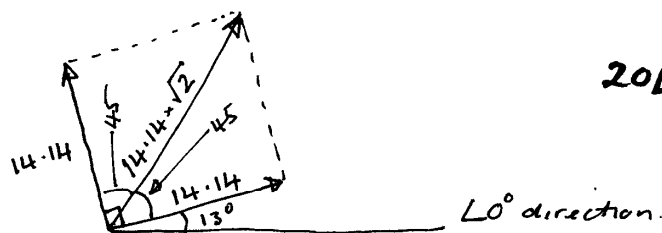

$$\mathbf{20 \angle 58}$$

(iii)

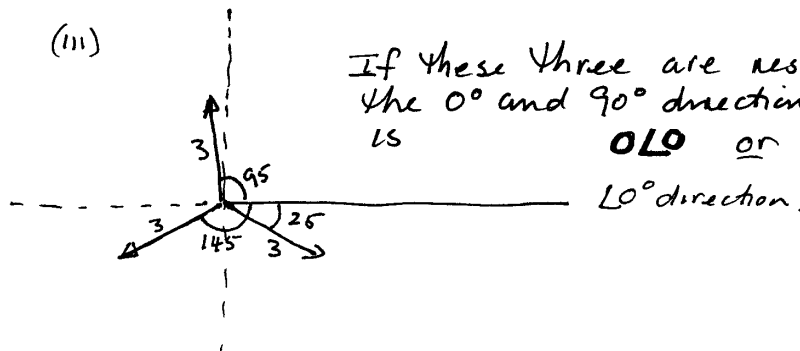

If these three are resolved along the 0° and 90° directions the answer is $\mathbf{0 \angle 0}$ or $\mathbf{0 + j 0}$

Q5 (i) The impedance of the components is

$$\frac{V}{I} = \frac{280 \angle 150}{11 \angle 140} = \frac{280}{11} \angle 10 = 25.46 \angle 10$$

$$25.46 \angle 10 = 25.1 + j4.42$$

Since the phase of V w.r.t. I is positive the circuit is inductive and since the phase is less than 90° there must be resistance involved

So the series combination is $L + R$.

(ii) The impedance of a series $L-R$ combination is

$$Z = R + j\omega L$$

and this must be equal to the impedance calculated from the given $V + I$

$$\therefore R + j\omega L = 25.1 + j4.42$$

$$\therefore \underline{R = 25.1 \Omega}$$

$$\omega L = 4.42 \quad \text{or} \quad L = \frac{4.42}{2\pi f} = \frac{4.42}{800} = \underline{5.5 \text{ mH}}$$

(iii) The peak value of current is 11 A and this flows through R

$$\therefore P_{\text{diss}} = \frac{I_p^2}{2} \times R = \frac{121}{2} \times 25.1 = \underline{1.52 \text{ kW}}$$

↑ mean squared value


Q6 $|Z| = \frac{230}{10} = \sqrt{2^2 + \omega^2 L^2}$

$$\left(\frac{230}{10}\right)^2 = 529 = 4 + \omega^2 L^2$$

$$L^2 = \frac{529 - 4}{\omega^2} = \frac{525}{(2\pi \cdot 50)^2} = 5.32 \times 10^{-3}$$

$$\therefore \underline{L = 73 \text{ mH}}$$
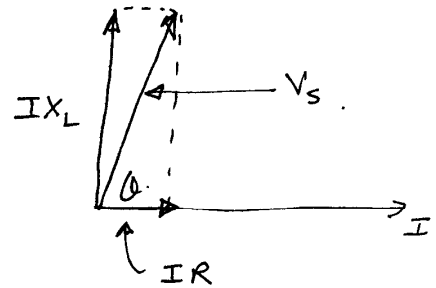
$$\begin{aligned} \phi &= \tan^{-1} \frac{X_L}{R} \\ &= \tan^{-1} \frac{22.9}{2} = 85^\circ \end{aligned}$$




$\therefore I$ lags V_s by 85° or
The phase of I wrt $V = \underline{\underline{-85^\circ}}$

$$\begin{aligned} \text{Q7 } |Z| &= 110 = \sqrt{47^2 + \frac{1}{\omega^2 C^2}} = \sqrt{47^2 + X_c^2} \\ 110^2 - 47^2 &= X_c^2 = 9.89 \times 10^3 \\ \therefore X_c &= \underline{\underline{99.5 \Omega}} \end{aligned}$$

$$X_c = \frac{1}{2\pi f C} \therefore C = \frac{1}{2\pi f \cdot X_c} = \underline{\underline{16 \mu F}}$$


$$\begin{aligned} \phi &= \tan^{-1} \frac{X_c}{R} = \tan^{-1} \frac{99.5}{47} \\ &= 64.7^\circ \end{aligned}$$

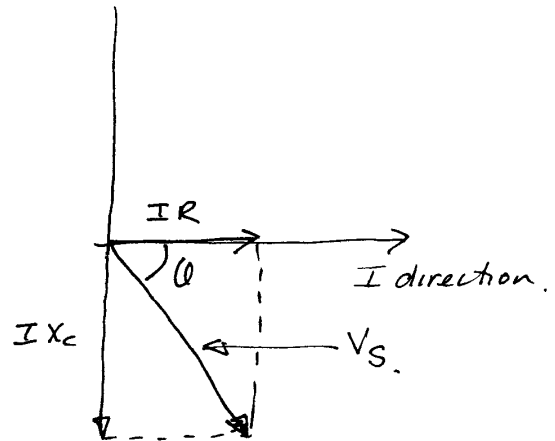In this case the current
leads the voltage so the
phase of I w.r.t. V is
64.7^\circ



Q8 at 50 Hz $X_L = j2\pi fL = j31.4$
 $X_C = \frac{1}{j2\pi fC} = -j63.7$

at 150 Hz $X_L = j94.2$
 $X_C = -j21.2$

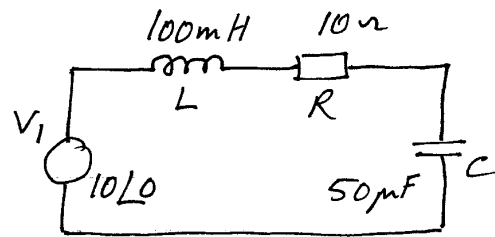

(i) for 50 Hz, $10 + j0 = I[j31.4 + 10 - j63.7]$

$$\therefore I = \frac{10 \angle 0}{10 - j32.3} = \frac{10 \angle 0}{33.8 \angle -72.8} = \underline{0.3 \angle 73^\circ}$$

$$\begin{aligned} V_C &= IX_C = -j63.7 (0.3 \angle 73^\circ) \\ &= (63.7 \angle -90^\circ)(0.3 \angle 73^\circ) \\ &= \underline{18.8 \angle -17^\circ} \end{aligned}$$

(ii) for 150 Hz $10 + j0 = I[j94.2 + 10 - j21.2]$
 $= I[10 + j73] = I[73.7 \angle 82^\circ]$

$$\therefore I = \frac{10 \angle 0}{73.7 \angle 82^\circ} = \underline{0.14 \angle -82^\circ}$$


$$\begin{aligned} V_C &= IX_C = (0.14 \angle -82^\circ)(0 - j21.2) \\ &= (0.14 \angle -82^\circ)(21.2 \angle -90^\circ) \\ &= \underline{2.9 \angle -172^\circ} \end{aligned}$$


Q9

$$V_{s1} = V_{s2} + V_3$$

$$\text{or } V_{s1} - V_{s2} = V_3$$

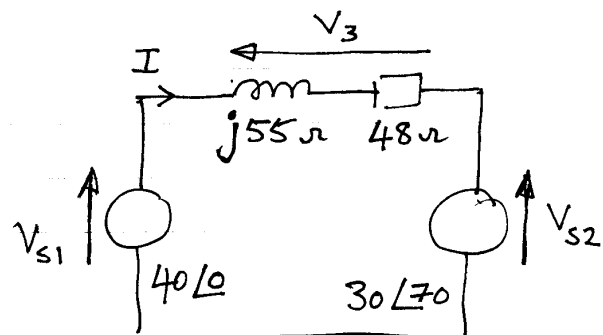we need a phasor diagram to represent this vector equation...



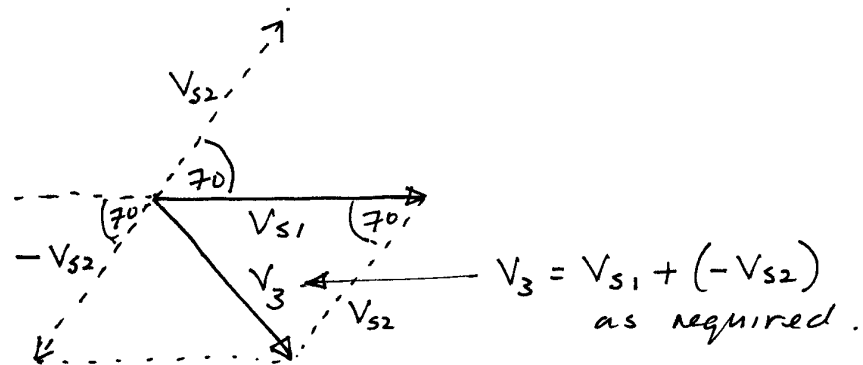

using the cosine rule ...

$$V_3^2 = V_{s1}^2 + V_{s2}^2 - 2V_{s1}V_{s2} \cos 70.$$

where all V 's are the moduli of the appropriate quantity

$$\therefore V_3^2 = 1600 + 900 - 2 \times 1200 \times 0.342$$

$$= 2500 - 821 = 1679 \text{ V}^2$$

$$\therefore \underline{\underline{V_3 = 41 \text{ V}}}$$

$$(ii) \quad 40 \angle 0 = 40 + j0$$

$$30 \angle 70 = 10.3 + j28.2.$$

$$(iii) \quad I = \frac{40 \angle 0 - 30 \angle 70}{Z} = \frac{40 + j0 - 10.3 - j28.2}{48 + j55}$$

$$= \frac{29.7 - j28.2}{48 + j55} = \frac{(29.7 - j28.2)(48 - j55)}{48^2 + 55^2}$$

$$= \underline{\underline{-0.024 - j0.561}}$$


$$\equiv \underline{\underline{0.56 \angle -92.4}}$$

All phases are measured with respect to V_{s1} .

Q10 (i) Total Z seen by source is

$$Z_T = \frac{V_s}{I} = \frac{50 \angle 45}{2.5 \angle -15}$$

$$= 20 \angle 60$$

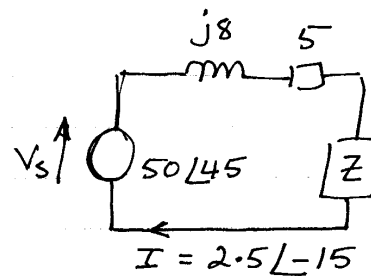

Z_T is also equal to the sum of impedances in the series circuit

$$Z_T = j8 + 5 + Z$$

$$\therefore 20 \angle 60 = j8 + 5 + Z = 10 + j17.3$$

$$\therefore Z = 10 + j17.3 - j8 - 5$$

$$= \underline{\underline{5 + j9.3}} = \underline{\underline{10.6 \angle 61.7}}$$

- (ii) Z has a real part + j term so the circuit is inductive and could consist of a resistance

$$R = 5 \Omega$$

in series with an inductance

$$X_L = j9.3 \Omega$$


- (iii) If the source phase is modified to $50 \angle 0$, all the other phases of voltages + currents are reduced by 45° so

$$I = 2.5 \angle -60$$

But Z depends only on the components and hence remains unchanged at

$$Z = 5 + j9.3$$

Q11

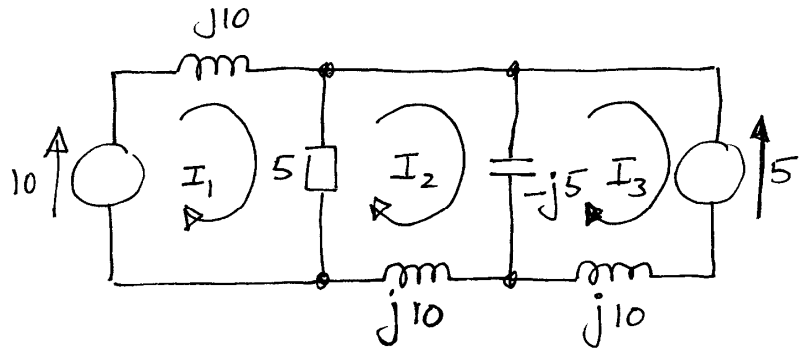

$$\begin{aligned} \text{loop } I_1: \quad 10 &= j10 I_1 + 5(I_1 - I_2) \\ 2 &= j2 I_1 + I_1 - I_2 \\ \therefore 2 &= I_1(1 + j2) - I_2 \quad \text{--- (1)} \end{aligned}$$

$$\begin{aligned} \text{loop } I_2: \quad 5(I_2 - I_1) + j10 I_2 - j5(I_2 - I_3) &= 0 \\ I_2 - I_1 + 2j I_2 - j I_2 + j I_3 &= 0 \\ I_2(1 + j) + j I_3 - I_1 &= 0 \quad \text{--- (2)} \end{aligned}$$

$$\begin{aligned} \text{loop } I_3: \quad 5 + j10 I_3 - j5(I_3 - I_2) &= 0 \\ 1 + j2 I_3 - j I_3 + j I_2 &= 0 \\ 1 + j I_3 + j I_2 &= 0 \quad \text{--- (3)} \end{aligned}$$

$$\begin{aligned} \text{sub (3) into (2)} \\ I_2(1 + j) - (1 + j I_2) - I_1 &= 0 \\ \cancel{I_2} + \cancel{j I_2} - 1 - \cancel{j I_2} - I_1 &= 0 \\ I_2 - I_1 - 1 &= 0 \quad \text{--- (4)} \end{aligned}$$

$$\begin{aligned} \text{sub (4) into (1)} \\ 2 &= I_1(1 + 2j) - I_1 - 1 \\ 2 &= \cancel{I_1} + 2j I_1 - \cancel{I_1} - 1 \\ 3 &= 2j I_1 \quad \text{or} \quad \underline{I_1 = -1.5j} \end{aligned}$$

$$\begin{aligned} \text{sub } I_1 \text{ into (1)} \\ 2 &= -1.5j(1 + 2j) - I_2 \\ 2 &= -1.5j + 3 - I_2 \end{aligned}$$

$$-1 + 1.5j = -I_2 \quad \text{or} \quad \underline{I_2 = 1 - 1.5j}$$

sub I_2 into ③.

$$1 + jI_3 + j(1 - 1.5j) = 0$$

$$1 + jI_3 + j + 1.5 = 0$$

$$\underline{2.5 + j} = -I_3 = -j2.5 + 1$$

$$\underline{\text{or } I_3 = -1 + j2.5}$$

$$\begin{aligned} \text{Power delivered to ct} &= 10 \times \text{real } I_1 + 5 \times \text{real } (-I_3) \\ &= 0 + 5 \\ &= \underline{5W}. \end{aligned}$$